

Position-to-Voltage Conversion

UC Berkeley

- To sense position (i.e., displacement), use a capacitive load

Again, here port-to-port I/O symmetry:

Brute-force approach:

$$\frac{V_o}{V_i} = \frac{\frac{1}{sC_D}}{R_x + \frac{1}{sC_x} + sL_x + \frac{1}{sC_D}}$$

$$\frac{V_o}{V_i} = \frac{\frac{C_x/C_D}{s^2 R_x C_x + 1 + s^2 L_x C_x + \frac{1}{s^2 C_D}}}{1 + sR_x C_x/C_D} = \frac{1}{1 + sR_x C_x/C_D + s^2 \frac{L_x C_x}{1 + sR_x C_x/C_D}}$$

$$= \frac{C_x/C_D}{1 + sR_x C_x/C_D} \frac{\frac{1}{s^2} \frac{R_x}{L_x C_x}}{s^2 + s\left(\frac{R_x}{L_x C_x}\right) + \left(1 + \frac{C_x/C_D}{s^2}\right)}$$

$$\left[\omega_0^2 = \frac{1}{L_x C_x} \rightarrow (\omega_0')^2 = \omega_0^2 \left(1 + \frac{C_x/C_D}{s^2}\right) \right]$$

$$\left[Q' = \frac{\omega_0' L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0'}{Q'}, Q' = \sqrt{1 + \frac{C_x/C_D}{s^2}} \right] \text{ then}$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 6

Position-to-Voltage Conversion

UC Berkeley

- To sense position (i.e., displacement), use a capacitive load

DC Gain Term

$$\frac{V_o}{V_i} = \frac{C_x/C_D}{1 + C_x/C_D} \frac{(s/\omega_0)^2}{s^2 + (s/\omega_0)^2 + (s/\omega_0)^2}$$

Lad-Pacr Biquad

To maximize gain $\rightarrow 1$, need $C_D \ll C_x$. (must minimize C_D)

Note: Can we similar short-cut to the R case.

- Get DC response $\rightarrow C$'s dominate.
- Then:

$$\frac{V_o}{V_i} = (\text{DC Gain}) \cdot \frac{1}{s} \cdot \Theta(s, \omega_0, Q') \cdot \omega_0 Q'$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 7

Position Sensing Circuits

UC Berkeley

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 13

Problems With Pure-C Position Sensing

UC Berkeley

- To sense position (i.e., displacement), use a capacitive load

Interconnect Band Pad

$$\frac{V_o}{V_i} = \frac{C_x/C_D}{1 + C_x/C_D} \cdot \frac{1}{s} \cdot \Theta(s, \omega_0, Q') \cdot \omega_0 s$$

Integration yields displacement.

To maximize gain, minimize sL . \Rightarrow Problem: parasitic capacitance

$$C_D \rightarrow C_D + C_{pi} + C_{pb}$$

\Rightarrow DC Gain: $\frac{C_x/(C_D + C_{pi} + C_{pb})}{1 + C_x/(C_D + C_{pi} + C_{pb})}$

Output will get smaller!

Remedy: Suppress C_p via use of op amps.

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 14



