

Lecture 24w: Equivalent Circuits IILecture 24: Equivalent Circuits IIAnnouncements:

- Reminder: 2<sup>nd</sup> project slide due this Friday
- HW #6 Due Next Tuesday
- - -
- Reading: Senturia, Chpt. 6, Chpt. 14

Lecture Topics:↳ Input Modeling


- Force-to-Velocity Equiv. Ckt.
- Input Equivalent Ckt.


↳ Current Modeling

- Output Current Into Ground
- Input Current
- Complete Electrical-Port Equiv. Ckt.

↳ Impedance & Transfer Functions

- - -
- Last Time:
- Finished Module 12
- Now start going through Module 13 (on Equivalent Circuits) through slide 8

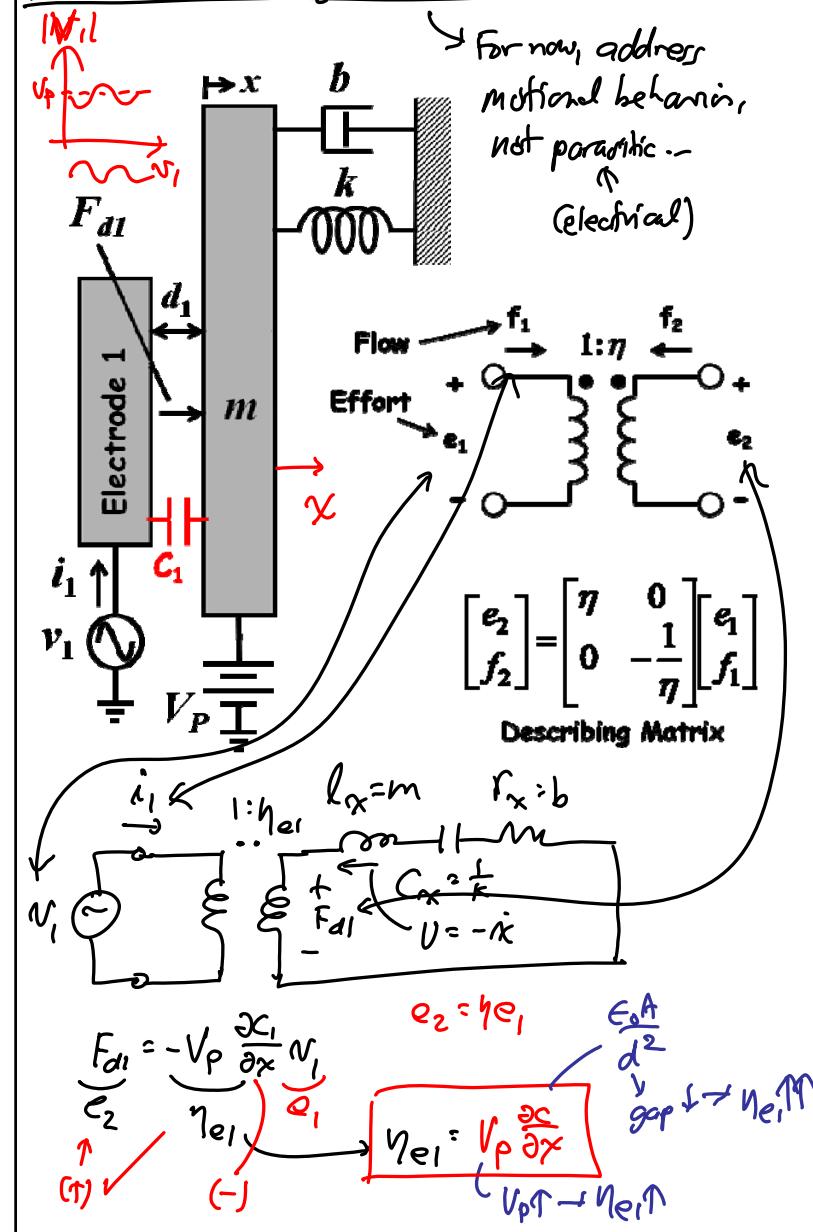[Input Electrical Equiv. Ckt.]

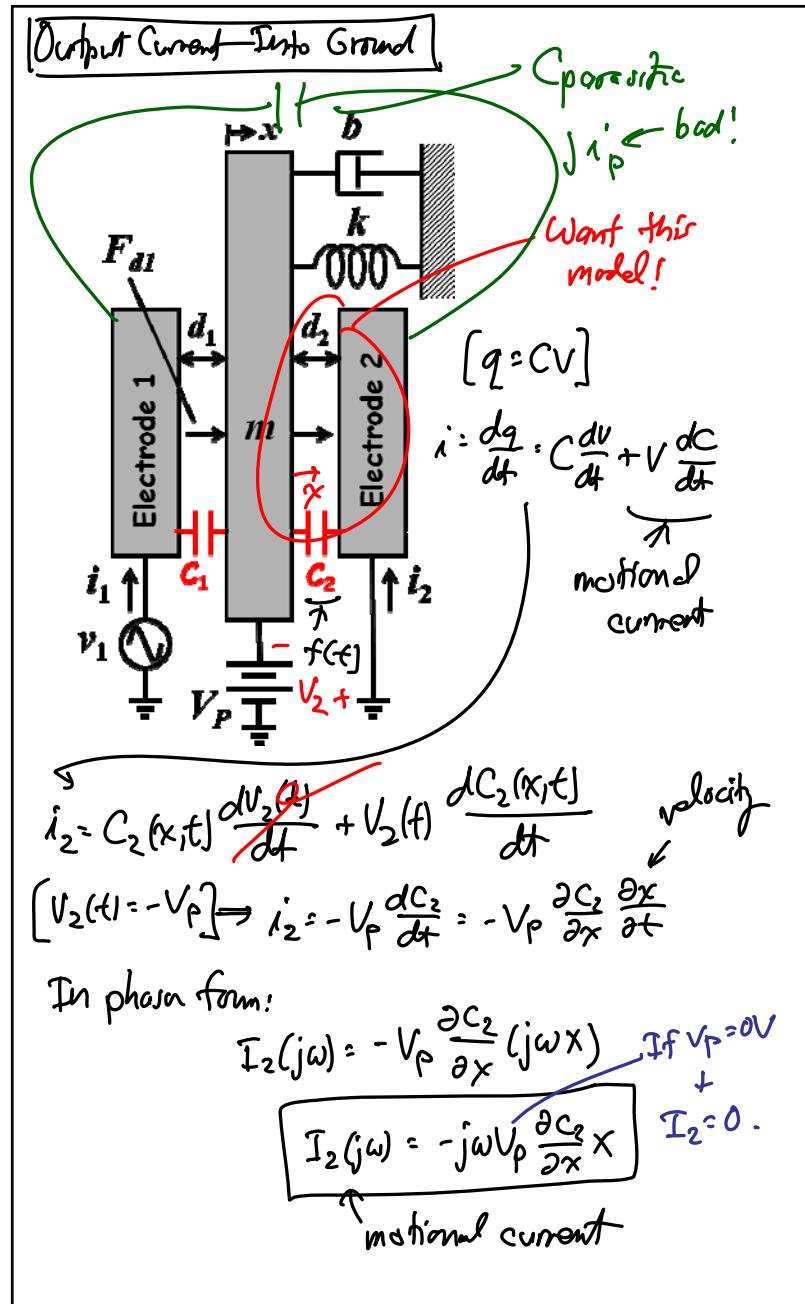Lecture 24w: Equivalent Circuits II

$$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X = -V_p \frac{\partial C_2}{\partial x} \dot{x}$$

$\pi$   
90° phase lag ( $\dot{x}$ )

$\eta_{e2}: 1$

$I_2 \leftarrow f_1$

$$f_2 = -\frac{1}{\eta_{e2}} f_1 \rightarrow f_1 = \eta_{e2} f_2$$

$$[f_1 = I_2, f_2 = \dot{x}] \Rightarrow I_2 = -\eta_{e2} \dot{x}$$


$\therefore \eta_{e2} = V_p \frac{\partial C_2}{\partial x}$

① resonances

~~X~~ ~~X~~ ~~X~~  
(left  $\omega / R$ )

## Lecture 24w: Equivalent Circuits II

Input Current Expression

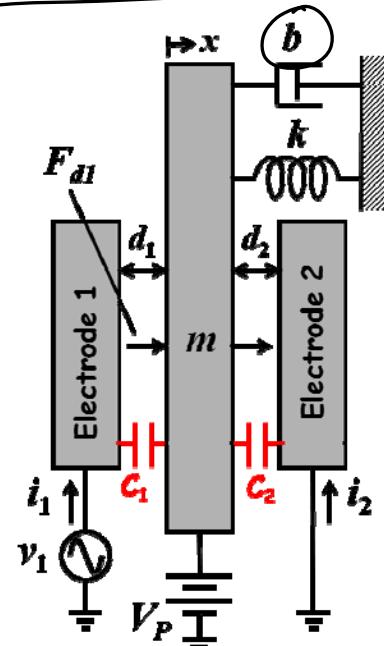

Get  $i_1(j\omega)$ :

$$i_1(t) = C_1(x, t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC_1(x, t)}{dt}$$

$$\left[ V_1(t) = V_i - V_p \right] \Rightarrow i_1 = C_1 \frac{dV_i}{dt} + (V_i - V_p) \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$$\therefore I_1(j\omega) = j\omega C_1 V_i + j\omega V_i \frac{\partial C_1}{\partial x} X - j\omega V_p \frac{\partial C_1}{\partial x} X$$

*Feedthrough Current*      *Motional Current*

$$@ DC: x = \frac{F_d}{k} = -\frac{1}{k} V_p \frac{\partial C_1}{\partial x} V_i$$

$$@ resonance x = \frac{Q F_d}{j k} = -\frac{Q}{j k} V_p \frac{\partial C_1}{\partial x} V_i = X$$

↑  
90° phase lag

Then: @  $\omega_0$  (resonance)

$$\star \rightarrow I_1(j\omega) = j\omega_0 C_1 V_i + j\omega_0 \left( V_p \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{j k} V_i$$

$$= j\omega_0 C_1 V_i + \omega_0 \frac{Q}{k} \eta_{ei}^2 V_i$$

↓  
90° phase shifted from  $V_i$

In phase  $\omega V_i$

This is a capacitor in shunt w/ the input!

This is an effective resistance seen (load) into electrode 1!

