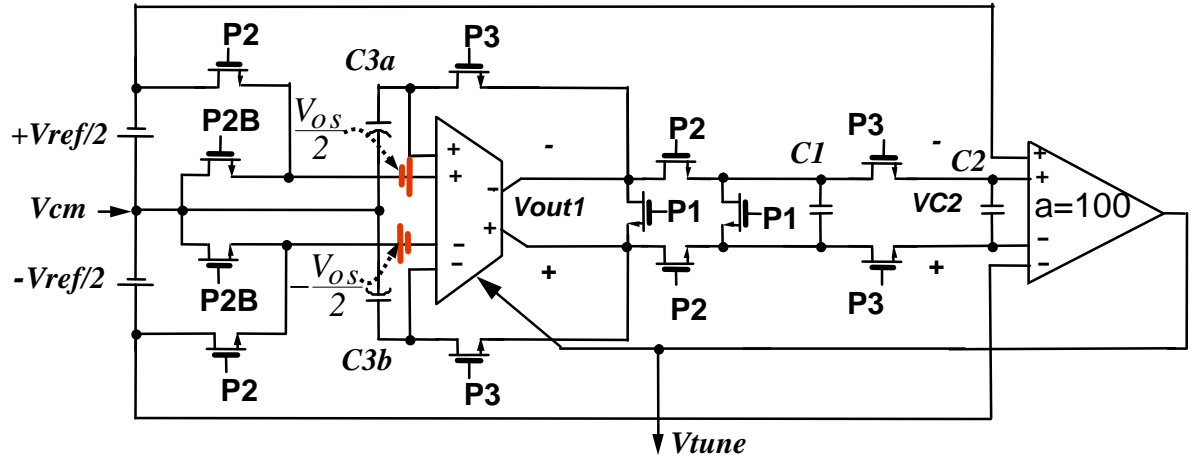


Solution to Homework #2 provided by Mr. Louis P. Alarcon



EE 247 Homework #2

Louis P. Alarcon

lalarcon@eecs.berkeley.edu

Problem #1:

Given parameters:

$$C_2 := 10\text{pF} \quad C_1 := \frac{C_2}{2} \quad C_1 = 5\text{pF} \quad V_{\text{ref}} := 0.5\text{V}$$

$$V_{\text{os}} := 10\text{mV} \quad T_2 := 100\text{ns}$$

$$G'_m(V_{\text{tune}}) := 40 \frac{\mu\text{A}}{\text{V}} + V_{\text{tune}} \cdot 20 \frac{\mu\text{A}}{\text{V}^2}$$

$$G'_{m_aux}(V_{\text{tune}}) := \frac{1}{8} \cdot G'_m(V_{\text{tune}})$$

$$a := 100$$

$$V_{\text{tunc}}(V_{\text{in}}) := \begin{cases} 0\text{V} & \text{if } V_{\text{in}} < 0\text{V} \\ 1\text{V} & \text{if } V_{\text{in}} > \frac{1\text{V}}{a} \\ a \cdot V_{\text{in}} & \text{otherwise} \end{cases}$$

For P3=1 (and P2B=1):

$$V_{c3} = -V_{\text{os}} \cdot \frac{G_m}{G_{m_aux}} = -8 \cdot V_{\text{os}} \quad V_{c3} := -8 \cdot V_{\text{os}} \quad V_{c3} = -80\text{mV}$$

$$V_{c2}^{\text{new}} = \frac{V_{c2}^{\text{prev}} \cdot C_2 + V_{c1} \cdot C_1}{C_1 + C_2}$$

For P1=1 (and P2B=1):

$$V_{c1} = 0$$

for P2=1 (and P2B=0):

$$V_{c1}(s) = \frac{1}{s \cdot C_1} \cdot \left[G_m \cdot (V_{\text{ref}} + V_{\text{os}}) + G_{m_aux} \cdot \left(-V_{\text{os}} \cdot \frac{G_m}{G_{m_aux}} \right) \right] = \frac{G_m \cdot V_{\text{ref}}}{s \cdot C_1}$$

$$V_{c1} = \frac{G_m}{C_1} \cdot \int_0^{T_2} V_{\text{ref}} dt = \frac{G_m}{C_1} \cdot V_{\text{ref}} \cdot T_2$$

For the first cycle:

$$\begin{aligned}V_{c2_0} &:= 0\text{ V} & V_{c2_0} &= 0\text{ V} \\V_{\text{tune}_0} &:= V_{\text{tune}}(V_{\text{ref}} - V_{c2_0}) & V_{\text{tune}_0} &= 1\text{ V} \\G_{m_0} &:= G_m(V_{\text{tune}_0}) & G_{m_0} &= 60 \frac{\mu\text{A}}{\text{V}} \\V_{c1_0} &:= \frac{G_{m_0}}{C_1} \cdot V_{\text{ref}} \cdot T_2 & V_{c1_0} &= 0.6\text{ V}\end{aligned}$$

For the second cycle:

$$\begin{aligned}V_{\text{tune}_1} &:= V_{\text{tune}}(V_{\text{ref}} - V_{c2_0}) & V_{\text{tune}_1} &= 1\text{ V} \\G_{m_1} &:= G_m(V_{\text{tune}_1}) & G_{m_1} &= 60 \frac{\mu\text{A}}{\text{V}} \\V_{c1_1} &:= \frac{G_{m_1}}{C_1} \cdot V_{\text{ref}} \cdot T_2 & V_{c1_1} &= 0.6\text{ V} \\V_{c2_1} &:= \frac{V_{c2_0} \cdot C_2 + V_{c1_1} \cdot C_1}{C_1 + C_2} & V_{c2_1} &= 0.2\text{ V}\end{aligned}$$

For the third cycle:

$$\begin{aligned}V_{\text{tune}_2} &:= V_{\text{tune}}(V_{\text{ref}} - V_{c2_1}) & V_{\text{tune}_2} &= 1\text{ V} \\G_{m_2} &:= G_m(V_{\text{tune}_2}) & G_{m_2} &= 60 \frac{\mu\text{A}}{\text{V}} \\V_{c1_2} &:= \frac{G_{m_2}}{C_1} \cdot V_{\text{ref}} \cdot T_2 & V_{c1_2} &= 0.6\text{ V} \\V_{c2_2} &:= \frac{V_{c2_1} \cdot C_2 + V_{c1_2} \cdot C_1}{C_1 + C_2} & V_{c2_2} &= 0.333\text{ V}\end{aligned}$$

For the fourth cycle:

$$V_{\text{tune}_3} := V_{\text{tune}}(V_{\text{ref}} - V_{c2_2}) \quad V_{\text{tune}_3} = 1 \text{ V}$$

$$G_{m_3} := G_m(V_{\text{tune}_3}) \quad G_{m_3} = 60 \frac{\mu\text{A}}{\text{V}}$$

$$V_{c1_3} := \frac{G_{m_3}}{C_1} \cdot V_{\text{ref}} \cdot T_2 \quad V_{c1_3} = 0.6 \text{ V}$$

$$V_{c2_3} := \frac{V_{c2_2} \cdot C_2 + V_{c1_3} \cdot C_1}{C_1 + C_2} \quad V_{c2_3} = 0.422 \text{ V}$$

During steady-state:

$$V_{c1} = V_{c2} = \frac{40 \cdot \frac{\mu\text{A}}{\text{V}} + V_{\text{tune_ss}} \cdot 20 \cdot \frac{\mu\text{A}}{\text{V}^2}}{C_1} \cdot V_{\text{ref}} \cdot T_2 = V_{\text{ref}} - \frac{V_{\text{tune_ss}}}{a}$$

$$V_{\text{tune_ss}} := 0.5 \text{ V}$$


Given

$$\frac{40 \cdot \frac{\mu\text{A}}{\text{V}} + V_{\text{tune_ss}} \cdot 20 \cdot \frac{\mu\text{A}}{\text{V}^2}}{C_1} \cdot V_{\text{ref}} \cdot T_2 = V_{\text{ref}} - \frac{V_{\text{tune_ss}}}{a}$$

$$V_{\text{tune_ss}} := \text{Find}(V_{\text{tune_ss}}) \quad V_{\text{tune_ss}} = 476.19 \text{ mV}$$

$$V_{c2_ss} := V_{\text{ref}} - \frac{V_{\text{tune_ss}}}{a} \quad V_{c2_ss} = 495.238 \text{ mV}$$
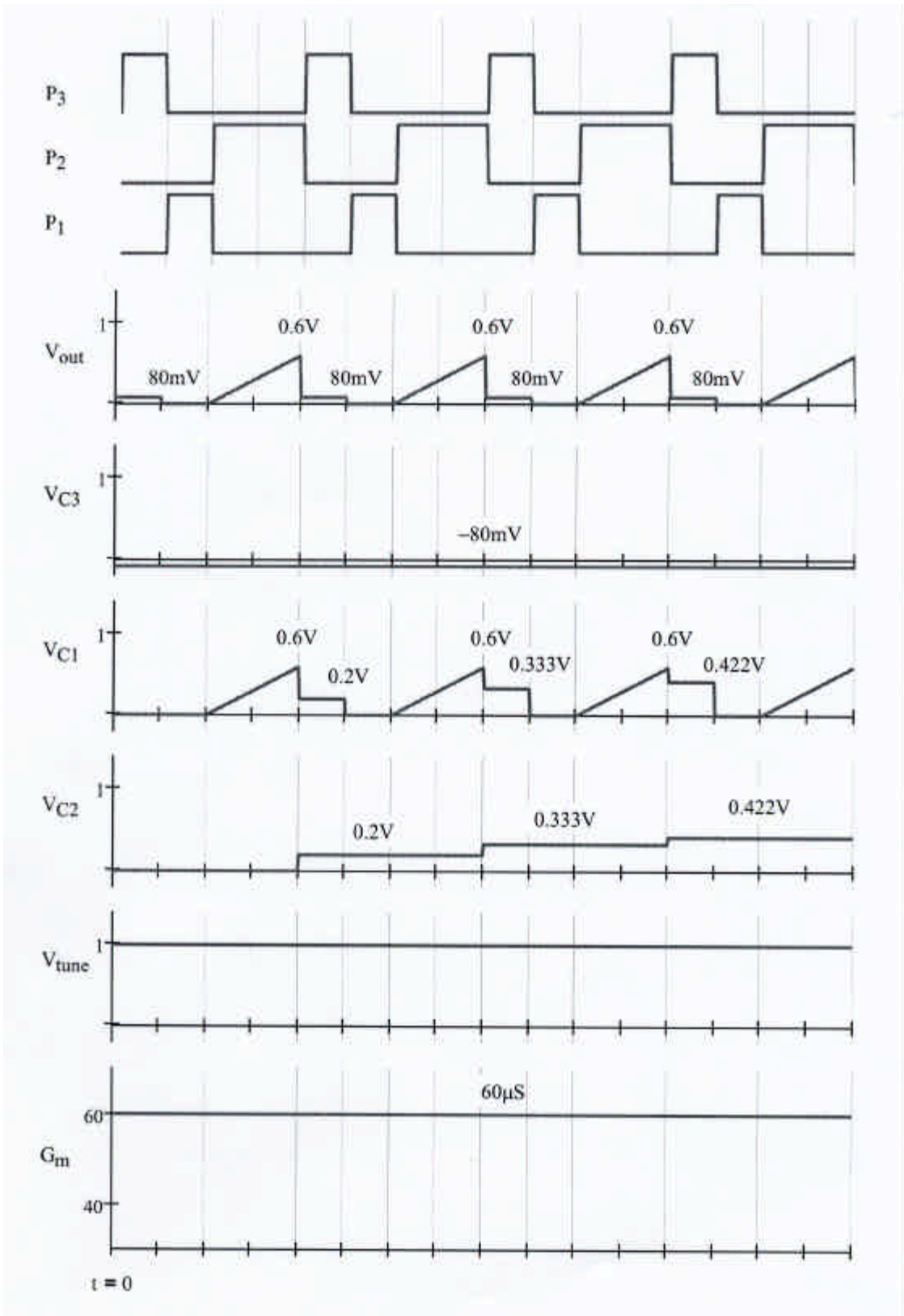
$$V_{c1_ss} := \frac{40 \cdot \frac{\mu\text{A}}{\text{V}} + V_{\text{tune_ss}} \cdot 20 \cdot \frac{\mu\text{A}}{\text{V}^2}}{C_1} \cdot V_{\text{ref}} \cdot T_2 \quad V_{c1_ss} = 495.238 \text{ mV}$$



Comment for problem 1 by H.K.:

For simplicity, a lowpass filter typically used at the output of the Vtune generating amplifier was deleted. Thus, if you attempted simulating the circuit, it should be oscillating after a few cycles!

Also, in practice C2 is chosen to be much larger than C1. This helps generate a cleaner Vtune and also stabilizes the circuit.

Problem 2:

Problem #2:

Transistors Q3 and Q4 provide a means to control the drain-to-source voltages of Q1 and Q2. Since transistors Q1 and Q2 are in the triode region, their transconductances are dependent on their respective drain-to-source voltages.

The amplifiers are added to provide the proper gate bias on Q3 and Q4, using negative feedback, to force the drain-to-source voltages of Q1 and Q2 to be equal to V_c . Thus, the transconductances of Q1 and Q2 are dependent on the control voltage V_c .

Given parameters:

$$k' := 100 \frac{\mu\text{A}}{\text{V}^2} \quad W := 10\mu\text{m} \quad L := 1\mu\text{m} \quad V_{th} := 0.5\text{V} \quad V_{cm} := 1\text{V}$$

For transistors in triode, we can find the transconductance as:

$$I_d = k' \cdot \frac{W}{L} \cdot \left[(V_{gs} - V_{th}) \cdot V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$$g_m = \frac{\partial}{\partial V_{gs}} I_d = k' \cdot \frac{W}{L} \cdot V_{ds} \quad g_m(V_c) := k' \cdot \frac{W}{L} \cdot V_c$$

$$g_m(0.2\text{V}) = 0.2\text{mS}$$

$$g_m(0.4\text{V}) = 0.4\text{mS}$$

The unity gain frequency of the integrator can be expressed as:

$$C_{int} := 10\text{pF}$$

$$\omega_u(V_c) := \frac{g_m(V_c)}{2 \cdot C_{int}} \quad f_u(V_c) := \frac{\omega_u(V_c)}{2 \cdot \pi}$$

$$f_u(0.2\text{V}) = 1.592\text{MHz}$$

$$f_u(0.4\text{V}) = 3.183\text{MHz}$$

When $V_i=0$, we can express the drain currents of Q1 and Q2 as:

$$I_d(V_c) := k' \cdot \frac{W}{L} \cdot \left[(V_{cm} - V_{th}) \cdot V_c - \frac{V_c^2}{2} \right]$$

$$I_d(0.2\text{V}) = 80\mu\text{A}$$

$$I_d(0.4\text{V}) = 120\mu\text{A}$$

