

EE247 Lecture 9


- Switched-Capacitor Filters
 - “Analog” sampled-data filters:
 - Continuous amplitude
 - Quantized time
 - Applications:
 - First commercial product: Intel 2912 voice-band CODEC chip, 1979
 - Oversampled A/D and D/A converters
 - Stand-alone filters
E.g. National Semiconductor LMF100

Switched-Capacitor Filters Today

- Emulating resistor via switched-capacitor network
- 1st order switched-capacitor filter
- Switch-capacitor filter considerations:
 - Issue of aliasing and how to avoid it
 - Tradeoffs in choosing sampling rate
 - Effect of sample and hold
 - Switched-capacitor filter electronic noise
 - Switched-capacitor integrator topologies

Switched-Capacitor Resistor

 - Capacitor C is the “switched capacitor”
- Non-overlapping clocks ϕ_1 and ϕ_2 control switches S1 and S2, respectively
- v_{IN} is sampled at the falling edge of ϕ_1
 - Sampling frequency f_s
- Next, ϕ_2 rises and the voltage across C is transferred to v_{OUT}
- Why does this behave as a resistor?



Switched-Capacitor Resistors

- Charge transferred from v_{IN} to v_{OUT} during each clock cycle is:


$$Q = C(v_{IN} - v_{OUT})$$

- Average current flowing from v_{IN} to v_{OUT} is:

$$i = Q/t = Q \cdot f_s$$

Substituting for Q :

$$i = f_s C(v_{IN} - v_{OUT})$$

 

Switched-Capacitor Resistors

$$i = f_s C (v_{IN} - v_{OUT})$$


With the current through the switched-capacitor resistor proportional to the voltage across it, the equivalent "switched capacitor resistance" is:

$$R_{eq} = \frac{1}{f_s C}$$

 Example:

$$f_s = 1\text{MHz}, C = 1\text{pF}$$

$$\rightarrow R_{eq} = 1\text{Mega}\Omega$$




Switched-Capacitor Filter


- Let's build a "switched-capacitor" filter ...
- Start with a simple RC LPF
- Replace the physical resistor by an equivalent switched-capacitor resistor
- 3-dB bandwidth:

$$\omega_{-3dB} = \frac{1}{R_{eq} C_2} = f_s \times \frac{C_1}{C_2}$$
 
$$f_{-3dB} = \frac{1}{2p} f_s \times \frac{C_1}{C_2}$$




 Switched-Capacitor Filters Advantage versus Continuous-Time Filters



$$f_{-3dB} = \frac{1}{2p} f_s \times \frac{C_1}{C_2}$$

 - Corner freq. proportional to: System clock (accurate to few ppm)
- C ratio accurate $\rightarrow < 0.1\%$




$$f_{-3dB} = \frac{1}{2p} \times \frac{1}{R_{eq} C_2}$$

- Corner freq. proportional to: Absolute value of Rs & Cs
- Poor accuracy $\rightarrow 20$ to 50%

→ Main advantage of SC filters \rightarrow inherent corner frequency accuracy

Typical Sampling Process

 Continuous-Time(CT) \Rightarrow Sampled Data (SD)




Uniform Sampling


Nomenclature:

Continuous time signal $x(t)$
 Sampling interval T
 Sampling frequency $f_s = 1/T$
 Sampled signal $x(kT) = x(k)$

 
- Problem: Multiple continuous time signals can yield exactly the same discrete time signal
- Let's look at samples taken at $1\mu\text{s}$ intervals of several sinusoidal waveforms ...




Sampling Sine Waves

 

Sampling Sine Waves

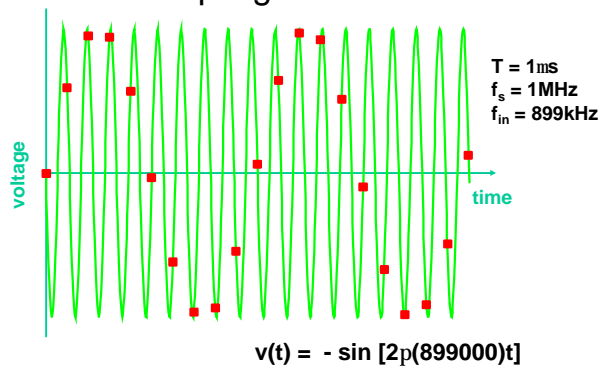

Sampling Sine Waves

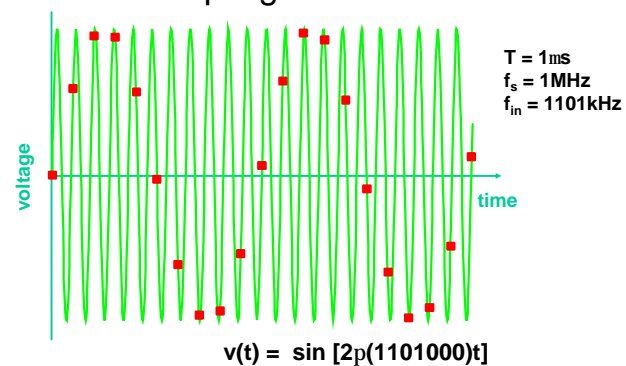

Sampling Sine Waves

Problem:

Identical samples for:



$$v(t) = \sin [2\pi f_{in} t]$$

$$v(t) = \sin [2\pi (f_{in} + f_s) t]$$

$$v(t) = \sin [2\pi (f_{in} - f_s) t]$$


→ Multiple continuous time signals can yield exactly the same discrete time signal

Sampling Sine Waves Frequency Spectrum

  


Frequency Domain Interpretation

Signal scenario
before sampling →

 

 Signal scenario
after sampling &
filtering →



Key point: Signals @ $nf_s \pm f_{max_signal}$ fold back into band of interest
→ Aliasing

Aliasing

- Multiple continuous time signals can produce identical series of samples
- The folding back of signals from $nf_s \pm f_{sig}$ down to f_{in} is called aliasing
 - Sampling theorem: $f_s > 2f_{max_Signal}$
- If aliasing occurs, no signal processing operation downstream of the sampling process can recover the original continuous time signal

How to Avoid Aliasing?


- Must obey sampling theorem:

$$f_{max_Signal} < f_s/2$$


- Two possibilities:
 1. Sample fast enough to cover all spectral components, including "parasitic" ones outside band of interest
 2. Limit f_{max_Signal} through filtering

How to Avoid Aliasing?

 
- 1- Push sampling frequency to x2 of the highest freq.
→ In most cases not practical



 - 2- Pre-filter signal to eliminate signals above $f_s/2$ then sample




Anti-Aliasing Filter Considerations

 

Case1 - $B = f_{max_Signal} = f_s/2$

- Non-practical since an extremely high order anti-aliasing filter (close to an ideal brickwall filter) is required
- Practical anti-aliasing filter → Nonzero filter "transition band"
- In order to make this work, we need to sample much faster than 2x the signal bandwidth
→ "Oversampling"


Practical Anti-Aliasing Filter

 

Case2 - $B = f_{max_Signal} \ll f_s/2$

- More practical anti-aliasing filter
- Preferable to have an anti-aliasing filter with:
 - The lowest order possible
 - No frequency tuning required (if frequency tuning is required then why use switched-capacitor filter, just use the prefilter!?)

 Tradeoff Oversampling Ratio versus Anti-Aliasing Filter Order




* Assumption → anti-aliasing filter is Butterworth type (not a necessary requirement)

→ Tradeoff: Sampling speed versus anti-aliasing filter order

Ref: R. v. d. Plassche, CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters, 2nd ed., Kluwer publishing, 2003, p.41


Effect of Sample & Hold

 


• Using the Fourier transform of a rectangular impulse:

$$|H(f)| = \frac{T_p}{T_s} \frac{\sin(pfT_p)}{pfT_p}$$

 
Effect of Sample & Hold on Frequency Response



 Sample & Hold Effect (Reconstruction of Analog Signals)




Magnitude drop due to $\sin x/x$ effect

 


Sample & Hold Effect (Reconstruction of Analog Signals)

Magnitude droop due to $\sin x/x$ effect:

Case 1) $f_{sig} = f_s/4$

 


Droop = -1dB

 

Sample & Hold Effect (Reconstruction of Analog Signals)


Magnitude droop due to $\sin x/x$ effect:

Case 2)
 $f_{sig} = f_s/32$

 


Droop = -0.0035dB

→ **High oversampling ratio desirable**

 

Sampling Process Including S/H

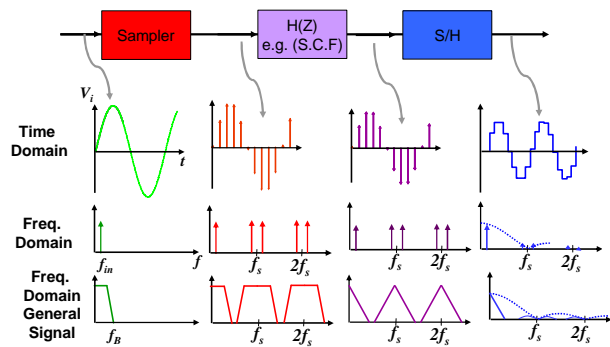


1st Order Filter Transient Analysis

1st Order RC / SC LPF

$b = 20\text{dB}$

$f_c = 50\text{Hz}$

$f_s = 1575\text{Hz}$

 


Transient Analysis to 200ns


Impractical

exaggerated

No problem

 


1st Order Filter Transient Analysis

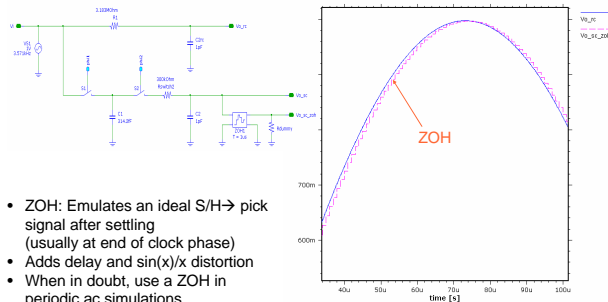


- ZOH: Emulates an ideal S/H → pick signal after settling (usually at end of clock phase)
- Adds delay and $\sin(x)/x$ distortion
- When in doubt, use a ZOH in periodic ac simulations

Periodic AC Analysis

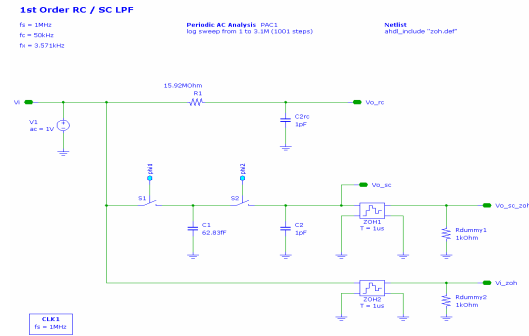

Magnitude Response

 

1. RC filter output
2. SC output after ZOH
3. Input after ZOH
4. Corrected output
 - (2) over (3)
 - Repeats filter shape around πf_s
 - Identical to RC for $f \ll f_s/2$

Periodic AC Analysis

- SPICE frequency analysis
 - ac linear, **time-invariant** circuits
 - pac linear, **time-variant** circuits
- SpectreRF statements


```
V1 ( Vi 0 ) vsource type=dc dc=0 mag=1 pacmag=1
PSS1 pss period=1u errpreset=conservative
PAC1 pac start=1 stop=1M lin=1001
```
- Output
 - Divide results by $\text{sinc}(f/f_s)$ to correct for ZOH distortion

Spectre Circuit File

```
rc_pac
simulator lang=spectre
ahdl_include "zoh.def"

S1 ( Vi c1 phi1 0 ) relay ropen=100G rclosed=1 vt1=-500m vt2=500m
S2 ( c1 Vo_sc phi2 0 ) relay ropen=100G rclosed=1 vt1=-500m vt2=500m
C1 ( c1 0 ) capacitor c=314.159f
C2 ( Vo_sc 0 ) capacitor c=1p
R1 ( Vi Vo_rc ) resistor r=3.1831M
C2rc ( Vo_rc 0 ) capacitor c=1p
CLK1_Vphil ( phi1 0 ) vsource type=pulse val0=-1 vall=1 period=1u
width=450n delay=50n rise=10n fall=10n
CLK1_Vphi2 ( phi2 0 ) vsource type=pulse val0=-1 vall=1 period=1u
width=450n delay=550n rise=10n fall=10n
V1 ( Vi 0 ) vsource type=dc dc=0 mag=1 pacmag=1
PSS1 pss period=1u errpreset=conservative
PAC1 pac start=1 stop=3.1M log=1001
ZOH1 ( Vo_sc_zoh 0 Vo_sc 0 ) zoh period=1u delay=500n aperture=1n tc=10p
ZOH2 ( Vi_zoh 0 Vi 0 ) zoh period=1u delay=0 aperture=1n tc=10p
```

ZOH Circuit File

```
// Copy from the SpectreRF Primer


module zoh (Pout, Nout, Pin, Nin) (period,
    delay, aperture, tc)
// Implement switch with effective series
// resistance of 1 Ohm
if ( ($time() > start) && ($time() <= stop))
    I(hold) <- V(hold) - V(Pin, Nin);
else
    I(hold) <- 1.0e-12 * (V(hold) - V(Pin, Nin));
// Implement capacitor with an effective
// capacitance of tc
I(hold) <- tc * dot(V(hold));

node [V,I] hold;
// Buffer output
V(Pout, Nout) <- V(hold);

// determine the point when aperture
// begins
n = ($time() - delay + aperture) / period
+ 0.5;
start = n*period + delay - aperture;
$break_point(start);
// determine the time when aperture ends
n = ($time() - delay) / period + 0.5;
stop = n*period + delay;
$break_point(stop);

// Control time step tightly during
// aperture and loosely otherwise
if (($time() >= start) && ($time() <= stop))
    $bound_step(tc);
else
    $bound_step(period/5);
endmodule
```

First Order S.C. Filter

 


Switched-Capacitor Filters → problem with aliasing

Sampled-Data Filters Anti-aliasing Requirements

- Frequency response repeats at f_s , $2f_s$, $3f_s$, ...
- High frequency signals close to f_s , $2f_s$, ... folds back into passband (aliasing)
- Most cases must pre-filter input to a sampled-data filter to remove signal at $f > f_s/2$ (Nyquist $\rightarrow f_{max} < f_s/2$)
- Usually, anti-aliasing filter included on-chip as continuous-time filter with relaxed specs. (no tuning)

 
Example : Anti-Aliasing Filter Requirements



- Voice-band SC filter $f_{-3dB} = 4kHz$ & $f_s = 256kHz$
- Anti-aliasing filter requirements:
 - Need 40dB attenuation at clock frequency
 - Incur no phase-error from 0 to 4kHz
 - Gain error 0 to 4kHz < 0.05dB
 - Allow +30% variation for anti-aliasing corner frequency (no tuning)

Need to find minimum required filter order

 Oversampling Ratio versus Anti-Aliasing Filter Order




* Assumption → anti-aliasing filter is Butterworth type

→ 2nd order Butterworth

→ Need to find minimum corner frequency for mag. droop < 0.05dB

 
Example : Anti-Aliasing Filter Specifications

- Normalized frequency for 0.05dB droop: need perform passband simulation → $0.34 \rightarrow 4kHz/0.34 = 12kHz$
- Set anti-aliasing filter corner frequency for minimum corner frequency 12kHz → Nominal corner frequency $12kHz/0.7 = 17.1kHz$
- Check if attenuation requirement is satisfied for widest filter bandwidth → $17.1 \times 1.3 = 22.28kHz$
- Normalized filter clock frequency to max. corner freq. → $256/22.2 = 11.48 \rightarrow$ make sure enough attenuation
- Check phase-error within 4kHz bandwidth: simulation



From: Williams and Taylor, p. 2-37

Example : Anti-Aliasing Filter

 


- Voice-band SC filter $f_{-3dB} = 4kHz$ & $f_s = 256kHz$
 - Anti-aliasing filter requirements:
 - Need 40dB attenuation at clock freq.
 - Incur no phase-error from 0 to 4kHz
 - Gain error 0 to 4kHz < 0.05dB
 - Allow +30% variation for anti-aliasing corner frequency (no tuning)
- 2-pole Butterworth LPF with nominal corner freq. of 17kHz & no tuning (12kHz to 22kHz corner frequency)

Summary

- Sampling theorem $\rightarrow f_s > 2f_{max_Signal}$
- Signals at frequencies $n f_s \pm f_{sig}$ fold back down to desired signal band, f_{sig}
 - \rightarrow This is called aliasing & usually dictates use of anti-aliasing pre-filters
- Oversampling helps reduce required order for anti-aliasing filter
- S/H function shapes the frequency response with $\frac{\sin x}{x}$
 - \rightarrow Need to pay attention to droop in passband due to $\frac{\sin x}{x}$
- If the above requirements are not met, CT signal can NOT be recovered from SD or DT without loss of information


Switched-Capacitor Noise

 - Resistance of switch S1 produces a noise voltage on C with variance kT/C
- The corresponding noise charge is $Q^2 = C^2 V^2 = kTC$
- This charge is sampled when S₁ opens



Switched-Capacitor Noise

 - Resistance of switch S2 contributes to an uncorrelated noise charge on C at the end of ϕ_2
- Mean-squared noise charge transferred from v_{IN} to v_{OUT} each sample period is $Q^2 = 2kTC$



Switched-Capacitor Noise

- The mean-squared noise current due to S1 and S2's kT/C noise is :

$$\overline{i^2} = (Qf_s)^2 = 2k_B T C f_s^2$$


- This noise is approximately white and distributed between 0 and $f_s/2$ (noise spectra \rightarrow single sided by convention)
The spectral density of the noise is:

$$\frac{\overline{i^2}}{\Delta f} = \frac{2k_B T C f_s^2}{f_s/2} = 4k_B T C f_s = \frac{4k_B T}{R_{EQ}} \quad \text{using} \quad R_{EQ} = \frac{1}{f_s C}$$

\rightarrow **S.C. resistor noise equals a physical resistor noise with same value!**

Periodic Noise Analysis


Sampling Noise from SC S/H

 

SpectreRF PNOISE: check
noisetype=timedomain
noisetimepoints=[...]
as alternative to ZOH.
noiseskipcount=large
might speed up things in this case.

PSS pss period=100n maxacfreq=1.5G errpreset=conservative
PNOISE (Vrc_hold 0) pnoise start=0 stop=20M lin=500 maxsideband=10


Sampled Noise Spectrum

 

Density of sampled noise
including sinc distortion

Sampled noise normalized
density corrected for sinc
distortion



Total Noise

 

Sampled noise in
0 ... $f_s/2$: $62.2\mu\text{V rms}$

(expect $64\mu\text{V}$ for 1pF)

Switched-Capacitor Integrator

  


for $f_{\text{signal}} \ll f_{\text{sampling}}$

$$\rightarrow V_0 = \frac{f_s \times C_s}{C_f} \int v_{in} dt$$

$$w_0 = f_s \times \frac{C_s}{C_f}$$

Main advantage: No tuning needed
→ critical frequency function of ratio of caps & clock freq.

Switched-Capacitor Integrator

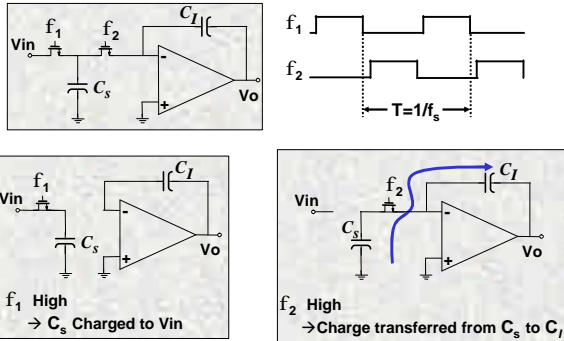

Continuous-Time versus Discrete Time Design Flow

Continuous-Time

- Write differential equation
- Laplace transform (F(s))
- Let $s=j\omega \rightarrow F(j\omega)$
- Plot $|F(j\omega)|$, phase(F(j ω))

Discrete-Time

- Write difference equation \rightarrow relates output sequence to input sequence

$$V_o(nT_s) = V_i[(n-1)T_s] - \dots$$


- Use delay operator Z^{-1} to transform the recursive realization to algebraic equation in Z domain

$$V_o(Z) = Z^{-1}V_i(Z) \dots$$


- Set $Z = e^{j\omega T}$

- Plot mag./phase versus frequency

Switched-Capacitor Integrator

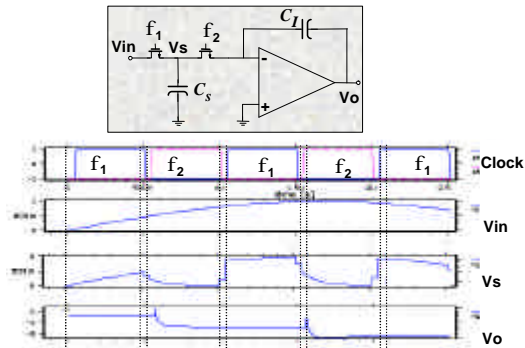

Switched-Capacitor Integrator

 

$$\Phi_1 \rightarrow Q_s[(n-1)T_s] = C_s V_i[(n-1)T_s], \quad Q_f[(n-1)T_s] = Q_f[(n-3/2)T_s]$$

$$\Phi_2 \rightarrow Q_s[(n-1/2)T_s] = 0, \quad Q_f[(n-1/2)T_s] = Q_f[(n-1)T_s] + Q_s[(n-1)T_s]$$

$$\Phi_1 \rightarrow Q_s[nT_s] = C_s V_i[nT_s], \quad Q_f[nT_s] = Q_f[(n-1)T_s] + Q_s[(n-1)T_s]$$


$$\text{Since } V_o = -Q_f/C_f \text{ \& } V_i = Q_s/C_s \rightarrow C_f V_o(nT_s) = C_f V_o[(n-1)T_s] - C_s V_i[(n-1)T_s]$$

Discrete Time Design Flow

- Transforming the recursive realization to algebraic equation in Z domain:
 - Use Delay operator Z :

$$\begin{aligned}
 nT_s &\dots\dots\dots \rightarrow 1 \\
 [(n-1)T_s] &\dots\dots\dots \rightarrow Z^{-1} \\
 [(n-1/2)T_s] &\dots\dots\dots \rightarrow Z^{-1/2} \\
 [(n+1)T_s] &\dots\dots\dots \rightarrow Z^{+1} \\
 [(n+1/2)T_s] &\dots\dots\dots \rightarrow Z^{+1/2}
 \end{aligned}$$

Switched-Capacitor Integrator

 

$$\begin{aligned}
 -C_I V_o(nT_s) &= -C_I V_o[(n-1)T_s] + C_S V_{in}[(n-1)T_s] \\
 V_o(nT_s) &= V_o[(n-1)T_s] - \frac{C_S}{C_I} V_{in}[(n-1)T_s] \\
 V_o(Z) &= Z^{-1} V_o(Z) - Z^{-1} \frac{C_S}{C_I} V_{in}(Z)
 \end{aligned}$$

$$\frac{V_o(Z)}{V_{in}(Z)} = -\frac{C_S}{C_I} \times \frac{Z^{-1}}{1-Z^{-1}}$$

DDI (Direct-Transform Discrete Integrator)

z-Plane Characteristics

- Consider variable $Z=e^{sT}$ for any s in left-half-plane (LHP):

$$S = -a + jb$$

$$Z = e^{-aT} \cdot e^{jbT} = e^{-aT} (\cos bT + j \sin bT)$$

$$|Z| = e^{-aT}, \text{ angle}(Z) = bT$$


→ For values of S in LHP $|Z| < 1$

→ For $a = 0$ (imag. axis in s-plane) $|Z| = 1$ (unit circle)
if $\text{angle}(Z) = \pi = bT$ then $b = \pi/T = \omega$

Then $\omega = \omega_s/2$


z-Domain Frequency Response

 - LHP singularities in s-plane map into inside of unit-circle in Z domain
- RHP singularities in s-plane map into outside of unit-circle in Z domain
- The $j\omega$ axis maps onto the unit circle




z-Domain Frequency Response

 - Particular values:
 - $f = 0 \rightarrow z = 1$
 - $f = f_s/2 \rightarrow z = -1$
- The frequency response is obtained by evaluating $H(z)$ on the unit circle at $z = e^{j\omega T} = \cos(\omega T) + j\sin(\omega T)$
- Once $z=1$ ($f_s/2$) is reached, the frequency response repeats, as expected



z-Domain Frequency Response

 - The angle to the pole is equal to 360° (or 2π radians) times the ratio of the pole frequency to the sampling frequency




DDI Integrator Pole-Zero Map in z-Plane

$Z-1=0 \rightarrow Z=1$
on unit circle


Pole from $f \rightarrow 0$
in s-plane mapped to
 $z=+1$

As frequency increases z domain pole moves on unit circle (CCW)

 Once pole gets to ($Z=-1$), ($f=f_s/2$), frequency response repeats



DDI Switched-Capacitor Integrator

 

$$\frac{V_o(z)}{V_{in}} = -\frac{C_s}{C_I} \times \frac{z^{-1}}{1-z^{-1}}$$

$$\frac{V_o(z)}{V_{in}} = -\frac{C_s}{C_I} \times \frac{1}{Z-1}, \quad Z = e^{j\omega T}$$

$$= -\frac{C_s}{C_I} \times \frac{1}{e^{j\omega T} - 1}$$

Series expansion for e^x

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} \dots$$

$$\frac{V_o(\omega)}{V_{in}} = -\frac{C_s}{C_I} \times \frac{1}{\left[1 + j\omega T + \frac{(j\omega T)^2}{2!} + \frac{(j\omega T)^3}{3!} + \dots\right] - 1}$$

$$= -\frac{C_s}{C_I} \times \frac{1}{j\omega T - \frac{(j\omega T)^2}{2!} + \frac{(j\omega T)^3}{3!} + \dots}$$

for $\omega T \ll 1$

$$\frac{V_o(\omega)}{V_{in}} = -\frac{C_s}{C_I} \times \frac{1}{j\omega T}$$

Since $T = 1/f_s$

$$\frac{V_o(\omega)}{V_{in}} = -\frac{C_s}{C_I} \times \frac{f_s}{s} = -\frac{1}{C_I R_{eq} s}$$

\rightarrow ideal integrator