

UC Berkeley

EE C247B - ME C218 Introduction to MEMS Design Spring 2014

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences
 University of California at Berkeley
 Berkeley, CA 94720

Lecture Module 13: Equivalent Circuits II

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 1

UC Berkeley

Lecture Outline

- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
 - ↪ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↪ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↪ Impedance & Transfer Functions

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 2

UC Berkeley

Input Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 3

UC Berkeley

Electromechanical Analogies

$F(t) = F \cos(\omega t) \rightarrow x(t) = X \cos \omega t$
 Equation of Motion:
 $m_{eq} \ddot{x} + c_{eq} \dot{x} + k_{eq} x = F(t)$
 \Rightarrow using phasor concepts:
 $F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + c_{eq} \dot{x}$
 \Rightarrow by analogy:

$F \rightarrow N$ $m_{eq} \rightarrow l_x$ $c_{eq} \rightarrow r_x$
 $\dot{x} \rightarrow \dot{q}$ $k_{eq} \rightarrow \frac{1}{c_x}$ $\frac{1}{j\omega} \rightarrow \frac{1}{j\omega} i$

Impedance looking in:
 $\frac{N}{i} = j\omega l_x + \frac{1}{j\omega c_x} + r_x$
 $N = j\omega l_x i + \frac{(1/c_x)}{j\omega} i + r_x i$

Parameter Relationships in the Current Analogy

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 4

Bandpass Biquad Transfer Function

$$F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + C_{eq} \dot{x}$$

$$\Rightarrow \text{Converting to full phasor form:}$$

$$F = (j\omega)(j\omega x) m_{eq} + \frac{k_{eq}}{j\omega} (j\omega x) + C_{eq} (j\omega x)$$

$$\frac{X}{F}(j\omega) = \frac{1}{k_{eq}} \left[-\omega^2 \frac{m_{eq}}{k_{eq}} + 1 + j \frac{C_{eq}\omega}{k_{eq}} \right]^{-1} = \frac{1}{k_{eq}} \left[-\left(\frac{\omega}{\omega_0}\right)^2 + 1 + j \frac{\omega}{Q\omega_0} \right]^{-1}$$

$$\left[\frac{k_{eq}}{m_{eq}} = \omega_0^2, Q = \frac{m_{eq}\omega_0}{C_{eq}} = \frac{k_{eq}}{\omega_0 C_{eq}} \rightarrow \frac{k_{eq}}{C_{eq}} = Q\omega_0 \right]$$

$$\frac{X}{F}(j\omega) = \frac{k_{eq}^{-1}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j \frac{\omega}{Q\omega_0}}$$

$X = \frac{F}{k_{eq}}$
 $X = \frac{QF}{k_{eq}}$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 5

Force-to-Velocity Relationship

- The relationship between input voltage v_1 and force F_{d1} :

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1$$
- When displacement x is the mechanical output variable:

$$\frac{X(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_o^2}{s^2 + (\omega_o/Q)s + \omega_o^2}$$
- When velocity v is the mechanical output variable:

$$\frac{v(s)}{F_{d1}(s)} = \frac{sX(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_o^2 s}{s^2 + (\omega_o/Q)s + \omega_o^2}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 6

Force-to-Velocity Equiv. Ckt.

- Combine the previous lumped LCR mechanical equivalent circuit with a circuit modeling the capacitive transducer \rightarrow circuit model for voltage-to-velocity

Electrical: Voltage V , Current I
 Mechanical: Velocity $U = -\dot{x}$, Force F_{d1}

$I_x = m \dot{x}$
 $r_x = b$
 $c_x = 1/k$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 7

Equiv. Circuit for a Linear Transducer

- A transducer ...
 - converts energy from one domain (e.g., electrical) to another (e.g., mechanical)
 - has at least two ports
 - is not generally linear, but is virtually linear when operated with small signals (i.e., small displacements)

Electrical: Voltage V , Current I
 Mechanical: Velocity $U = -\dot{x}$, Force F

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 8

Equiv. Circuit for a Linear Transducer

Electrical | Mechanical

- For physical consistency, use a transformer equivalent circuit to model the energy conversion from the electrical domain to mechanical domain

$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix}$$

Describing Matrix

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 9

Electromechanical Equivalent Circuit

- $e_2 = F_{d1}$, $e_1 = v_1$, just need η_1 :
- From the matrix: $e_2 = \eta e_1$

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1 \rightarrow \eta_1 = \left| V_P \frac{\partial C_1}{\partial x} \right|$$

Electrical | Mechanical

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 10

Output Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 11

Output Current Into Ground

- When the mass moves with time-dependent displacement $x(t)$, the electrode-to-mass capacitors $C_1(x, t)$ and $C_2(x, t)$ vary with time
- This generates an output current:

$$[q = CV] \Rightarrow i = \frac{dq}{dt} = C \frac{\partial v}{\partial t} + v \frac{\partial C}{\partial t}$$

$$i_2(t) = C_2(x, t) \frac{dV_2(t)}{dt} + V_2(t) \frac{dC_2(x, t)}{dt}$$

$$[V_2(t) = -V_P] \Rightarrow i_2 = -V_P \frac{dC_2}{dt} = -V_P \frac{\partial C_2}{\partial x} \frac{\partial x}{\partial t}$$

In phasor form:

$$I_2(j\omega) = -j\omega V_P \frac{\partial C_2}{\partial x} X$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 12

Output Current Into Ground

$I_2(j\omega) = -j\omega V_P \frac{\partial C_2}{\partial x} X = -V_P \frac{\partial C_2}{\partial x} X$
 90° phase lag
 $(+)$ $(-)$ $\rightarrow I_2 = (-)$ when $x = (+)$ ✓
 • Again, model with a transformer:
 Velocity $\rightarrow U = \dot{x}$
 $\eta_2:1$ Current
 $f_2 = -\frac{1}{\eta_2} f_1 \rightarrow f_1 = -\eta_2 f_2$
 $[f_1 = I_2, f_2 = U] \Rightarrow I_2 = -\eta_2 U$
 $\therefore \eta_2 = \left| V_P \frac{\partial C_2}{\partial x} \right|$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 13

Input Current Expression

Get $I_1(j\omega)$:
 $i_1(t) = C_1(x,t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC_1(x,t)}{dt}$
 $[V_1(t) \cdot \eta_1 - V_P] \Rightarrow i_1 = C_1 \frac{dV_1}{dt} + [\eta_1 - V_P] \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$
 $\therefore I_1(j\omega) = C_1(j\omega V_1) + V_1 \frac{\partial C_1}{\partial x}(j\omega X) - V_P \frac{\partial C_1}{\partial x}(j\omega X)$
 $= j\omega C_1 V_1 + j\omega V_1 \frac{\partial C_1}{\partial x} X - j\omega V_P \frac{\partial C_1}{\partial x} X$
 $[V_1 \ll V_P] \Rightarrow I_1(j\omega) = j\omega C_1 V_1 - j\omega V_P \frac{\partial C_1}{\partial x} X$
 Feedthrough Current Motional Current (due to mass motion)
 $@ DC: X = \frac{F_{d1}}{k} = -\frac{1}{k} V_P \left(\frac{\partial C_1}{\partial x} \right) \eta_1$
 $@ resonance: X = \frac{Q F_{d1}}{jk} = -\frac{Q}{jk} V_P \frac{\partial C_1}{\partial x} \eta_1$
 $\approx 90^\circ$ phase lag

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 14

Input Current Expression (cont)

Thus: (@ resonance)
 $I_1(j\omega) = j\omega C_1 V_1 + j\omega V_P \left(\frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{jk} V_1$
 $= j\omega C_1 V_1 + \omega_0 \frac{Q}{k} \eta_1^2 V_1$
 90° phase-shifted from V_1
 This is a Capacitor in shunt w/ the input.
 In phase w/ V_1
 This is an effective resistance seen looking into Electrode 1
 Motional Resistance:
 $R_{x1} \frac{V_1}{I_1} = \frac{k}{\omega_0 Q \eta_1^2} = \frac{m\omega_0}{Q \eta_1^2} = \frac{b}{\eta_1^2} = R_{x1}$
 (The equivalent ckt. better get this right!)

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 15

Complete Electrical-Port Equiv. Circuit

Static electrode-to-mass overlap capacitance
 $l_x = m$
 $c_x = \frac{1}{k}$
 $r_x = \frac{b}{\eta_1^2} = \frac{4kT \eta_1}{\omega_0^2}$
 $\eta_{e1} = V_P \frac{\partial C_1}{\partial x} = V_P \frac{C_{o1}}{d_1}$
 $\eta_{e2} = V_P \frac{\partial C_2}{\partial x} = V_P \frac{C_{o2}}{d_2}$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 16