

Lecture 24w: Equiv. Ckts. IILecture 24: Equivalent Circuits II


- Announcements:
- Module 13 now online
- HW#6 due this Friday at 9 a.m.
-
- Equivalent Circuits II Lecture Topics:
 - Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - Impedance & Transfer Functions
-
- Last Time:
- Finished comb-drive
- Project Notes:


I want this table:

Parameter	Before Minimization	After Minimization
Power (mW)	100W	1mW

- Start Module 13 and go through slides 1-9

Input Electrical Equiv. Ckt.

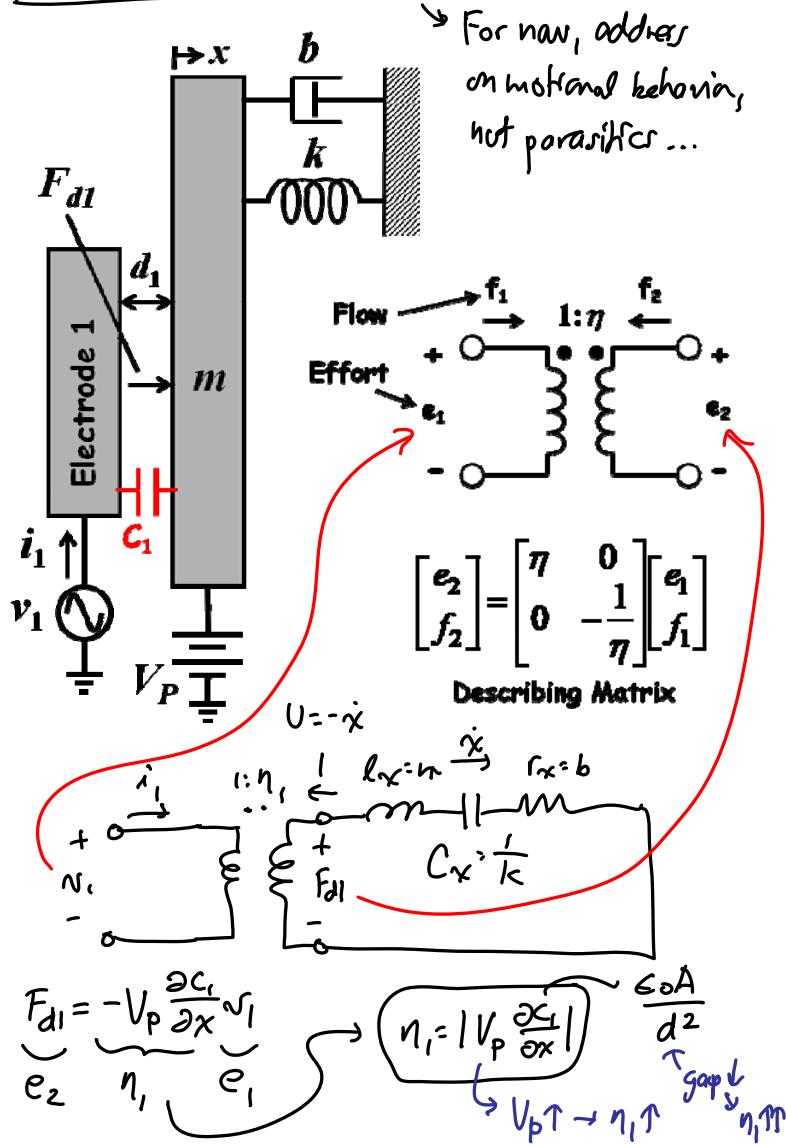

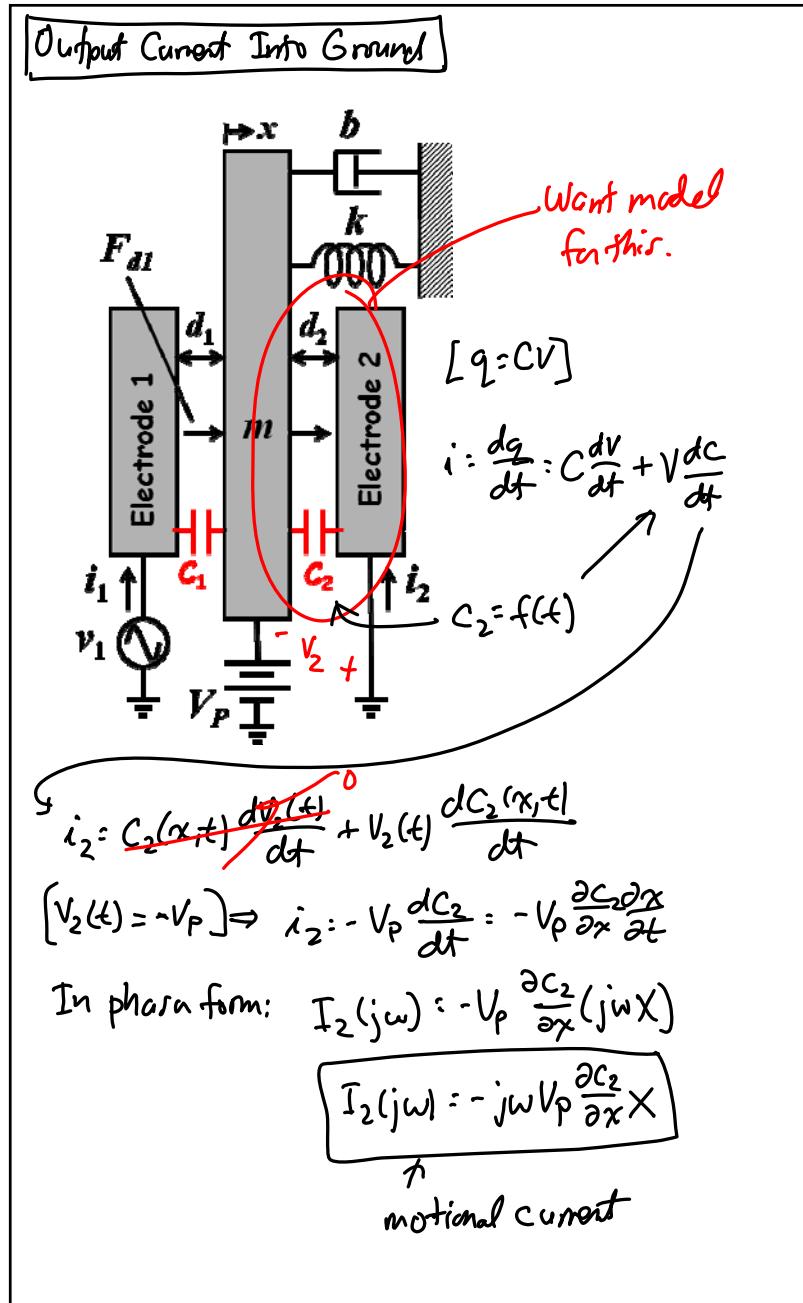Lecture 24w: Equiv. Ckts. II

$$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X = -V_p \frac{\partial C_2}{\partial x} \dot{x}$$


\uparrow \uparrow \uparrow
 90° phase lag (+) $\rightarrow I_2 = \frac{90^\circ \text{ lag}}{f_1}$ when $X = (+)$

$f_2 = -\frac{1}{Y_{21}} f_1 \rightarrow f_1 = -Y_{21} f_2$

$[f_1 = I_2, f_2 = \dot{x}] \Rightarrow I_2 = -Y_{21} \dot{x}$

$\therefore Y_{21} = |V_p \frac{\partial C_2}{\partial x}|$

Flow $\rightarrow f_1$ $1:\eta$ f_2
Effort $\rightarrow e_1$ e_2 $\left[\begin{matrix} e_2 \\ f_2 \end{matrix} \right] = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \left[\begin{matrix} e_1 \\ f_1 \end{matrix} \right]$
Describing Matrix

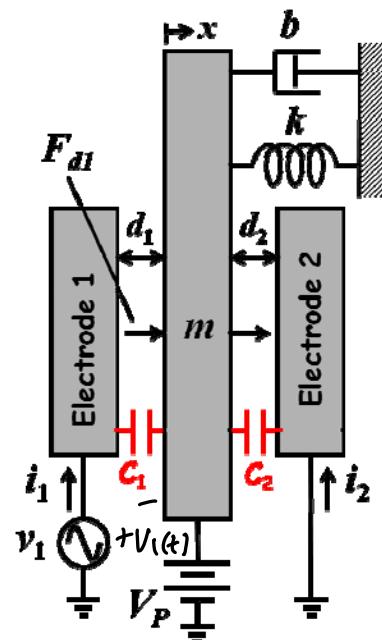Lecture 24w: Equiv. Ckts. IIInput Current ExpressionGet $I_1(j\omega)$:

$$i_1(t) = C_1(x_f) \frac{dV_i(t)}{dt} + V_i(t) \frac{dC_1(x_f)}{dt}$$

due to mass motion

$$[V_i(t) = N_i - V_p] \Rightarrow i_1 = C_1 \frac{dV_i}{dt} + [N_i - V_p] \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

low f(t)
case

$$\therefore I_1(j\omega) = j\omega C_1 V_i + j\omega N_i \frac{\partial C_1}{\partial x} X - j\omega V_p \frac{\partial C_1}{\partial x} X$$

negl. ($N_i \times$ term is small)

feedthrough Current

Motional Current

$$@ DC: x = \frac{F_d l}{K} = -\frac{1}{k} V_p \left(\frac{\partial C_1}{\partial x} \right) N_i$$

a@
low freq.

$$* @ resonance: x = \frac{Q F_d l}{j k} = -\frac{Q}{jk} V_p \frac{\partial C_1}{\partial x} N_i = X$$

$\rightarrow 90^\circ$ phase shift $N_i \rightarrow x$

Thru (@ resonance)

$$I_1(j\omega) = j\omega_0 C_1 V_i + j\omega_0 (V_p \frac{\partial C_1}{\partial x})^2 \frac{Q}{jk} N_i$$

$$= j\omega_0 C_1 V_i + \underbrace{\omega_0 \frac{Q}{k} \eta_{e1}^2 N_i}_{\text{ip}} \quad \text{In phase w/ } V_i.$$

ip

"electrical"

ix

ix


ip

ix

ix

\therefore this is an effective resistance seen "looking into electrode 1"

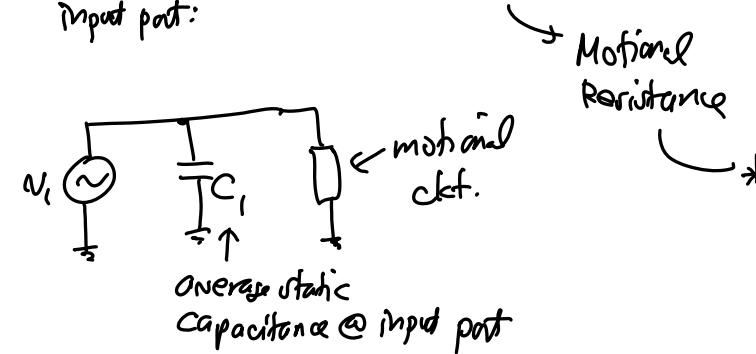This is a capacitor in shunt w/ the input port:



* Motional Resistance:

$$R_{X1} = \frac{V_1}{I_1} = \frac{k}{\omega_0 Q \eta_{e1}} = \frac{m \omega_0}{Q \eta_{e1}^2} = \boxed{\frac{b}{\eta_{e1}^2} = R_{X1}}$$

"motion"



The equivalent ckts better
get thru right!

$$\boxed{\frac{V_n^2}{\Delta f} = 4kTR_{X1}} \leftarrow \text{noise!}$$

- Look at Module 13, slide 16