

Lecture 26: Sensing Circuits I

- Announcements:
- Module 14 & 15 online
- HW#7 online since Friday last week
 - ↳ Due Friday, May 9
- Project Slide 3 due this Friday
- Project Outbrief Signups:
 - ↳ Now up on my door; sign up!
-
- Reading: Senturia, Chpt. 14, Chpt. 16, Chpt. 21
- Lecture Topics:
 - ↳ Gyroscopes
- Reading: Senturia, Chpt. 14
- Lecture Topics:
 - ↳ Detection Circuits
 - Velocity Sensing
 - Position Sensing
-
- Last Time:
- Going through Module 15 on Gyros
- Continue with this ... go through slides 11-16

over

Velocity to-Voltage Conversion

represent velocity

V_i V_P V_O R_D i_o cantilever

in phase w/ velocity
 $\frac{1}{2}$ 90° phase shift
 fl displacement

$\frac{|V_O|}{V_i}$ ω

$\omega_0 = \frac{Q F_d}{k}$
 $\omega_b = \frac{\omega_0 Q}{k}$

F_{d1} i_o x V_P output ground

$\frac{x}{F_{d1}}(s) = \frac{\omega_0 Q}{k} (H)(s)$


$[F_{d1} = \eta_{e1} V_i]$

$\frac{x}{V_i}(s) = \eta_{e1} \frac{\omega_0 Q}{k} (H)(s)$

$[i_o = \eta_{e2} x] \Rightarrow \frac{i_o}{V_i}(s) = \eta_{e1} \eta_{e2} \frac{\omega_0 Q}{k} (H)(s)$

$\frac{1}{R \times I_2} = \frac{\eta_{e1} \eta_{e2} Q}{m \omega_0} (H)(s)$

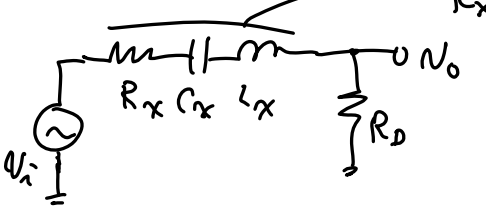Now, include R_D : $Q = \frac{\omega_0 L_x}{R_x}$



$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x + \frac{1}{sC_x} + sL_x} = \dots \text{math} \dots$$

$$= \frac{R_D}{R_D + R_x} \frac{s \left(\frac{R_x + R_D}{L_x} \right)}{s^2 + s \left(\frac{R_x + R_D}{L_x} \right) + \frac{1}{L_x C_x}}$$

Gain Term Freq. Shaping Term


$$\left[Q \cdot \frac{\omega_0 L_x}{R_x} \rightarrow Q' = \frac{\omega_0 L_x}{R_x + R_D} \rightarrow \frac{R_x + R_D}{L_x} = \frac{\omega_0}{Q'} \right]$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \frac{s(\omega_0/Q')}{s^2 + s(\omega_0/Q') + \omega_0^2}$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \cdot \mathcal{H}(s, Q')$$

$Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$


proportional to velocity

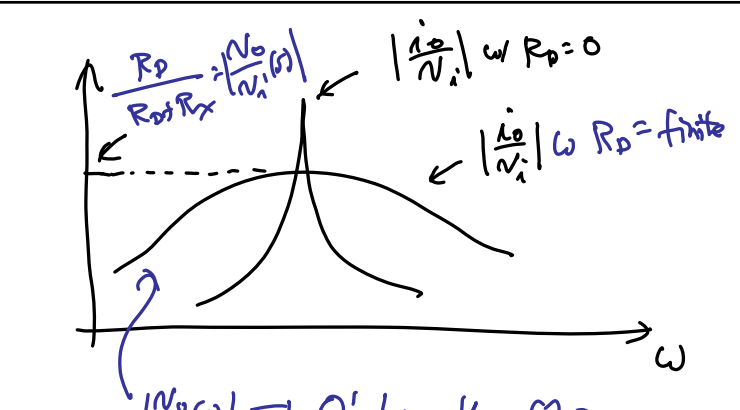

$\frac{R_D}{R_D + R_x} \cdot \left(\frac{v_o}{v_i} \right)$ $\left| \frac{v_o}{v_i} \right| \omega R_D = 0$
 $\left| \frac{v_o}{v_i} \right| \omega R_D = \text{finite}$

$\left| \frac{v_o}{v_i}(s) \right| \Rightarrow Q' \text{ lower than } Q$
 $= Q \left(\frac{R_x}{R_x + R_D} \right) < 1$ } Big Problem!

Analysis @ Resonance:


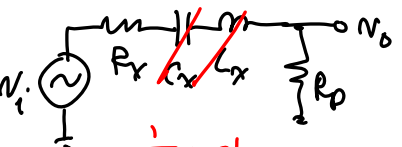


$\frac{1}{sC_x} = sL_x$
 + cancel:

v_i $v_o = \left(\frac{R_D}{R_D + R_x} \right) v_i$
 @ resonance

Convert to general freqs: $\times \mathcal{H}(s, Q')$
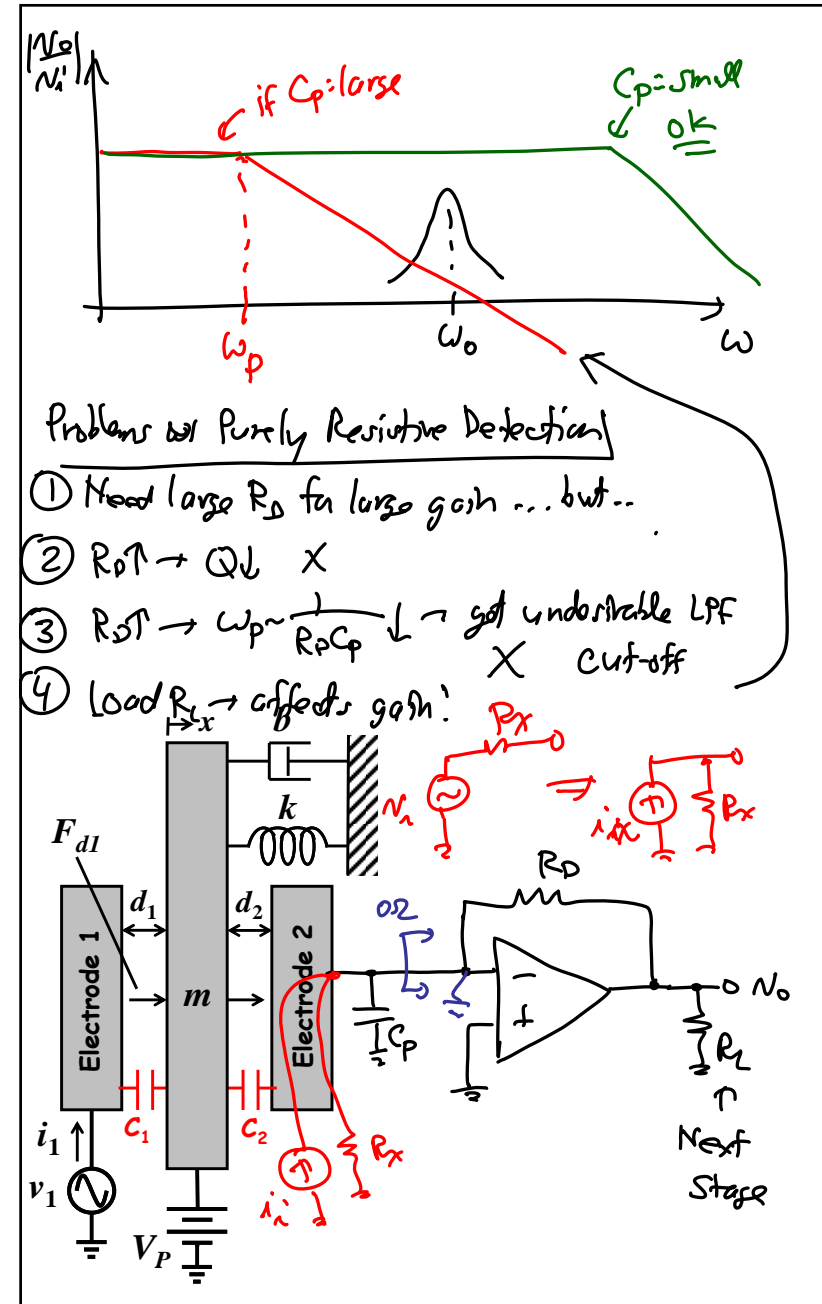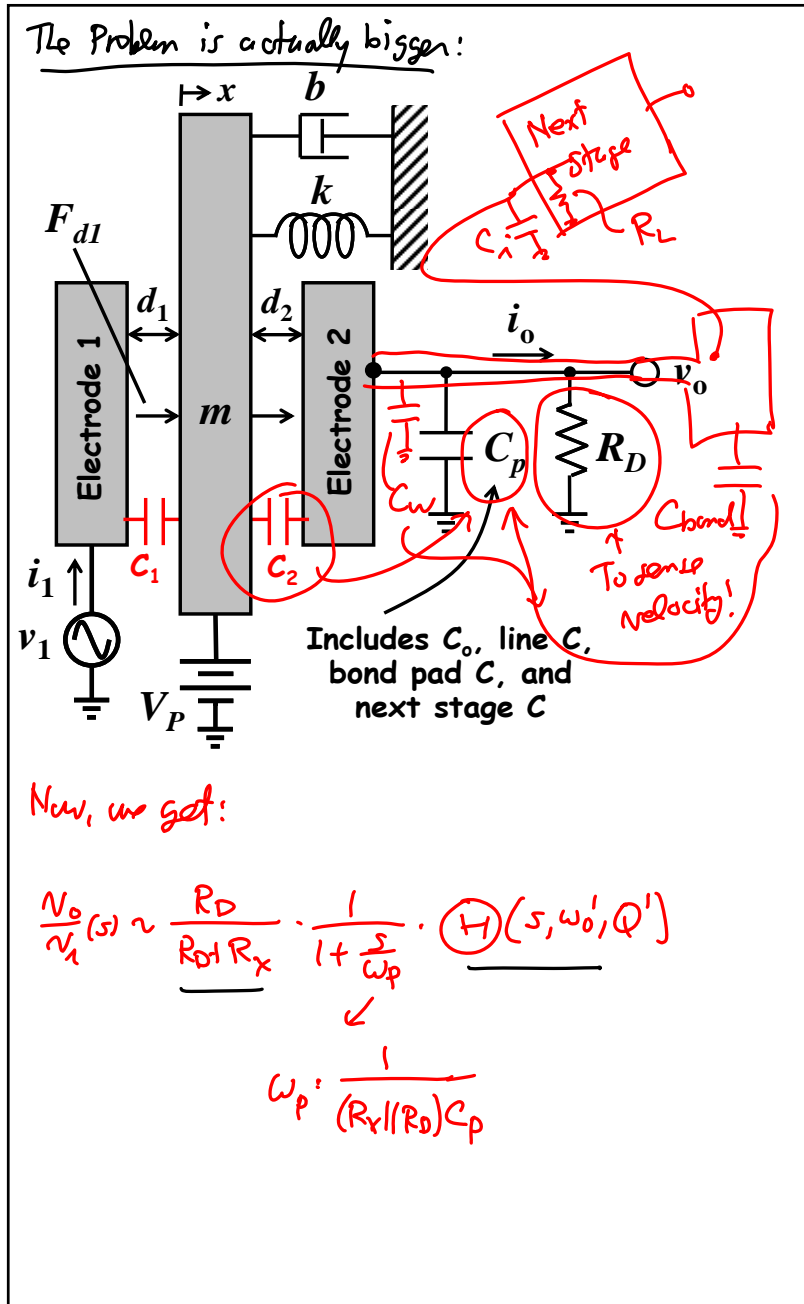
$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \mathcal{H}(s, Q'), \text{ where } Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$$



Ideal Op Amp Laws:

- ① $R_i \rightarrow \infty \rightarrow i_- = 0, i_+ = 0$
- ② $R_o = 0$
- ③ Gain $\rightarrow A_o = \infty$

neg. FB $\rightarrow v_o = \infty(v_+ - v_-) = \text{finite}$
 $0 \rightarrow v_+ = v_-$

can't say this!

~~Blows Up! (+) FB~~

neg. FB \checkmark
 that's good

$R_D = -i_i R_D$

$v_o = -i_i R_D$

notional resistance

"virtual ground"
 since there are no voltage variations across C_p !

$\frac{v_o}{i_i} = -R_D$ @ resonance

$\frac{v_o(s)}{i_i(s)} = -\frac{R_D}{R_x} (1) (s)$ no Q degradation

$(v_+ = i_i R_x)$