

Position-to-Voltage Conversion

To sense position (i.e., displacement), use a capacitive load

Again, have port-to-port I/O symmetry:

$$\frac{V_o}{V_i} = \frac{\frac{1}{C_D}}{R_x + \frac{1}{SC_x} + SL_x + \frac{1}{SC_D}}$$

Brute-force approach:

$$\frac{V_o}{V_i}(s) = \frac{\frac{1}{C_D}}{1 + \frac{1}{C_x/C_D} + s^2 \frac{L_x C_x}{C_D}}$$

$$= \frac{C_x/C_D}{1 + C_x/C_D} \frac{\frac{1}{C_x/C_D}}{s^2 + s \left(\frac{R_x}{C_x} + \frac{1 + C_x/C_D}{L_x C_x} \right)}$$

$$= \frac{C_x/C_D}{1 + C_x/C_D} \frac{\frac{1}{C_x/C_D}}{s^2 + s \left(\frac{R_x}{C_x} + \frac{1 + C_x/C_D}{L_x C_x} \right)}$$

$$= \frac{C_x/C_D}{1 + C_x/C_D} \frac{\frac{1}{C_x/C_D}}{s^2 + s \left(\frac{R_x}{C_x} + \frac{1 + C_x/C_D}{L_x C_x} \right)}$$

$$= \frac{C_x/C_D}{1 + C_x/C_D} \frac{\frac{1}{C_x/C_D}}{s^2 + s \left(\frac{R_x}{C_x} + \frac{1 + C_x/C_D}{L_x C_x} \right)}$$

$$= \frac{C_x/C_D}{1 + C_x/C_D} \frac{\frac{1}{C_x/C_D}}{s^2 + s \left(\frac{R_x}{C_x} + \frac{1 + C_x/C_D}{L_x C_x} \right)}$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 6

Position-to-Voltage Conversion

To sense position (i.e., displacement), use a capacitive load

$\frac{V_o}{V_i}(s) = \frac{C_x/C_D}{1 + C_x/C_D} \frac{\frac{1}{C_x/C_D}}{s^2 + (\frac{R_x}{C_x})s + (\frac{w_0}{C_D})^2}$

DC Gain Term

Lad-Pacr Biquad

To maximize gain $\rightarrow 1$, need $C_D \ll C_x$. (must minimize C_D)

Note: Can we similar short-cut to the R case.

- Get DC response $\rightarrow C$'s dominate.
- Then:

$$\frac{V_o}{V_i}(s) = (\text{DC Gain}) \cdot \frac{1}{s} \cdot \Theta(s, w_0, Q') \cdot w_0 Q'$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 7

Position Sensing Circuits

To sense position (i.e., displacement), use a capacitive load

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 13

Problems With Pure-C Position Sensing

To sense position (i.e., displacement), use a capacitive load

Interconnect Band Pad

$$\frac{V_o}{V_i}(s) = \frac{C_x/C_D}{1 + C_x/C_D} \cdot \frac{1}{s} \cdot \Theta(s, w_0, Q') \cdot w_0 s$$

Integration yields displacement.

To maximize gain, minimize C_D . \Rightarrow Problem: parasitic capacitance

$C_D \rightarrow C_D + C_{pi} + C_{pb}$





\Rightarrow DC Gain: $\frac{C_x/(C_D + C_{pi} + C_{pb})}{1 + C_x/(C_D + C_{pi} + C_{pb})}$

Output will get smaller!

Remedy: Suppress C_p via use of op amps.

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 14

Lecture 27m1: Sensing Circuits

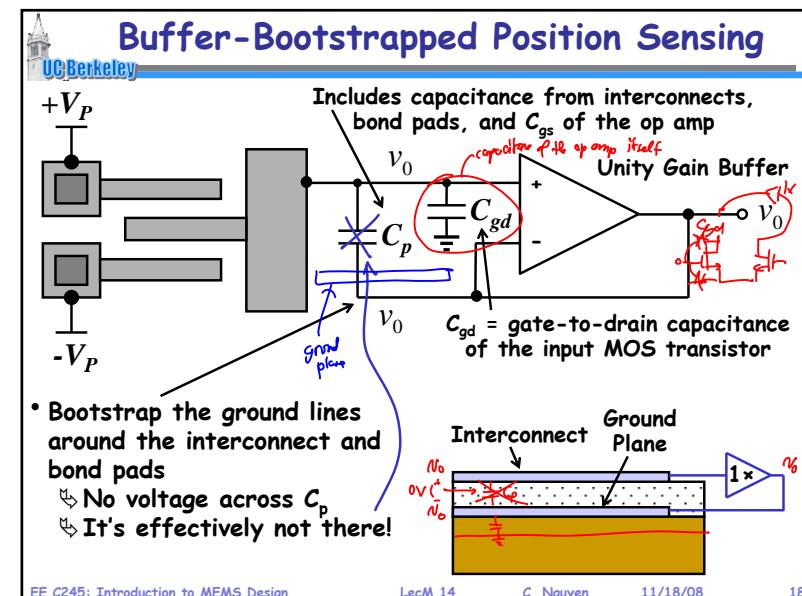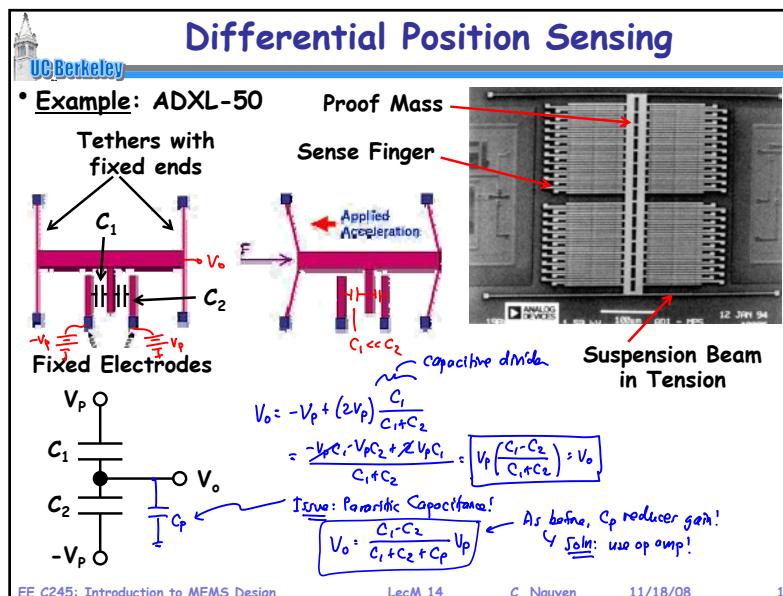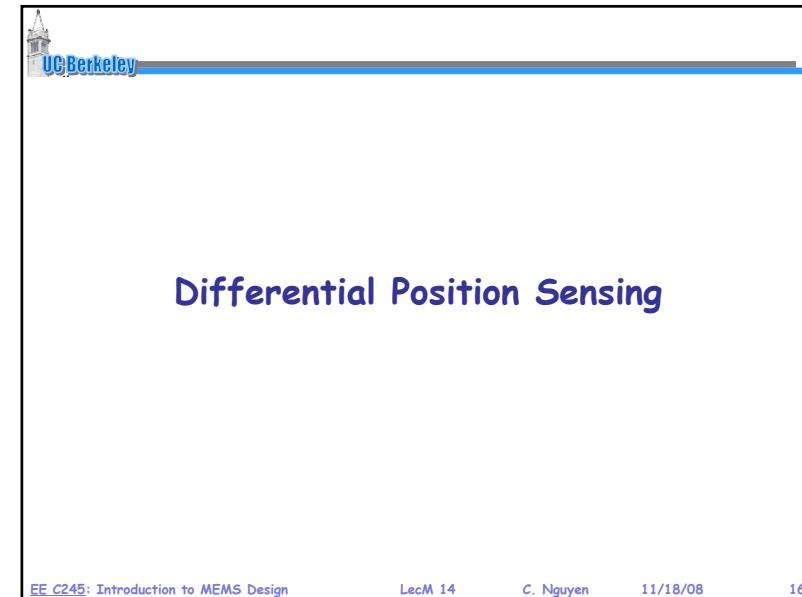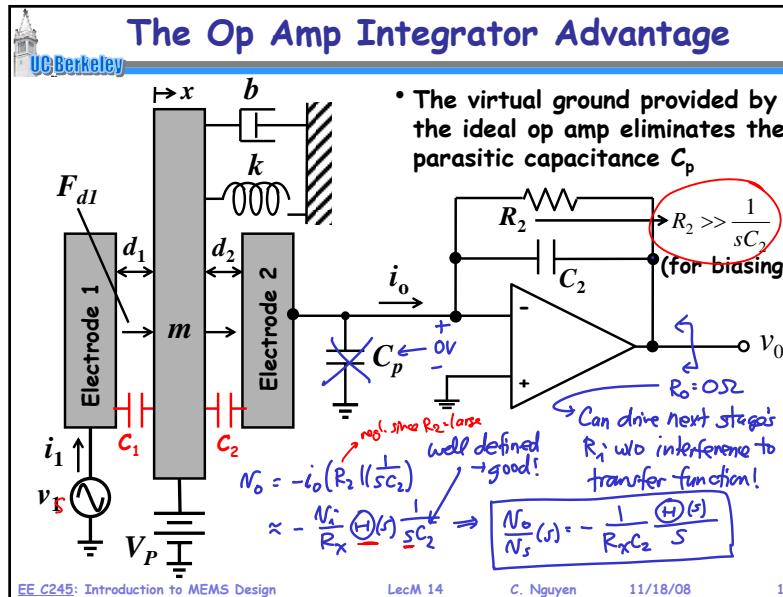

Lecture 27m1: Sensing Circuits

