

Lecture 27: Sensing Circuits II

- Announcements:
- HW#7 due Friday, May 9
- Project Slide 3 due this Friday (tomorrow)
- Project Outbrief Signup sheet has been on my door
 - ↳ If not already signed up, please do
- Handed out Final Exam Info
-
- Reading: Senturia, Chpt. 14
- Lecture Topics:
 - ↳ Detection Circuits
 - Velocity Sensing
 - Position Sensing
- Reading: Senturia, Chpt. 14, Chpt. 16, Chpt. 21
- Lecture Topics:
 - ↳ Gyroscopes & MDS (brief skim)
 - ↳ Course Wrap Up
-
- Last Time:
- Considering the benefits of op amp-based sensing circuits ... continue with this

over

Velocity to-Voltage Conversion

represent velocity

V_i V_P V_o R_D i_o cantilever

in phase w/ velocity
90° phase shift
fl displacement

$\frac{|V_o|}{V_i}$ ω

$\omega_0 = \frac{QF_0}{K}$
 $\omega_0 = \frac{\omega_0 Q F_0}{K}$

F_{d1} i_o V_P output ground

$\frac{\ddot{x}}{F_{d1}}(s) = \frac{\omega_0 Q}{K} (H)(s)$


$[F_{d1} = \eta e_1 V_i]$

$\frac{\ddot{x}}{V_i}(s) = \eta e_1 \frac{\omega_0 Q}{K} (H)(s)$

$[i_o = \eta e_2 \ddot{x}] \Rightarrow \frac{i_o}{V_i}(s) = \eta e_1 \eta e_2 \frac{\omega_0 Q}{K} (H)(s)$

$\frac{1}{R \times I_2} = \frac{\eta e_1 \eta e_2 Q}{m \omega_0} (H)(s)$

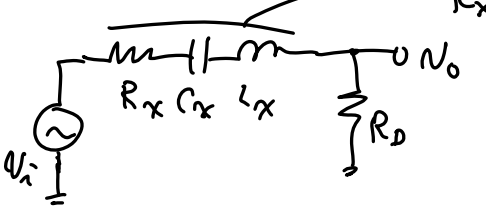Now, include R_D : $Q = \frac{\omega_0 L_x}{R_x}$



$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x + \frac{1}{sC_x} + sL_x} = \dots \text{math} \dots$$

$$= \frac{R_D}{R_D + R_x} \frac{s \left(\frac{R_x + R_D}{L_x} \right)}{s^2 + s \left(\frac{R_x + R_D}{L_x} \right) + \frac{1}{L_x C_x}}$$

Gain Term Freq. Shaping Term


$$\left[Q \cdot \frac{\omega_0 L_x}{R_x} \rightarrow Q' = \frac{\omega_0 L_x}{R_x + R_D} \rightarrow \frac{R_x + R_D}{L_x} = \frac{\omega_0}{Q'} \right]$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \frac{s(\omega_0/Q')}{s^2 + s(\omega_0/Q') + \omega_0^2}$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \cdot \mathcal{H}(s, Q')$$

$Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$


proportional to velocity

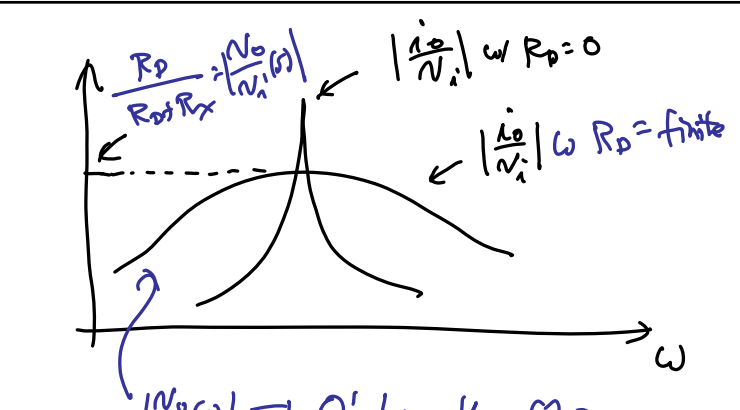

$\frac{R_D}{R_D + R_x} \cdot \left| \frac{v_o}{v_i}(s) \right| \Rightarrow Q' \text{ lower than } Q$

$= Q \left(\frac{R_x}{R_x + R_D} \right) < 1$ } Big Problem!

Analysis @ Resonance:


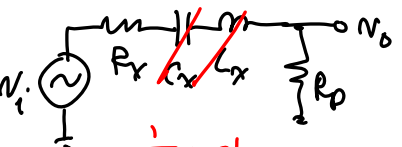


$\frac{1}{sC_x} = sL_x$ cancel:

@ resonance

Convert to general freqs: $\times \mathcal{H}(s, Q')$
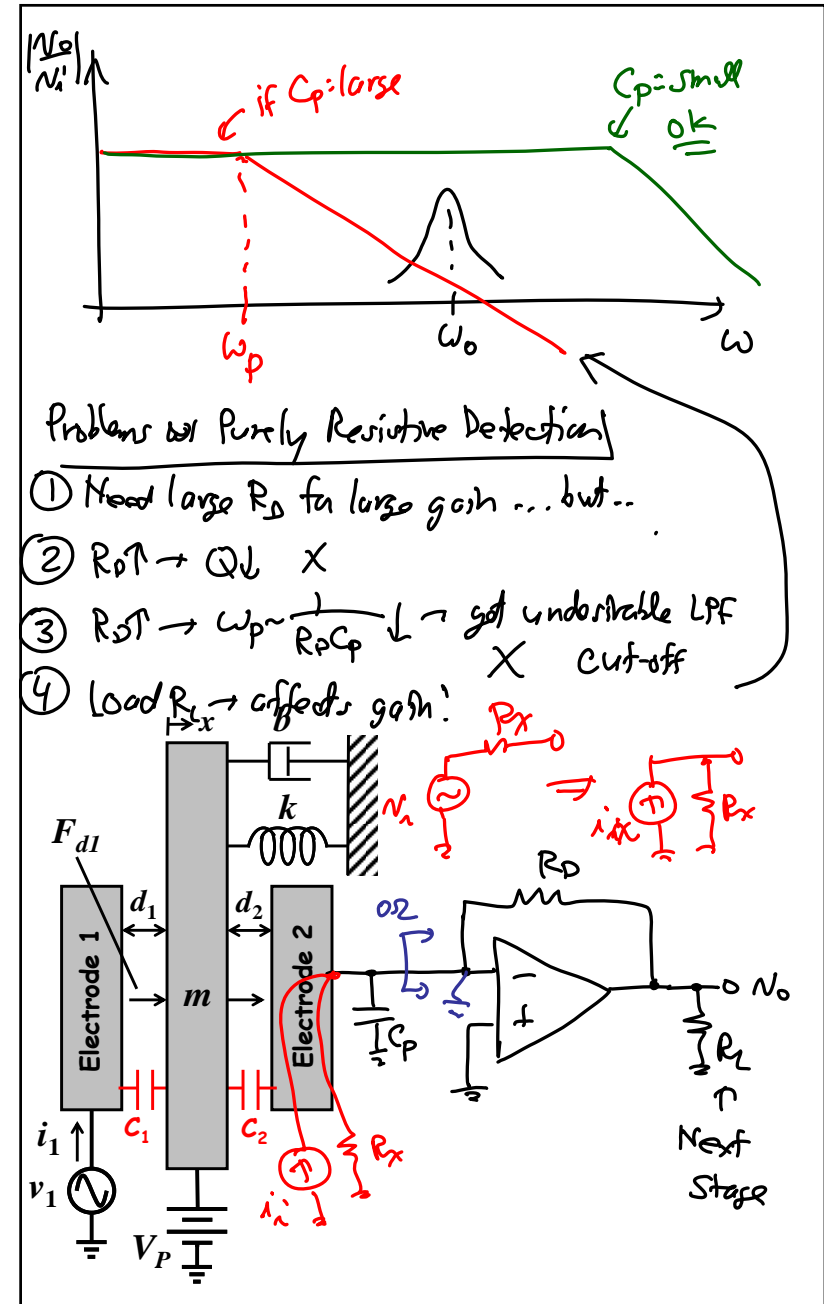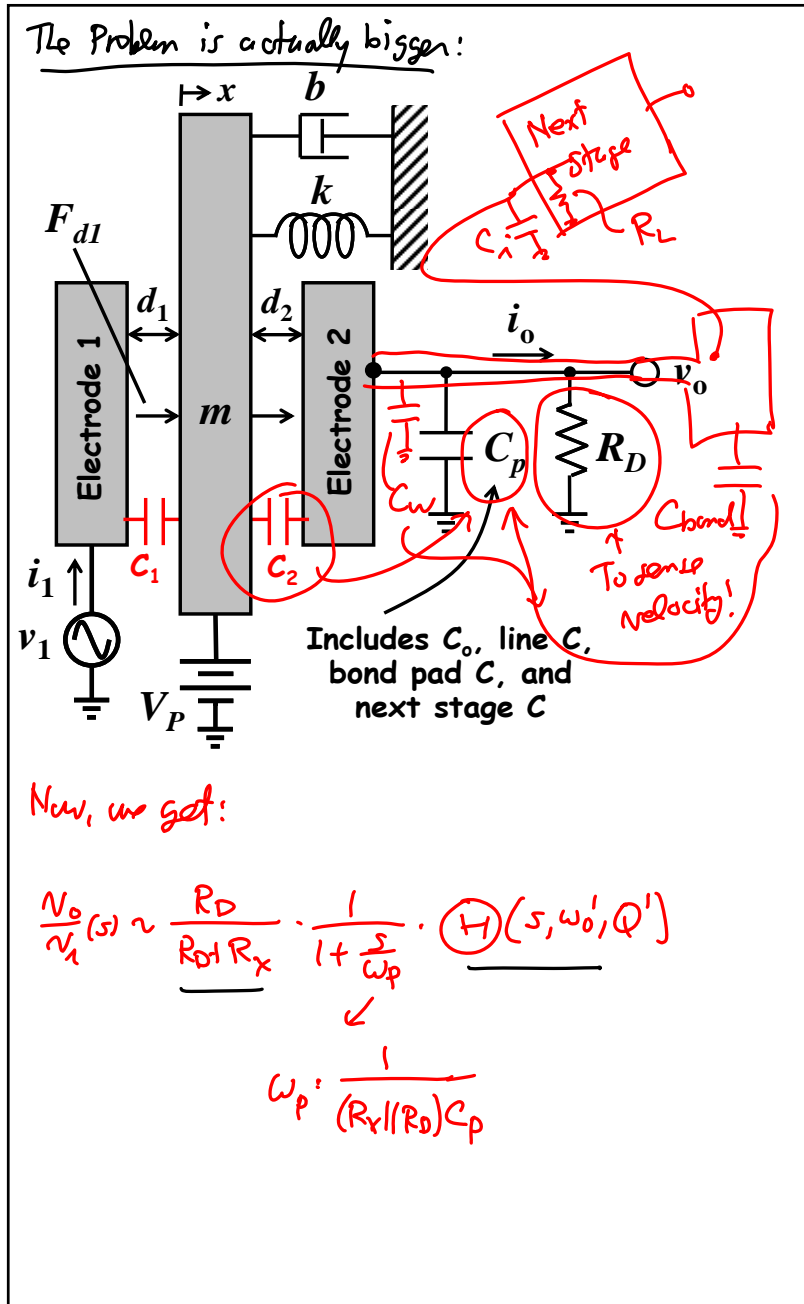
$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \mathcal{H}(s, Q'), \text{ where } Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$$



Ideal Op Amp Laws:

- ① $R_i \rightarrow \infty \rightarrow i_i = 0, i_f = 0$
- ② $R_o = 0$
- ③ Gain $\rightarrow A_o = \infty$

neg. FB $\rightarrow v_o = \infty(v_+ - v_-) = \text{finite}$
 $\infty \rightarrow v_+ = v_-$ ← can't say "vir!"

Blows Up! (+) FB X

neg. FB ✓ that's good

"virtual ground"
 since there are no voltage variations across C_p !

notional resistance

$v_o = -i_i R_D$

$\frac{v_o}{v_i} = -R_D$ @ resonance

$\frac{v_o(s)}{v_i(s)} = -\frac{R_D}{R_x} (1) (s)$ ← no Q degradation

$(v_i = i_i R_x)$

- Note: Previous 7 pages are just review of last time
- This is where the new material of this lecture really starts
- Go through Module 14 on Sensing Circuits, slides 6-7 and 13-20
- Go through Final Exam Info Sheet
- Course Wrap up - next page ...

- Related courses at UC Berkeley:
 - ⇒ EE 143: Microfabrication Technology
 - ~~⇒~~ EE 147/247A: Introduction to MEMS
 - ~~⇒~~ ME 119: Introduction to MEMS (mainly fabrication)
 - ✓ ⇒ BioEng 121: Introduction to Micro and Nano Biotechnology and BioMEMS
 - ✓ ⇒ ME C219 - EE C246: MEMS Design
 - ⇒ EE 290M?