
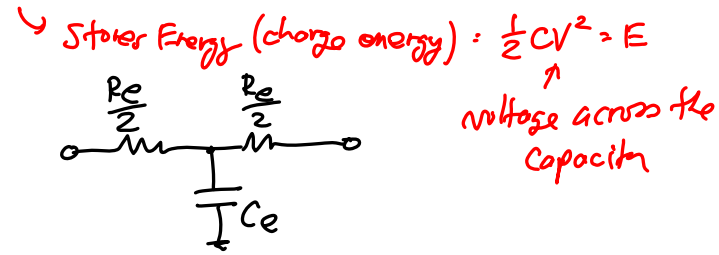


Lecture 4: Benefits of Scaling III


- Announcements:
- This is our make-up lecture for last Tuesday
- HW#1 online
- -----
- Today:
- Reading: Senturia, Chapter 1
- Lecture Topics:
 - ↳ Benefits of Miniaturization
 - ↳ Examples
 - GHz micromechanical resonators
 - Chip-scale atomic clock
 - Thermal Circuits
 - Micro gas chromatograph
- -----
- Last Time: Covering thermal circuit modeling ... which we now continue ...

Review Electrical Resistance First


(then attach the thermal R analogy)


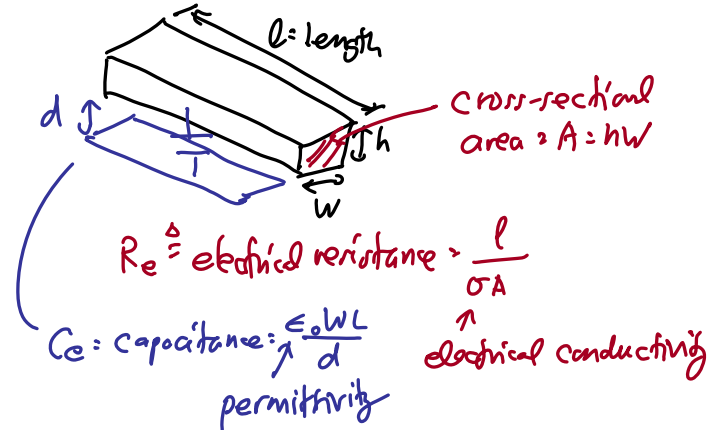


⇒ if want to be more exact:

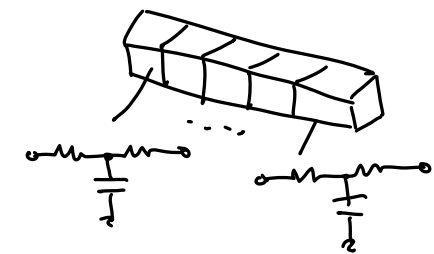

Thermal Ckt.

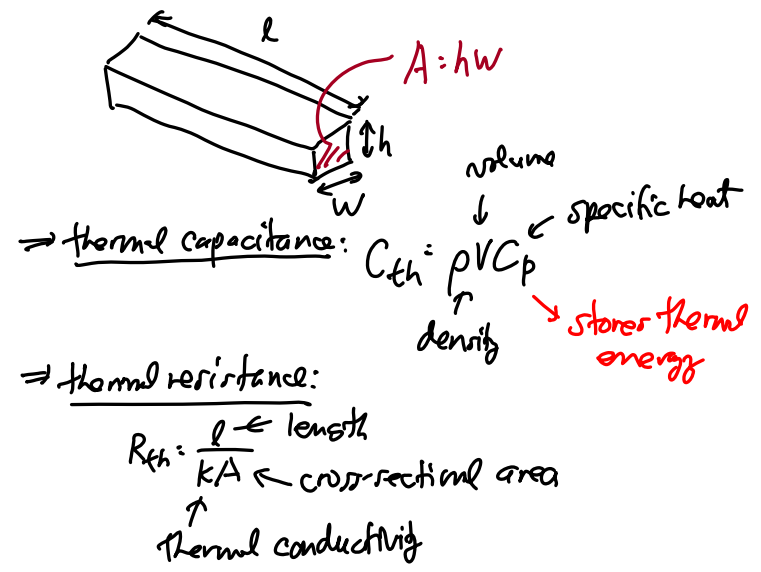

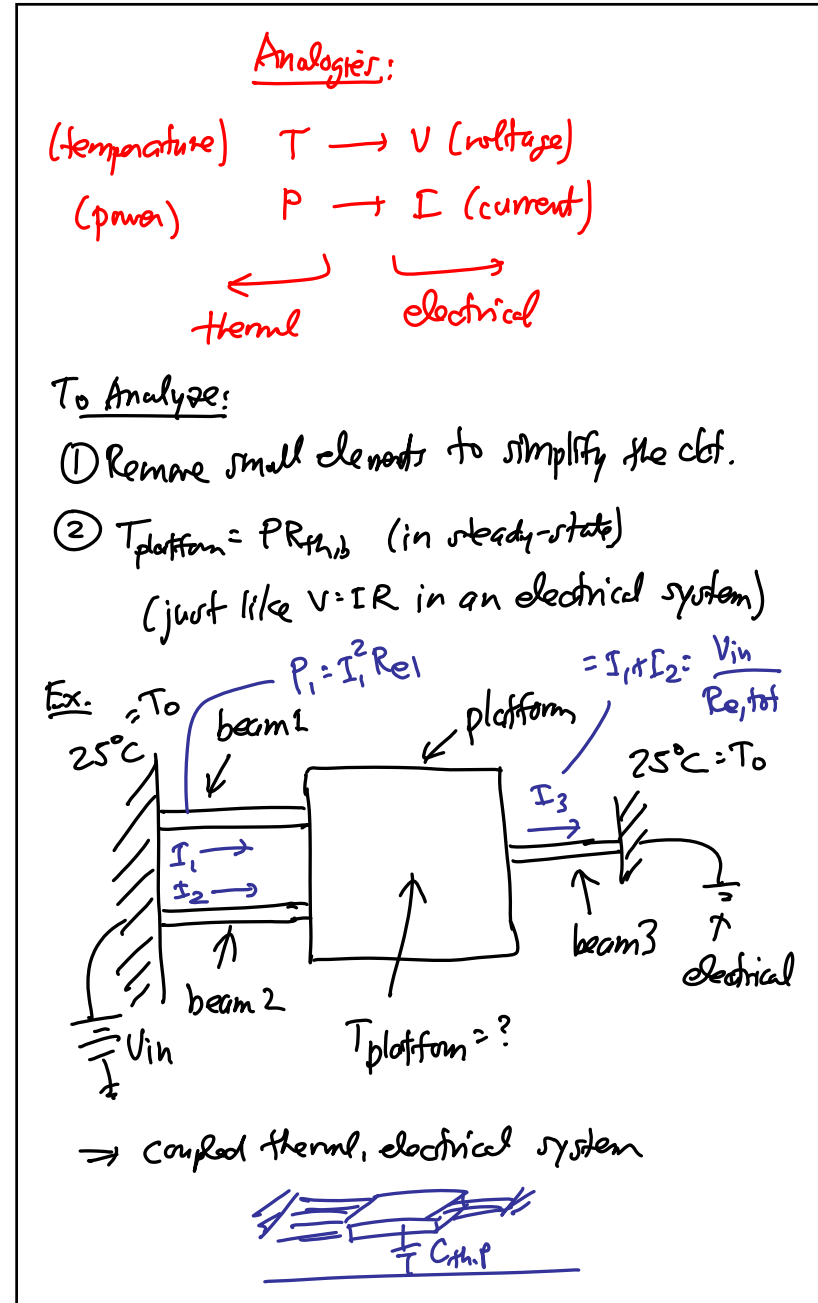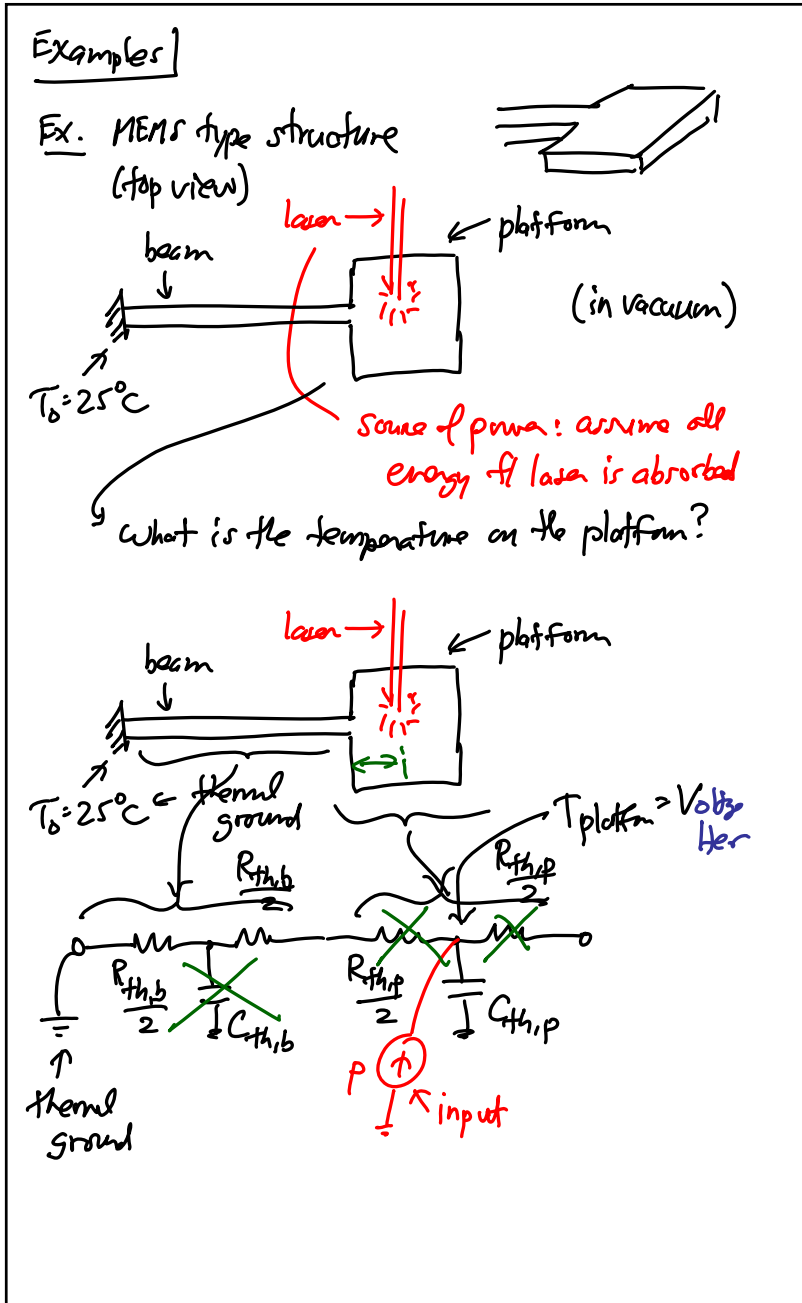




⇒ Draw the thermal ckt.



To Analyze:

- ① $I_3 = I_1 + I_2 = \frac{V_{in}}{R_{e,tot}}$ (electrical analysis)
- ② Get P_i 's. (power)
- ③ Use superposition to solve the thermal ckt.
handle one power source at a time & sum the temperatures (i.e., thermal voltages) to get the total temperature at any node

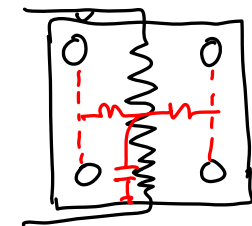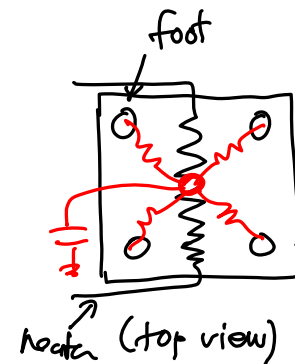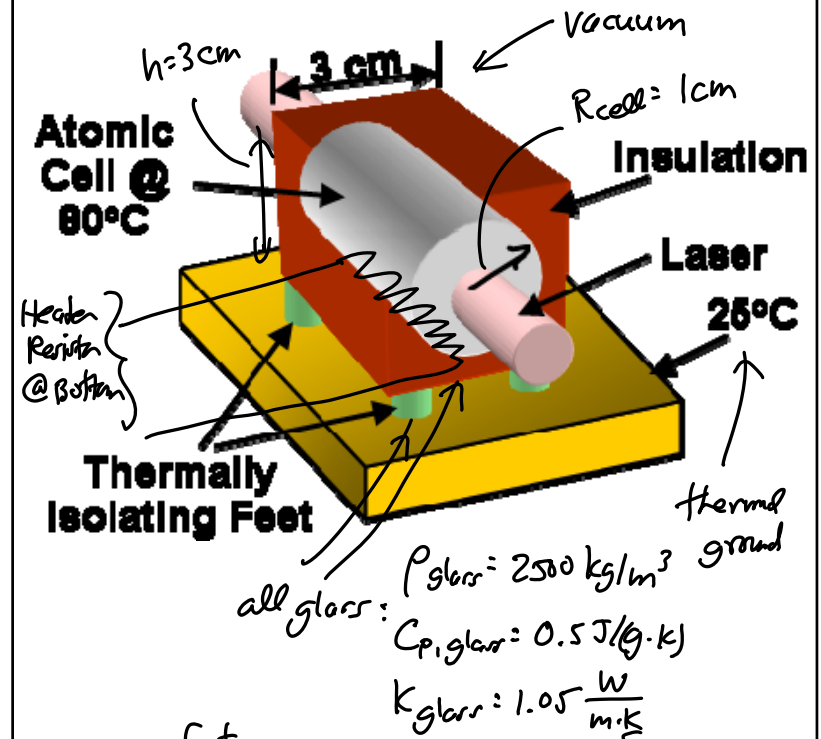Example: Thermal Ckt.

⇒ determine the power needed to get this atomic cell to 80°C (from RT) & how fast



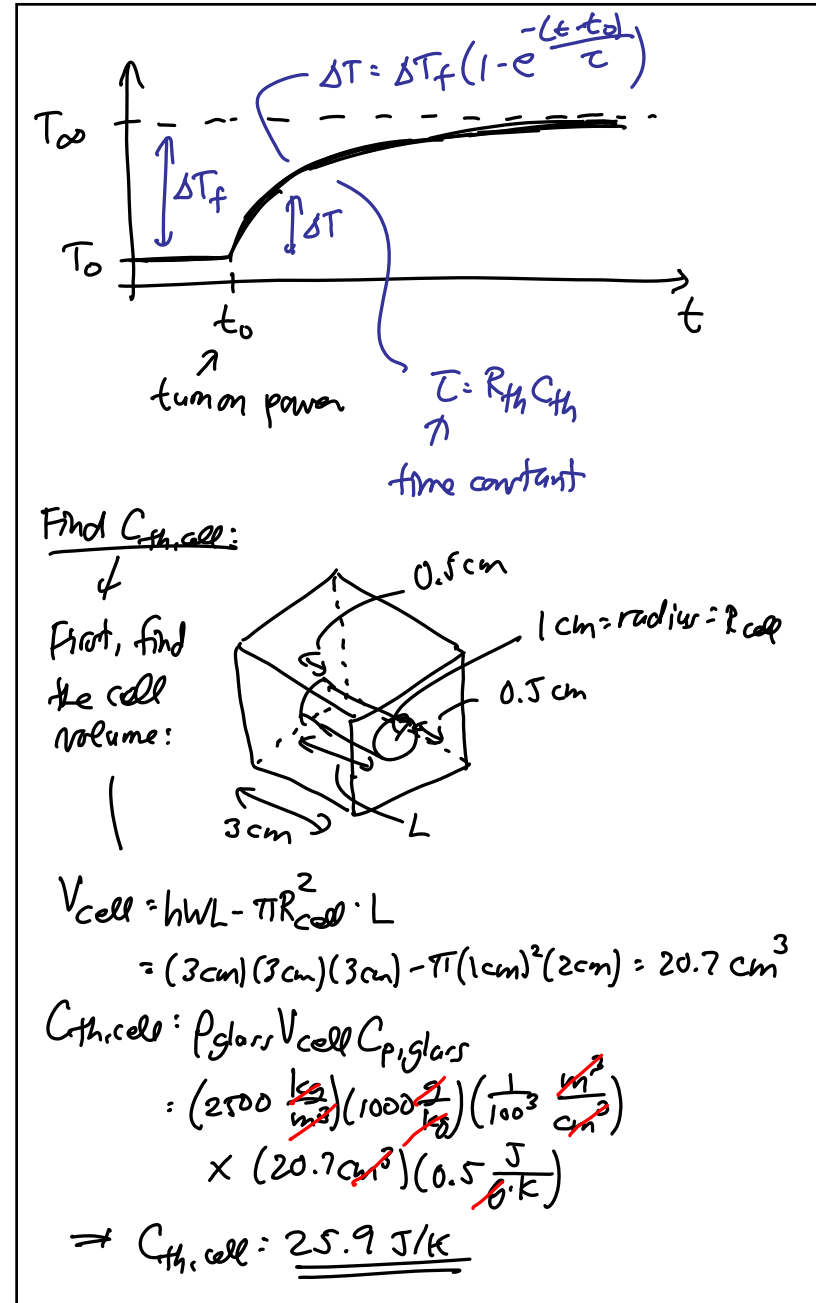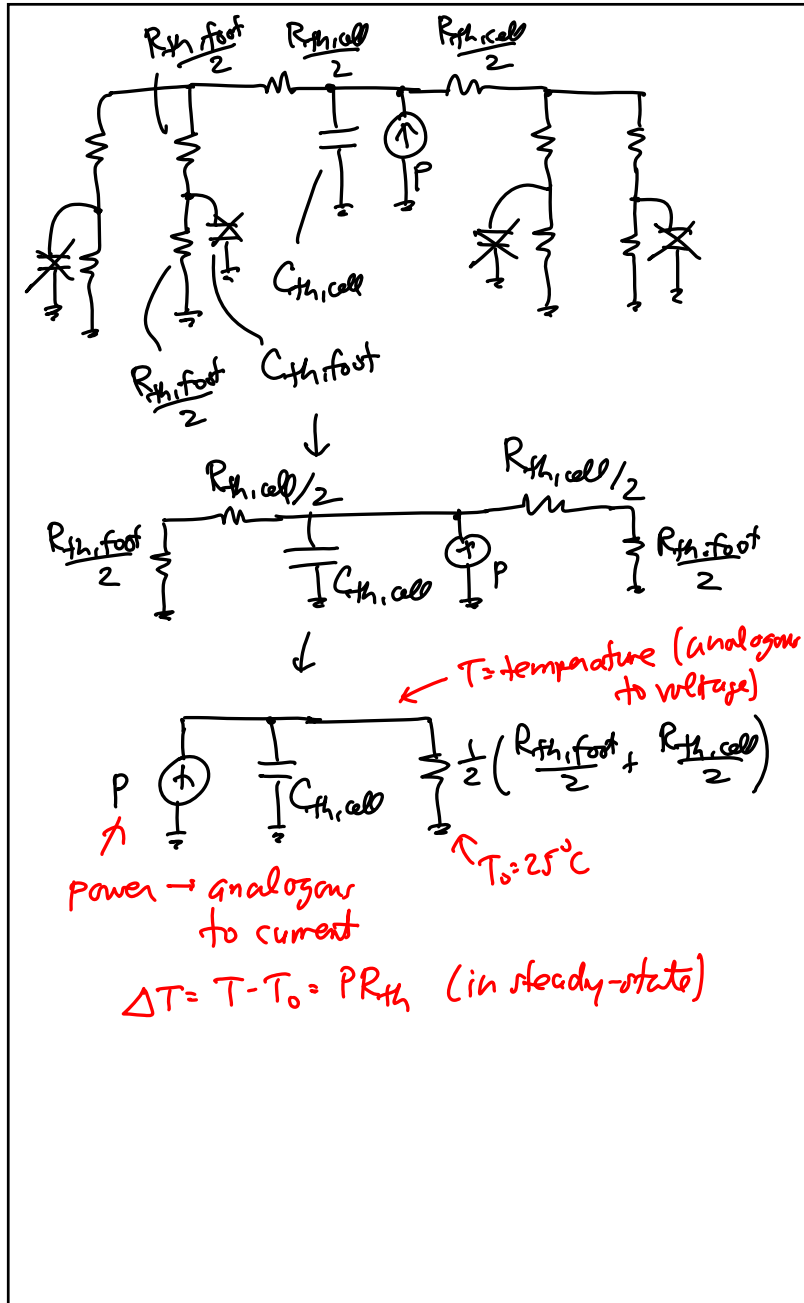

Find $\frac{R_{th,cell}}{2}$

(cross-section)

$R_{th,cell}/2$

$C_{th,cell}$

$$\frac{R_{th,cell}}{2} = \frac{\frac{3}{4}}{k(3)(\frac{1}{2})} + \frac{\frac{3}{4}}{k(3)(1)} = \frac{1}{k} \left(\frac{1}{2} + \frac{1}{4} \right) = \frac{3}{4} \frac{1}{k}$$

$\left[R_{th} = \frac{l}{kA} \right] \quad \therefore \frac{R_{th,cell}}{2} = \frac{3}{4} \frac{1}{1.05} \times (100 \frac{cm}{m})$

$= \underline{\underline{35.7 \text{ K/W}}}$