


Lecture 19w: Equivalent Circuits II

Lecture 19: Equivalent Circuits II

- Announcements:
 - HW#5 online; due Wednesday, April 15
 - Module 13 on Equivalent Circuits II online
 - Project slide #1 due Friday, April 10
 - I will be on travel next week; will either record lectures or do make-up lectures next Friday
 - Will announce via Piazza
 - -----
 - Reading: Senturia, Chpt. 6, Chpt. 14
 - Lecture Topics:
 - ↳ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↳ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↳ Impedance & Transfer Functions
 - -----
 - Last Time:
 - Finished comb-drive
 - Project Notes:

| Parameter | Today (50A) | After Scaling | Factor |
|-----------|-------------|---------------|--------|
| Speed | 60s | 1ms | |

Input Electrical Equiv. Ckt.

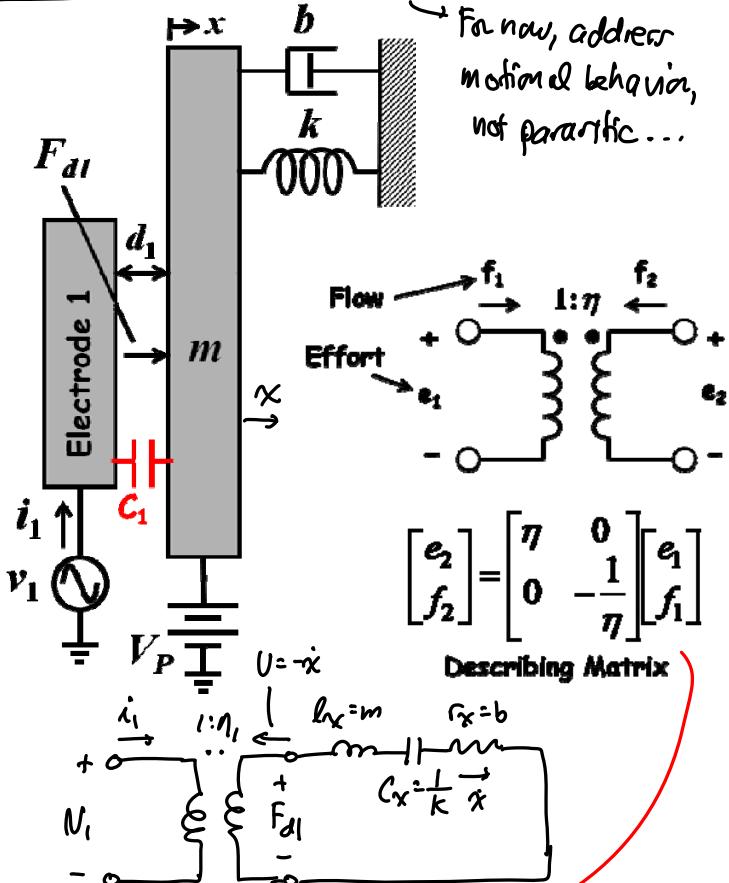


$$F_{dl} = -V_p \frac{\partial C}{\partial x} N_1$$

$$\frac{e_2}{\eta_1} e_1$$

$$\eta_1 = V_p \frac{\partial C_1}{\partial x} = V_p \frac{\epsilon_0 A}{d_1^2}$$


Lecture 19w: Equivalent Circuits II

Output Current Into Ground

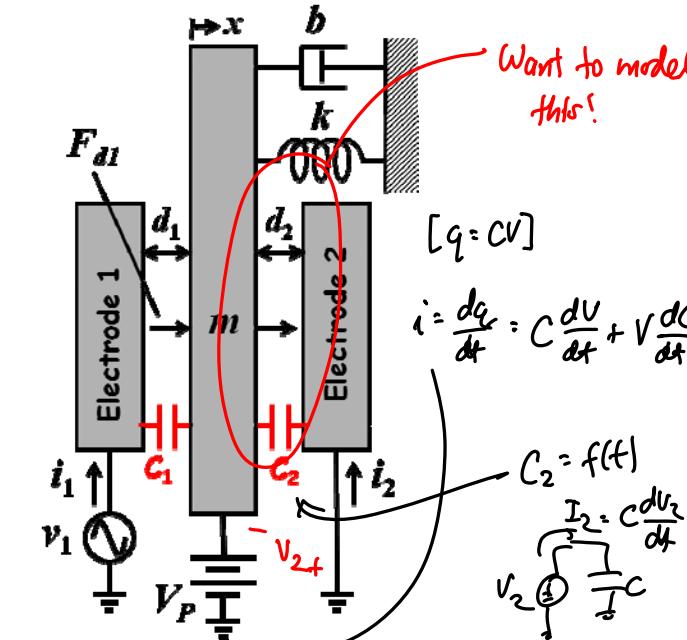

$$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X = -V_p \frac{\partial C_2}{\partial x} \dot{x}$$

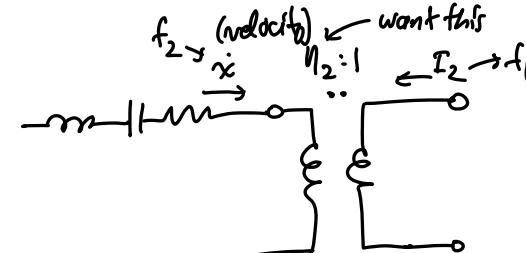90° phase lag $(t) \rightarrow I_2 = (-) \text{ when } x = (t)$ ✓



$$f_2 = -\frac{1}{\eta_2} f_1$$

$$f_1 = -\eta_2 f_2$$


$$[f_1 = F_2, f_2 = \dot{x}]$$

$$I_2 = -\eta_2 \dot{x}$$


$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix}$$

Describing Matrix
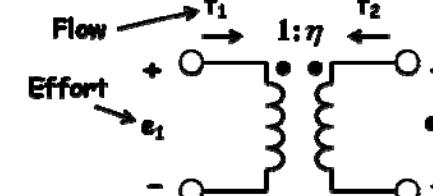
$$\therefore \boxed{\eta_2 = V_p \frac{\partial C_2}{\partial x}}$$



Input Current Expression (more complete)

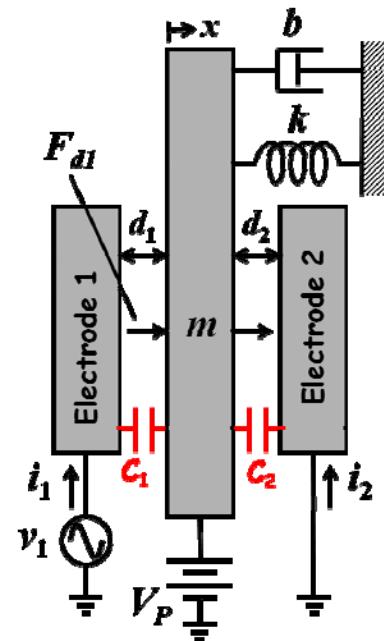

Get $I_1(j\omega)$:

$$i_1(t) = C_1(x, t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC(x, t)}{dt}$$

$$(V_1(t) = V_i - V_p \Rightarrow i_1 = C_1 \frac{dV_i}{dt} + [V_i - V_p] \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t})$$

$$\therefore I_1(j\omega) = j\omega C_1 V_i + j\omega V_i \frac{\partial C_1}{\partial x} X - j\omega V_p \frac{\partial C_1}{\partial x} X$$

Feedthrough Current

Motion Current (due to mass motion)

What's X ?

$$@ DC: x = \frac{F_{d1}}{k} = -\frac{1}{k} V_p \left(\frac{\partial C_1}{\partial x} \right) V_i$$

$$@ resonance: x = \frac{Q F_{d1}}{j\omega k} = -\frac{Q}{j\omega k} V_p \frac{\partial C_1}{\partial x} V_i = X$$


Thur: (@ resonance) ω_0

$$I_1(j\omega) = j\omega_0 C_1 V_i + j\omega_0 \left(V_p \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{j\omega k}$$

$$= j\omega_0 C_1 V_i + \omega_0 \frac{Q}{k} n_{er}^2 V_i$$


$j\omega$ phase-shifted from V_i parasitic, i_p In phase ωV_i , motion current i_x

⇒ on a spectrum analyzer:

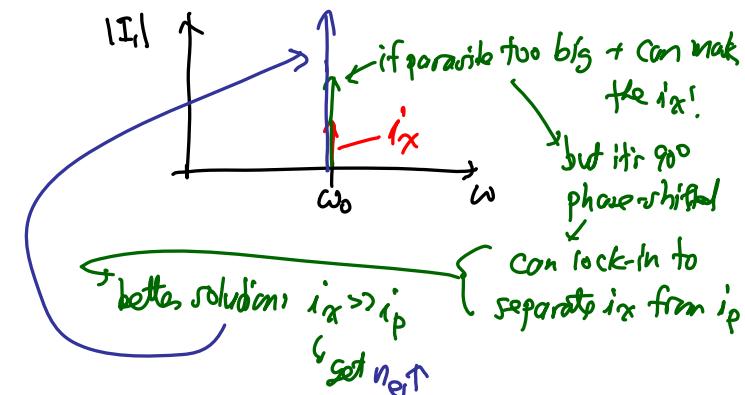

Lecture 19w: Equivalent Circuits II

The equiv. ckt. becomes:

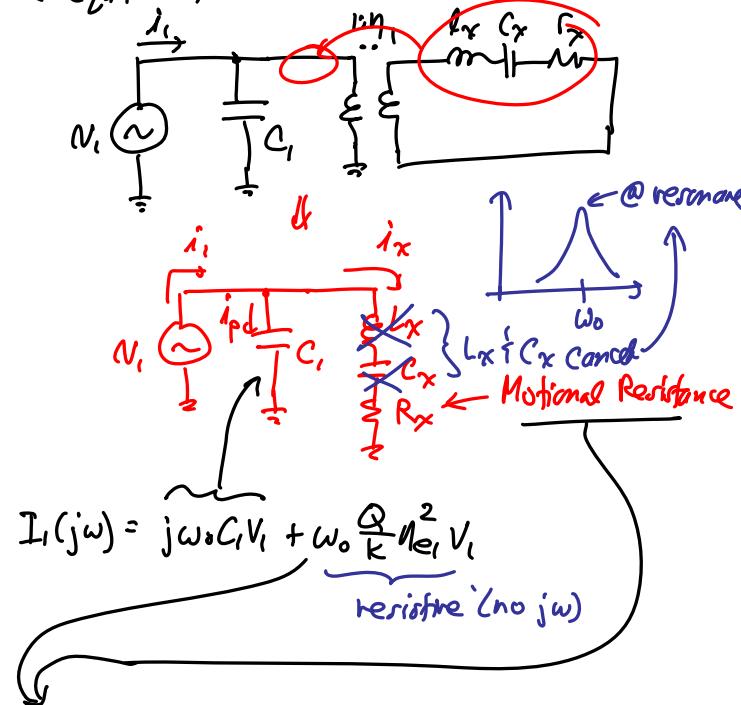


Motional Resistance:

$$R_{x1} = \frac{V_1}{I_1} \Big|_{\omega_0} = \frac{k}{\omega_0 Q \eta_{ei}^2} = \frac{M \omega_0}{Q \eta_{ei}^2} = \frac{b}{\eta_{ei}^2} = R_{x1}$$

\hookrightarrow equiv. ckt. gets this right!

- Look at Module 13, slide 16

Input Impedance Into Port 1

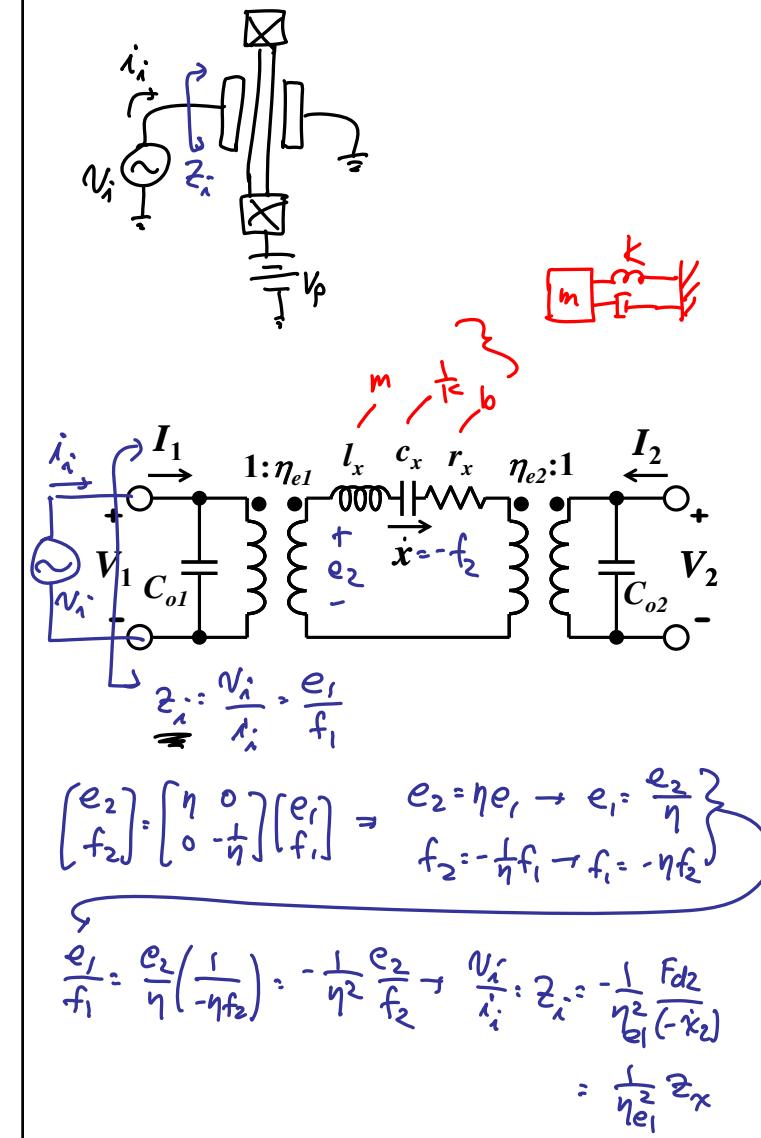

$$\begin{aligned} Z_i &= \frac{1}{\eta_{ei}^2} \left(j\omega l_{xi} + \frac{1}{j\omega C_x} + r_x \right) \\ &= j\omega \left(\frac{l_x}{\eta_{ei}^2} \right) + \frac{1}{j\omega (\eta_{ei}^2 C_x)} + \frac{r_x}{\eta_{ei}^2} \end{aligned}$$

$\underbrace{l_{xi}}_{L_{xi}}$ $\underbrace{\frac{1}{j\omega (\eta_{ei}^2 C_x)}}_{C_{xi}}$ $\underbrace{\frac{r_x}{\eta_{ei}^2}}_{R_{xi}}$

to model noise!

$\overline{V_n^2} = 4kT R_x$ (Brownian Motion)

} Purely Electric
Equiv. Ckt.