

$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix} \Rightarrow e_2 = \eta e_1 \rightarrow e_1 = \frac{e_2}{\eta}$$

$$f_2 = -\frac{1}{\eta} f_1 \rightarrow f_1 = -\eta f_2$$

$$\frac{e_1}{f_1} = \frac{e_2}{\eta} \left(\frac{1}{-\eta f_2} \right) = -\frac{1}{\eta^2} \frac{e_2}{f_2} \rightarrow \frac{V_i}{i_i} = Z_i = -\frac{1}{\eta^2} \frac{F_{d2}}{(-\dot{x}_2)}$$

$$Z_i = \frac{1}{\eta^2} Z_x$$

$$Z_i = \frac{1}{\eta^2} \left(j\omega L_x + \frac{1}{j\omega C_x} + r_x \right)$$

$$= j\omega \left(\frac{L_x}{\eta^2} \right) + \frac{1}{j\omega (\eta^2 C_x)} + \frac{r_x}{\eta^2}$$

L_{x1} C_{x1} R_{x1} $\frac{N_1^2}{\eta^2} = 4kTR_x \Delta f$

to model noise!

* Purely Electrical Equiv. Ckt.



Transformer Inspection Analysis

Input Impedance Into Port 2

$$Z_i = \frac{N_1^2}{i_i} = \frac{Z_x}{\eta_{e2}^2}$$

$$= j\omega \left(\frac{L_x}{\eta_{e2}^2} \right) + \frac{1}{j\omega (\eta_{e2}^2 C_x)} + \frac{r_x}{\eta_{e2}^2}$$

L_{x2} C_{x2} R_{x2}

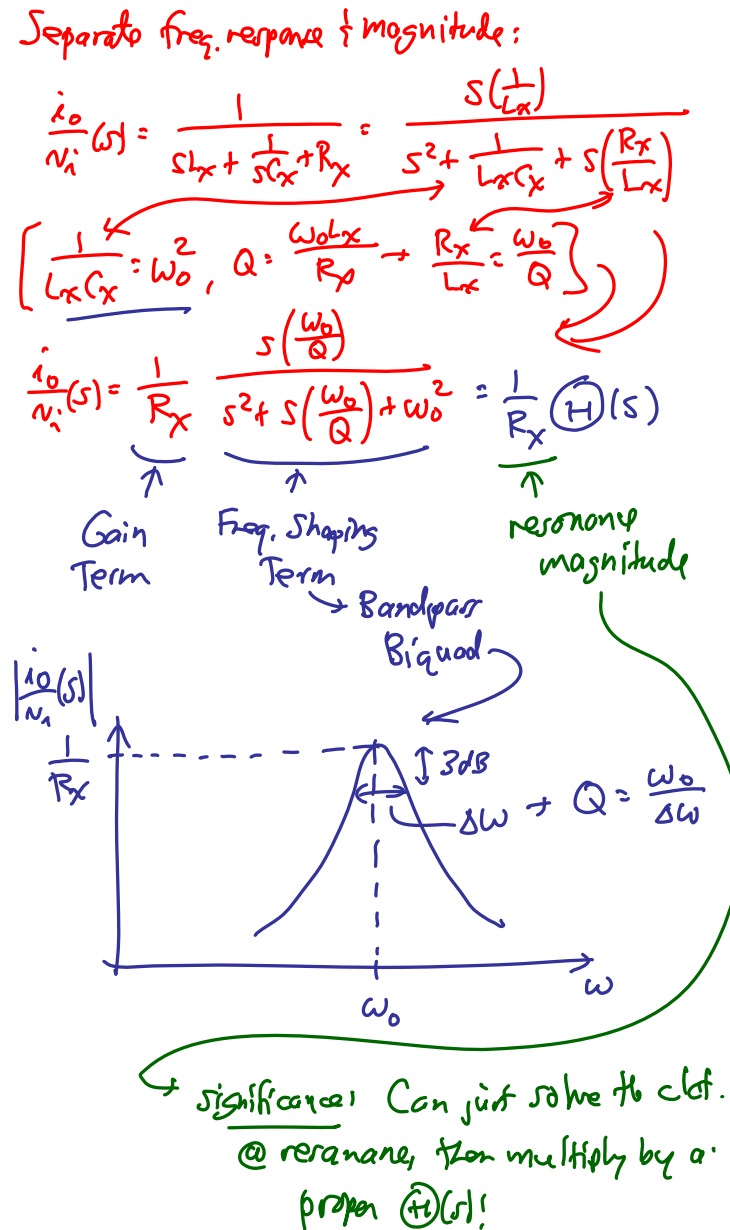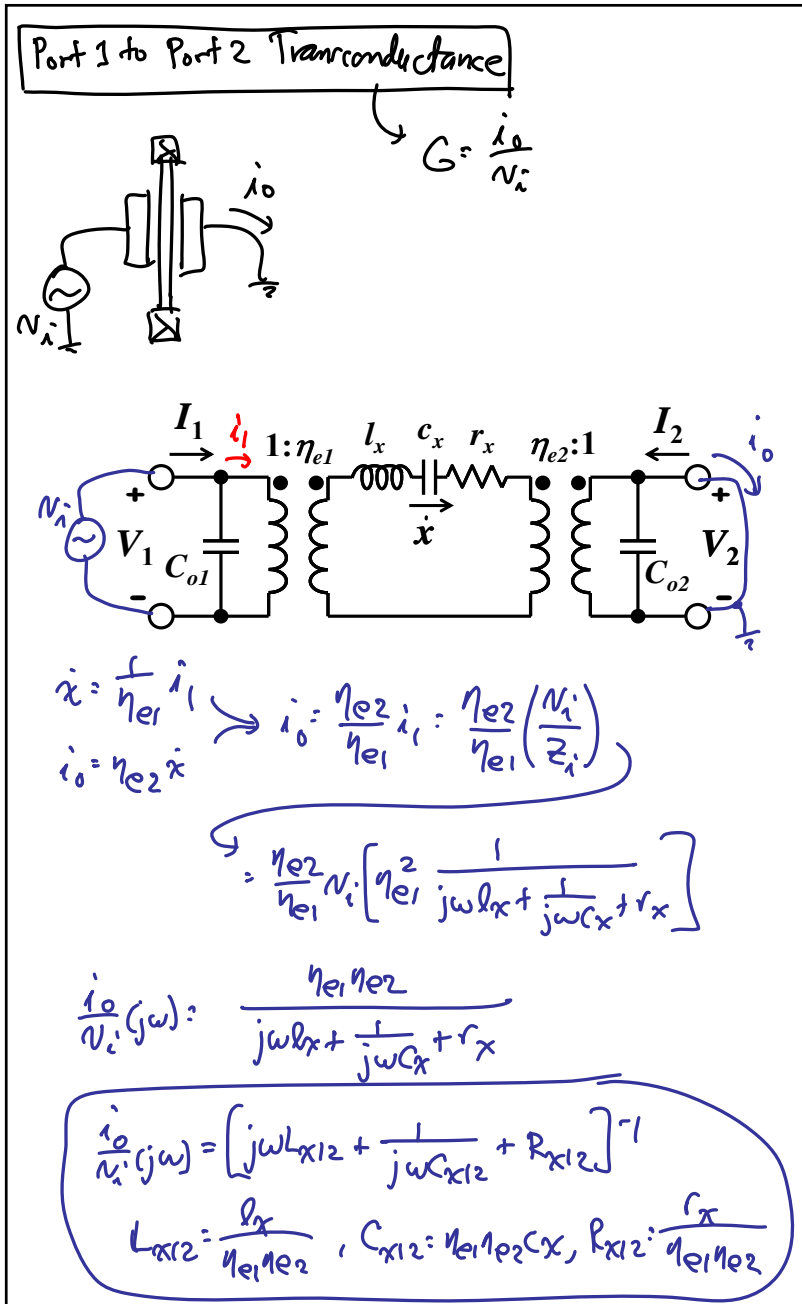

- Go through Module 15 slides 1-12

Velocity to-Voltage Conversion

represent velocity \downarrow

V_i V_P V_o R_D cantilever i_o

in phase w/ velocity
 \downarrow 90° phase shift
 \downarrow w/ displacement

$\frac{|V_o|}{V_i}$

ω

$x = \frac{QF_d}{k}$
 $\dot{x} = \frac{\omega_0 Q F_d}{k}$

F_d i_o V_P output ground

$\frac{\dot{x}}{F_d}(s) = \frac{\omega_0 Q}{k} (H)(s)$


$[F_d = \eta_1 V_i]$

$\frac{\dot{x}}{V_i}(s) = \eta_1 \frac{\omega_0 Q}{k} (H)(s)$

$[i_o = \eta_2 x] \Rightarrow \frac{i_o}{V_i}(s) = \eta_1 \eta_2 \frac{\omega_0 Q}{k} (H)(s)$

$\frac{1}{R \times 12} = \frac{\eta_1 \eta_2 Q}{m \omega_0} (H)(s)$

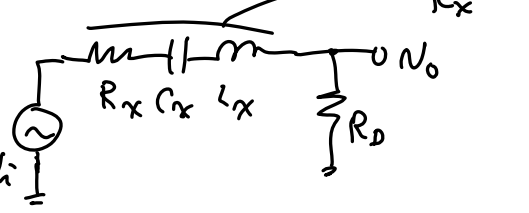Now, include R_D : $Q = \frac{\omega_0 L_x}{R_x}$



$$\frac{v_o(s)}{v_i(s)} = \frac{R_D}{R_D + R_x + \frac{1}{sC_x} + sL_x} = \dots \text{math} \dots$$

$$= \frac{R_D}{R_D + R_x} \frac{s \left(\frac{R_x + R_D}{L_x} \right)}{s^2 + s \left(\frac{R_x + R_D}{L_x} \right) + \frac{1}{L_x C_x}}$$

Gain Term Freq. Shaping Term

$$\left[Q \cdot \frac{\omega_0 L_x}{R_x} \rightarrow Q' = \frac{\omega_0 L_x}{R_x + R_D} \rightarrow \frac{R_x + R_D}{L_x} = \frac{\omega_0}{Q'} \right]$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \frac{s(\omega_0/Q')}{s^2 + s(\omega_0/Q') + \omega_0^2}$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_D + R_x} \cdot \textcircled{H}(s, Q')$$

\uparrow
 $Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$

proportional to velocity

