


Lecture 22: Sense Circuit Non-Ideality & Integration

- Announcements:
- Modules 16 online
- HW#6 online and due this coming Friday morning
- Project slide #3 due Friday, May 1
- -----
- Reading: Senturia Chpt. 14, 15
- Lecture Topics:
 - ↳ Ideal Op Amps
 - ↳ Op Amp Non-Idealities
 - ↳ MEMS-Transistor Integration
 - Mixed
 - MEMS-First
 - MEMS-Last
 - ↳ Op Amp Non-Idealities (cont.)
- -----
- Last Time:
- Discussed sensing circuits; ended up in Module 15
- Interrupt this a bit and go to Module 16 on Sense Circuit Non-Ideality & Integration

↪ over

Effect of Finite Gain & BW

Example: Non-Inverting Amplifier

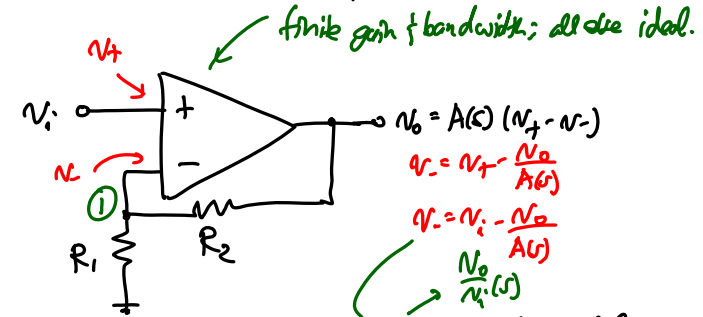

Find an expression for gain as a function of frequency.

$$\text{KCL } \textcircled{1}: \frac{v_o - v_-}{R_2} = \frac{v_-}{R_1} \rightarrow \frac{v_o}{R_2} = v_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{v_o}{R_2} = \left(v_i - \frac{v_o}{A(s)} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{v_o}{v_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$$

$$\left[A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \Rightarrow \frac{v_o}{v_i}(s) = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b \left(\frac{R_1 + R_2}{R_1} \right)}} \quad j\omega$$

Gain Term Freq. Shaping Term

Now $\omega_{-3dB} = A_0 \omega_b \left(\frac{R_1}{R_1 + R_2} \right) > \omega_b$

Now Gain: $\left(1 + \frac{R_2}{R_1} \right) < A_0$

In fact, $A_0 \omega_b = \text{constant}$