

Lecture 24: Equivalent Input-Referred Noise

- Announcements:
- HW#7 online next week and due Friday morning, May 8
- Project slide #3 due Friday, May 1
- -----
- Reading: Senturia Chpt. 16
- Lecture Topics:
 - ↳ Minimum Detectable Signal
 - ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
 - ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination
- -----
- Last Time:
- Noise & noise calculations, ending up in Module 17, slide 29
- Now, continue with input referred noise

over

Gyroscope Drive-to-Sense Xfr Fcn

Drive/Response Spectra:

Rotation-Induced Coriolis Force:

$$\vec{a}_c = 2\vec{x}_d \times \vec{\Omega}$$

$= 2\omega_d \vec{x}_d \times \vec{\Omega} \rightarrow$ acts in the sense mode direction

$$a_s = a_c = 2\omega_d x_d \Omega \sin 90^\circ$$

$a_s = 2\omega_d x_d \Omega$

↑ rotation rate

↑ drive radian frequency ↑ drive displacement amplitude

$$F_c = m a_s = m a_c$$

Example: Trans R Amplifier Input Referred Noise

Case I

Case II

Want to find these

Noiseless

Input-referred Current Noise:

Open inputs; equate output voltage noise for Case I & II:

Case I:

$i_{io}^2: N_{out1} = i_{io} R_f \rightarrow N_{out1}^2 = i_{io}^2 R_f^2$ → power @ output generated by noise source

$i_f^2: N_{out2} = i_f R_f \rightarrow N_{out2}^2 = i_f^2 R_f^2$

$N_{1a}^2: N_{out3} = N_{1a} \rightarrow N_{out3}^2 = N_{1a}^2$

$\therefore N_{out}^2 = i_{io}^2 R_f^2 + i_f^2 R_f^2 + N_{1a}^2$

Case II: $N_{out}^2 = i_{eq}^2 R_f^2$

Now, set $N_{out}^2 = N_{out}^2$: $i_{eq}^2 = i_{io}^2 + i_f^2 + \frac{N_{1a}^2}{R_f^2}$

Now, get the input-referred voltage-noise:

Short inputs; equate output voltage noise.

Case I

Case II

Want to find these

Noiseless

Case I: $N_{out} = a N_{1a} \rightarrow N_{out}^2 = a^2 N_{1a}^2$

Case II: $N_{out} = a N_{eq} \rightarrow N_{out}^2 = a^2 N_{eq}^2$

$N_{out}^2 = N_{out}^2: N_{eq}^2 = N_{1a}^2$