

Lecture 25: Equivalent Input-Referred Noise

- Announcements:
- HW#7 online next week and due Friday morning, May 8
- Project slide #3 due Friday, May 1
- You should be sending me these slides to get feedback
- Project Outbrief Sign-up: → Tu, W
- This is our last lecture

• Reading: Senturia Chpt. 16

• Lecture Topics:

↳ Minimum Detectable Signal

↳ Noise

- Circuit Noise Calculations
- Noise Sources
- Equivalent Input-Referred Noise

↳ Gyro MDS

- Equivalent Noise Circuit
- Example ARW Determination

- Course Wrap Up
- Final Exam Info
- Course evaluations

• Last Time:

- Input referred noise

↪ over

Gyroscope Drive-to-Sense Xfr Fcn

Drive Mode
Driven Velocity: $\dot{x}_d = \omega_d x_d$

Sense Mode
Sense Velocity: $\dot{x}_s = \omega_s x_s$

Drive/Sense Response Spectra:

Rotation-Induced Coriolis Force:

$$\vec{a}_c = 2\vec{x}_d \times \vec{\Omega}$$

$= 2\omega_d \vec{x}_d \times \vec{\Omega} \rightarrow$ acts in the sense mode direction

$$a_s = a_c = 2\omega_d x_d \Omega \sin 90^\circ$$

$a_s = 2\omega_d x_d \Omega$

rotation rate

drive radian frequency drive displacement amplitude

$$F_c = m a_s = m a_c$$

Example: Trans R Amplifier Input Referred Noise

Case I

Case II

Want to find these

Noiseless

Input-referred Current Noise:

Open inputs; equate output voltage noise for Case I & II:

Case I:

$i_{io}^2: N_{oI1} = i_{io} R_f \rightarrow N_{oI1}^2 = i_{io}^2 R_f^2$ → power @ output generated by noise source

$i_f^2: N_{oI2} = i_f R_f \rightarrow N_{oI2}^2 = i_f^2 R_f^2$

$N_{1a}^2: N_{oI3} = N_{1a} \rightarrow N_{oI3}^2 = N_{1a}^2$

$\therefore N_{oI}^2 = i_{io}^2 R_f^2 + i_f^2 R_f^2 + N_{1a}^2$

Case II: $N_{oII}^2 = i_{eq}^2 R_f^2$

Now, set $N_{oI}^2 = N_{oII}^2: i_{eq}^2 = i_{io}^2 + i_f^2 + \frac{N_{1a}^2}{R_f^2}$

Now, get the input-referred voltage-noise:
Short inputs; equate output voltage noise.

Case I

Case II


Want to find these

Noiseless

Case I: $N_{oI} = a N_{1a} \rightarrow N_{oI}^2 = a^2 N_{1a}^2$

Case II: $N_{oII} = a N_{eq} \rightarrow N_{oII}^2 = a^2 N_{eq}^2$

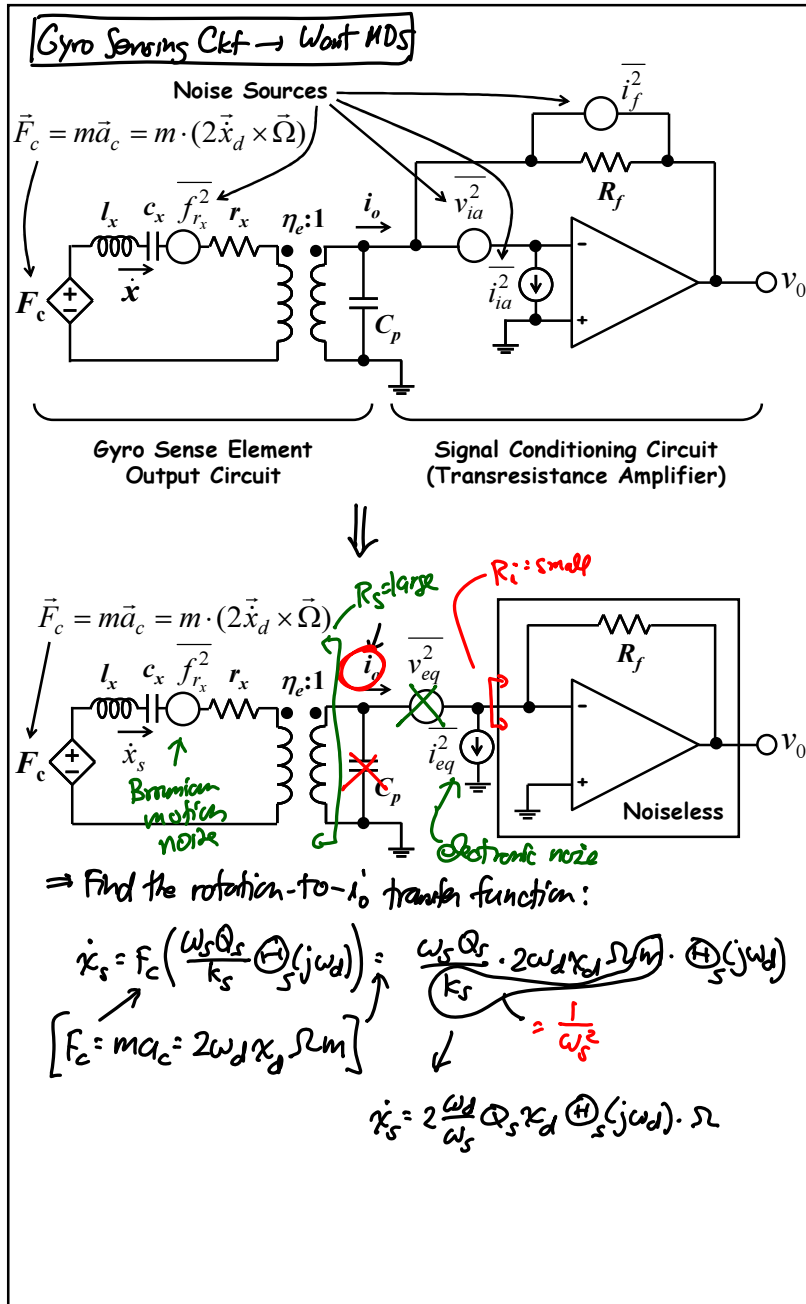$N_{oI}^2 = N_{oII}^2: N_{eq}^2 = N_{1a}^2$




$$\mathcal{H}(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$s=0: \mathcal{H}(0) = 0$

$s=j\omega_0: \mathcal{H}(j\omega_0) = 1$

$s=\infty: \mathcal{H}(\infty) = 0$

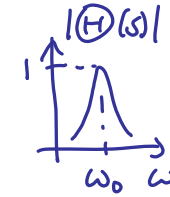

$$i_o = \eta_e \dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \dot{x}_d \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$$

$A \triangleq \text{scale factor}$

$$\Rightarrow i_o = A \Omega, \text{ where } A = 2 \frac{\omega_d}{\omega_s} Q_s \dot{x}_d \eta_e \mathcal{H}_s(j\omega_d)$$

input rotation

When $\Omega = \Omega_{min} \triangleq \text{MDS} \rightarrow i_o = i_{eqTOT}$

input-referred noise current enters the same amplifier (in pA/√Hz)

$\therefore i_{eqTOT} = A \Omega_{min}$

$$\Omega_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) \left[\frac{(\circ/hr)}{\sqrt{Hz}} \right]$$

$$\text{Angle Random Walk} = \text{ARW} = \frac{1}{60} \Omega_{min} \left[\frac{\circ}{\sqrt{hr}} \right]$$

↳ Easier to determine directional error as a function of elapsed time.

- Related courses at UC Berkeley:
 - ↳ EE 143: Microfabrication Technology
 - ↳ EE 147/247A: Introduction to MEMS
 - ↳ ME 119: Introduction to MEMS (mainly fabrication)
 - ↳ BioEng 121: Introduction to Micro and Nano Biotechnology and BioMEMS
 - ↳ ME C219 - EE C246: MEMS Design
 - ↳ EE 290M?