

Lecture 23: Mechanical Circuit Analysis

- **Announcements:**

- **Module 13 on Equivalent Circuits II** online
  - **HW#6** online and due Friday, April 22
  - **Module 14 on Sensing Circuits** online
  - **Module 15 on Gyros, Noise, & MDS** online
  - **Project slide #2** due Friday, April 15
  - -----
  - **Reading:** Senturia, Chpt. 6, Chpt. 14
  - **Lecture Topics:**

Input Modeling

- Force-to-Velocity Equiv. Ckt.
  - Input Equivalent Ckt.

## Current Modeling


- #### -Output Current Into Ground

### — Input Current

- #### -Complete Electrical-Port Equiv. Ckt.


◀ Impedance & Transfer Functions

- Reading: Senturia, Chpt. 14, Chpt. 16, Chpt. 21
  - Lecture Topics:
    - ↳ Gyroscopes
  - Reading: Senturia, Chpt. 14
  - Lecture Topics:
    - ↳ Detection Circuits
      - Velocity Sensing
      - Position Sensing

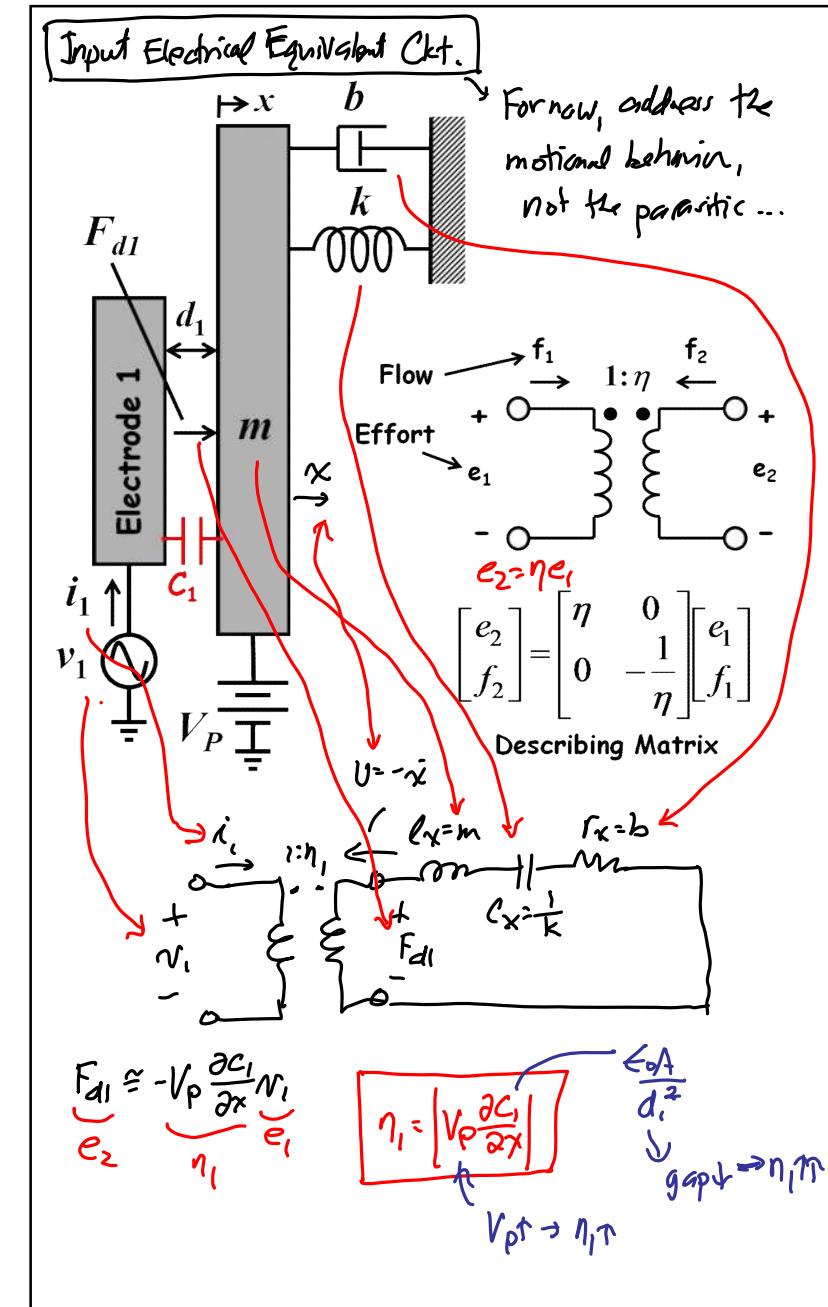

Lecture 23w: Mechanical Circuit Analysis

Output Current Into Ground

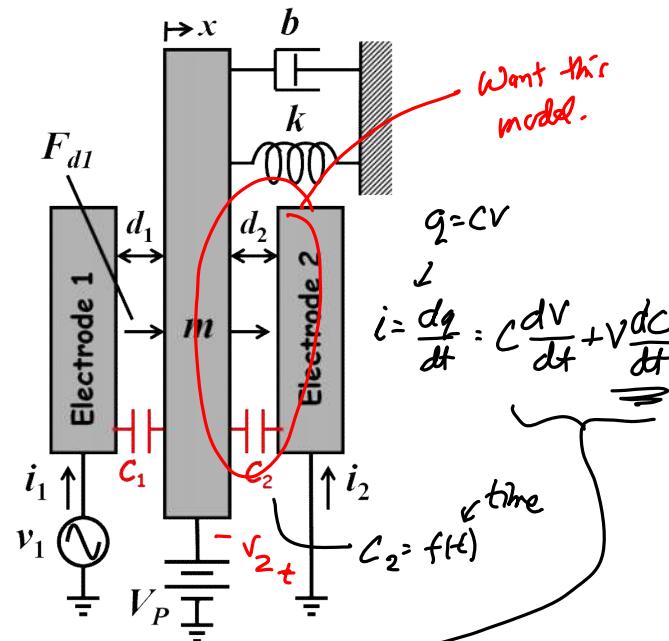

$$i_2 = C_2(x, t) \frac{dV_2(t)}{dt} + V_2(t) \frac{dC_2(x, t)}{dt}$$

$$\{V_2(t) = -V_p\} \Rightarrow i_2 = -V_p \frac{dC_2}{dt} = -V_p \frac{\partial C_2}{\partial x} \frac{\partial x}{\partial t}$$

In phasor form:


$$I_2(j\omega) = -V_p \frac{\partial C_2}{\partial x} (j\omega x)$$

$$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X$$

↳ motion current

$$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X = -V_p \frac{\partial C_2}{\partial x} \dot{x}$$

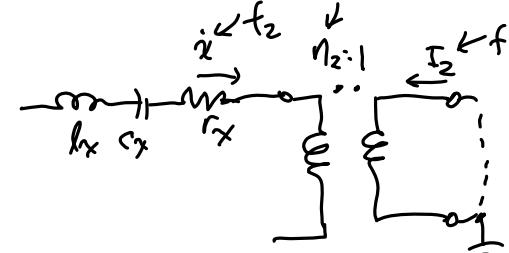
90° phase lag (+) →  $I_2 = (-)$  when  $x > (t)$




$$f_2 = -\frac{1}{\eta_2} f_1 \rightarrow f_1 = -\eta_2 f_2$$

$$\{f_1 = I_2, f_2 = \dot{x}\} \Rightarrow I_2 = -\eta_2 \dot{x}$$

$$\therefore \eta_2 = |V_p \frac{\partial C_2}{\partial x}|$$

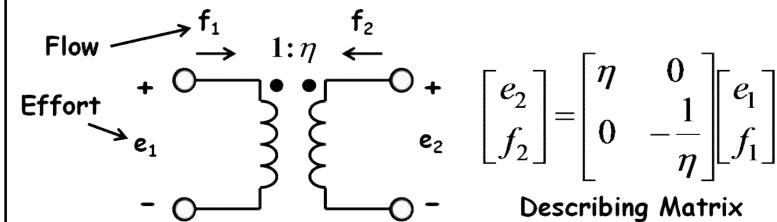

Input Current Expression

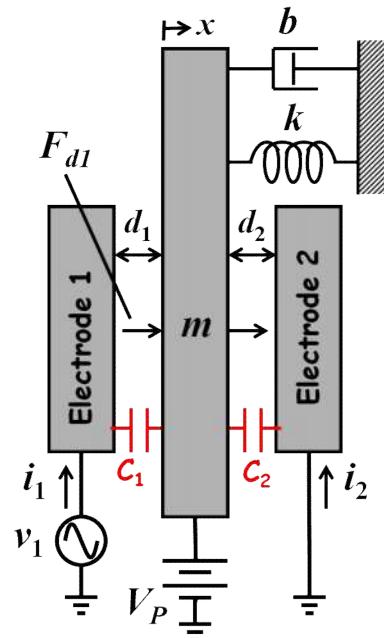

Get  $I_1(j\omega)$ :

$$i_1(t) = C_1(x, t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC_1(x, t)}{dt}$$

$$\left[ V_1(t) = N_1 - V_p \right] \Rightarrow i_1 = C_1 \frac{dV_1}{dt} + [N_1 - V_p] \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$\uparrow$   
 $t(t)$

due to mass motion

$$\therefore I_1(j\omega) = j\omega C_1 V_1 + j\omega N_1 \frac{\partial C_1}{\partial x} X - j\omega V_p \frac{\partial C_1}{\partial x} X$$

Feedthrough Current

Motional Current

$$@DC: x = \frac{F_{d1}}{k} = -\frac{1}{k} V_p \frac{\partial C_1}{\partial x} N_1$$

$$@resonance: x = \frac{Q F_{d1}}{jk} = -\frac{Q}{jk} V_p \frac{\partial C_1}{\partial x} N_1 = \underline{x}$$

$\rightarrow \omega_0$        $\uparrow 90^\circ$  phase lag

Thus: (@resonance)


$$I_1(j\omega) = j\omega_0 C_1 V_1 + \omega_0 \frac{Q}{k} \eta_{e1}^2 N_1$$

$\uparrow$        $\uparrow$   
 $i_p$        $i_x$

$90^\circ$  phase-shifted  
from  $V_1$

In phase w/  $N_1$ .

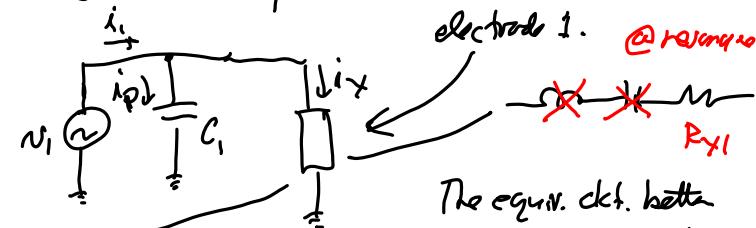This is an effective  
resistance @  $\omega_0$   
seen looking into  
electrode 1.



The equiv. ckt. better  
got this right!



Motional Resistance:

$$R_{xi} = \frac{N_1}{i_1} = \frac{k}{\omega_0 Q \eta_{e1}^2} = \frac{m \omega_0}{Q \eta_{e1}^2} = \boxed{\frac{b}{\eta_{e1}^2} = R_{xi}}$$

- Look at slide 16 in Module 13

Lecture 23w: Mechanical Circuit Analysis


Input Impedance Into Port 1

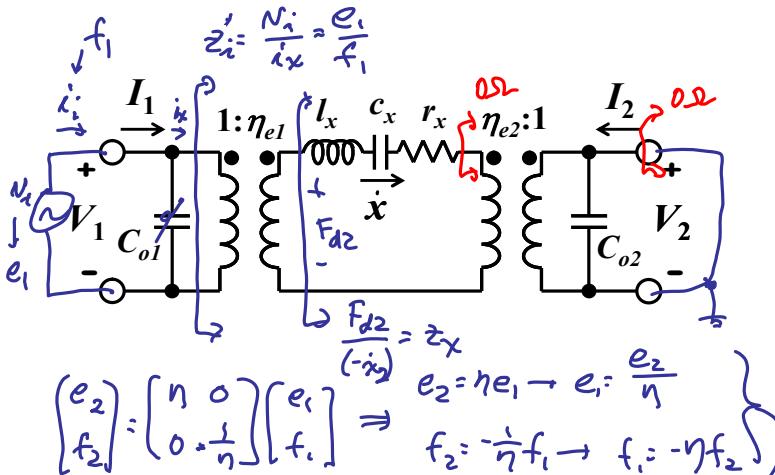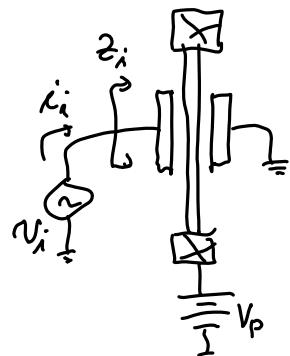


$$\frac{e_1}{i_1} = \frac{e_2}{i_1} \left( -\frac{1}{n f_2} \right) = -\frac{1}{n^2 f_2} e_2 \rightarrow \frac{N_i}{Z_i} = z_i' = -\frac{1}{n_e1^2} \frac{F_{d2}}{(-i_2)} = \frac{1}{n_e1^2} Z_x$$


$$Z_x = j\omega L_x + \frac{1}{j\omega C_x} + R_x$$
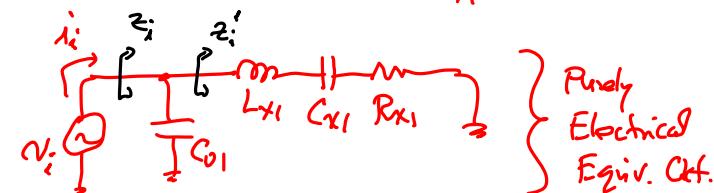
$$z_i' = \frac{1}{n_e1^2} Z_x = \frac{1}{n_e1^2} (j\omega L_x + \frac{1}{j\omega C_x} + R_x) \\ = j\omega \underbrace{\left( \frac{L_x}{n_e1^2} \right)}_{L_{x1}} + \frac{1}{j\omega \underbrace{(n_e1^2 C_x)}_{C_{x1}}} + \frac{R_x}{n_e1^2} \underbrace{\rightarrow R_{x1}}$$



Xforma Inspection Analysis

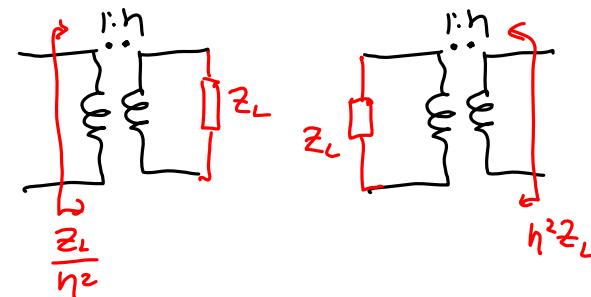

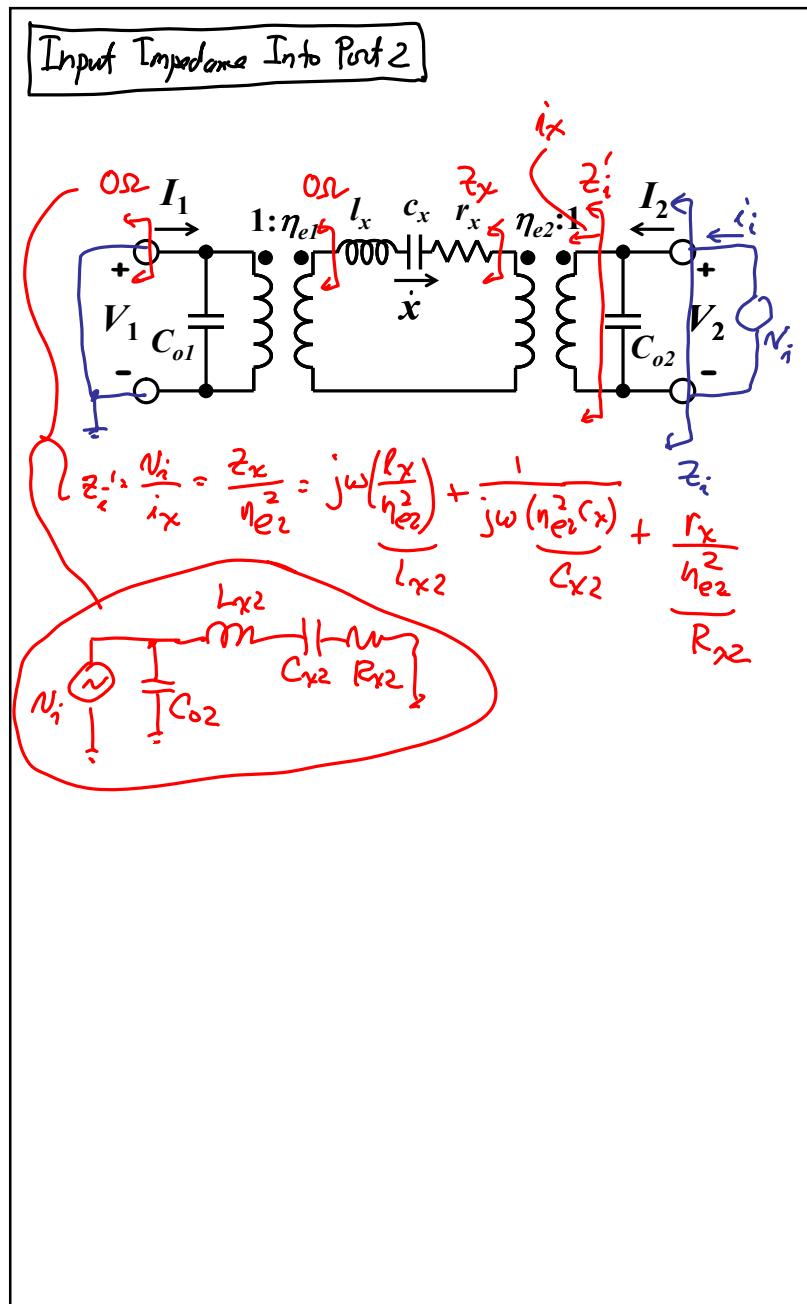Lecture 23w: Mechanical Circuit Analysis

Port 1 to Port 2 Transconductance

$$G = \frac{i_o}{V_i}$$

$$i_x = \frac{1}{n_{e1}} i_1$$

$$i_o = n_{e2} i_x \rightarrow i_o = \frac{n_{e2}}{n_{e1}} i_1 = \frac{n_{e2}}{n_{e1}} \left( \frac{V_i}{Z_i} \right)$$

$$= \frac{n_{e2}}{n_{e1}} \left[ \frac{V_i^2}{j\omega R_x + \frac{1}{j\omega C_x} + f_x} \right]$$

$$\therefore G = \frac{i_o}{V_i} (j\omega) = \frac{n_{e1} n_{e2}}{j\omega R_x + \frac{1}{j\omega C_x} + f_x}$$

$$= \left[ j\omega L_{x12} + \frac{1}{j\omega C_{x12}} + R_{x12} \right]^{-1}$$

\*

Lecture 23w: Mechanical Circuit Analysis


$$L_{x12} = \frac{l_x}{\eta_e, \eta_{e2}}, C_{x12} = \eta_{e1} \eta_{e2} C_x, R_{x12} = \frac{r_x}{\eta_{e1}, \eta_{e2}}$$

$\Rightarrow$  Separate freq. response & magnitude

$$\frac{i_o}{N_i}(s) = \frac{1}{sL_x + \frac{1}{sC_x} + R_x} = \frac{s(\frac{1}{L_x})}{s^2 + \frac{1}{L_x C_x} + s(\frac{R_x}{L_x})}$$

$$\left[ \frac{1}{L_x C_x} = \omega_0^2, Q = \frac{\omega_0 L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0}{Q} \right]$$
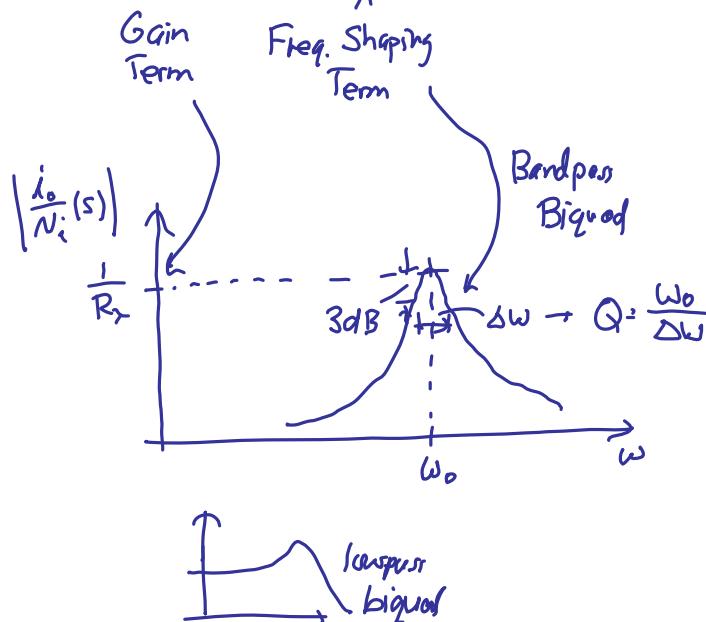
$$\frac{i_o}{N_i}(s) = \frac{1}{R_x} \frac{s(\frac{\omega_0}{Q})}{s^2 + s(\frac{\omega_0}{Q}) + \omega_0^2} = \frac{1}{R_x} H(s)$$



- Now, go through slides 21-22 in Module 13
- Then, start gyroscopes by going through slides 1-6 in Module 15