

Position-to-Voltage Conversion

UC Berkeley

- To sense position (i.e., displacement), use a capacitive load

Again, have port-to-port I/O symmetry:

Brute force approach:

$$\frac{N_o}{V_i}(s) = \frac{1}{R_x + \frac{1}{sC_x} + sLx + \frac{1}{sC_D}}$$

$$\frac{N_o}{V_i}(s) = \frac{\frac{AC_x}{sC_D}}{sR_xC_x + 1 + s^2LxC_x + \frac{AC_x}{sC_D}} = \frac{C_x/C_D}{1 + \frac{sR_xC_x}{1+C_x/C_D} + s^2 \frac{LxC_x}{1+C_x/C_D}}$$

$$= \frac{C_x/C_D}{1 + C_x/C_D} \frac{1}{s^2 + s \left(\frac{R_x}{Lx} \right) + \left(\frac{1+C_x/C_D}{LxC_x} \right)}$$

$\omega_0^2 = \frac{1}{LxC_x} \rightarrow (\omega_0')^2 = \omega_0^2 (1 + C_x/C_D)$
 $Q' = \frac{\omega_0' Lx}{R_x} \rightarrow \frac{R_x}{Lx} = \frac{\omega_0'^2}{Q'}$, $Q = Q' \sqrt{1 + C_x/C_D}$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 6

Position-to-Voltage Conversion

UC Berkeley

- To sense position (i.e., displacement), use a capacitive load

$\frac{N_o}{V_i}(s) = \frac{C_x/C_D}{1 + C_x/C_D} \frac{(\omega_0')^2}{s^2 + \left(\frac{\omega_0'}{Q'} \right) s + (\omega_0')^2}$
 DC Gain Term Low-Pass Biquad

To maximize gain $\rightarrow 1$, need $C_D \ll C_x$. (must minimize C_D)

Note: Can we similar short-cut to the R case.

- Get DC response $\rightarrow C$'s dominate.
- Then:

$\frac{N_o}{V_i}(s) = (\text{DC Gain}) \cdot \frac{1}{s} \cdot \Theta(s, \omega_0', Q')$

Voltage Representing Position vs ω

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 7

Velocity Sensing Circuits

UC Berkeley

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 8

Velocity-to-Voltage Conversion

UC Berkeley

- To convert velocity to a voltage, use a resistive load

Since this structure has completely symmetrical I/O ports:

Work @ resonance: (to simplify the analysis)

$$\frac{N_o}{V_i} = \frac{R_D}{R_x + R_D} \text{ (@ resonance)}$$

Then, generalize to off resonance:

$$\frac{N_o}{V_i} = \frac{R_D}{R_x + R_D} \Theta(s, Q')$$
, where $Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$

Voltage Representing Velocity vs ω

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 9

Problems With Purely Resistive Sensing

Now, we get: (Approximately)

$$\frac{N_0}{N_i}(s) \sim \frac{R_0}{R_x + R_0} \cdot \frac{1}{1 + \frac{s}{\omega_p}} \cdot \Theta(s, \omega_b, Q')$$

$\omega_p = \frac{1}{(R_x || R_0) C_p}$ Depend on both R_0 & C_p .

Impact depends on where ω_p is relative to ω_b .

Includes C_o , line C, bond pad C, and next stage C

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 10

Problems With Purely Resistive Sensing

- In general, the sensor output must be connected to the inputs of further signal conditioning circuits → input R_i of these circuits can load R_D .

These change w/ hook-up → not good.

Problem: need a sensing circuit that is immune to parasitics or loading.

Soln: use op amps.

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 11

The TransR Amplifier Advantage

- The virtual ground provided by the ideal op amp eliminates the parasitic capacitance C_p and R_i .
- The zero output resistance of the (ideal) op amp can drive virtually anything.

Virtual Ground ⇒ No voltage across C_p
⇒ C_p effectively isn't there!

$$N_0 = -\frac{R_2}{R_x} \Theta(s) N_i$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 12

Position Sensing Circuits

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 13

Problems With Pure-C Position Sensing

• To sense position (i.e., displacement), use a capacitive load

$$\frac{N_o}{N_i}(s) = \frac{C_x C_D}{1 + C_x C_D} \cdot \frac{1}{s} \cdot \Theta(s, \omega_0, Q) \cdot \omega_0^2$$

Integration yields displacement.
To maximize gain, minimize C_D .
⇒ Problem: parasitic capacitance
 $C_D \rightarrow C_D + C_{p1} + C_{p2}$
⇒ DC Gain: $\frac{C_x / (C_D + C_{p1} + C_{p2})}{1 + C_x / (C_D + C_{p1} + C_{p2})}$
Output will get smaller!
Remedy: Suppress C_p via use of op amps.

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 14

The Op Amp Integrator Advantage

• The virtual ground provided by the ideal op amp eliminates the parasitic capacitance C_p

$R_2 \gg \frac{1}{sC_2}$ (for biasing)
 $R_0 = 0\Omega$
Can drive next stages R_i w/o interference to transfer function!
negl. since $R_2 = \text{large}$ well defined → good!
 $N_o = -i_o (R_2 \parallel \frac{1}{sC_2})$
 $x = \frac{N_i}{R_x} \Theta(s) \frac{1}{sC_2} \Rightarrow \frac{N_o}{N_i}(s) = -\frac{1}{R_x C_2} \Theta(s) \frac{1}{s}$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 15

Differential Position Sensing

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 16

Differential Position Sensing

• Example: ADXL-50

Proof Mass
Sense Finger
Applied Acceleration
Fixed Electrodes
Suspension Beam in Tension

$C_1 \gg C_2$ Capacitive divider
 $V_o = -V_p + (2V_p) \frac{C_1}{C_1 + C_2}$
 $= \frac{-V_p C_1 - V_p C_2 + 2V_p C_1}{C_1 + C_2} = V_p \frac{C_1 - C_2}{C_1 + C_2} = V_o$
Irrig: Parasitic Capacitance
 $V_o = \frac{C_1 - C_2}{C_1 + C_2} V_p$ Arbitrary, C_p reduces gain!
Soln: use op amp!

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 17

Buffer-Bootstrapped Position Sensing

Includes capacitance from interconnects, bond pads, and C_{gs} of the op amp
 Unity Gain Buffer
 C_{gd} = gate-to-drain capacitance of the input MOS transistor

- Bootstrap the ground lines around the interconnect and bond pads
- ↳ No voltage across C_p
- ↳ It's effectively not there!

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 18

Effect of Finite Op Amp Gain

Total ADXL-50 Sense $C \sim 100\text{fF}$
 Unity Gain Buffer

Get $Z_i = \frac{V_i}{I_i}$: $I_i = (V_i - V_o) s C_p = V_i \left(1 - \frac{A_o}{1+A_o}\right) s C_p = V_i \frac{1}{1+A_o} s C_p$

$\therefore \frac{N_i}{I_i} = Z_i = \frac{1}{s \left[\frac{C_p}{1+A_o} \right]}$ $\rightarrow C_{\text{eff}} = \frac{C_p}{1+A_o}$

Ex: $A_o = 100, C_p = 2\text{pF}$
 $\Rightarrow C_{\text{eff}} = \frac{2\text{pF}}{101} = 20\text{fF}$

↳ Not negligible compared w/ ADXL-50 $C_{\text{tot}} \sim 100\text{fF}$!

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 19

Integrator-Based Diff. Position Sensing

$R_2 \gg \frac{1}{s C_2}$ (for biasing)
 $R_o = 0\Omega$
 Can drive next stage's R_i w/o interference to transfer function!

$i_o = i_1 + i_2 = N_p(s C_1) - N_p(s C_2) = V_p s (C_1 - C_2)$

$\therefore V_o = -i_o \left(\frac{1}{s C_F} \right) = -N_p \left(\frac{C_1 - C_2}{C_F} \right)$

$\frac{V_o}{V_p} = - \frac{C_1 - C_2}{C_F} \Rightarrow$ A seemingly perfect differential sensor/amplifier output! ... but only when the op amp is ideal...

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 20