

Lecture 25: Sensing Circuits II

- Announcements:
- HW#6 online and due Friday, April 22
- Module 16 on "Sensing Circuit Non-Idealities and Integration" is online
- Project slide #3 due Friday, April 29
- I am at the EECS Retreat today; this is a pre-recorded lecture

• Reading: Senturia, Chpt. 14

• Lecture Topics:

↳ Detection Circuits

- Velocity Sensing
- Position Sensing

↳ MEMS-Transistor Integration

- Mixed
- MEMS-First
- MEMS-Last

• Reading: Senturia Chpt. 16

• Lecture Topics:

↳ Minimum Detectable Signal

↳ Noise


- Circuit Noise Calculations
- Noise Sources
- Equivalent Input-Referred Noise

↳ Gyro MDS

- Equivalent Noise Circuit
 - Example ARW Determination
-

• Last Time:

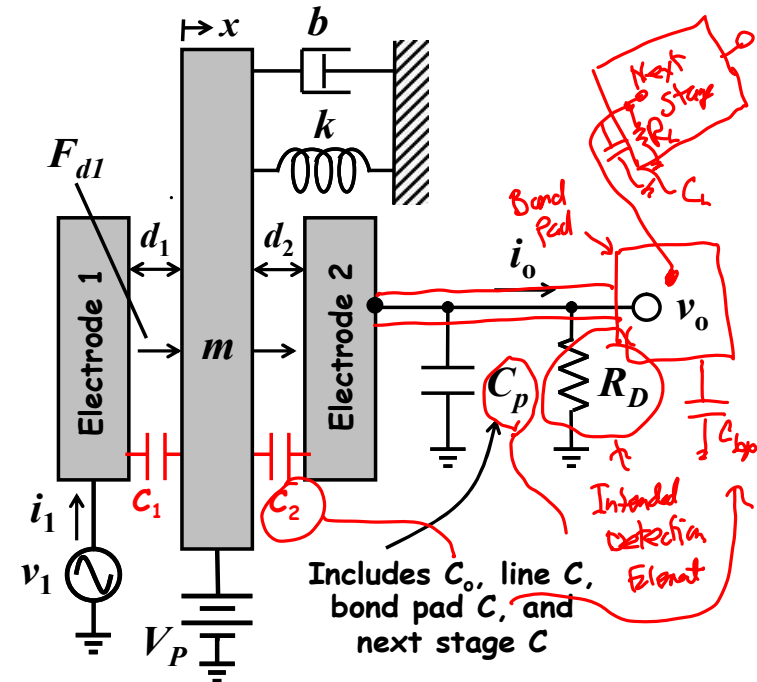
- Discussing velocity sensing; simplest way is via a resistive output load R_D
- Problem: parasitics (resistance and capacitance)



Now, we get:

$$\frac{v_o}{v_i}(s) \sim \frac{R_o}{R_x + R_D} \cdot \frac{1}{1 + \frac{s}{\omega_p}} \cdot \mathcal{H}(s, \omega_o', Q')$$


$$\omega_p = \frac{1}{(R_x/R_D)C_p}$$

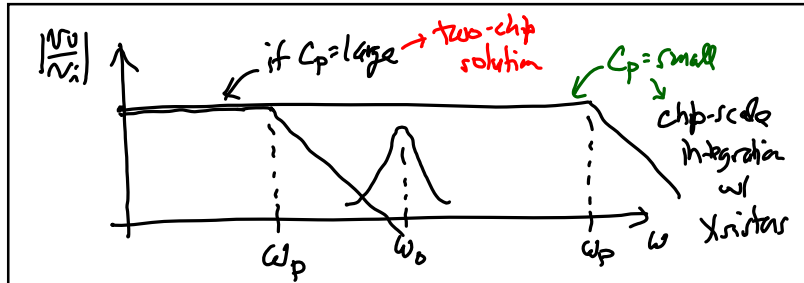

Problems w/ Purely Resistive Detectors


- ① Need large R_D for large gain... but...
- ② $R_D \uparrow \rightarrow Q \downarrow$
- ③ $R_D \uparrow \rightarrow \omega_p \propto \frac{1}{R_D C_p} \downarrow \rightarrow$ got undesirable LFP cut-off
- ④ Load $R_L \rightarrow$ affects gain!

Solution: use Xsistms \rightarrow op amp

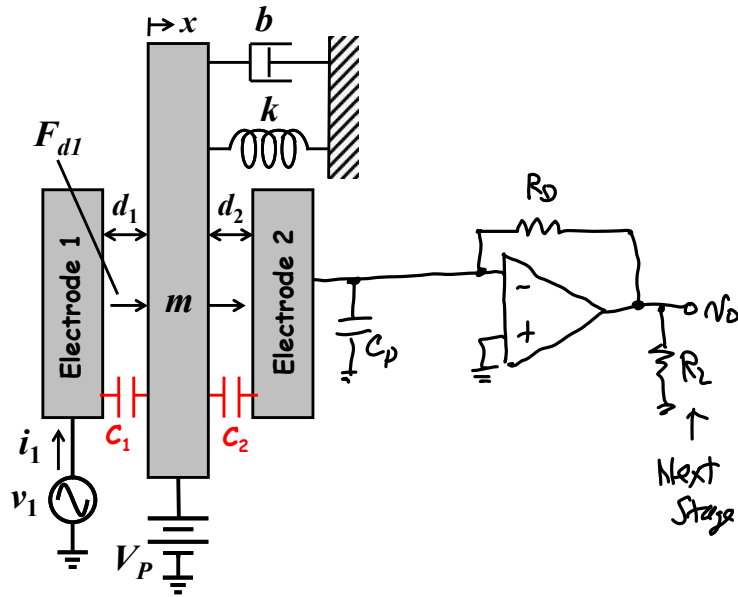



Ideal Op Amp Laws

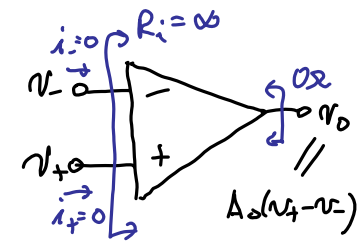- ① $R_i = \infty \rightarrow i_- = i_+ = 0$
- ② $R_o = 0$
- ③ Gain = $A_o = \infty$



neg. FB $\rightarrow v_+ = v_-$
 $v_o = \text{finite} \propto \underbrace{(v_+ - v_-)}_0 = \text{finite}$

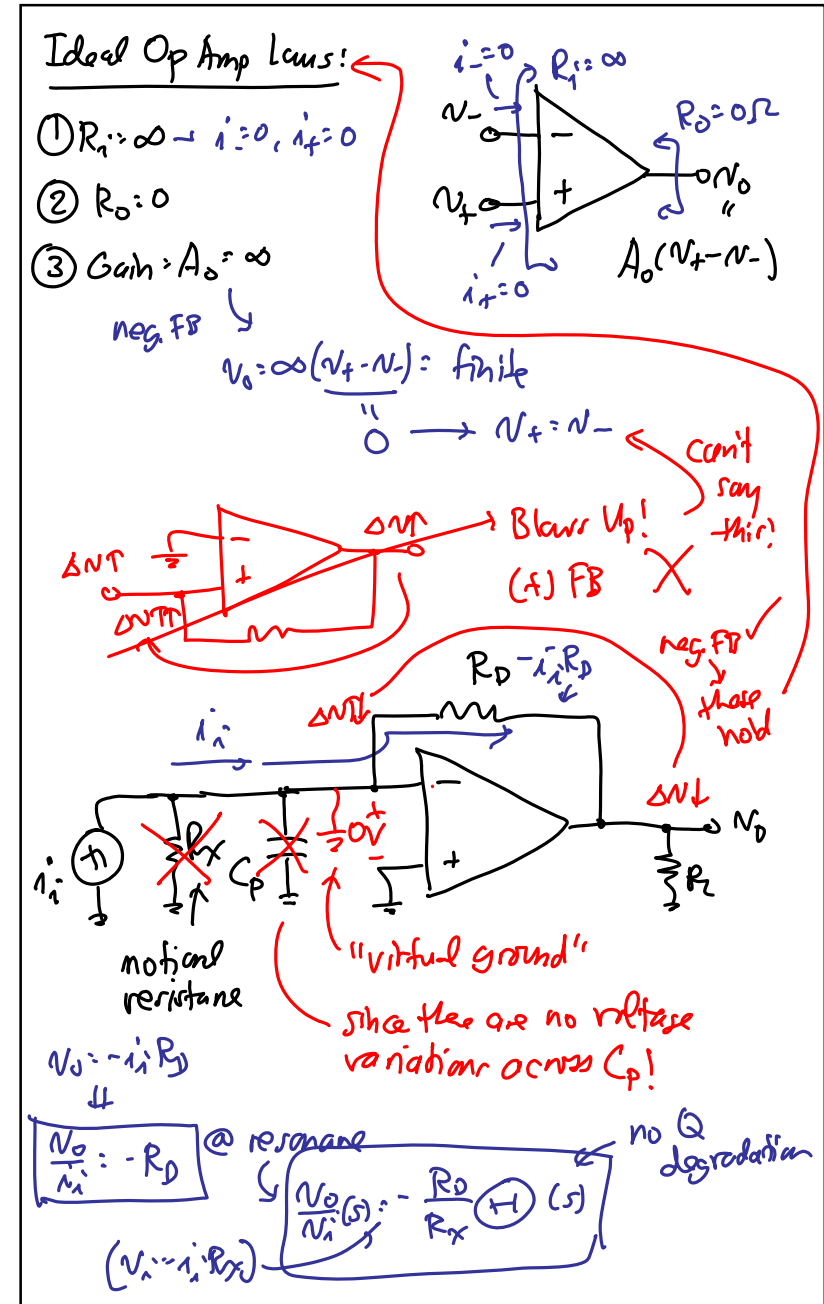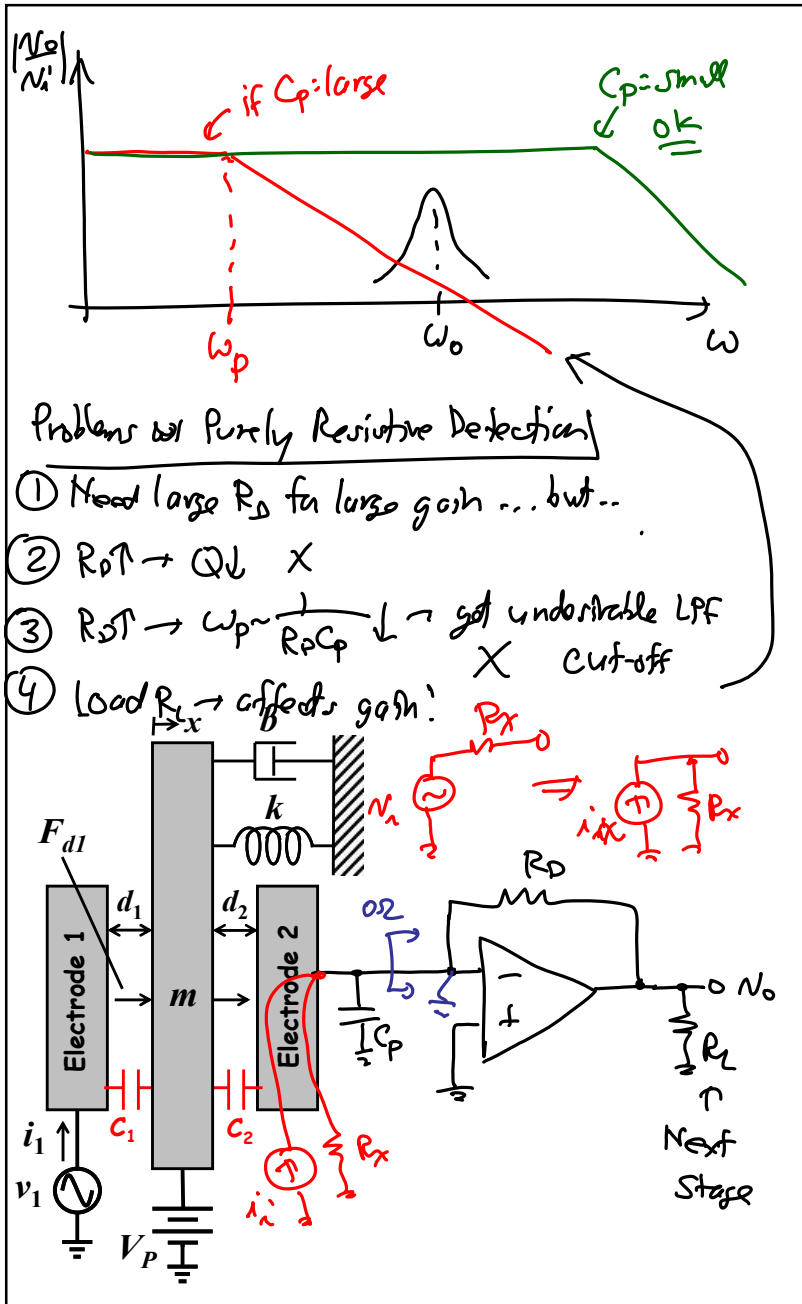- Transitioned to pre-recorded version at this point, which starts on the next page



Circuit Noise Calculations

Inputs $N_i(j\omega)$ $S_i(\omega)$ **Deterministic** **Random** **Linear Time-Invariant System** $H(j\omega)$ **Outputs** $N_o(j\omega)$ $S_o(\omega)$

$N_o(j\omega) = H(j\omega) N_i(j\omega)$

Deterministic Signals:

$N_o(j\omega) = H(j\omega) N_i(j\omega)$

Random Signals:

Mean-Square Spectral Density

$$S_o(\omega) = [H(j\omega) H^*(j\omega)] S_i(\omega) = |H(j\omega)|^2 S_i(\omega)$$

$$\sqrt{S_o(\omega)} = |H(j\omega)| \sqrt{S_i(\omega)} \rightarrow \text{How is it we can do this?}$$

Rest mean-square amplitudes

$\omega_j \rightarrow$ noise has random phase, so j is pointless!

(Handling Noise Deterministically)

$$\frac{\overline{N_{nr}^2}}{\Delta f} = S_i(f) \rightarrow N_{nr} = \sqrt{S_i(f) B}$$

Can approximate this by a sinusoidal voltage generator (esp. when B is small, say 1Hz)

Why is this the case? white noise

$\tau \sim \frac{1}{B}$

Neither the amplitude nor the phase of a signal can change appreciably within a time period $\sim 1/B$!

Systematic Noise Calculation Procedure

General Ckt. w/ several Noise Sources

Assume noise sources are uncorrelated.

- ① For i_{n1}^2 , replace w/ a deterministic source of value $i_{nr} = \sqrt{\frac{i_{n1}^2}{\Delta f} \cdot (1Hz)}$
- ② Calculate $N_{out}(\omega) = i_{nr}(\omega) H_c(j\omega)$ (treating it like a deterministic signal)
- ③ Determine $N_{out}^2 = i_{nr}^2 \cdot |H_c(j\omega)|^2$
- ④ Repeat for each noise source:
 $N_{n2}^2, N_{n3}^2, i_{n4}^2, \dots \rightarrow$ output

- ⑤ Add noise power (mean-square values)

$$\overline{N_{out}^2} = \overline{N_{out1}^2} + \overline{N_{out2}^2} + \overline{N_{out3}^2} + \overline{N_{out4}^2} + \dots$$

$$N_{out} = \sqrt{\overline{N_{out1}^2} + \overline{N_{out2}^2} + \overline{N_{out3}^2} + \overline{N_{out4}^2} + \dots}$$

↑
total rms value

- Go through Module 17, slides 12-16

Why $\frac{N_{nr}^2}{\Delta f} \approx 4kTR$? (a heuristic argument)

Consider an RC ckt:

$$E = \frac{1}{2}kT = \frac{1}{2}C\overline{N_c^2}$$

$$\therefore \overline{N_c^2} = \frac{kT}{C} \leftarrow \text{integrated noise over all freq. (total mean-square voltage integrated over all freq.)}$$

* →

Question: What value of $\frac{\overline{V_R^2}}{\Delta f}$ gives us this (assuming white noise) *

$$\overline{V_C^2} = \int_0^\infty \left| \frac{1}{1+j\omega RC} \right|^2 \frac{\overline{V_R^2}}{\Delta f} d\omega$$


[noise is white] $\rightarrow = \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \int_0^\infty \frac{\omega_b^2}{\omega_b^2 + \omega^2} d\omega$
 $[\omega_b = \frac{1}{RC}]$

$$\left[\int \frac{dx}{x^2+a^2} = \frac{1}{a} \tan^{-1}\left(\frac{x}{a}\right) \right]$$

$$= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \frac{\omega_b^2}{\omega_b} \tan^{-1}\left(\frac{\omega}{\omega_b}\right) \Big|_0^\infty$$



$$= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \left(\frac{\pi}{2} \omega_b - 0 \right) = \frac{1}{4} \omega_b \frac{\overline{V_R^2}}{\Delta f} = \frac{KT}{C}$$
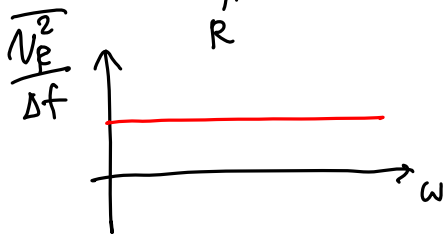
$$\frac{\overline{V_R^2}}{\Delta f} = 4KT \left(\frac{\omega_b}{C} \right) \Rightarrow \frac{\overline{V_R^2}}{\Delta f} = 4KTR$$




• Go through Module 17, slides 19-20

Example. Typical Noise Numbers

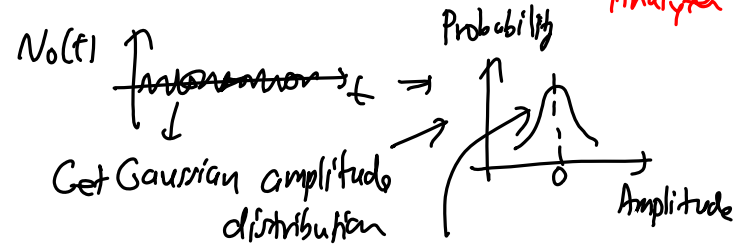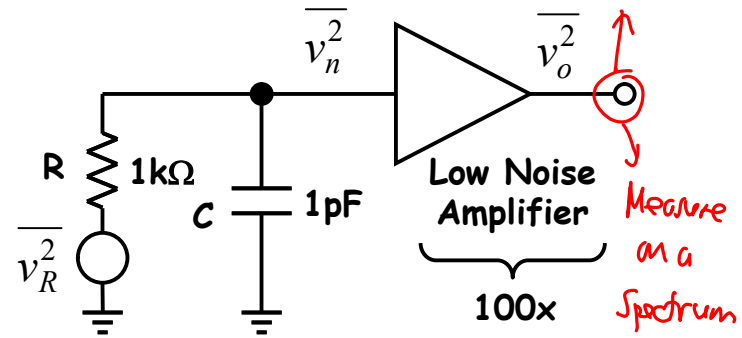

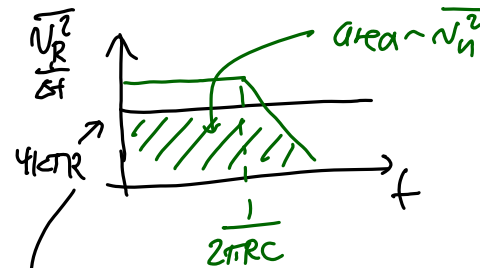68% within $\pm\sigma$
99.7% within $\pm 3\sigma$



$$R = 1k\Omega \rightarrow \sqrt{(1.66 \times 10^{-20}) / (1K)}$$


* - $1k\Omega$: $4nV/\sqrt{Hz}$ (for every $1k\Omega$)

$$1pF: \sqrt{\frac{kT}{C}} = 64\mu V_{rms}$$

Case: AC Voltmeter

$$\sqrt{N_0^2} = (100)(64\mu V_{rms}) = \underline{6.4mV_{rms}}$$

Case: Spectrum Analyzer

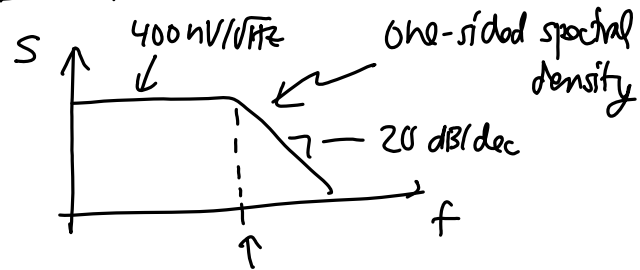

$$\frac{1}{2\pi(1k)(1p)} = 60MHz$$

• Go through Module 17, slides 23-29