

Lecture 26: Equivalent Input Noise

• Announcements:

- HW#7 online and due Friday, May 6
 - ↳ No need to turn in HW#7; we'll just give you time to do it, then release solutions on May 6
 - ↳ You will need to understand this material for the Final Exam, so it's in your best interest to do the homework
- Project slide #3 due Friday, April 29, at 8 a.m.
- Project outbrief sign up sheet will be on Prof. Nguyen's office door tonight
 - ↳ Slots will be on Thursday and Friday of next week

• Reading: Senturia Chpt. 16




• Lecture Topics:

- ↳ Minimum Detectable Signal
- ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
- ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination

• Last Time:

- Noise & noise calculations, ending up in Module 17, slide 29
- Now, continue with input referred noise

Example. Typical Noise Numbers

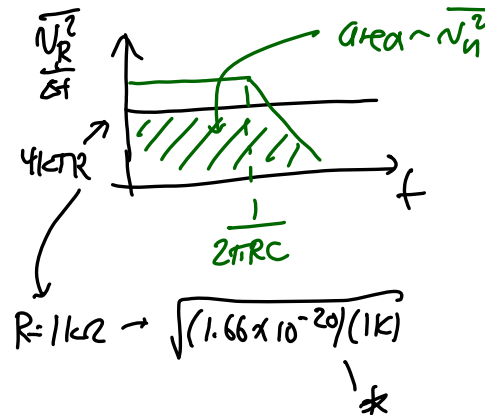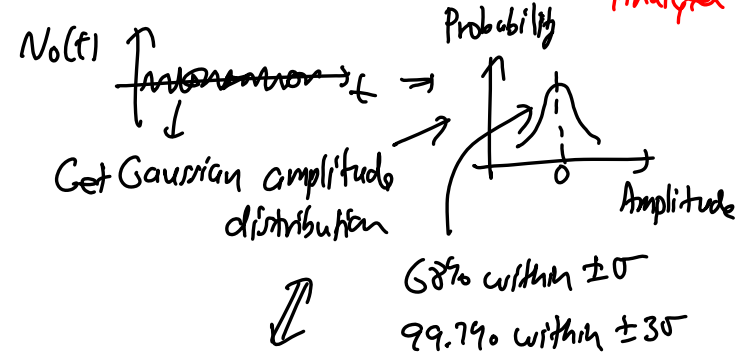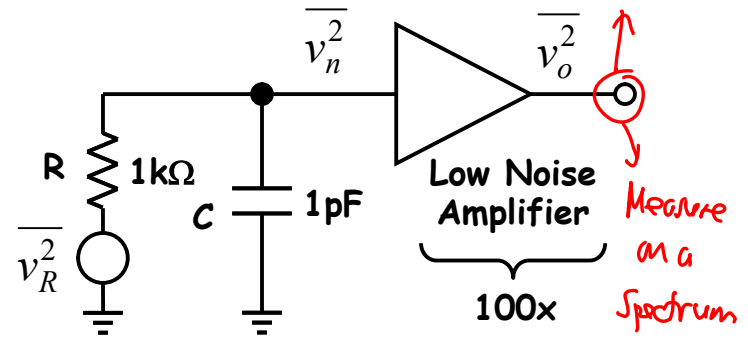


* - $1k\Omega$: $4nV/\sqrt{Hz}$ (for every $1k\Omega$)

$$1pF: \sqrt{\frac{KT}{C}} = 64\mu V_{rms}$$

Case: AC Voltmeter

$$\sqrt{N_0^2} = (100)(64\mu V_{rms}) = \underline{6.4mV_{rms}}$$




Case: Spectrum Analyzer

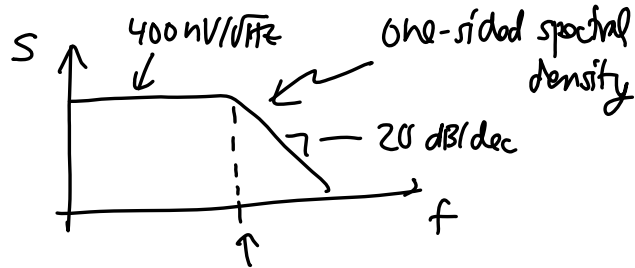

$$\frac{1}{2\pi(1k)(1p)} = 60MHz$$

- Go through Module 17, slides 23-29
- Actually, went quickly through quite a few slides from Module 17, since it seems not many actually finished watching the video from last Thursday

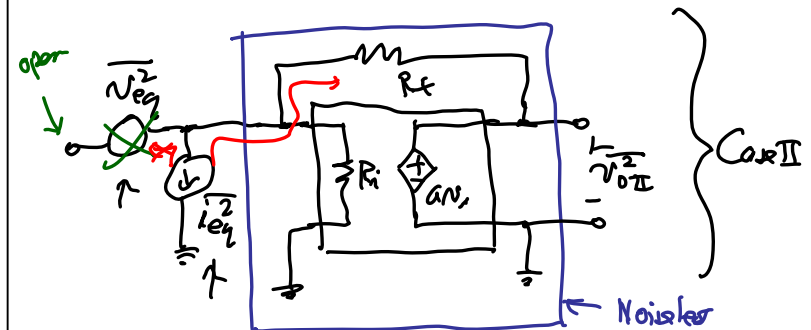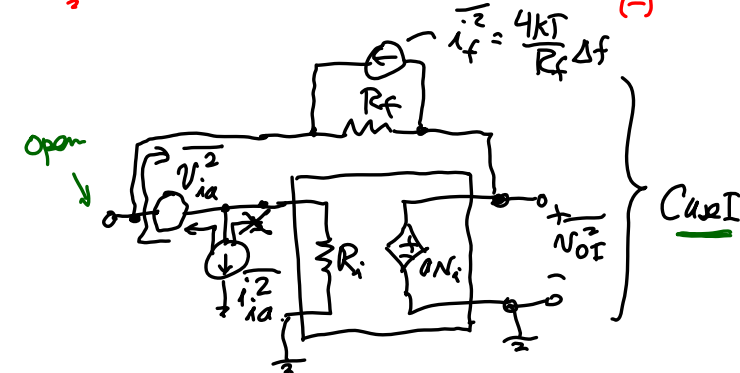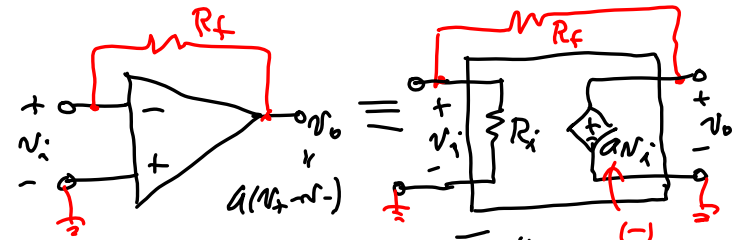Example: Trans R Amplifier Input-Referred Noise




Input-Referenced Current Noise:

Open inputs; equate output voltage noise for
 Case I & Case II \rightarrow solve for i_{eq}^2

Case I: (w/ superposition)

$i_{ia}^2: N_{oI1} = i_{ia} R_f \rightarrow \overline{N_{oI1}^2} = \overline{i_{ia}^2} R_f^2$
 $i_f^2: N_{oI2} = i_f R_f \rightarrow \overline{N_{oI2}^2} = \overline{i_f^2} R_f^2$

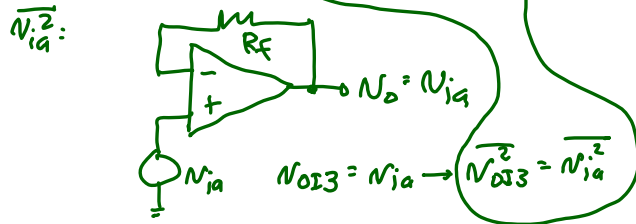power @
output
generated
by noise
sources



$\therefore \overline{N_{oI}^2} = \overline{i_{ia}^2} R_f^2 + \overline{i_f^2} R_f^2 + \overline{N_{ia}^2}$

Case II: $N_{oII} = i_{eq} R_f \rightarrow \overline{N_{oII}^2} = \overline{i_{eq}^2} R_f^2$

Now, set $\overline{N_{oI}^2} = \overline{N_{oII}^2}$:

$$\overline{i_{eq}^2} = \overline{i_{ia}^2} + \overline{i_f^2} + \frac{\overline{N_{ia}^2}}{R_f^2}$$