

Example: Gyro MDS Calculation (cont)

$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$

Now, find the i_{eqTOT} entering the amplifier input:

$$i_{eqTOT}^2 = i_s^2 + i_{eq}^2 \rightarrow i_{eqTOT}^2 = i_s^2 + i_f^2 + i_{ia}^2 + \frac{N_{ia}^2}{R_f^2}$$

$\frac{f_{rx}^2}{\Delta f} = 4kTR_x$

Brownian motion noise of the sense element \rightarrow determined entirely by the noise in $r_x \rightarrow f_{rx}^2$
 \rightarrow easiest to convert to an all electrical equiv. ckt.

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 43

Example: Gyro MDS Calculation (cont)

Where $L_x = \frac{R_x}{\eta_c^2}$, $C_x = \eta_c^2 C_x$, $R_x = \frac{r_x}{\eta_c^2}$

$$i_s^2 = N_{R_x} \left(\frac{1}{R_x} \right) | \oplus (j\omega d) |^2 \rightarrow \frac{i_s^2}{\Delta f} = 4kTR_x \left(\frac{1}{R_x} \right) | \oplus (j\omega d) |^2$$

$$\Rightarrow \frac{i_s^2}{\Delta f} = \frac{4kT}{R_x} | \oplus (j\omega d) |^2$$

Thus:

$$\frac{i_{eqTOT}^2}{\Delta f} = \frac{4kT}{R_x} | \oplus (j\omega d) |^2 + \frac{4kT}{R_f} + \frac{i_{ia}^2}{\Delta f} + \frac{N_{ia}^2}{\Delta f} \left(\frac{1}{R_f} \right)$$

Learn to get these from EE240.
 \rightarrow or just get them from a data sheet ...

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 44

LF356 Op Amp Data Sheet

LF155/LF156/LF256/LF257/LF355/LF356/LF357
JFET Input Operational Amplifiers

General Description

- Logarithmic amplifiers
- Photocell amplifiers
- Sample and Hold circuits

Common Features

- Low input bias current: 30pA
- Low Input Offset Current: 3pA
- High input impedance: $10^{12} \Omega$
- Low input noise current: $0.01 \text{ pA}/\sqrt{\text{Hz}}$
- High common-mode rejection ratio: 100 dB
- Large dc voltage gain: 106 dB

Features

Advantages

- Replace expensive hybrid and module FET op amps
- Rugged JFETs allow blow-out free handling compared with MOSFET input devices
- Excellent for low noise applications using either high or low source impedance — very low 1/f corner
- Offset adjust does not degrade drift or common-mode rejection as in most monolithic amplifiers
- New output stage allows use of large capacitive loads (5,000 pF) without stability problems
- Internal compensation and large differential input voltage capability

Applications

- Precision high speed integrators
- Fast D/A and A/D converters
- High impedance buffers
- Wideband, low noise, low drift amplifiers

Uncommon Features

	LF155/ LF355	LF156/ LF256/ (A _v =5)	LF257/ LF357	Units
Extremely fast settling time to 0.01%	4	1.5	1.5	μs
Fast slew rate	5	12	50	V/ μs
Wide gain bandwidth	2.5	5	20	MHz
Low input noise voltage	20	12	12	nV/ $\sqrt{\text{Hz}}$

$\frac{i_{ia}^2}{\Delta f} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$

$\frac{N_{ia}^2}{\Delta f} = 12 \text{ nV}/\sqrt{\text{Hz}}$

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 45

Example ARW Calculation

Example Design:

Sensor Element:

- $m = (100\mu\text{m})(100\mu\text{m})(20\mu\text{m})(2300\text{kg}/\text{m}^3) = 4.6 \times 10^{-10} \text{ kg}$
- $\omega_s = 2\pi(15\text{kHz})$
- $\omega_d = 2\pi(10\text{kHz})$
- $k_s = \omega_s^2 m = 4.09 \text{ N/m}$
- $x_d = 20 \mu\text{m}$
- $Q_s = 50,000$
- $V_p = 5\text{V}$
- $h = 20 \mu\text{m}$
- $d = 1 \mu\text{m}$

Sensing Circuitry:

- $R_f = 1\text{M}\Omega$
- $i_{ia} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$
- $v_{ia} = 12 \text{ nV}/\sqrt{\text{Hz}}$

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 46

Example ARW Calculation (cont)

Get rotation rate to output current scale factor:

$$A = 2 \frac{W_d}{\omega_s} Q_s \gamma_d \eta_e |\Theta(j\omega_d)| = 2 \left(\frac{10k}{15k} \right) (50k) (20\mu) (5) (2000\epsilon_0) (0.000024) = 2.83 \times 10^{-12} \text{C}$$

$$\Theta(j\omega_d) = \frac{(j\omega_d)(\omega_s/\omega_s)}{-\omega_d^2 + j\omega_d\omega_s + \omega_s^2} = \frac{j(10k)(15k)/(15k)}{(15k)^2 - (10k)^2 + j(10k)(15k)} = \frac{j(3k)}{1.25 \times 10^8 + j(3k)}$$

$$\rightarrow |\Theta(j\omega_d)| = \frac{3k}{\sqrt{(1.25 \times 10^8)^2 + (3k)^2}} = 0.000024 \quad 8.854 \times 10^{-8} \text{F/m}$$

$$\left[\frac{\partial C}{\partial x} = \frac{C_0}{d} = \frac{\epsilon_0 h W_p}{d} = \frac{\epsilon_0 (20\mu)(100\mu)}{(1\mu)^2} = 2000\epsilon_0 \rightarrow \eta_e = V_p \frac{\partial C}{\partial x} = 5(2000\epsilon_0) \right]$$

Assume electrode covers the whole sidewall. $8.854 \times 10^{-12} \text{F/m}$

Then, get noise:

$$\frac{\overline{i_{eqTOT}^2}}{\Delta f} = \frac{4kT}{R_x} |\Theta(j\omega_d)|^2 + \frac{4kT}{R_f} + \frac{\overline{i_{ia}^2}}{\Delta f} + \frac{\overline{N_{if}^2}}{\Delta f} \left(\frac{1}{R_f} \right)$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 47

Example ARW Calculation (cont)

$$\left[R_x = \frac{\omega_s m}{Q_s^2 e} = \frac{2\pi(15k)(4.6 \times 10^{-10})}{(50k)(8.854 \times 10^{-8})^2} = 110.6 \text{k}\Omega \right]$$

$$\frac{\overline{i_{eqTOT}^2}}{\Delta f} = \frac{(1.66 \times 10^{-29}) (0.000024)^2}{(110.6k)} + \frac{(1.66 \times 10^{-29})}{1M} + (0.01p)^2 + \frac{(12n)^2}{(1M)^2}$$

$8.64 \times 10^{-35} \text{A}^2/\text{Hz}$ $1.66 \times 10^{-26} \text{A}^2/\text{Hz}$ $1 \times 10^{-28} \text{A}^2/\text{Hz}$ $1.44 \times 10^{-28} \text{A}^2/\text{Hz}$
 sensor element noise Insignificant Noise from R_f dominates!

$$\therefore \frac{\overline{i_{eqTOT}^2}}{\Delta f} = 1.68 \times 10^{-26} \text{A}^2/\text{Hz} \rightarrow i_{eqTOT} = \sqrt{\frac{\overline{i_{eqTOT}^2}}{\Delta f}} = 1.30 \times 10^{-13} \text{A}/\sqrt{\text{Hz}}$$

$$\therefore \Omega_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) = \frac{1.30 \times 10^{-13}}{2.83 \times 10^{-12}} (3600) \left(\frac{180^\circ}{\pi} \right) = 9448 (\%/hr)/\sqrt{\text{Hz}}$$

And finally:

$$ARW = \frac{1}{60} \Omega_{min} = \frac{1}{60} (9448) = 157 \%/hr = ARW \Rightarrow \text{Almost turned around in 1 hour!}$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 48

What if $\omega_d = \omega_s$?

If $\omega_d = \omega_s = 15k\text{Hz}$, then $|\Theta(j\omega_d)| = 1$ and

$$A = 2 \frac{W_d}{\omega_s} Q_s \gamma_d \eta_e |\Theta(j\omega_d)| = 2 Q_s \gamma_d \eta_e = 2(50k)(20\mu)(5)(2000\epsilon_0) = 1.77 \times 10^{-7} \text{C}$$

$$\frac{\overline{i_{eqTOT}^2}}{\Delta f} = \frac{(1.66 \times 10^{-29}) (1)^2}{(110.6k)} + \frac{(1.66 \times 10^{-29})}{1M} + (0.01p)^2 + \frac{(12n)^2}{(1M)^2}$$

$1.51 \times 10^{-25} \text{A}^2/\text{Hz}$ $1.66 \times 10^{-26} \text{A}^2/\text{Hz}$ $1 \times 10^{-28} \text{A}^2/\text{Hz}$ $1.44 \times 10^{-28} \text{A}^2/\text{Hz}$
 Now, the sensor element dominates!

$$\therefore \frac{\overline{i_{eqTOT}^2}}{\Delta f} = 1.67 \times 10^{-25} \text{A}^2/\text{Hz} \rightarrow i_{eqTOT} = \sqrt{\frac{\overline{i_{eqTOT}^2}}{\Delta f}} = 4.08 \times 10^{-13} \text{A}/\sqrt{\text{Hz}}$$

$$\therefore \Omega_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) = \frac{4.08 \times 10^{-13}}{1.77 \times 10^{-7}} (3600) \left(\frac{180^\circ}{\pi} \right) = 0.476 (\%/hr)/\sqrt{\text{Hz}}$$

And finally:

$$ARW = \frac{1}{60} \Omega_{min} = \frac{1}{60} (0.476) = 0.0079 \%/hr = ARW \Rightarrow \text{Navigation grade!}$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 49