

Lecture 27: Gyro Minimum Detectable Signal (MDS)

Announcements:

- HW#7 online and due Friday, May 6
 - ↳ No need to turn in HW#7; we'll just give you time to do it, then release solutions on May 6
 - ↳ You will need to understand this material for the Final Exam, so it's in your best interest to do the homework
- Project slide #3 due Friday, April 29, at 5 p.m.
- Project out-brief sign up sheet on Prof. Nguyen's office door
 - ↳ People have already taken slots
- Old Final Exams passed out
- Final Exam Info Sheet online
-
- Reading: Senturia Chpt. 16
- Lecture Topics:

↳ Minimum Detectable Signal

↳ Noise

- Circuit Noise Calculations
- Noise Sources
- Equivalent Input-Referred Noise

↳ Gyro MDS

- Equivalent Noise Circuit
- Example ARW Determination


↳ Course Wrap Up (Final Exam Info)

↳ Course Evaluations

Last Time:

- Going through input referred noise
- Now, continue with this

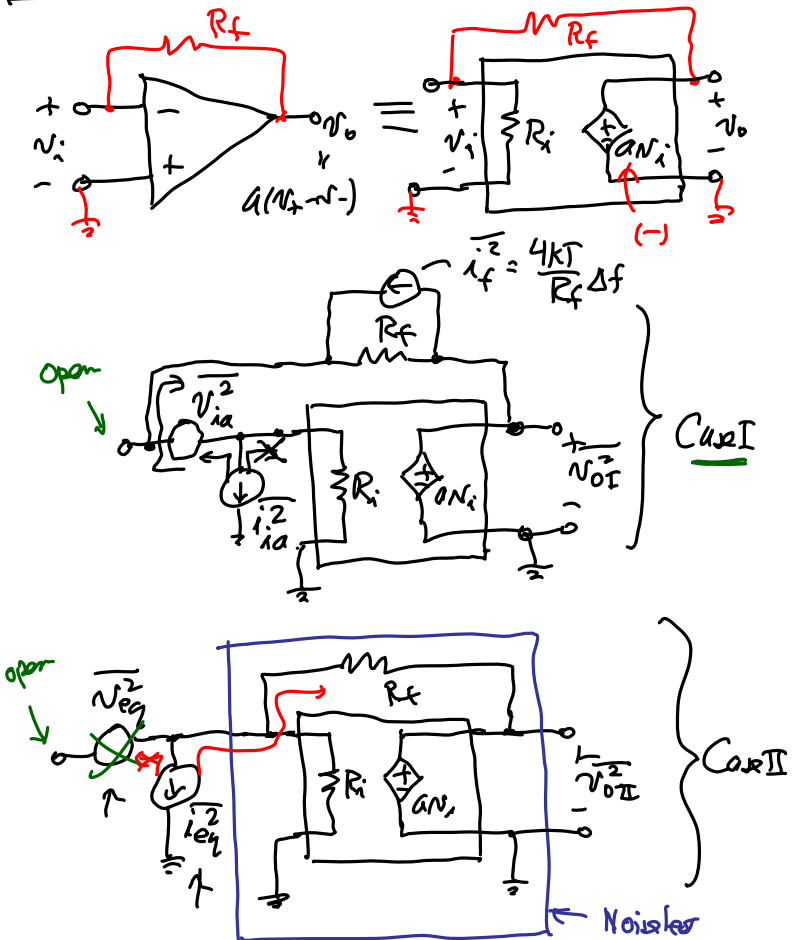Example: Trans R Amplifier Input-Referred Noise




Input-Referenced Current Noise:

Open inputs; equate output voltage noise for Case I & Case II \rightarrow solve for i_{eq}^2

Case I: (w/ superposition)

$i_{ia}^2: N_{oI1} = i_{ia} R_f \rightarrow N_{oI1}^2 = i_{ia}^2 R_f^2$
 $i_f^2: N_{oI2} = i_f R_f \rightarrow N_{oI2}^2 = i_f^2 R_f^2$

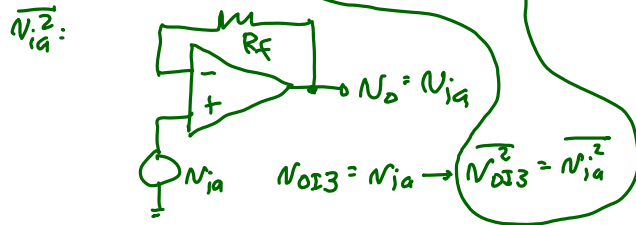power @ output generated by noise sources



$\therefore N_{oI}^2 = i_{ia}^2 R_f^2 + i_f^2 R_f^2 + N_{ia}^2$



Case II: $N_{oII} = i_{eq} R_f \rightarrow N_{oII}^2 = i_{eq}^2 R_f^2$

Now, set $N_{oI}^2 = N_{oII}^2$:

$$i_{eq}^2 = i_{ia}^2 + i_f^2 + \frac{N_{ia}^2}{R_f^2}$$

Now, get the input-referenced voltage noise v_{eq}^2 :

Short inputs; equate output voltage noise for Cases I & II

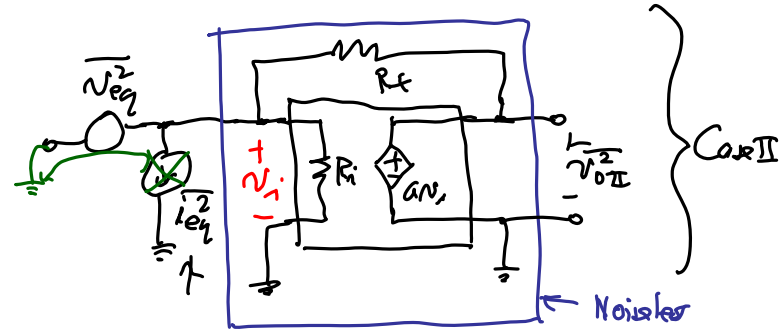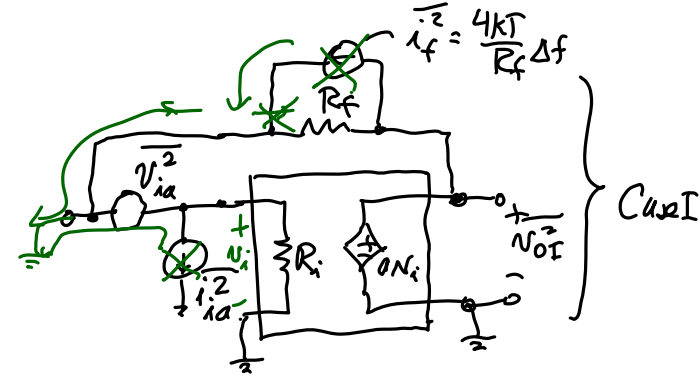

Case I: $N_{oI} = a N_{ia} \rightarrow N_{oI}^2 = a^2 N_{ia}^2$

Case II: $N_{oII} = a N_{eq} \rightarrow N_{oII}^2 = a^2 N_{eq}^2$

$N_{oI}^2 = N_{oII}^2 \rightarrow N_{eq}^2 = N_{ia}^2$

Gyro Sensing Ckt → Want MDS ensures current generated

⇒ First, need $\frac{i_o}{\Omega}$. rotation input @ output capacitive transducer

Noise Sources

$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$

$\vec{F}_c = m\vec{a}_c = 2\omega_d k_d \Omega m$

⇒ Find the rotation-to- i_o (Ω -to- i_o) transfer fn:

$$\dot{x}_s = \frac{F_c \omega_s}{k_{eff}} = F_c \left(\frac{\omega_s Q_s}{k_s} \right) \mathcal{H}_s(j\omega_d) \quad \alpha_s = \frac{F_c}{k}$$

$\left[F_c = m a_c = 2\omega_d k_d \Omega m \right]$


$\dot{x}_s = \frac{\omega_s Q_s \cdot 2\omega_d k_d \Omega m}{k_s} \mathcal{H}_s(j\omega_d) \cdot \frac{1}{\omega_s^2}$

$$\mathcal{H}(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$$s=0: \mathcal{H}(0) = 0$$

$$s=j\omega_0: \mathcal{H}(j\omega_0) = 1$$

$$s=\infty: \mathcal{H}(\infty) = 0$$

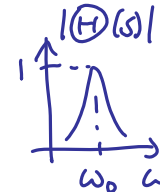

$$\dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \alpha_d \mathcal{H}_s(j\omega_d) \cdot \Omega$$

$$i_o = \eta_e \dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \alpha_d \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$$

$A \triangleq$ scale factor

$$\therefore i_o = A \Omega, \text{ where } A = 2 \frac{\omega_d}{\omega_s} Q_s \alpha_d \eta_e \mathcal{H}_s(j\omega_d)$$

input rotation sense freq. drive freq.

When $\Omega = \Omega_{min} \triangleq$ MDS $\rightarrow i_o = i_{egrot}$

input-referred noise current entering the sense amplifier (in pA/√Hz)

$$\Omega_{min} = \frac{i_{egrot}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) \left[\frac{^\circ/hr}{\sqrt{Hz}} \right]$$

$$\text{Angle Random Walk (ARW)} = \frac{1}{60} \Omega_{min} \left[\frac{^\circ}{\sqrt{hr}} \right]$$

Now get i_{eq} : (noise)

$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$

$i_{eq}^2 = i_s^2 + i_{eq}^2 = i_s^2 + i_f^2 + i_{ia}^2 + \frac{N_{i_a}^2}{R_f^2}$

Browmian motion $\rightarrow f_{r_x}^2 = 4kTR_x \Delta f$

where $L_x = \frac{l_x}{\eta_e^2}$, $C_x = \eta_e^2 c_x$, $R_x = \frac{r_x}{\eta_e^2}$

$\therefore i_s^2 = N_{R_x} \left(\frac{1}{R_x} \right) |H_s(j\omega_d)|^2 \rightarrow \frac{i_s^2}{\Delta f} = 4kTR_x \left(\frac{1}{R_x} \right) |H_s(j\omega_d)|^2$

$\Rightarrow \frac{i_s^2}{\Delta f} = \frac{4kT}{R_x} |H_s(j\omega_d)|^2$

• Go through slides 43-49 in Module 17

• Related courses at UC Berkeley:

- ↗ EE 143: Microfabrication Technology
- ↗ EE 147/247A: Introduction to MEMS
- ↗ ME 119: Introduction to MEMS (mainly fabrication)
- ↗ BioEng 121: Introduction to Micro and Nano Biotechnology and BioMEMS
- ↗ ME C219 - EE C246: MEMS Design
- ↗ EE 290M?