

EE C247B - ME C218

Introduction to MEMS Design


Fall 2016

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences
University of California at Berkeley
Berkeley, CA 94720

Module 17: Noise & MDS

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 1



Lecture Outline

- Reading: Senturia Chpt. 16
- Lecture Topics:
 - ↳ Minimum Detectable Signal
 - ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
 - ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 2

UC Berkeley

Determining Sensor Resolution

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 3

UC Berkeley

Minimum Detectable Signal (MDS)

- **Minimum Detectable Signal (MDS):** Input signal level when the signal-to-noise ratio (SNR) is equal to unity

The diagram illustrates the signal path from a sensed signal to the final output. It consists of two main blocks: a **Sensor** and a **Signal Conditioning Circuit**. The **Sensor** block receives a **Sensed Signal** and adds **Sensor Noise** to it, with the result passing through a **Sensor Scale Factor**. The output of the sensor then enters the **Signal Conditioning Circuit**, which adds **Circuit Output Noise** and passes the signal through **Circuit Gain**. The final **Output** is the sum of the scaled signal and the circuit noise, which includes the desired output plus noise.

- The sensor scale factor is governed by the sensor type
- The effect of noise is best determined via analysis of the equivalent circuit for the system

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 4

UC Berkeley

Noise


EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 5

UC Berkeley

Noise

- **Noise:** Random fluctuation of a given parameter $I(t)$
- In addition, a noise waveform has a zero average value

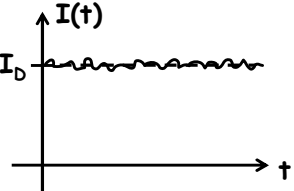Avg. value (e.g. could be DC current) $\rightarrow I_D$



- We can't handle noise at instantaneous times
- But we can handle some of the averaged effects of random fluctuations by giving noise a power spectral density representation
- Thus, represent noise by its mean-square value:
Let $i(t) = I(t) - I_D$
Then $\overline{i^2} = \overline{(I - I_D)^2} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T |I - I_D|^2 dt$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 6

Noise Spectral Density

UC Berkeley

- We can plot the spectral density of this mean-square value:

$\overline{i^2} = \text{integrated mean-square noise spectral density over all frequencies (area under the curve)}$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 7

Circuit Noise Calculations

UC Berkeley

Inputs

$v_i(j\omega)$

$S_i(\omega)$

Deterministic

$H(j\omega)$

Linear Time-Invariant System

Random

Outputs

$v_o(j\omega)$

$S_o(\omega)$

No j → noise has random phase, so j is pointless!

$v_o(t)$

$\frac{2\pi}{\omega_o}$

$v_o(j\omega)$

$S_o(t)$

Mean square spectral density

$S_o(j\omega)$

- Deterministic:** $v_o(j\omega) = H(j\omega)v_i(j\omega)$
- Random:** $S_o(\omega) = [H(j\omega)H^*(j\omega)]S_i(\omega) = |H(j\omega)|^2 S_i(\omega)$

$\sqrt{S_o(\omega)} = |H(j\omega)|\sqrt{S_i(\omega)}$ → How is it we can do this?

Root mean square amplitudes

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 8

Handling Noise Deterministically

UC Berkeley

- Can do this for noise in a tiny bandwidth (e.g., 1 Hz)

$\frac{v_{n1}^2}{\Delta f} = S_1(f) \rightarrow v_{n1} = \sqrt{S_1(f) \cdot B}$

Can approximate this by a sinusoidal voltage generator (especially for small B, say 1 Hz)

$v_o(t) = |A| \cos \omega_0 t$

$\tau \sim \frac{1}{B}$

[This is actually the principle by which oscillators work → oscillators are just noise going through a tiny bandwidth filter] ← Why? Neither the amplitude nor the phase of a signal can change appreciably within a time period 1/B.

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 9

Systematic Noise Calculation Procedure

UC Berkeley


General Circuit With Several Noise Sources

- Assume noise sources are uncorrelated

- For i_{n1}^2 , replace w/ a deterministic source of value

$$i_{n1} = \sqrt{\frac{i_{n1}^2}{\Delta f}} \cdot (1 \text{ Hz})$$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 10



Systematic Noise Calculation Procedure


2. Calculate $v_{on1}(\omega) = i_{n1}(\omega)H(j\omega)$ (treating it like a deterministic signal)
3. Determine $\overline{v_{on1}^2} = \overline{i_{n1}^2} \cdot |H(j\omega)|^2$
4. Repeat for each noise source: $\overline{i_{n1}^2}, \overline{v_{n2}^2}, \overline{v_{n3}^2}$
5. Add noise power (mean square values)

$$\overline{v_{onTOT}^2} = \overline{v_{on1}^2} + \overline{v_{on2}^2} + \overline{v_{on3}^2} + \overline{v_{on4}^2} + \dots$$

$$v_{onTOT} = \sqrt{\overline{v_{on1}^2} + \overline{v_{on2}^2} + \overline{v_{on3}^2} + \overline{v_{on4}^2} + \dots}$$


↖
Total rms value

EEEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 11



Noise Sources


EEEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 12



Thermal Noise


- **Thermal Noise in Electronics:** (Johnson noise, Nyquist noise)
 - ↳ Produced as a result of the thermally excited random motion of free e⁻'s in a conducting medium
 - ↳ Path of e⁻'s randomly oriented due to collisions
- **Thermal Noise in Mechanics:** (Brownian motion noise)
 - ↳ Thermal noise is associated with all dissipative processes that couple to the thermal domain
 - ↳ Any damping generates thermal noise, including gas damping, internal losses, etc.
- **Properties:**
 - ↳ Thermal noise is white (i.e., constant w/ frequency)
 - ↳ Proportional to temperature
 - ↳ Not associated with current
 - ↳ Present in any real physical resistor

EEEC247B/MEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
13




Circuit Representation of Thermal Noise

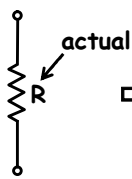- Thermal Noise can be shown to be represented by a series voltage generator $\overline{v_R^2}$ or a shunt current generator $\overline{i_R^2}$




actual

⇒

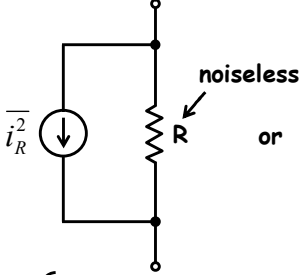

noiseless

or

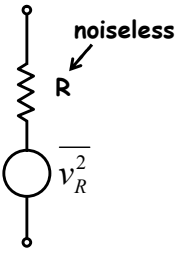

noiseless

$$\frac{\overline{i_R^2}}{\Delta f} = \frac{4kT}{R}$$

$$\frac{\overline{v_R^2}}{\Delta f} = 4kTR$$

Note: These are one-sided mean-square spectral densities! To make them 2-sided, must divide by 2.


where $4kT = 1.66 \times 10^{-20} \text{ V} \cdot \text{C}$
and where these are spectral densities.


EEEC247B/MEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
14

Noise in Capacitors and Inductors?

UC Berkeley

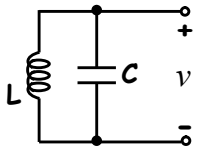
- Resistors generate thermal noise
- Capacitors and inductors are noiseless → why?




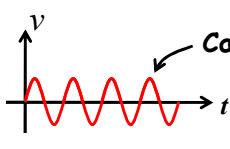

Can oscillate forever

- Now, add a resistor:

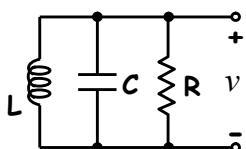

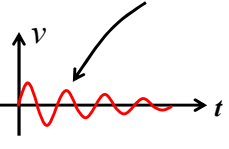

Decays to zero

But this violates the laws of thermodynamics, which require that things be in constant motion at finite temperature

Need to add a forcing function, like a noise voltage $\overline{v_R^2}$ to keep the motion going → and this noise source is associated with R

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 15

Why 4kTR?

UC Berkeley

- Why is $\overline{v_R^2} = 4kTR\Delta f$ (a heuristic argument)
- The Equipartition Theorem of Statistical Thermodynamics says that there is a mean energy $(1/2)kT$ associated w/ each degree of freedom in a given system
- An electronic circuit possesses two degrees of freedom:
 - ↪ Current, i , and voltage, v
 - ↪ Thus, we can write:

$$\frac{1}{2}Li^2 = \frac{1}{2}k_B T \quad , \quad \overbrace{\frac{1}{2}Cv^2}^{\text{Energy}} = \frac{1}{2}k_B T$$
- Similar expressions can be written for mechanical systems
 - ↪ For example: for displacement, x

$$\text{Spring constant} \quad \frac{1}{2}kx^2 = \frac{1}{2}k_B T$$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 16

Why 4kTR? (cont)

UC Berkeley

- Why is $\overline{v_R^2} = 4kTR\Delta f$? (a heuristic argument)
- Consider an RC circuit:

$E = \frac{1}{2}kT = \frac{1}{2}C\overline{v_C^2}$
 $\therefore \overline{v_C^2} = \frac{kT}{C}$ ← integrated noise over all freqs.
 (total mean square voltage integrated over all freqs.)

Question: What value of $\frac{\overline{v_R^2}}{\Delta f}$ (assuming white noise) gives us this?

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 17

Why 4kTR? (cont)

UC Berkeley

Question: What value of $\frac{\overline{v_R^2}}{\Delta f}$ (assuming white noise) gives us $\overline{v_C^2} = \frac{kT}{C}$?

$\overline{v_C^2} = \int_0^\infty \left| \frac{1}{1+j\omega RC} \right|^2 \frac{\overline{v_R^2}}{\Delta f} d\omega$
 [noise is white] → $= \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \int_0^\infty \frac{\omega_b^2}{\omega_b^2 + \omega^2} d\omega$
 [$\omega_b = \frac{1}{RC}$]

$\left[\int \frac{dx}{x^2+a^2} = \frac{1}{a} \tan^{-1}\left(\frac{x}{a}\right) \right]$
 $= \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \frac{\omega_b^2}{\omega_b} \tan^{-1}\left(\frac{\omega}{\omega_b}\right) \Big|_0^\infty = \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \left(\frac{\pi}{2}\omega_b - 0 \right)$
 $= \frac{1}{4} \omega_b \frac{\overline{v_R^2}}{\Delta f} = \frac{kT}{C} \rightarrow \frac{\overline{v_R^2}}{\Delta f} = 4kT \left(\frac{\omega_b}{C} \right) \Rightarrow \frac{\overline{v_R^2}}{\Delta f} = 4kTR \quad \checkmark$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 18

Shot Noise

- Associated with direct current flow in diodes and bipolar junction transistors
- Arises from the random nature by which e⁻s and h⁺s surmount the potential barrier at a pn junction
- The DC current in a forward-biased diode is composed of h⁺s from the p-region and e⁻s from the n-region that have sufficient energy to overcome the potential barrier at the junction
 → noise process should be proportional to DC current
- **Attributes:**
 - ↳ Related to DC current over a barrier
 - ↳ Independent of temperature
 - ↳ White (i.e., const. w/ frequency)
 - ↳ Noise power ~ I_D & bandwidth

pn-junction

$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D$$

Charge on an e⁻
(=1.6×10⁻¹⁹C)

DC Current

EEEC247B/MEEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
19

Flicker (1/f) Noise

- In general, associated w/ random trapping & release of carriers from "slow" states
- Time constant associated with this process gives rise to a noise signal w/ energy concentrated at low frequencies
- Often, get a mean-square noise spectral density that looks like this:

$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D + K \left(\frac{I_D^a}{f^b} \right)$$

I_D = DC current
 K = const. for a particular device
 a = 0.5 → 2
 b ~ 1

EEEC247B/MEEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
20

Example: Typical Noise Numbers

UC Berkeley

- Hookup the circuit below and make some measurements

Measure w/ AC voltmeter
 Measure w/ spectrum analyzer
 Get Gaussian amplitude distribution

$4kTR$

$\frac{1}{2\pi RC}$

area $\sim N_n^2$

Probability

Amplitude

68% within $\pm\sigma$
 99.7% within $\pm 3\sigma$

$1k\Omega: 4nV/\sqrt{Hz}$ (for every 1k of R)
 $1pF: \sqrt{\frac{kT}{C}} = 64\mu V_{rms}$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 21

Example: Typical Noise Numbers

UC Berkeley

- Hookup the circuit below and make some measurements

Measure w/ AC voltmeter
 Measure w/ spectrum analyzer

AC Voltmeter

$$\sqrt{N_o^2} = (100)(64\mu V_{rms}) = 6.4mV_{rms}$$

Spectrum Analyzer

$\frac{1}{(2\pi)(1k)(1p)} = 60\text{ MHz}$

400 nV/√Hz

20 dB/dec

one-sided spectral density

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 22

UC Berkeley

Back to Determining Sensor Resolution



EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 23

UC Berkeley

MEMS-Based Tuning Fork Gyroscope

[Zaman, Ayazi, et al, MEMS'06]

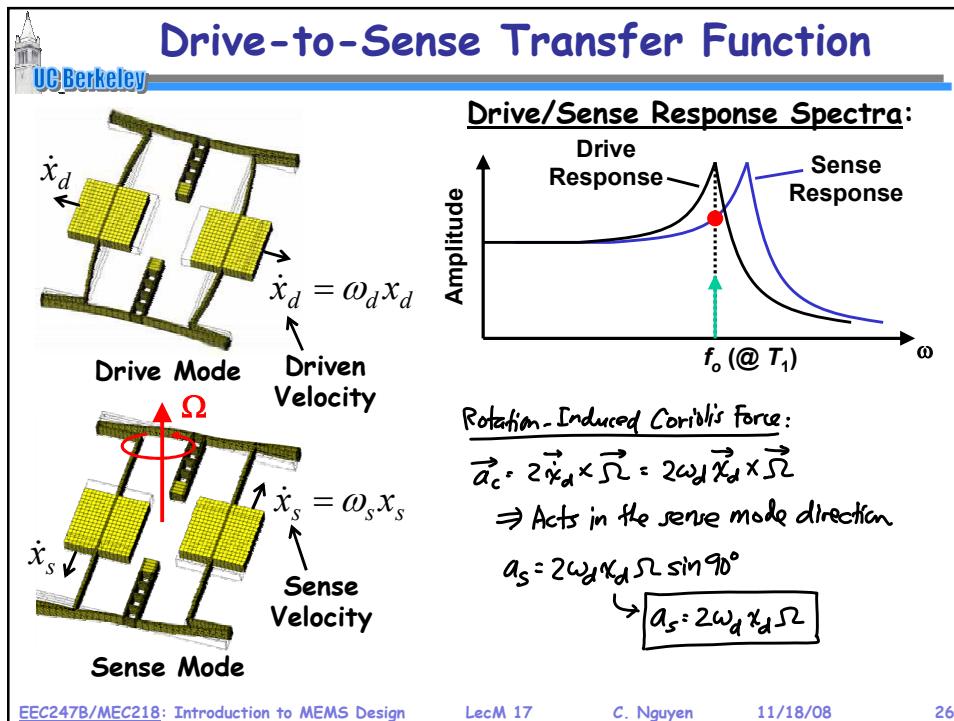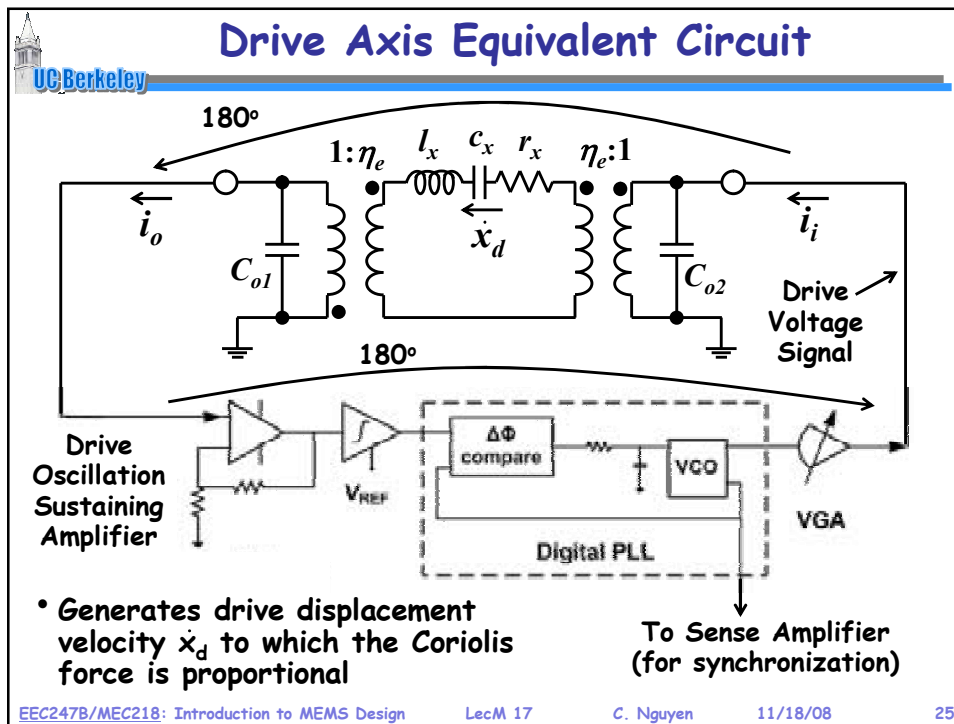EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 24



**Gyro Readout Equivalent Circuit
(for a single tine)**

$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$

• Easiest to analyze if all noise sources are summed at a common node

EEC247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 27

Minimum Detectable Signal (MDS)

• Minimum Detectable Signal (MDS): Input signal level when the signal-to-noise ratio (SNR) is equal to unity

• The sensor scale factor is governed by the sensor type
• The effect of noise is best determined via analysis of the equivalent circuit for the system

EEC247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 28

UC Berkeley

Move Noise Sources to a Common Point

- Move noise sources so that all sum at the input to the amplifier circuit (i.e., at the output of the sense element)
- Then, can compare the output of the sensed signal directly to the noise at this node to get the MDS

EEEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 29

UC Berkeley

Equivalent Input-Referred Voltage and Current Noise Sources

EEEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 30

Equivalent Input v , i Noise Generators

• Take a noisy 2-port network and represent it by a noiseless network with input v and i noise generators that generate the same total output noise

• **Remarks:**

1. Works for linear time-invariant networks
2. v_{eq} and i_{eq} are generally correlated (since they are derived from the same sources)
3. In many practical circuits, one of v_{eq} and i_{eq} dominates, which removes the need to address correlation
4. If correlation is important \rightarrow easier to return to original network with internal noise sources

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 31

Calculation of v_{eq}^2 and i_{eq}^2

a) To get v_{eq}^2 for a two-port:

Case I **Case II**

- 1) Short input, find v_{0I}^2 (or i_{0I}^2)
- 2) For eq. network, short input, find v_{0II}^2 (or i_{0II}^2)

$$\begin{array}{ccc} \parallel & & \parallel \\ f(v_{eq}^2) & & f(v_{eq}^2) \end{array}$$

- 3) Set $v_{0I}^2 = v_{0II}^2 \rightarrow$ solve for v_{eq}^2 (or $i_{0I}^2 = i_{0II}^2$)

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 32

UC Berkeley

Calculation of $\overline{v_{eq}^2}$ and $\overline{i_{eq}^2}$ (cont)

b) To get $\overline{i_{eq}^2}$ for a 2-port:

- 1) Open input, find $\overline{v_{0I}^2}$ (or $\overline{i_{0I}^2}$)
- 2) Open input for eq. circuit, find $\overline{v_{0II}^2}$ (or $\overline{i_{0II}^2}$)
- 3) Set $\overline{v_{0I}^2} = \overline{v_{0II}^2} (\overline{i_{eq}^2}) \rightarrow$ solve for $\overline{i_{eq}^2}$ (or $\overline{i_{0I}^2} = \overline{i_{0II}^2} (\overline{i_{eq}^2})$)

- Once the equivalent input-referred noise generators are found, noise calculations become straightforward as long as the noise generators can be treated as uncorrelated

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 33

UC Berkeley

Cases Where Correlation Is Not Important

- There are two common cases where correlation can be ignored:
 1. Source resistance R_s is **small** compared to input resistance $R_i \rightarrow$ i.e., voltage source input
 2. Source resistance R_s is **large** compared to input resistance $R_i \rightarrow$ i.e., current source input

1) $R_s =$ small (ideally = 0 for an ideal voltage source):

$\overline{i_{eq}^2}$ Current shorted out!

\therefore For $R_s =$ small, $\overline{i_{eq}^2}$ can be neglected \rightarrow only $\overline{v_{eq}^2}$ is important!
(Thus, we need not deal with correlation)

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 34

Cases Where Correlation Is Not Important

2) $R_s = \text{large}$ (Ideally = ∞ for an ideal current source)

Voltage $\overline{v_{eq}^2}$ effectively "opened" out!

$v_i = \frac{R_{in}}{\infty + R_{in}} v_{eq} = 0!$

∴ For $R_s = \text{large}$, $\overline{v_{eq}^2}$ can be neglected!
 → only $\overline{i_{eq}^2}$ is important!
 (... and again, we need not deal with correlation)

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 35

Example: TransR Amplifier Noise

Input-referred current noise:
 Open inputs; equate output voltage noise.

Case I:
 $N_{oI1} = i_{ia} R_f$
 $N_{oI2} = i_f R_f$
 $N_{oI3} = N_{ia}$
 Move N_{ia} through R_{in} to N_{ia} This is unity gain!

$\therefore N_{oI}^2 = i_{ia}^2 R_f^2 + i_f^2 R_f^2 + N_{ia}^2$

Case II: $N_{oII}^2 = \overline{i_{eq}^2} R_f^2$

$\therefore \overline{i_{eq}^2} = i_{ia}^2 + i_f^2 + \frac{N_{ia}^2}{R_f^2}$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 36

Example: TransR Amplifier Noise (cont)

UC Berkeley

Input-referred voltage noise:
 Short inputs; equate output voltage noise

Case I:
 $\overline{N_{oI}^2} = \overline{N_{ia}^2} a^2$
 (Both i_{ia}^2 & i_f^2 are shorted out.)

Case II:
 $\overline{N_{oII}^2} = \overline{N_{eq}^2} a^2$
 $\therefore \overline{N_{eq}^2} = \overline{N_{ia}^2}$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 37

Example: TransR Amplifier Noise (cont)

UC Berkeley

- To summarize, for a transresistance amplifier, the equivalent input-referred current and voltage noise generators are given by:

$$\overline{i_{eq}^2} = \overline{i_{ia}^2} + \overline{i_f^2} + \frac{\overline{v_{ia}^2}}{R_f^2}$$

$$\overline{v_{eq}^2} = \overline{v_{ia}^2}$$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 38

UC Berkeley

Back to Gyro Noise & MDS

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 39

UC Berkeley


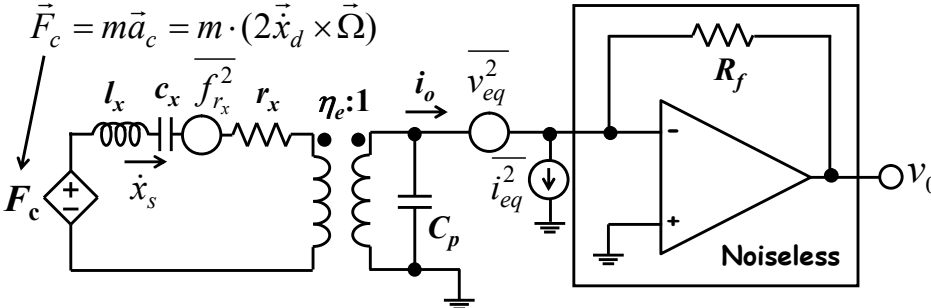
Example: Gyro MDS Calculation

$$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$$

- The gyro sense presents a large effective source impedance
 - ↳ Currents are the important variable; voltages are “opened” out
 - ↳ Must compare i_o with the total current noise i_{eqTOT} going into the amplifier circuit

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 40

Example: Gyro MDS Calculation (cont)

$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$

- First, find the rotation to i_o transfer function:


$$\dot{x}_s = \frac{\omega_s Q_s}{k_s} (H_s(j\omega_d)) F_s = \frac{\omega_s Q_s \cdot 2\omega_d \kappa_d \Omega m}{k_s} (H_s(j\omega_d)) \cdot \frac{1}{\omega_s^2}$$

$$[F_s = F_c = 2\omega_d \kappa_d \Omega m]$$

$$\dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \kappa_d (H_s(j\omega_d)) \cdot \Omega$$

EEEC247B/MEEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
41

Example: Gyro MDS Calculation (cont)



$$i_o = \eta_e \dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s \kappa_d \eta_e (H_s(j\omega_d)) \cdot \Omega \Rightarrow i_o = A\Omega$$

$A \triangleq$ scale factor

$Where A = 2 \frac{\omega_d}{\omega_s} Q_s \kappa_d \eta_e (H_s(j\omega_d))$

When $\Omega = \Omega_{min} \triangleq MDS$, $i_o = i_{eqTOT}$ ← input-referred noise current entering the sense amplifier → in pA/√Hz


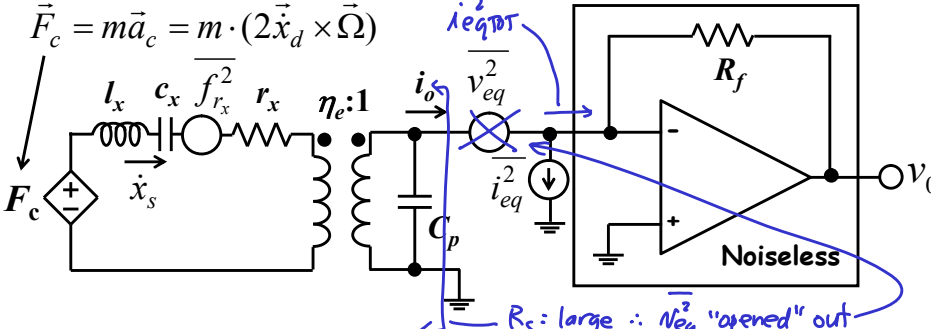
$$\therefore i_{eqTOT} = A\Omega_{min} \rightarrow \Omega_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) [(\%hr)/\sqrt{Hz}]$$

$Angle Random Walk: ARW = \frac{1}{60} \Omega_{min} [^\circ/\sqrt{hr}]$

↪ Easier to determine directional error as a function of elapsed time.

EEEC247B/MEEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
42

Example: Gyro MDS Calculation (cont)

$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{\dot{x}}_d \times \vec{\Omega})$

• Now, find the i_{eqTOT} entering the amplifier input:


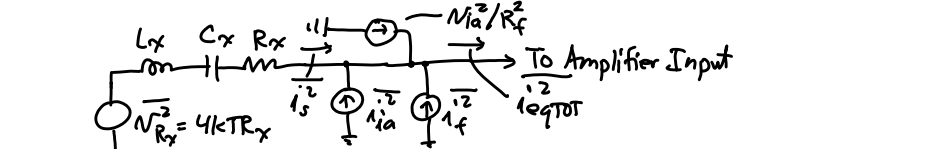
$$i_{eqTOT}^2 = i_s^2 + i_{eq}^2 \rightarrow i_{eqTOT}^2 = i_s^2 + i_f^2 + i_{ia}^2 + \frac{N_{ia}^2}{R_f^2}$$

$\frac{f_{rx}^2}{\Delta f} = 4kTR_x$
 ↗ Brownian motion noise of the sense element → determined entirely by the noise in $r_x \rightarrow f_{rx}^2$
 ↘ easiest to convert to an all electrical equiv. ckt.

R_s : large $\therefore N_{eq}^2$ "opened" out

EEEC247B/MEEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
43

Example: Gyro MDS Calculation (cont)

Where $L_x = \frac{R_x}{\eta_e^2}$, $C_x = \eta_e^2 C_x$, $R_x = \frac{r_x}{\eta_e^2}$

$$\therefore i_s = N_{R_x} \left(\frac{1}{R_x} \right) |H_s(j\omega_d)|^2 \rightarrow \frac{i_s^2}{\Delta f} = 4kTR_x \left(\frac{1}{R_x^2} \right) |H_s(j\omega_d)|^2$$

$$\Rightarrow \frac{i_s^2}{\Delta f} = \frac{4kT}{R_x} |H_s(j\omega_d)|^2$$

Thus:

$$\frac{i_{eqTOT}^2}{\Delta f} = \frac{4kT}{R_x} |H_s(j\omega_d)|^2 + \frac{4kT}{R_f} + \frac{i_{ia}^2}{\Delta f} + \frac{N_{ia}^2}{\Delta f} \left(\frac{1}{R_f^2} \right)$$

Learn to get there from EE240.
 ↘ or just get them from a data sheet ...

EEEC247B/MEEC218: Introduction to MEMS Design
LecM 17
C. Nguyen
11/18/08
44

LF356 Op Amp Data Sheet

UC Berkeley

LF155/LF156/LF256/LF257/LF355/LF356/LF357 JFET Input Operational Amplifiers

General Description
 These are the first monolithic JFET input operational amplifiers to incorporate well matched, high voltage JFETs on the same chip with standard bipolar transistors (BI-FET™ Technology). These amplifiers feature low input bias and offset currents/low offset voltage and offset voltage drift, coupled with offset adjust which does not degrade drift or common-mode rejection. The devices are also designed for high slew rate, wide bandwidth, extremely fast settling time, low voltage and current noise and a low 1/f noise corner.

Common Features

- Logarithmic amplifiers
- Photocell amplifiers
- Sample and Hold circuits
- Low input bias current: 30pA
- Low Input Offset Current: 3pA
- High input impedance: $10^{12}\Omega$
- Low input noise current: $0.01 \text{ pA}/\sqrt{\text{Hz}}$ (Handwritten: $\sqrt{\frac{0.2 \text{ pA}}{\Delta f}} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$)
- High common-mode rejection ratio: 100 dB
- Large dc voltage gain: 106 dB

Uncommon Features

	LF155/ LF355	LF156/ LF256/ LF356	LF257/ LF357 ($A_V=5$)	Units
Extremely fast settling time to 0.01%	4	1.5	1.5	μs
Fast slew rate	5	12	50	V/ μs
Wide gain bandwidth	2.5	5	20	MHz
Low input noise voltage	20	12	12	nV/ $\sqrt{\text{Hz}}$ (Handwritten: $\sqrt{\frac{12 \text{ nV}}{\Delta f}} = 12 \text{ nV}/\sqrt{\text{Hz}}$)

Features

Advantages

- Replace expensive hybrid and module FET op amps
- Rugged JFETs allow blow-out free handling compared with MOSFET input devices
- Excellent for low noise applications using either high or low source impedance—very low 1/f corner
- Offset adjust does not degrade drift or common-mode rejection as in most monolithic amplifiers
- New output stage allows use of large capacitive loads (5,000 pF) without stability problems
- Internal compensation and large differential input voltage capability

Applications

- Precision high speed integrators
- Fast D/A and A/D converters
- High impedance buffers
- Wideband, low noise, low drift amplifiers

45

Example ARW Calculation

UC Berkeley

• **Example Design:**

↳ **Sensor Element:**

$$m = (100\mu\text{m})(100\mu\text{m})(20\mu\text{m})(2300\text{kg}/\text{m}^3) = 4.6 \times 10^{-10}\text{kg}$$

$$\omega_s = 2\pi(15\text{kHz})$$

$$\omega_d = 2\pi(10\text{kHz})$$

$$k_s = \omega_s^2 m = 4.09 \text{ N/m}$$

$$x_d = 20 \mu\text{m}$$

$$Q_s = 50,000$$

$$V_p = 5\text{V}$$

$$h = 20 \mu\text{m}$$

$$d = 1 \mu\text{m}$$

↳ **Sensing Circuitry:**

$$R_f = 100\text{k}\Omega$$

$$i_{ia} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$$

$$v_{ia} = 12 \text{ nV}/\sqrt{\text{Hz}}$$

46

Example ARW Calculation (cont)

UC Berkeley

Get rotation rate to output current scale factor:

$$A = Z \frac{\omega_d}{\omega_s} Q_s \kappa_d \eta_e |\Theta_s(j\omega_d)| = Z \left(\frac{10k}{15k} \right) (50k) (20\mu) (5) (2000\epsilon_0) (0.000024) = \underline{2.83 \times 10^{-12} C}$$

$$\Theta_s(j\omega_d) = \frac{(j\omega_d)(\omega_s/Q_s)}{-\omega_d^2 + \frac{j\omega_d\omega_s}{Q_s} + \omega_s^2} = \frac{j(10k)(15k)/(50k)}{(15k)^2 - (10k)^2 + \frac{j(10k)(15k)}{50k}} = \frac{j(3k)}{1.25 \times 10^8 + j(3k)}$$

$$\Rightarrow |\Theta_s(j\omega_d)| = \frac{3k}{\sqrt{(1.25 \times 10^8)^2 + (3k)^2}} = 0.000024 \quad 8.854 \times 10^{-8} F/m$$

$$\frac{\partial C}{\partial x} = \frac{C_0}{d} = \frac{\epsilon_0 h \omega_p}{d} = \frac{\epsilon_0 (20\mu)(100\mu)}{(1\mu)^2} = 2000\epsilon_0 \rightarrow \eta_e = V_p \frac{\partial C}{\partial x} = 5(2000\epsilon_0) = 8.854 \times 10^{-12} F/m$$

Assume electrode covers the whole sidewall.

Then, get noise:

$$\frac{\overline{i_{eq}^2}}{\Delta f} = \frac{4kT}{R_x} |\Theta_s(j\omega_d)|^2 + \frac{4kT}{R_f} + \frac{\overline{i_{ia}^2}}{\Delta f} + \frac{\overline{N_{ie}^2}}{\Delta f} \left(\frac{1}{R_f} \right)$$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 47

Example ARW Calculation (cont)

UC Berkeley

$$R_x = \frac{\omega_s m}{Q_s \eta_e^2} = \frac{2\pi(15k)(4.6 \times 10^{-10})}{(50k)(8.854 \times 10^{-8})^2} = 110.6 k\Omega$$

$$\frac{\overline{i_{eqTOT}^2}}{\Delta f} = \frac{(1.66 \times 10^{-29})}{(110.6k)} (0.000024)^2 + \frac{(1.66 \times 10^{-29})}{1M} + (0.01p)^2 + \frac{(12n)^2}{(1M)^2}$$

$\rightarrow 8.64 \times 10^{-35} A^2/Hz$ $1.66 \times 10^{-26} A^2/Hz$ $1 \times 10^{-28} A^2/Hz$ $1.44 \times 10^{-28} A^2/Hz$
 sensor element noise Noise from R_f dominates!
 insignificant

$$\therefore \frac{\overline{i_{eqTOT}^2}}{\Delta f} = 1.68 \times 10^{-26} A^2/Hz \rightarrow i_{eqTOT} = \sqrt{\frac{\overline{i_{eqTOT}^2}}{\Delta f}} = 1.30 \times 10^{-13} A/\sqrt{Hz}$$

$$\therefore \Omega_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) = \frac{1.30 \times 10^{-13}}{2.83 \times 10^{-12}} (3600) \left(\frac{180}{\pi} \right) = 9448 (\%hr)/\sqrt{Hz}$$

And finally:

$$ARW = \frac{1}{60} \Omega_{min} = \frac{1}{60} (9448) = 157 \%hr = ARW \Rightarrow \text{Almost turned around in 1 hour!}$$

EEEC247B/MEEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 48

What if $\omega_d = \omega_s$?

UC Berkeley

If $\omega_d = \omega_s = 15\text{kHz}$, then $|\Theta(j\omega_d)| = 1$ and

$$A = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d \eta_e |\Theta(j\omega_d)| = 2 Q_s \chi_d \eta_e = 2(50k)(20\mu)(5)(2000\epsilon_0) = 1.77 \times 10^{-7} \text{C}$$

$$\frac{i_{eqTOT}^2}{\Delta f} = \frac{(1.66 \times 10^{-29})^2}{(110.6k)^2} + \frac{(1.66 \times 10^{-29})^2}{1M} + (0.01p)^2 + \frac{(12n)^2}{(1M)^2}$$

$\swarrow 1.51 \times 10^{-25} \text{ A}^2/\text{Hz}$
 $\swarrow 1.66 \times 10^{-26} \text{ A}^2/\text{Hz}$
 $\swarrow 1 \times 10^{-28} \text{ A}^2/\text{Hz}$
 $\swarrow 1.44 \times 10^{-28} \text{ A}^2/\text{Hz}$

Now, the sensor element dominates!

$$\therefore \frac{i_{eqTOT}^2}{\Delta f} = 1.67 \times 10^{-25} \text{ A}^2/\text{Hz} \rightarrow i_{eqTOT} = \sqrt{\frac{i_{eqTOT}^2}{\Delta f}} = 4.08 \times 10^{-13} \text{ A}/\sqrt{\text{Hz}}$$

$$\therefore \Sigma_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) = \frac{4.08 \times 10^{-13}}{1.77 \times 10^{-7}} (3600) \left(\frac{180}{\pi} \right) = 0.476 (\%/hr)/\sqrt{\text{Hz}}$$

And finally:

$$ARW = \frac{1}{60} \Sigma_{min} = \frac{1}{60} (0.476) = 0.0079 \%/hr = ARW \Rightarrow \text{Navigation grade!}$$

EECS247B/MECS218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 49