

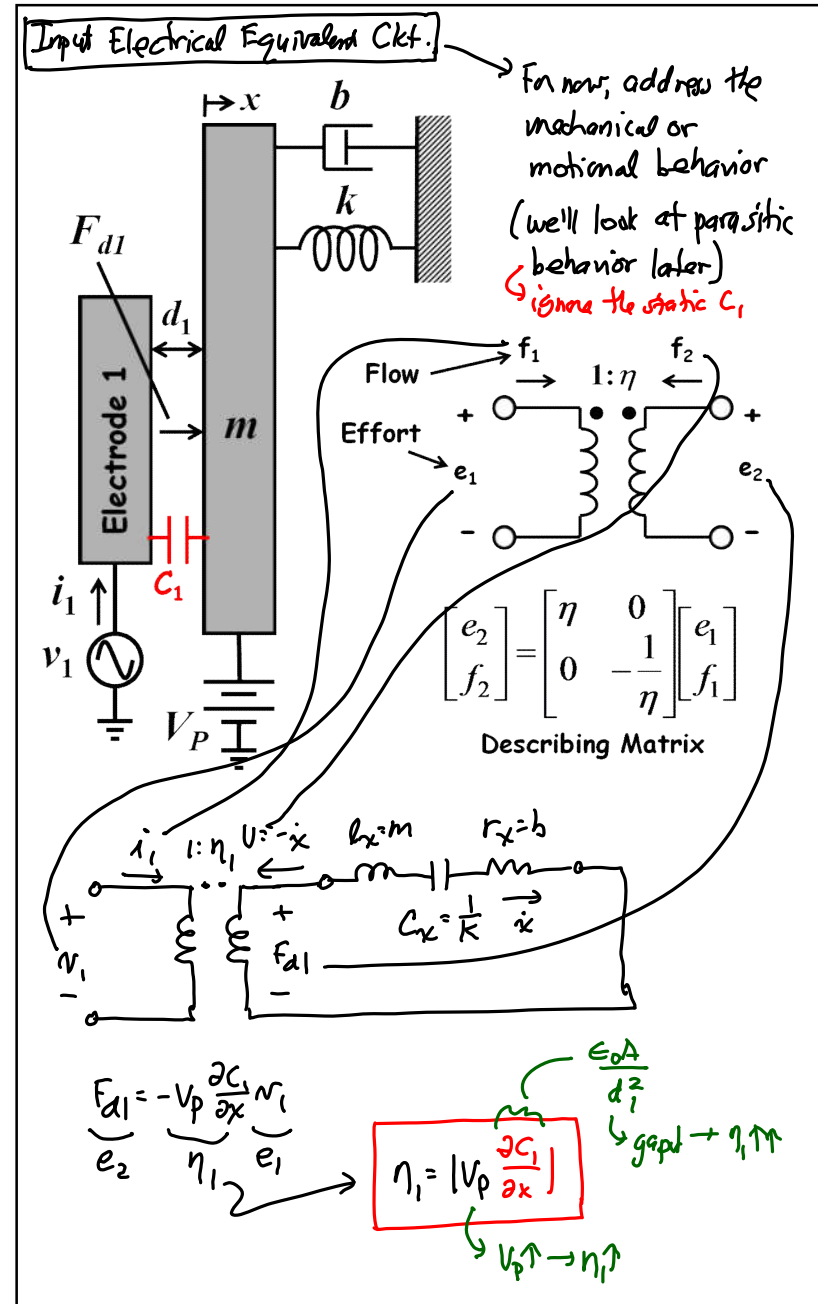


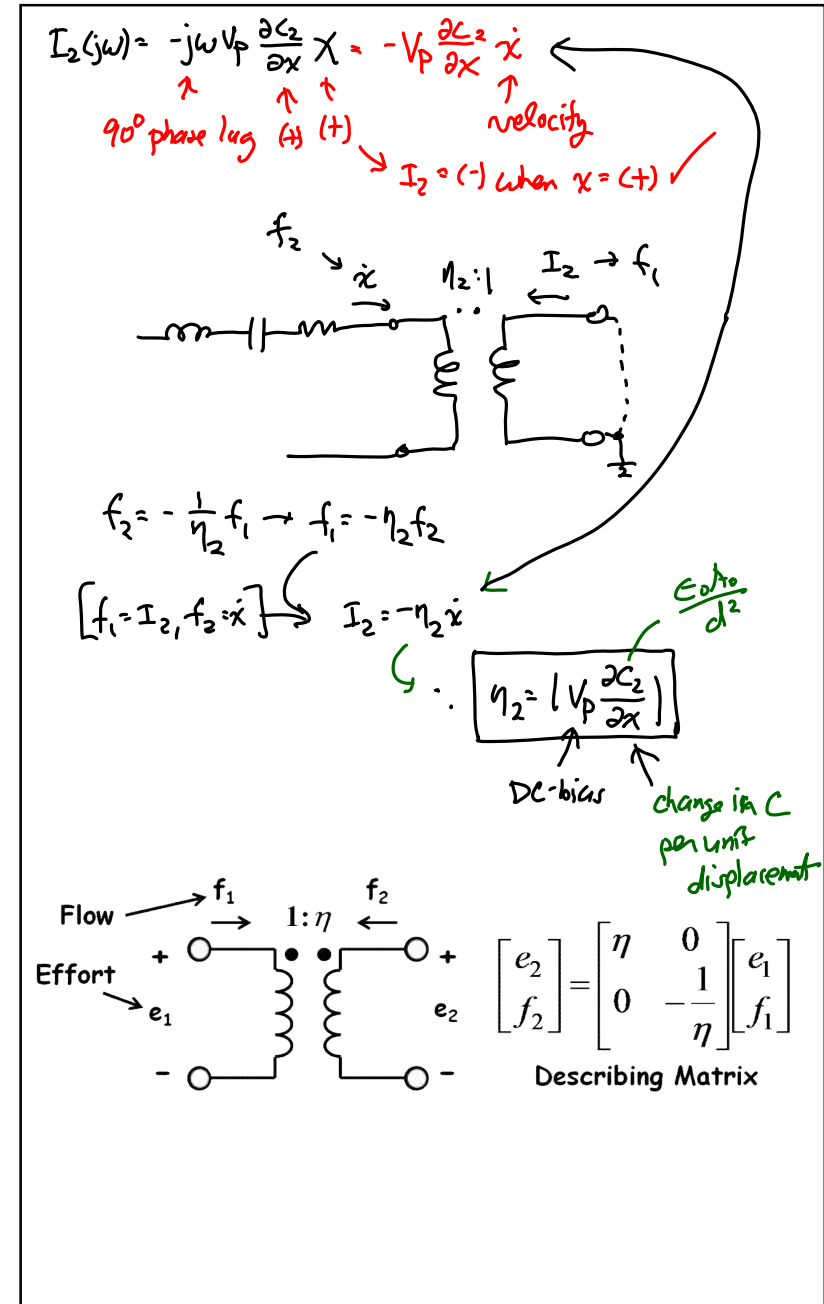**Lecture 22: Equivalent Circuits II**

- Announcements:
- Module 13 on Equivalent Circuits II online
- HW#5 online and due Thursday, April 13
- Project Slide Set #1 due Friday, April 14
- -----
- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
  - ↳ Input Modeling
    - Force-to-Velocity Equiv. Ckt.
    - Input Equivalent Ckt.
  - ↳ Current Modeling
    - Output Current Into Ground
    - Input Current
    - Complete Electrical-Port Equiv. Ckt.
  - ↳ Impedance & Transfer Functions
- -----
- Last Time:
- Finished Capacitive Transducers
- Now, model the transducer in an equivalent circuit



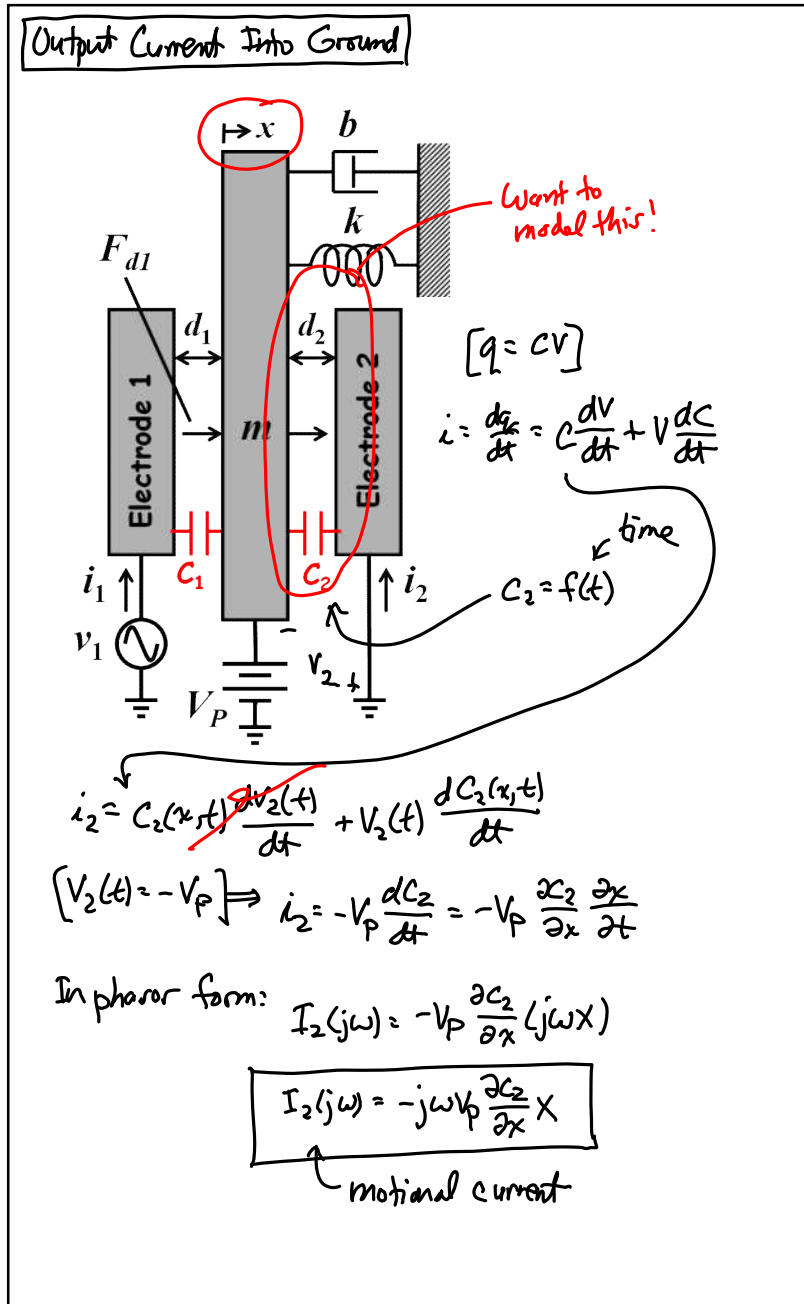

Input Current Expression

Get  $I_1(j\omega) =$

$$i_1(t) = C_1(x, t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC_1(x, t)}{dt}$$

$$V_1(t) = V_i - V_p \Rightarrow i_1 = C_1 \frac{dx}{dt} + (v_i - v_p) \frac{\partial C_1}{\partial t} \frac{\partial x}{\partial t}$$

$f(t)$

$$\therefore I_1(j\omega) = \underbrace{j\omega C_1 V_1}_{\text{Feedthrough Current}} + \underbrace{j\omega V_i \frac{\partial C_1}{\partial x} X - j\omega V_p \frac{\partial C_1}{\partial x} X}_{\text{Motional Current (due to motion of structure)}}$$

@ DC:  $x = \frac{Fd1}{k} = -\frac{1}{kV_p} \frac{\partial C_1}{\partial x} V_i$

@ resonance:  $x = \frac{QFd1}{jk} = -\frac{Q}{jk} V_p \frac{\partial C_1}{\partial x} V_i = X$   
 ↑  
 90° phase lag

Thus: (@ resonance,  $\omega_0$ )

\*  $I_1(j\omega) = j\omega_0 C_1 V_i + j\omega_0 (V_p \frac{\partial C_1}{\partial x}) = \frac{Q}{jk} V_i$

$$= \underbrace{j\omega_0 C_1 V_i}_{\substack{90^\circ \text{ phase shifted} \\ \text{from } V_i}} + \underbrace{\omega_0 \frac{Q}{k} \eta_{el}^2 V_i}_{\substack{\text{in phase} \\ \omega/V_i}}$$

This is a capacitor in shunt with the input!

This is an effective resistance seen @ resonance "looking into Electrode 1!"

"Motional Resistance"


Motional Resistance:

$$R_{x1} = \frac{V_1}{I_1} = \frac{k}{\omega_0 Q \eta_{e1}^2} = \frac{m \omega_0^2}{Q \eta_{e1}^2} = \frac{b}{\eta_{e1}^2} = R_{x1}$$


$\uparrow$  "motion"                       $\uparrow$   $\omega_0^2 = \frac{k}{m}$                        $\uparrow$  In design, this is a very important parameter!

- Look at slide 16 in Module 13

Input Impedance Into Port 1

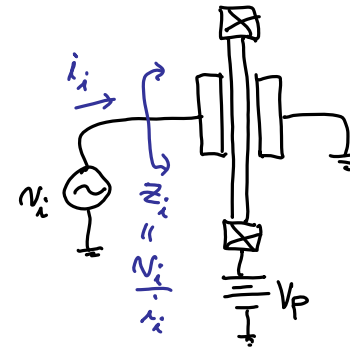

Find  $Z_i$ ??

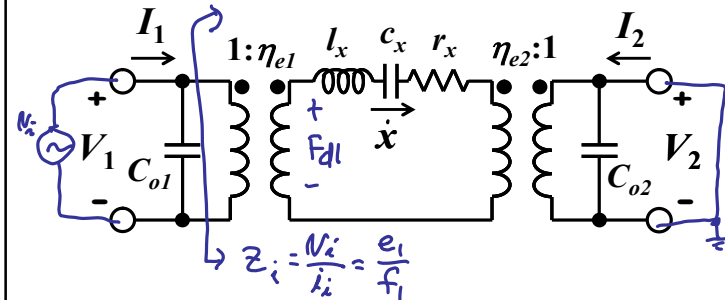

$$Z_i = \frac{V_i}{i_i} = \frac{e_1}{f_1}$$

For now, neglect  $C_{o1}$  &  $C_{o2}$ .  
(Most interested in the mechanical input impedance.)

$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix} \Rightarrow \left. \begin{aligned} e_2 = \eta e_1 \rightarrow e_1 = \frac{e_2}{\eta} \\ f_2 = -\frac{1}{\eta} f_1 \rightarrow f_1 = -\eta f_2 \end{aligned} \right\}$$

$$\frac{e_1}{f_1} = \frac{e_2}{\eta (-\eta f_2)} = -\frac{1}{\eta^2} \frac{e_2}{f_2} \rightarrow \frac{V_i}{i_i} = Z_i = -\frac{1}{\eta_{e1}^2} \frac{F_{d1}}{(-\dot{x})} = \frac{1}{\eta_e^2} Z_x$$

$$z_i = \frac{1}{\eta_{ei}^2} (j\omega l_x + \frac{1}{j\omega c_x} + r_x)$$

$$= \underbrace{j\omega \left( \frac{l_x}{\eta_{ei}^2} \right)}_{L_{x1}} + \underbrace{\frac{1}{j\omega (\eta_{ei}^2 c_x)}}_{C_{x1}} + \underbrace{\frac{r_x}{\eta_{ei}^2}}_{R_{x1}}$$

$\overline{N_n^2} = 4kTR_x$

to model noise!

} Purely Electrical  
Equiv. Ckt.