

Lecture 24: Sensing Circuits I

• Announcements:

- Module 14 on Sensing Circuits online
- Module 15 on Gyros, Noise, & MDS online
- HW#6 online and due Thursday, April 27
- Responded to emails on Slide Set#1
- Project Slide Set #2 due Friday, April 21

• Reading: Senturia, Chpt. 14

• Lecture Topics:

↳ Detection Circuits

- Velocity Sensing
- Position Sensing

• Last Time:

- Went through Module 15 parts that introduce gyroscopes

↳ over

Velocity to-Voltage Conversion

represent velocity  
↓  
 $V_o$   
in phase with velocity  
↓  
in phase with  $\dot{x}$   
90°-shifted from displacement

Review Case when Output goes to Ground

output grounded

$$\frac{\dot{x}}{F_{dl}}(s) = \frac{\omega_0 Q}{k} \Theta(s)$$

$$\frac{\dot{x}}{V_i}(s) = \eta e_1 \frac{\omega_0 Q}{k} \Theta(s)$$

$$[i_o = \eta e_2 \dot{x}] \Rightarrow \frac{i_o}{V_i}(s) = \eta e_1 e_2 \frac{\omega_0 Q}{k} \Theta(s) = \frac{\eta e_1 e_2 Q}{m \omega_0} \Theta(s)$$

$\perp$   
 $R_{x12}$

Now, include  $R_D$ :  $Q = \frac{\omega_0 L_x}{R_x}$

$v_o \leftarrow$  proportional to velocity  
 $R_D \leftarrow$  detector resistance

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_x + \frac{1}{sC_x} + sL_x + R_D} = \dots \text{math} \dots$$

$$= \frac{R_D}{R_x + R_D} \frac{s \left( \frac{R_x + R_D}{L_x} \right)}{s^2 + s \left( \frac{R_x + R_D}{L_x} \right) + \frac{1}{L_x C_x}}$$

Gain Term      Freq. Shaping Term

$$\left[ Q = \frac{\omega_0 L_x}{R_x} \rightarrow Q' = \frac{\omega_0 L_x}{R_x + R_D} \rightarrow \frac{R_x + R_D}{L_x} = \frac{\omega_0}{Q'} \right]$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_x + R_D} \frac{s(\omega_0/Q')}{s^2 + s(\omega_0/Q') + \omega_0^2}$$

$$\frac{v_o}{v_i}(s) = \frac{R_D}{R_x + R_D} \cdot \mathcal{H}(s, Q')$$

$Q' = Q \left( \frac{R_x}{R_x + R_D} \right)$

Transfer fun for Resistive Detection of Velocity

$< 1 \therefore Q' < Q$   
**Bad!**

Transformer-Based Ckt:

$v_o$  proportional to velocity

$R_D$  detector resistance

$C_x: n^2 C_x$   
 $L_x: \frac{L_x}{n^2}$   
 $R_x: \frac{R_x}{n^2}$

$\omega$

$\frac{v_o}{v_i}(s) \rightarrow Q' \sim$  lower than  $Q$   
 $= Q \left( \frac{R_x}{R_x + R_D} \right) \left. \vphantom{\frac{v_o}{v_i}(s)} \right\}$  Big Problem!  
 $< 1$

$\omega$   $R_D$  detection  $\rightarrow Q' \text{ lower!} = Q' < Q$   
original "unused" mechanical device  
 $\rightarrow Q$   
mechanical resonance  $\rightarrow$  large

Analysis @ Resonance:

$\frac{1}{sC_x} = sL_x$   
cancel!

$v_o = \frac{R_D}{R_x + R_D} v_i$   
@ resonance

convert to general freq.:  $X(H(s, Q'))$

$\frac{v_o}{v_i}(s) = \frac{R_D}{R_x + R_D} H(s, Q')$ , where  $Q' = Q \left( \frac{R_x}{R_x + R_D} \right)$

The Problem is actually bigger:

Includes  $C_o$ , line C, bond pad C, and next stage C

Next stage C

Now, we get:

$\frac{v_o}{v_i}(s) \sim \frac{R_D || R_L}{R_x + R_D || R_L} \cdot \frac{1}{1 + \frac{s}{\omega_p}} \cdot H(s, \omega'_0, Q')$

$\omega_p = \frac{1}{(R_x || R_D || R_L) C_p}$

