

Lecture 27: Gyro Minimum Detectable Signal

- Announcements:
- Project Slide Set #3 due Friday, April 28
- Sign up sheet for Project Outbriefs on my door: please sign up
 - ↳ Wednesday, 5/3, 4-5:20 p.m.
 - ↳ Thursday, 5/11, 11-12, 2-2:40 p.m.
- Wrap up course
- Go through Final Exam info
- Pass out three sample final exams
- HKN will come at end for course evaluations
- -----
- Reading: Senturia Chpt. 16
- Lecture Topics:
 - ↳ Minimum Detectable Signal
 - ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
 - ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination
- -----
- Last Time:
- Started with gyro MDS analysis
- Continue with this ...

Determine MDS

$\vec{F}_c = m\vec{a}_c = m \cdot (2\dot{\vec{x}}_d \times \vec{\Omega})$

Gyro Sense Element Output Circuit

Signal Conditioning Circuit (Transresistance Amplifier)

Noise Sources: i_f^2 , i_{ia}^2 , i_{ia}^2

$R_{xs} \sim \text{typ. } 100\text{ k}\Omega - 1\text{ M}\Omega$

$R_f \sim 100\text{ n}\Omega - 1\text{ k}\Omega$
 $= \text{DSR (ideal)}$

$N_f = \omega$

① Determine N_o^2
 \Rightarrow use superposition one source at a time

i_{ia}^2 : $N_{o1} = i_{ia} R_f \rightarrow N_{o1}^2 = i_{ia}^2 R_f^2 = \frac{4kT\Delta f}{R_f} R_f^2 = 4kTR_f\Delta f$

i_f^2 : $N_{o2} = -i_f R_f \rightarrow N_{o2}^2 = i_f^2 R_f^2$

v_{ia}^2 : $N_{o3} = v_{ia}$

f_x^2 : $N_{o4} = -\frac{f_x}{r_x} \eta_e R_f + N_{o4}^2 = \frac{f_x^2}{r_x^2} \eta_e^2 R_f^2$

$\Rightarrow = \frac{4kT\Delta f}{r_x^2} \eta_e^2 R_f^2$

$N_o^2 = i_{ia}^2 R_f^2 + N_{o1}^2 + 4kTR_f(1 + \eta_e^2 \frac{R_f}{r_x}) \Delta f$

Total output mean-square noise

② Find N_o in terms of rotation rate Ω :

Noise Sources

$\vec{F}_c = m\vec{a}_c = m \cdot (2\dot{x}_d \times \vec{\Omega})$

\vec{x}_s

i_x c_x f_{r_x} r_x $\eta_e:1$ i_o v_{ia}^2 i_{ia}^2 R_f V_o C_p

Gyro Sense Element Output Circuit

Signal Conditioning Circuit (Transresistance Amplifier)

\Rightarrow Find the rotation-to- i_o transfer function

$\dot{x}_s = F_c k_s^{-1}(j\omega) = F_c \left(\frac{\omega_s Q_s}{K_s} \mathcal{H}_s(j\omega_d) \right)$

$\left[F_c = m a_c = 2\omega_d x_d \Omega m \right]$

$\dot{x}_s = \frac{\omega_s Q_s}{K_s} \cdot 2\omega_d x_d \Omega m \mathcal{H}_s(j\omega_d)$

$\dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s x_d \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$

$\mathcal{H}(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$

$s=0: \mathcal{H}(0) = 0$

$s=j\omega_0: \mathcal{H}(j\omega_0) = 1$

$s=\infty: \mathcal{H}(\infty) = 0$

$i_o = \eta_e \dot{x}_s = 2 \frac{\omega_d}{\omega_s} Q_s x_d \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$

$\therefore N_o = i_o R_f = 2 R_f \frac{\omega_d}{\omega_s} Q_s x_d \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega$

$A \triangleq \text{scale factor}$

$N_o = A \Omega$ $\leftarrow \text{rms noise voltage}$

③ $\Omega = \Omega_{min}$ when $N_o = \sqrt{N_o^2}$

\uparrow
minimum detectable rotation rate (MDS)

$2 R_f \frac{\omega_d}{\omega_s} Q_s x_d \eta_e \mathcal{H}_s(j\omega_d) \cdot \Omega_{min} = \sqrt{1_{ia}^2 R_f^2 + N_{ia}^2 + 4kTR_f(1+\eta_e^2) \left| \frac{\omega_r Q_s}{K_s} \mathcal{H}_s(j\omega_d) \right|^2 \frac{R_f}{K_x}}$

Solve for Ω_{min} :

$\Omega_{min} = \frac{\sqrt{1_{ia}^2 R_f^2 + N_{ia}^2 + 4kTR_f(1+\eta_e^2) \left| \frac{\omega_r Q_s}{K_s} \mathcal{H}_s(j\omega_d) \right|^2 \frac{R_f}{K_x}}}{2 R_f \frac{\omega_d}{\omega_s} Q_s x_d \eta_e \mathcal{H}_s(j\omega_d)}$

$\times \left(\frac{3600s}{1hr} \right) \left(\frac{180^\circ}{\pi} \right) \rightarrow \left[\frac{^\circ}{hr} \right] / \sqrt{Hz}$

Angle Random Walk = ARW = $\frac{1}{60} \Omega_{min} \left(\frac{^\circ}{\sqrt{hr}} \right)$

\uparrow
Easier to determine directional error as a function of elapsed time.

- **Related courses at UC Berkeley:**
 - ↳ **EE 143: Microfabrication Technology**
 - ↳ **EE 147/247A: Introduction to MEMS**
 - ↳ **ME 119: Introduction to MEMS (mainly fabrication)**
 - ↳ **BioEng 121: Introduction to Micro and Nano Biotechnology and BioMEMS**
 - ↳ **ME C219 - EE C246: MEMS Design**
 - ↳ **EE 290M?**