

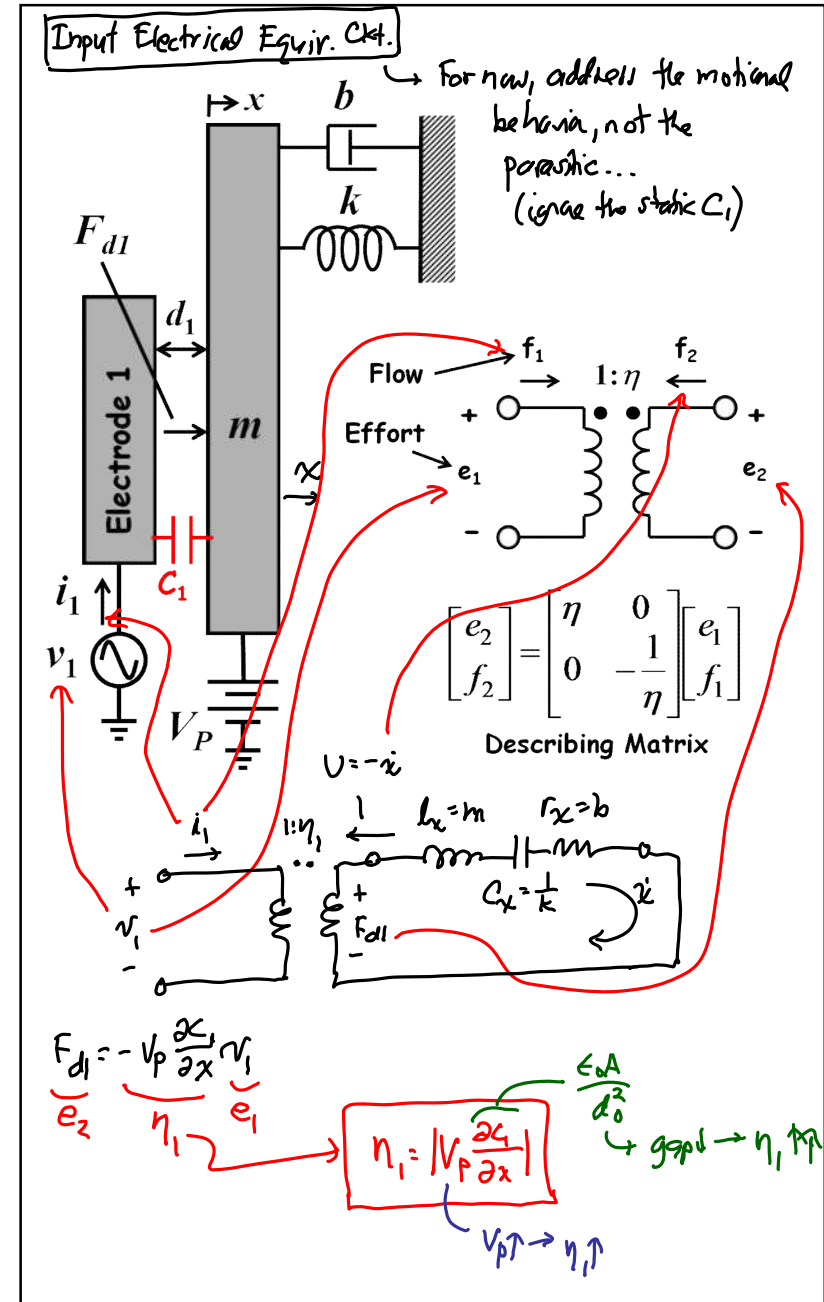


Lecture 22: Equivalent Circuits II

- Announcements:
- Module 13 on Equivalent Circuits II online
- HW#6 online and due Tuesday, April 17
- Project Slide Set #1 due Friday, April 13
- 
- Reading: Senturia, Chpt. 5, Chpt. 6
- Lecture Topics:
  - ↳ Energy Conserving Transducers
    - Charge Control
    - Voltage Control
  - ↳ Parallel-Plate Capacitive Transducers
    - Linearizing Capacitive Actuators
    - Electrical Stiffness
  - ↳ Electrostatic Comb-Drive
    - 1<sup>st</sup> Order Analysis
    - 2<sup>nd</sup> Order Analysis
- 
- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
  - ↳ Input Modeling
    - Force-to-Velocity Equiv. Ckt.
    - Input Equivalent Ckt.
  - ↳ Current Modeling
    - Output Current Into Ground
    - Input Current
    - Complete Electrical-Port Equiv. Ckt.
  - ↳ Impedance & Transfer Functions
- 
- Last Time: Finishing up Module 12 ... continue ...

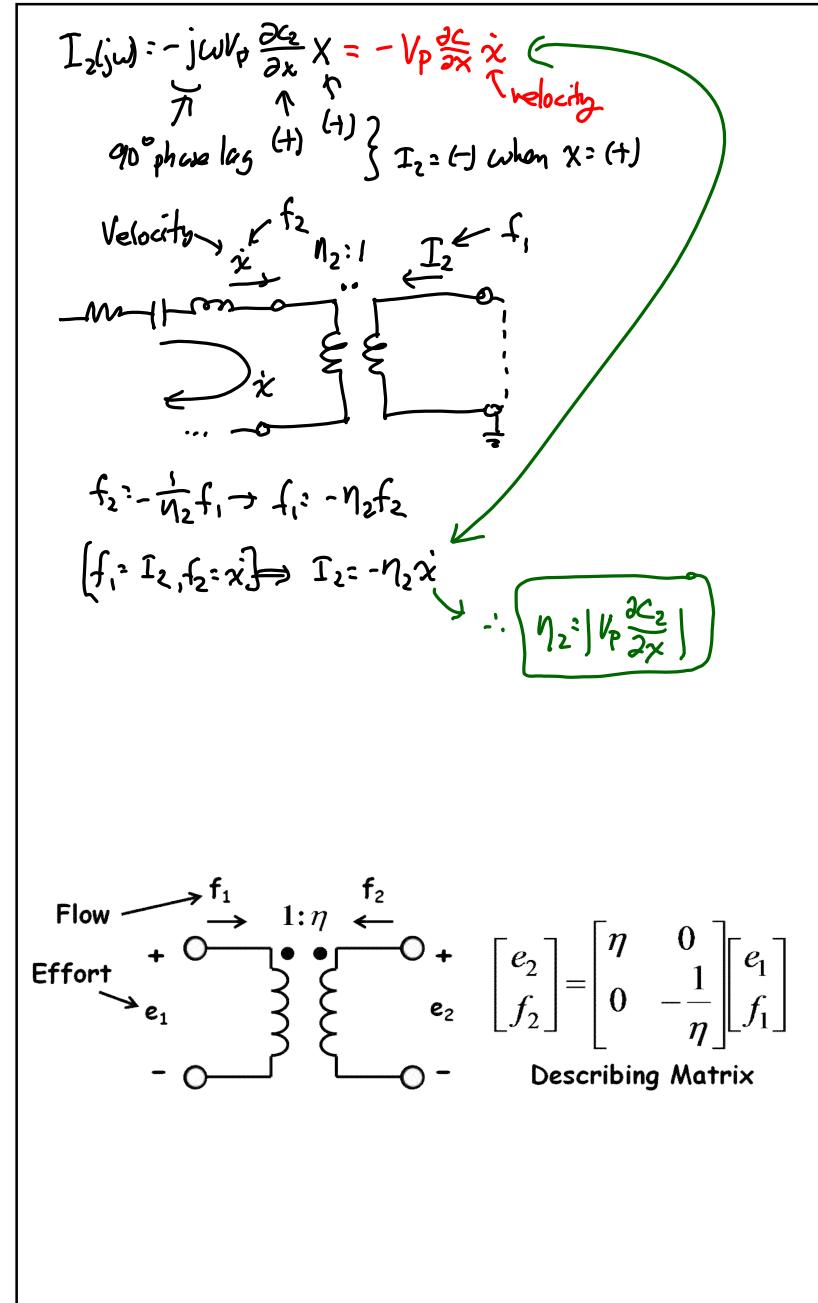

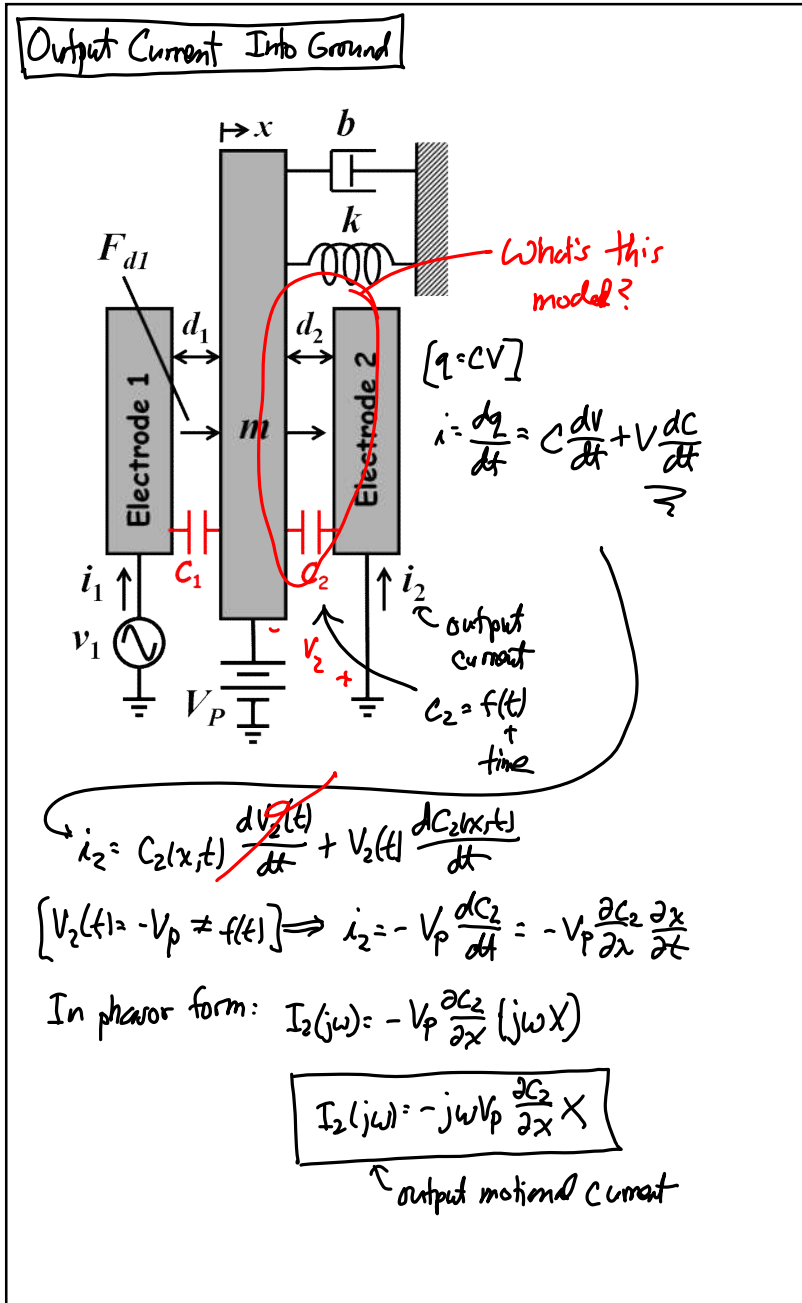

Input Current Expression  $\Rightarrow$  then yields complete equivalent input ckt

Get  $I_1(j\omega)$ :

$$i_1(t) = C_1(x,t) \frac{dv_1(t)}{dt} + v_1(t) \frac{dC_1(x,t)}{dt}$$

$$(v_1(t) = N_1 - V_p) \Rightarrow i_1 = C_1 \frac{dv_1}{dt} + (N_1 - V_p) \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$\uparrow$   
f(t)

magnitude of  $N_1 = \omega_0^2 m$

$$\therefore I_1(j\omega) = \underbrace{j\omega C_1 N_1}_{\text{Feedthrough Current}} + \underbrace{j\omega N_1 \frac{\partial C_1}{\partial x} X}_{\text{Motional Current due to mass motion}} - j\omega V_p \frac{\partial C_1}{\partial x} X \quad *$$

@DC:  $x = \frac{F_d1}{k} = -\frac{1}{k} V_p \frac{\partial C_1}{\partial x} N_1$

@ resonance:  $x = \frac{Q F_d1}{k} = -\frac{Q}{jk} V_p \frac{\partial C_1}{\partial x} N_1 = X$

$\uparrow$   
90° phase lag

Thus: (@ resonance)  $\omega_0$

$$I_1(j\omega) = j\omega_0 C_1 |v_1| + j\omega_0 \left( V_p \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{jk} |N_1|$$

$$= j\omega_0 C_1 |v_1| + \omega_0 \frac{Q}{k} N_1^2 |v_1|$$

$\downarrow$  90° phase-shifted from  $N_1$

$\uparrow$  In phase w/  $N_1$ !

$\uparrow$  This is an effective resistance @  $\omega_0$  seen looking into the electrode!