

**Lecture 23: Mechanical Circuit Analysis & Gyros**

- **Announcements:**
- Module 13 on Equivalent Circuits II online
- Module 14 on Sensing Circuits online
- Module 15 on Gyros, Noise, & MDS
- HW#6 online and due Tuesday, April 17
- Project Slide Set #1 due Friday, April 13
- You do need to be in groups of three
  - ↳ Not 2, not 4
  - ↳ Part of the learning experience in any project entails how to work with others
- Next Tuesday, April 17, Eta Kappa Nu will show up at the beginning of class to guide you through course evaluations
  - ↳ Bring your computer
- -----
- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
  - ↳ Input Modeling
    - Force-to-Velocity Equiv. Ckt.
    - Input Equivalent Ckt.
  - ↳ Current Modeling
    - Output Current Into Ground
    - Input Current
    - Complete Electrical-Port Equiv. Ckt.
  - ↳ Impedance & Transfer Functions
- -----

- -----
- Reading: Senturia, Chpt. 14, Chpt. 16, Chpt. 21
- Lecture Topics:
  - ↳ Gyroscopes
- Reading: Senturia, Chpt. 14
- Lecture Topics:
  - ↳ Detection Circuits
    - Velocity Sensing
    - Position Sensing
- -----
- **Last Time:**
- In the midst of generating the full equivalent circuit

Input Current Expression  $\Rightarrow$  then yields complete equivalent input ckt

Get  $I_1(j\omega)$ :

$$i_1(t) = C_1(x,t) \frac{dv_1(t)}{dt} + v_1(t) \frac{dC_1(x,t)}{dt}$$

$$(v_1(t) = v_1 - v_p) \Rightarrow i_1 = C_1 \frac{dv_1}{dt} + (v_1 - v_p) \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$\uparrow$   
f(t)

magnitude of  $v_1 = \omega_1 r_{par} \omega t$

$$\therefore I_1(j\omega) = \underbrace{j\omega C_1 v_1}_{\text{Feedthrough Current}} + \underbrace{j\omega (v_1 - v_p) \frac{\partial C_1}{\partial x} X}_{\text{Motional Current due to mass motion}} - j\omega v_p \frac{\partial C_1}{\partial x} X \quad *$$

@DC:  $x = \frac{F_{d1}}{k} = -\frac{1}{k} v_p \frac{\partial C_1}{\partial x} v_1$

@ resonance:  $x = \frac{Q F_{d1}}{k} = -\frac{Q}{jk} v_p \frac{\partial C_1}{\partial x} v_1 = X$

Thus: (@ resonance)  $\omega_0$   $\uparrow$  90° phase lag  $\downarrow$  del  $\leftarrow$  plug in to \*

$$I_1(j\omega) = j\omega_0 C_1 |v_1| + j\omega_0 \left( v_p \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{jk} |v_1|$$



$$= \underbrace{j\omega_0 C_1 |v_1|}_{90^\circ \text{ phase-shifted from } v_1} + \underbrace{\omega_0 \frac{Q}{k} \eta_{ei}^2 |v_1|}_{\text{In phase w/ } v_1!}$$



This is a capacitor in shunt w/ input!  $\downarrow$  This is an effective resistance @  $\omega_0$  seen looking into the electrode!  $\uparrow$

Motional Resistance:

$$R_{x1} = \frac{V_1}{I_1} = \frac{k}{\omega_0 Q \eta_{ei}^2} = \frac{m \omega_0}{Q \eta_{ei}^2} = \frac{b}{\eta_{ei}^2} = R_{x1}$$

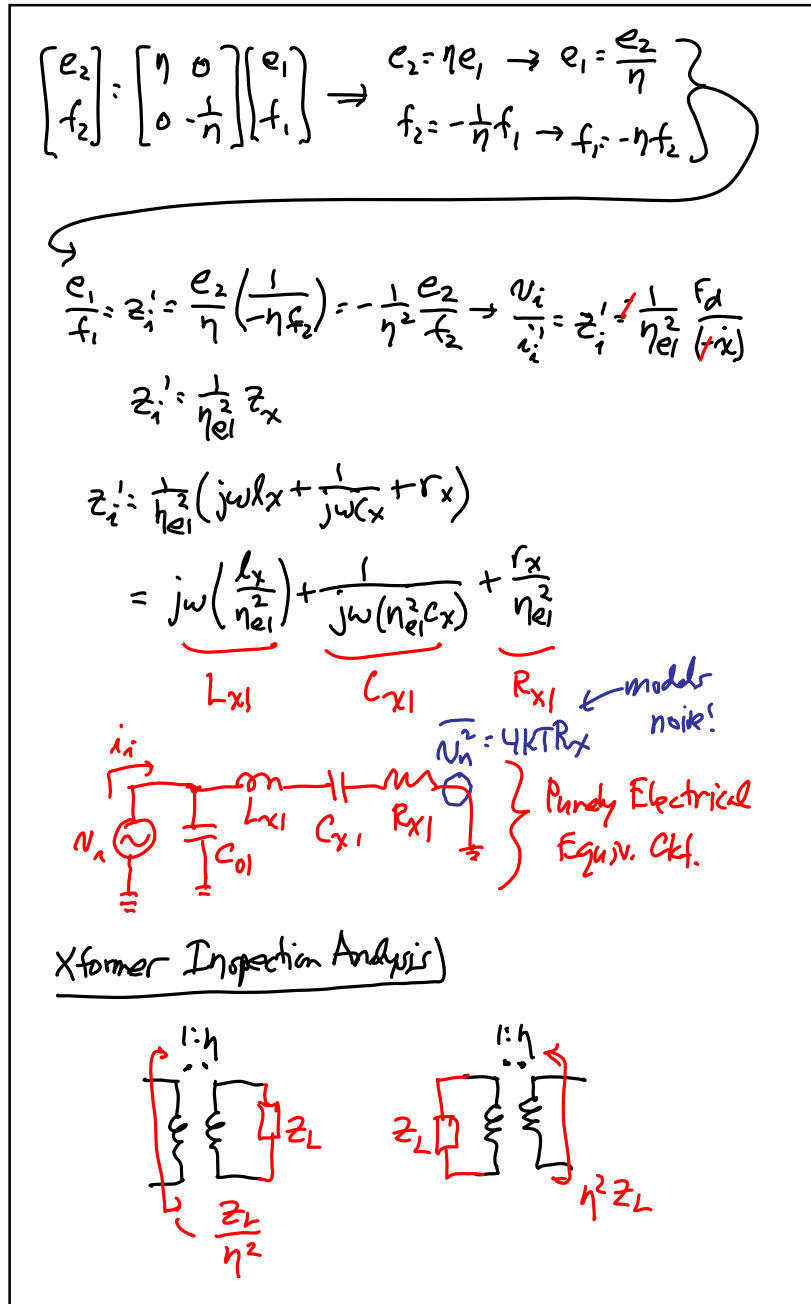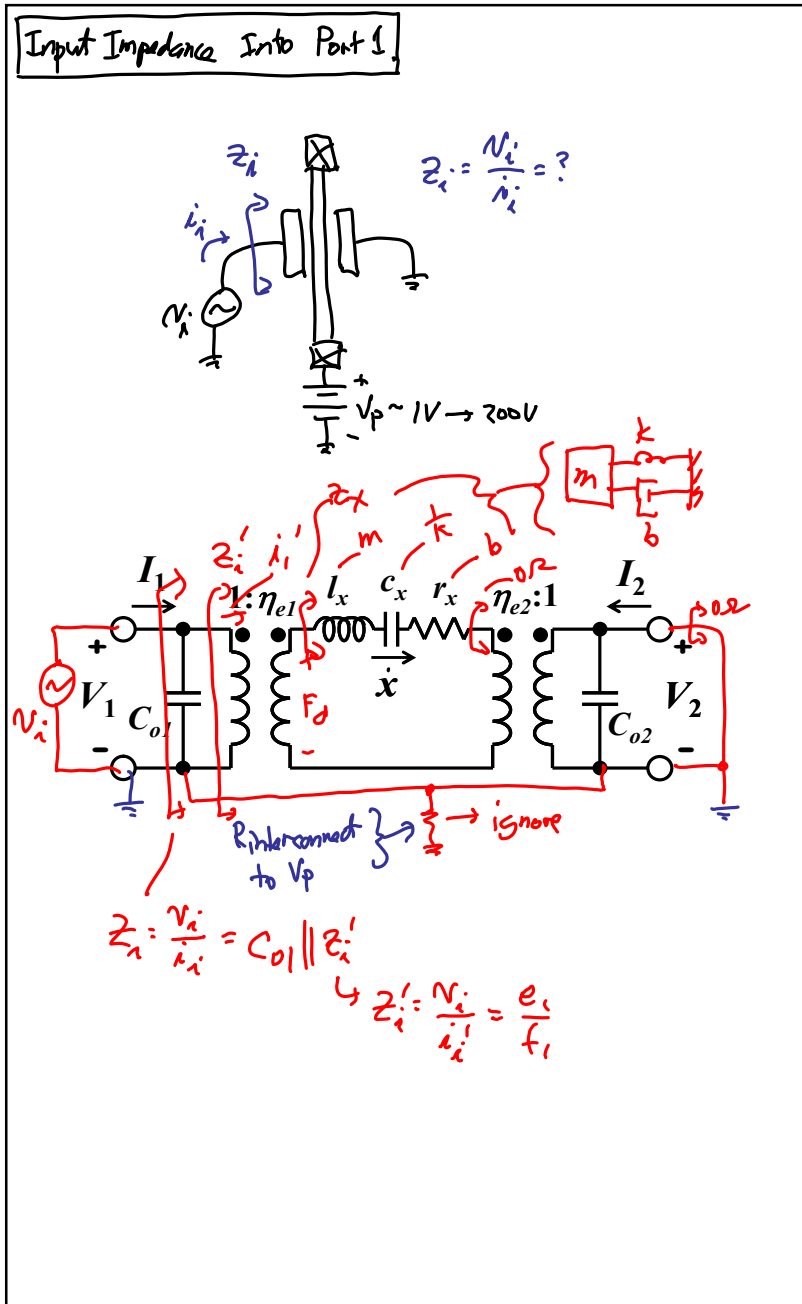The equivalent ckt. better get this right!



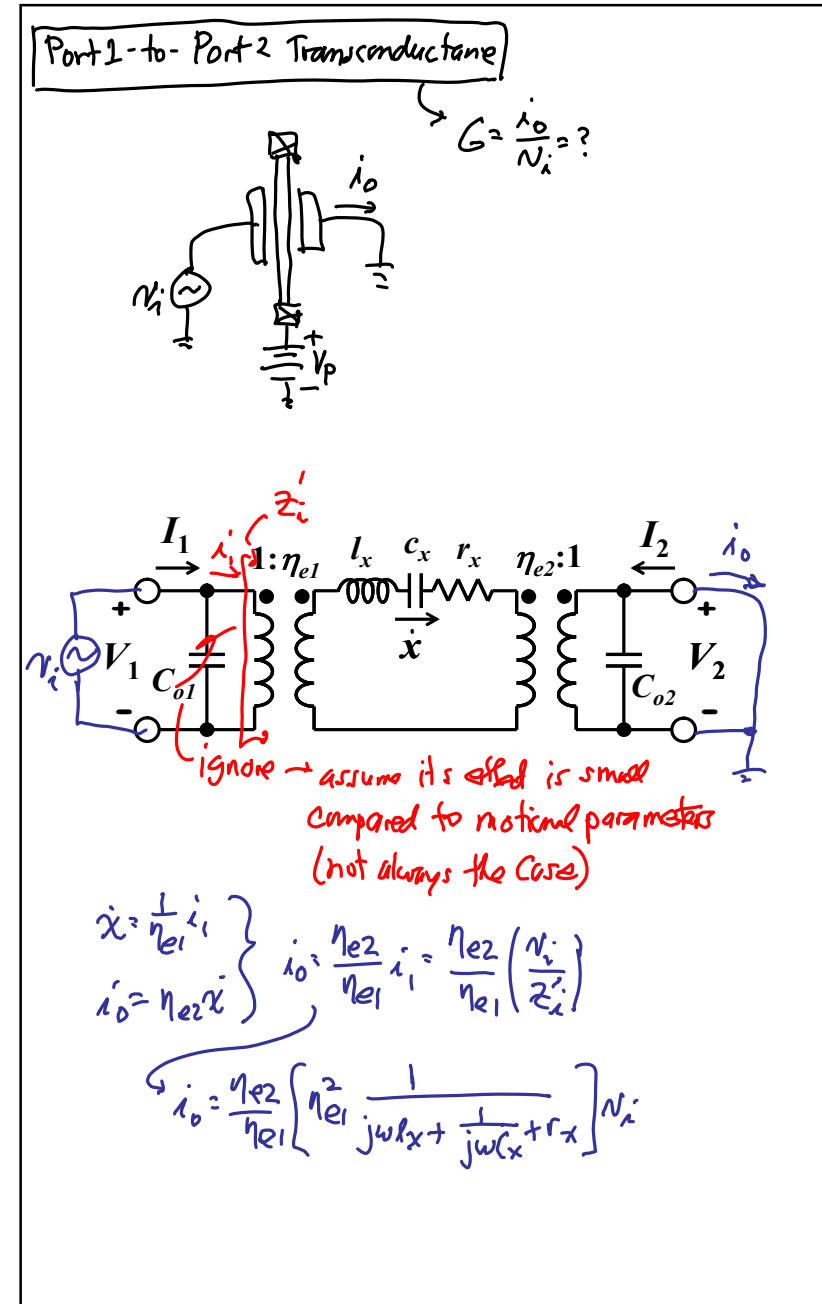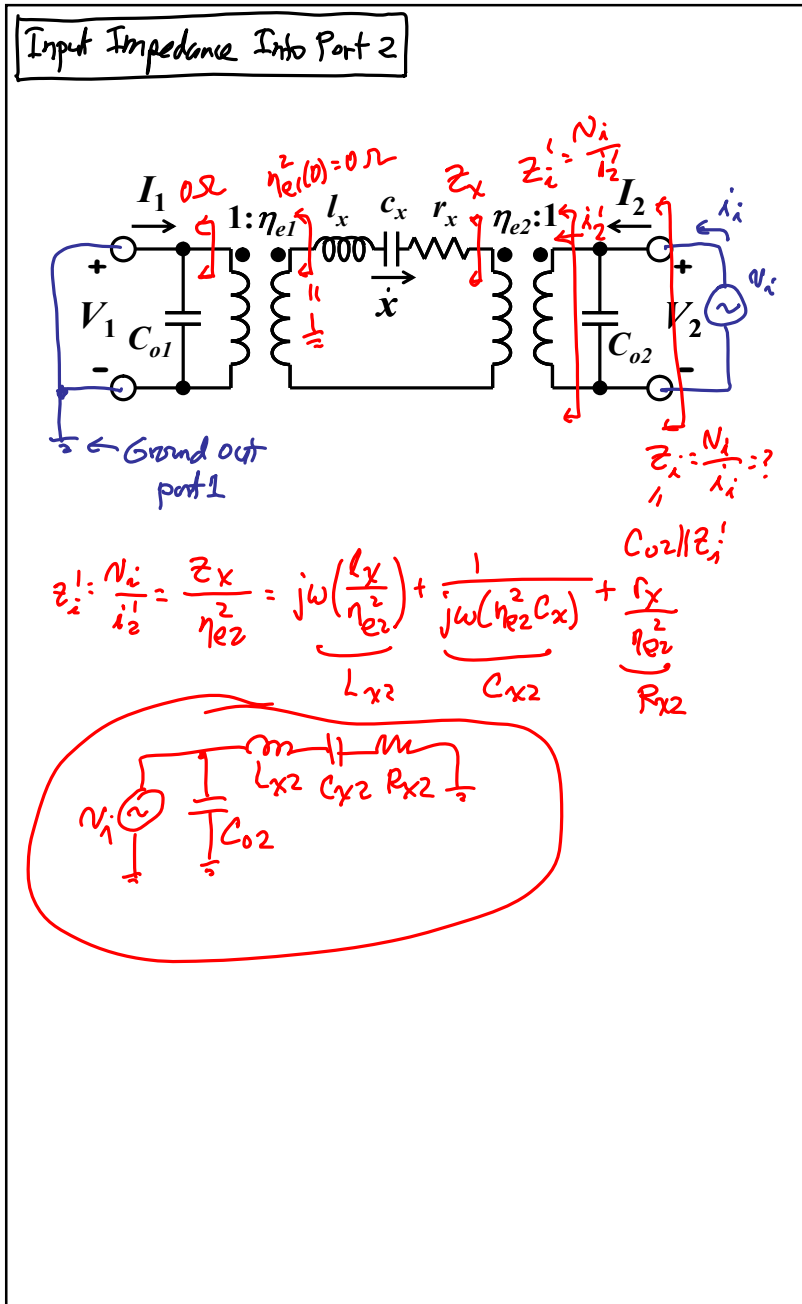

$$\therefore \frac{i_o}{N_i}(j\omega) = \frac{n_1 n_2}{j\omega L_x + \frac{1}{j\omega C_x} + R_x}$$

$$\frac{i_o}{N_i}(j\omega) = \left[ j\omega L_{x12} + \frac{1}{j\omega C_{x12}} + R_{x12} \right]^{-1}$$

where  $L_{x12} = \frac{L_x}{n_1 n_2}$ ,  $C_{x12} = n_1 n_2 C_x$   
 $R_{x12} = \frac{R_x}{n_1 n_2}$

$\Rightarrow$  separate into magnitude & freq. response components

$$\frac{i_o}{N_i}(s) = \frac{1}{sL_x + \frac{1}{sC_x} + R_x} = \frac{s(\frac{1}{L_x})}{s^2 + \frac{1}{L_x C_x} + s(\frac{R_x}{L_x})}$$

$\left( \frac{1}{L_x C_x} = \omega_0^2, Q = \frac{\omega_0 L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0}{Q} \right)$

$$\frac{i_o}{N_i}(s) = \frac{1}{R_x} \frac{s(\frac{\omega_0}{Q})}{s^2 + s(\frac{\omega_0}{Q}) + \omega_0^2} = \frac{1}{R_x} \textcircled{H}(s)$$

Gain Term      Frequency Shaping Term      resonance magnitude

\*

$\frac{i_o}{N_i}(s)$  vs  $\omega$

\* Bandpass Signal

$\frac{1}{R_x}$

$\omega_0$

$\omega$

To analyze mechanical ckt. problems:

- ① Just solve the ckt. @ resonance  $\rightarrow$  easy, since L & C cancel
- ② Then multiply the result by  $\textcircled{H}(s)$ !

- Now, go through slide 21 in Module 13
- Then, start gyroscopes in Module 15