

### Position-to-Voltage Conversion

UC Berkeley

To sense position (i.e., displacement), use a capacitive load

Again, have port-to-port I/O symmetry:

Brute force approach:

$$\frac{N_o}{V_i}(s) = \frac{1}{R_x + \frac{1}{sC_x} + sL_x + \frac{1}{sC_D}}$$

$$\frac{N_o}{V_i}(s) = \frac{\frac{sC_x}{sR_x C_x + 1 + s^2 L_x C_x + \frac{sC_x}{sC_D}}{1 + C_x/C_D} = \frac{C_x/C_D}{1 + \frac{sR_x C_x}{1 + C_x/C_D} + s^2 \frac{L_x C_x}{1 + C_x/C_D}}$$

$$\omega_0^2 = \frac{1}{L_x C_x} \rightarrow (\omega_0)^2 = \omega_0^2 (1 + C_x/C_D)$$

$$Q = \frac{\omega_0 L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0^2}{Q^2}, Q = Q\sqrt{1 + C_x/C_D}$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 6

### Position-to-Voltage Conversion

UC Berkeley

To sense position (i.e., displacement), use a capacitive load

DC Gain Term

Low-Pass Biquad

To maximize gain  $\rightarrow 1$ , need  $C_D \ll C_x$ . (must minimize  $C_D$ )

Note: Can we similar short-cut to the R case.

- Get DC response  $\rightarrow C$ 's dominate.
- Then:

$$\frac{N_o}{V_i}(s) = (\text{DC Gain}) \cdot \frac{1}{s} \cdot \Theta(s, \omega_0, Q) \cdot \omega_0^2 Q'$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 7

### Velocity Sensing Circuits

UC Berkeley

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 8

### Velocity-to-Voltage Conversion

UC Berkeley

To convert velocity to a voltage, use a resistive load

Since this structure has completely symmetrical I/O ports:

Work @ resonance: (to simplify the analysis)

$$\frac{N_o}{V_i} = \frac{R_D}{R_x + R_D} \text{ (@ resonance)}$$

Then, generalize to off resonance:

$$\frac{N_o}{V_i} = \frac{R_D}{R_x + R_D} \Theta(s, Q'), \text{ where } Q' = Q \left( \frac{R_x}{R_x + R_D} \right)$$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 9

### Problems With Purely Resistive Sensing

Now, we get: (Approximately)  
 $\frac{N_0}{N_i}(s) \sim \frac{R_0}{R_x + R_0} \cdot \frac{1}{1 + \frac{s}{\omega_p}} \cdot (-1)(s, \omega_b, Q^2)$

$\omega_p = \frac{1}{(R_x || R_0) C_p}$  Depend on both  $R_0$  &  $C_p$ .

Impact depends on where  $\omega_p$  is relative to  $\omega_b$ .

Includes  $C_o$ , line C, bond pad C, and next stage C

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 10

### Problems With Purely Resistive Sensing

In general, the sensor output must be connected to the inputs of further signal conditioning circuits  $\rightarrow$  input  $R_i$  of these circuits can load  $R_D$ .

These change w/ hook-up  $\rightarrow$  not good.

Problem: need a sensing circuit that is immune to parasitics or loading.

Soln: use op amps.

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 11

### The TransR Amplifier Advantage

The virtual ground provided by the ideal op amp eliminates the parasitic capacitance  $C_p$  and  $R_i$ .

The zero output resistance of the (ideal) op amp can drive virtually anything.

Virtual Ground  $\Rightarrow$  No voltage across  $C_p$   
 $\Rightarrow C_p$  effectively isn't there!

$N_0 = \frac{-R_2}{R_x} (-1)(s) N_i$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 12

### Position Sensing Circuits

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 13

### Problems With Pure-C Position Sensing

• To sense position (i.e., displacement), use a capacitive load

$$\frac{N_o}{N_i}(s) = \frac{C_x C_D}{1 + C_x C_D} \cdot \frac{1}{s} \cdot \Theta(s, \omega_0, Q) \cdot \omega_0^2$$

Integration yields displacement.  
To maximize gain, minimize  $C_D$ .  
⇒ Problem: parasitic capacitance  
 $C_D \rightarrow C_D + C_{p1} + C_{p2}$   
⇒ DC Gain:  $\frac{C_x / (C_D + C_{p1} + C_{p2})}{1 + C_x / (C_D + C_{p1} + C_{p2})}$   
Output will get smaller!  
Remedy: Suppress  $C_p$  via use of op amps.

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 14

### The Op Amp Integrator Advantage

• The virtual ground provided by the ideal op amp eliminates the parasitic capacitance  $C_p$

$R_2 \gg \frac{1}{sC_2}$  (for biasing)  
 $R_0 = 0\Omega$   
Can drive next stages  $R_i$  w/o interference to transfer function!  
negl. since  $R_2$  = large well defined → good!  
 $N_o = -i_o (R_2 \parallel \frac{1}{sC_2})$   
 $x = \frac{N_i}{R_x} \Theta(s) \frac{1}{sC_2} \Rightarrow \frac{N_o}{N_i}(s) = -\frac{1}{R_x C_2} \Theta(s) \frac{1}{s}$

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 15

### Differential Position Sensing

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 16

### Differential Position Sensing

• Example: ADXL-50

Proof Mass  
Sense Finger  
Applied Acceleration  
Fixed Electrodes  
Suspension Beam in Tension

$C_1 \gg C_2$  Capacitive divider  
 $V_o = -V_p + (2V_p) \frac{C_1}{C_1 + C_2}$   
 $= -V_p C_1 - V_p C_2 + 2V_p C_1 = \frac{V_p (C_1 - C_2)}{C_1 + C_2} = V_o$   
Irrig: Parasitic Capacitance  
 $V_o = \frac{C_1 - C_2}{C_1 + C_2} V_p$  Arbitrary,  $C_p$  reduces gain!  
Soln: use op amp!

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 17

### Buffer-Bootstrapped Position Sensing

Includes capacitance from interconnects, bond pads, and  $C_{gs}$  of the op amp

Unity Gain Buffer

$C_{gd}$  = gate-to-drain capacitance of the input MOS transistor

• Bootstrap the ground lines around the interconnect and bond pads  
 ↳ No voltage across  $C_p$   
 ↳ It's effectively not there!

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 18

### Effect of Finite Op Amp Gain

Total ADXL-50 Sense  $C \sim 100\text{fF}$

Unity Gain Buffer

Get  $Z_i = \frac{V_i}{I_i}$ :  $I_i = (V_i - V_o) s C_p = V_i \left(1 - \frac{A_o}{1 + A_o}\right) s C_p = V_i \frac{1}{1 + A_o} s C_p$

$\therefore \frac{N_i}{I_i} = Z_i = \frac{1}{s \left[ \frac{C_p}{1 + A_o} \right]}$   $\rightarrow C_{\text{eff}} = \frac{C_p}{1 + A_o}$

Ex:  $A_o = 100, C_p = 2\text{pF}$   
 $\Rightarrow C_{\text{eff}} = \frac{2\text{pF}}{101} = 20\text{fF}$   
 ↳ Not negligible compared w/ ADXL-50  $C_{\text{tot}} \sim 100\text{fF}$ !

No longer zero!

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 19

### Integrator-Based Diff. Position Sensing

$R_2 \gg \frac{1}{s C_2}$  (for biasing)

$R_o = 0\Omega$

Can drive next stage's  $R_i$  w/o interference to transfer function!

$i_o = i_1 + i_2 = N_p(s C_1) - N_p(s C_2) = V_p s (C_1 - C_2)$

$\therefore V_o = -i_o \left( \frac{1}{s C_F} \right) = -N_p \left( \frac{C_1 - C_2}{C_F} \right)$

$\frac{V_o}{V_p} = - \frac{C_1 - C_2}{C_F} \Rightarrow$  A seemingly perfect differential sensor/amplifier output! ... but only when the op amp is ideal...

EE C245: Introduction to MEMS Design LecM 14 C. Nguyen 11/18/08 20