

Lecture 26: Noise

- **Announcements:**
- This is a recorded lecture, since I am presently on travel
- HW#7 online since Tuesday and due Friday, May 4, 10 a.m.
- Project slide #3 due Friday, April 27
- Project outbrief sign up sheet will be on Prof. Nguyen's office door this coming Thursday
 - ↳ Slots will be on Monday and Tuesday of Finals week
-
- Reading: Senturia Chpt. 16
- Lecture Topics:
 - ↳ Minimum Detectable Signal
 - ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
 - ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination
-
- **Last Time:**
- Finished MEMS/transistor integration
- Now, move on to noise starting with Module 17, slides 1-7

Circuit Noise Calculations

Linear Time-Invariant System

Deterministic Signals:

$N_o(j\omega) = H(j\omega) N_i(j\omega)$

Random Signals:

Mean-Square Spectral Density

$$S_o(\omega) = [H(j\omega) H^*(j\omega)] S_i(\omega) = |H(j\omega)|^2 S_i(\omega)$$

$$\sqrt{S_o(\omega)} = |H(j\omega)| \sqrt{S_i(\omega)} \rightarrow \text{How is it we can do this?}$$

Root mean-square amplitudes

Handling Noise Deterministically

$\frac{N_{ni}^2}{\Delta f} = S_i(f) \rightarrow N_{ni} = \sqrt{S_i(f) B}$

Can approximate this by a sinusoidal voltage generator (esp. when B is small, say 1Hz)

Why is this the case?
white noise

Neither the amplitude nor the phase of a signal can change appreciably within a time period $\sim 1/B$!

Systematic Noise Calculation Procedure

General Ckt. w/ several Noise Sources

Assume noise sources are uncorrelated.

- For i_{ni}^2 , replace w/ a deterministic source of value $i_{ni} = \sqrt{\frac{i_{ni}^2}{\Delta f}} \cdot (1\text{Hz})$
- Calculate $N_{onr}(w) = i_{ni}(w) H_i(jw)$ (treating it like a deterministic signal)
- Determine $N_{onr}^2 = i_{ni}^2 \cdot |H_i(jw)|^2$
- Repeat for each noise source: $N_{n2}^2, N_{n3}^2, i_{n4}^2, \dots \rightarrow \text{output}$

⑤ Add noise powers (mean-square values)

$$\overline{N_{\text{TOT}}^2} = \overline{N_{\text{on}1}^2} + \overline{N_{\text{on}2}^2} + \overline{N_{\text{on}3}^2} + \overline{N_{\text{on}4}^2} + \dots$$


$$N_{\text{TOT}} = \sqrt{\overline{N_{\text{on}1}^2} + \overline{N_{\text{on}2}^2} + \overline{N_{\text{on}3}^2} + \overline{N_{\text{on}4}^2} + \dots}$$

↑
total rms value

• Go through Module 17, slides 12-16

Why $\frac{\overline{N_R^2}}{\Delta f} = 4kTR$? (a heuristic argument)

Consider an RC ckt:

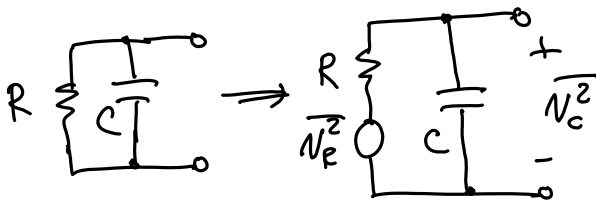

$$E = \frac{1}{2}kT = \frac{1}{2}C\overline{N_C^2}$$

∴ $\overline{N_C^2} = \frac{kT}{C}$ ← integrated noise over all freq. (total mean-square voltage integrated over all freq.)

* →

Question: What value of $\frac{\overline{V_R^2}}{\Delta f}$ gives us this (assuming white noise) *

$$\overline{N_C^2} = \int_0^\infty \left| \frac{1}{1+j\omega RC} \right|^2 \frac{\overline{V_R^2}}{\Delta f} d\omega$$


[noise is white] → $= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \int_0^\infty \frac{\omega_b^2}{\omega_b^2 + \omega^2} d\omega$
 $(\omega_b = \frac{1}{RC})$

$$\left[\int \frac{dx}{x^2+a^2} = \frac{1}{a} \tan^{-1}\left(\frac{x}{a}\right) \right]$$

$$= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \frac{\omega_b^2}{\omega_b} \tan^{-1}\left(\frac{\omega}{\omega_b}\right) \Big|_0^\infty$$

$$= \frac{1}{2\pi} \frac{\overline{V_R^2}}{\Delta f} \left(\frac{\pi}{2} \omega_b - 0 \right) = \frac{1}{4} \omega_b \frac{\overline{V_R^2}}{\Delta f} = \frac{kT}{C}$$
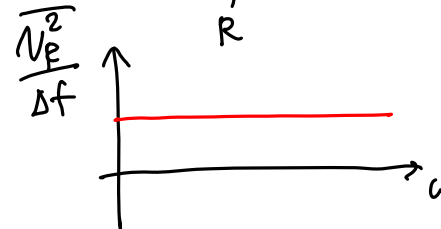
$$\frac{\overline{V_R^2}}{\Delta f} = 4kT \left(\frac{\omega_b}{C} \right) \Rightarrow \frac{\overline{V_R^2}}{\Delta f} = 4kTR$$



• Go through Module 17, slides 19-20

Example. Typical Noise Numbers

Measure w/ AC voltmeter

Measure on a Spectrum Analyzer

100x

Get Gaussian amplitude distribution

Probability

Amplitude

68% within $\pm\sigma$

99.7% within $\pm 3\sigma$

Area $\sim \sqrt{v_n^2}$

$\frac{\sqrt{v_R^2}}{\Delta f}$

$4kTR$

$\frac{1}{2\pi RC}$

$R = 1k\Omega \rightarrow \sqrt{(1.66 \times 10^{-20}) / (1k)}$


* $1k\Omega: 4nV/\sqrt{Hz}$ (for every 1k of R)

$1pF: \sqrt{\frac{kT}{C}} = 64\mu V_{rms}$

Case: AC Voltmeter


$\sqrt{N_0^2} = (100)(64\mu V_{rms}) = \underline{6.4mV_{rms}}$

Case: Spectrum Analyzer

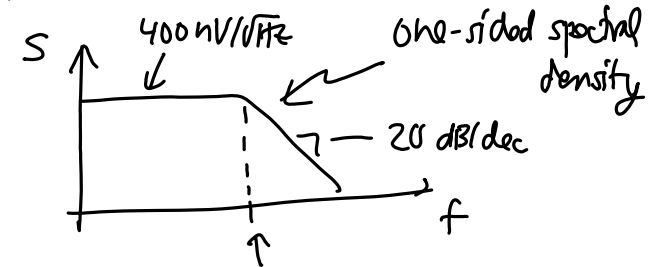

$\frac{1}{2\pi(1k)(1p)} = 60MHz$

• Go through Module 17, slides 23-29

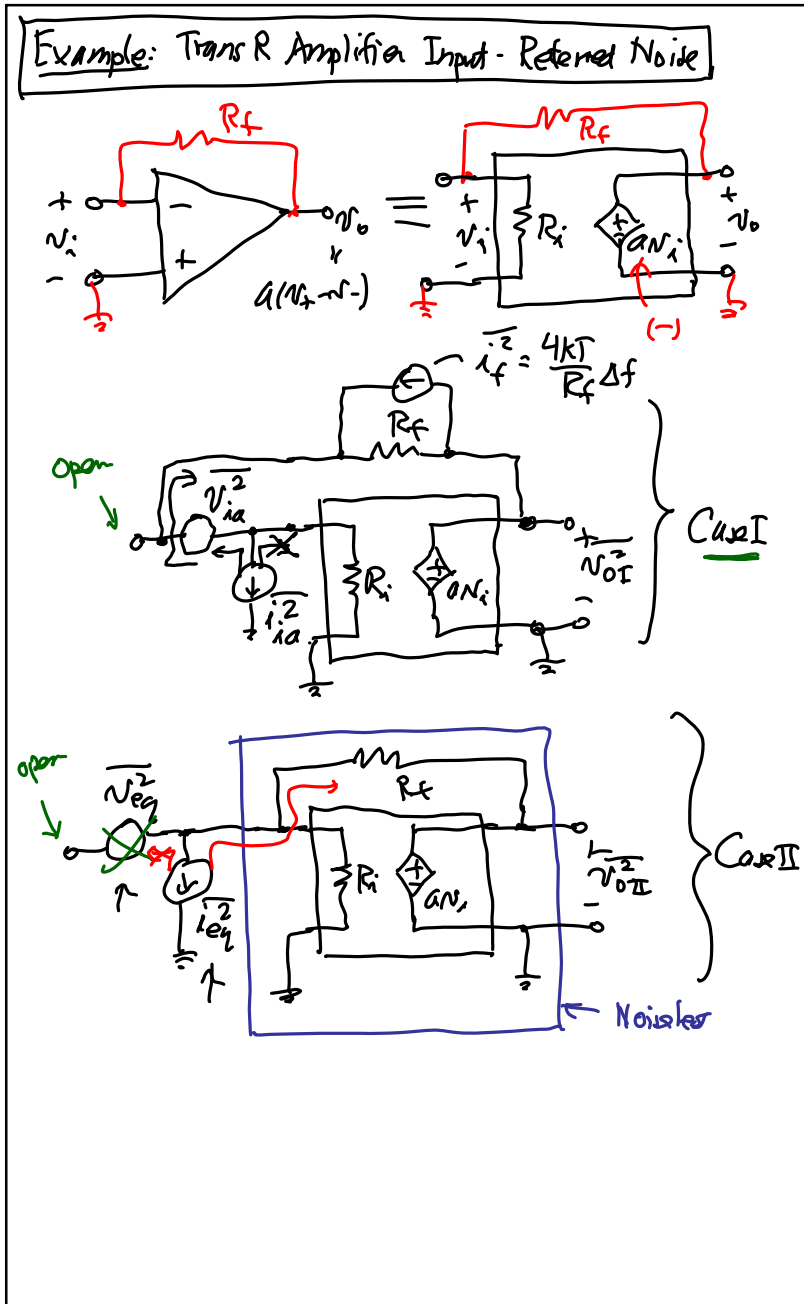

Input-Referred Current Noise:

Open inputs; equate output voltage noise for Case I + Case II \rightarrow solve for i_{eq}^2

Case I: (use superposition)


$i_{ia}^2: N_{OI1} = i_{ia} R_f \rightarrow N_{OI1}^2 = i_{ia}^2 R_f^2$

$i_f^2: N_{OI2} = i_f R_f \rightarrow N_{OI2}^2 = i_f^2 R_f^2$

$N_{ia}^2:$

$N_{OI3} = N_{ia} \rightarrow N_{OI3}^2 = N_{ia}^2$

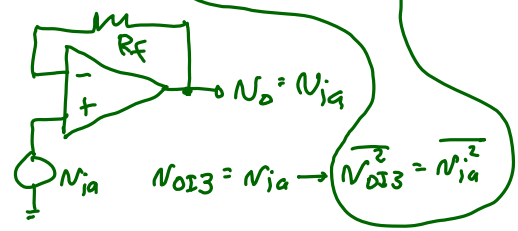power @ output generated by noise sources



$\therefore N_{OI}^2 = i_{ia}^2 R_f^2 + i_f^2 R_f^2 + N_{ia}^2$

Case II: $N_{OI} = i_{eq} R_f \rightarrow N_{OI}^2 = i_{eq}^2 R_f^2$

Now, set $N_{OI}^2 = N_{OI}^2$:

$i_{eq}^2 = i_{ia}^2 + i_f^2 + \frac{N_{ia}^2}{R_f^2}$