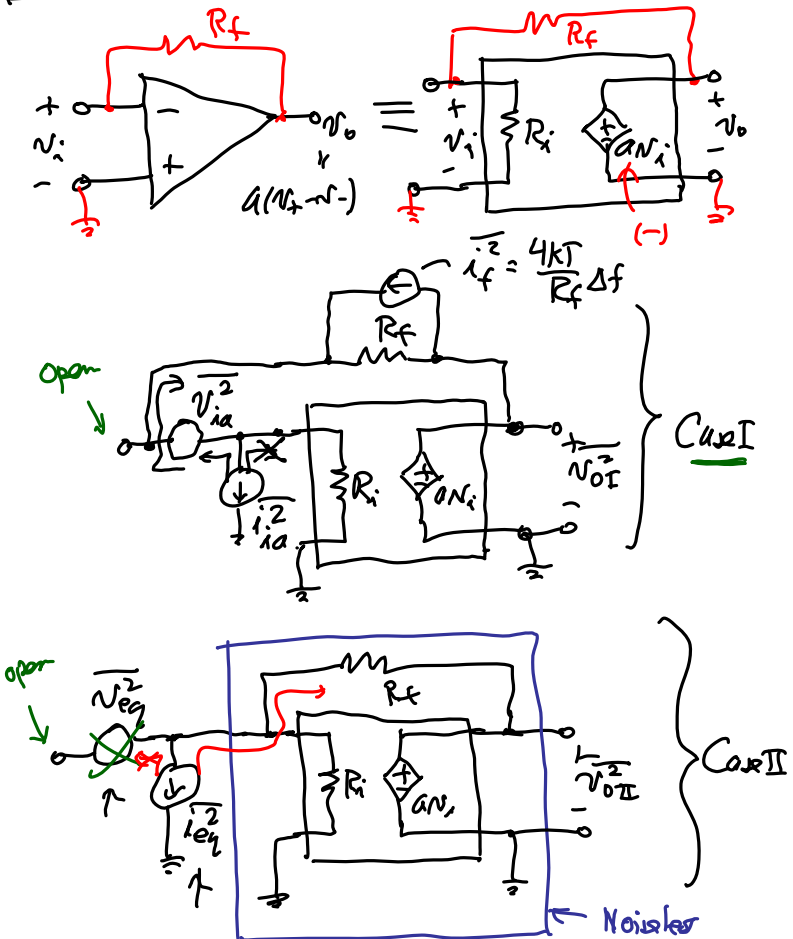


Lecture 27: Gyro Minimum Detectable Signal (MDS)

- **Announcements:**
- This is our last lecture
- HW#7 online since Tuesday and due Friday, May 4, 10 a.m.
- Project slide #3 due Friday, April 27
- Project outbrief sign up sheet will be on Prof. Nguyen's office door later today
 - ↳ Slots will be on Monday and Tuesday of Finals week
- Old Final Exams passed out
- Final Exam Info Sheet will be online
- Review Session at a time and location TBD
-
- Reading: Senturia Chpt. 16
- Lecture Topics:
 - ↳ Minimum Detectable Signal
 - ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
 - ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination
 - ↳ Course Wrap Up (Final Exam Info)
-
- **Last Time:**
- Going through input referred noise
- Now, continue with this

Example: Trans R Amplifier Input-Referred Noise




Input-Referenced Current Noise:

Open inputs; equate output voltage noise for Case I & Case II \rightarrow solve for i_{eq}^2

Case I: (w/ superposition)

$i_{ia}^2: N_{oI1} = i_{ia} R_f \rightarrow N_{oI1}^2 = i_{ia}^2 R_f^2$
 $i_f^2: N_{oI2} = i_f R_f \rightarrow N_{oI2}^2 = i_f^2 R_f^2$

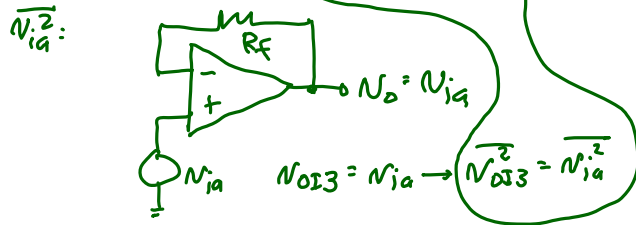power @ output generated by noise sources



$\therefore N_{oI}^2 = i_{ia}^2 R_f^2 + i_f^2 R_f^2 + N_{ia}^2$



Case II: $N_{oII} = i_{eq} R_f \rightarrow N_{oII}^2 = i_{eq}^2 R_f^2$

Now, set $N_{oI}^2 = N_{oII}^2:$

$$i_{eq}^2 = i_{ia}^2 + i_f^2 + \frac{N_{ia}^2}{R_f^2}$$

Now, get the input-referenced voltage-noise:


Short input; equate output voltage noise.

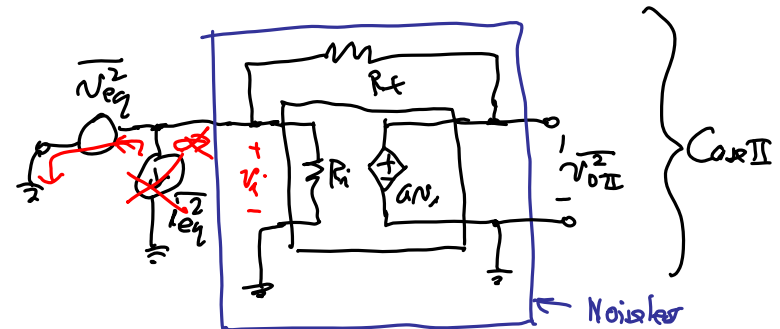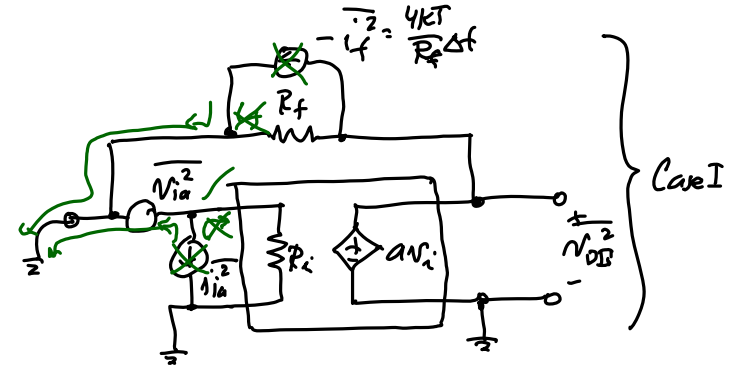

Case I: $N_{oI} = a N_{ia} \rightarrow N_{oI}^2 = a^2 N_{ia}^2$

Case II: $N_{oII} = a N_{eq} \rightarrow N_{oII}^2 = a^2 N_{eq}^2$

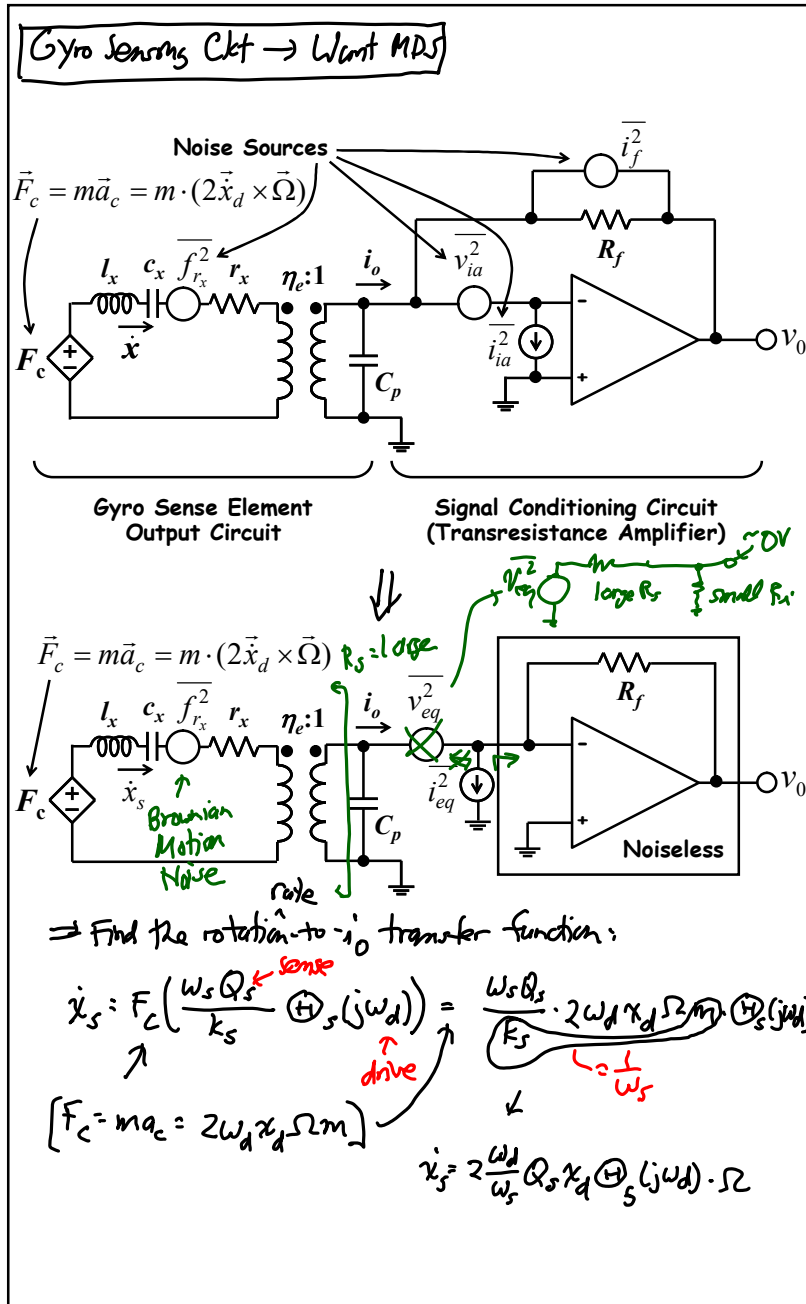$N_{oI}^2 = N_{oII}^2 \rightarrow N_{eq}^2 = N_{ia}^2$



$$\Theta(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$s=0: \Theta(0) = 0$
 $s=j\omega_0: \Theta(j\omega_0) = 1$
 $s=\infty: \Theta(\infty) = 0$

$$i_o = \eta_e \kappa_r = 2 \frac{\omega_d}{\omega_s} Q_s \kappa_d \eta_e \Theta_s(j\omega_d) \cdot \Omega$$

$A \hat{=}$ scale factor

$$\Rightarrow i_o = A \Omega, \text{ where } A = 2 \frac{\omega_d}{\omega_s} Q_s \kappa_d \eta_e \Theta_s(j\omega_d)$$

input rotation

When $\Omega = \Omega_{min} \hat{=} MDS \rightarrow i_o = i_{eqTOT}$

noise current entering the sense amplifier

$$\therefore i_{eqTOT} = A \Omega_{min}$$

$$\Omega_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) \left[(^\circ/hr) / \sqrt{Hz} \right]$$

$$\text{Angle Random Walk} = ARW = \frac{1}{60} \Omega_{min} \left[^\circ/\sqrt{hr} \right]$$


↪ Easier to determine directional error as a function of elapsed time

⇒ the total current entering the amplifier input: (i_{eTOT})

$$i_{eTOT} = i_{rx} + i_{e2} \rightarrow \overline{i_{eTOT}^2} = \overline{i_{rx}^2} + \overline{i_f^2} + \overline{i_{ia}^2} + \frac{\overline{V_{ia}^2}}{R_f^2}$$

Brownian motion noise of the sense element
↳ determined entirely by noise in $r_x \rightarrow \overline{f_{rx}^2}$

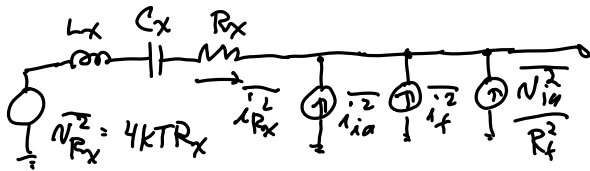easiest to see when convert to all electrical ckt.



where $L_x = \frac{l_x}{\eta^2}$, $C_x = \eta^2 c_x$, $R_x = \frac{r_x}{\eta^2}$

$$\therefore i_{rx} = \sqrt{R_x} \left(\frac{1}{R_x} \right) \mathcal{H}_s(j\omega) + \frac{\overline{i_{rx}^2}}{\Delta f} = 4kTR_x \left(\frac{1}{R_x^2} \right) \mathcal{H}_s(j\omega)^2$$

$$\Rightarrow \frac{\overline{i_{rx}^2}}{\Delta f} = \frac{4kT}{R_x} |\mathcal{H}_s(j\omega)|^2$$

← current noise from Brownian motion that gets to the transR amp input

Thus:

$$\frac{\overline{i_{eTOT}^2}}{\Delta f} = \frac{4kT}{R_x} |\mathcal{H}_s(j\omega)|^2 + \frac{4kT}{R_f} + \frac{\overline{i_{ia}^2}}{\Delta f} + \frac{\overline{V_{ia}^2}}{\Delta f R_f^2}$$

$$i_{eTOT} = \sqrt{\frac{\overline{i_{eTOT}^2}}{\Delta f} \times \text{BW}}$$

↑
Bandwidth

- Go through slides 45-49 in Module 17
- Related courses at UC Berkeley:
 - ↳ EE 143: Microfabrication Technology
 - ↳ EE 147/247A: Introduction to MEMS
 - ↳ ME 119: Introduction to MEMS (mainly fabrication)
 - ↳ BioEng 121: Introduction to Micro and Nano Biotechnology and BioMEMS
 - ↳ ME C219 - EE C246: MEMS Design
 - ↳ EE 290M?