



EE C247B - ME C218
Introduction to MEMS Design
Spring 2018

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences
University of California at Berkeley
Berkeley, CA 94720

Lecture Module 13: Equivalent Circuits II

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 1



Lecture Outline

- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
 - ↳ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↳ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↳ Impedance & Transfer Functions

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 2

UC Berkeley

Input Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 3

UC Berkeley

Electromechanical Analogies

$F(t) = F \cos(\omega t) \rightarrow x(t) = X \cos\omega t$
Equation of Motion:
 $m_{eq} \ddot{x} + c_{eq} \dot{x} + k_{eq} x = F(t)$
 \Rightarrow using phasor concepts:
 $F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + c_{eq} x$
 \Rightarrow by analogy:
 $F \rightarrow N \quad m_{eq} \rightarrow l_x \quad c_{eq} \rightarrow r_x$
 $\dot{x} \rightarrow i \quad k_{eq} \rightarrow \frac{1}{c_x}$

$i(t) = I \cos\omega t \rightarrow N = I \cos\omega t$
Impedance looking in:
 $\frac{N}{I} = j\omega l_x + \frac{1}{j\omega c_x} + r_x$
 $N = j\omega l_x i + \frac{1}{j\omega} i + r_x i$

[Parameter Relationships] in the Current Analogy

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 4

Bandpass Biquad Transfer Function

$F = j\omega m_{eq} \ddot{x} + \frac{k_{eq}}{j\omega} \dot{x} + C_{eq}x$

⇒ Converting to full phasor form:

$F = (j\omega)(j\omega X) m_{eq} + \frac{k_{eq}}{j\omega} (j\omega X) + C_{eq}(j\omega X)$

$\frac{X}{F}(j\omega) = \frac{1}{k_{eq}} \left[-\omega^2 \frac{m_{eq}}{k_{eq}} + 1 + j \frac{C_{eq}\omega}{k_{eq}} \right]^{-1} = \frac{1}{k_{eq}} \left[-\left(\frac{\omega}{\omega_0}\right)^2 + 1 + j \frac{\omega}{Q\omega_0} \right]^{-1}$

$\left[\frac{k_{eq}}{m_{eq}} = \omega_0^2, Q = \frac{m_{eq}\omega_0}{C_{eq}} = \frac{k_{eq}}{\omega_0 C_{eq}} \rightarrow \frac{k_{eq}}{C_{eq}} = Q\omega_0 \right]$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 5

Force-to-Velocity Relationship

- The relationship between input voltage v_1 and force F_{d1} :

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1$$



- When displacement x is the mechanical output variable:



$$\frac{X(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_o^2}{s^2 + (\omega_o/Q)s + \omega_o^2}$$

- When velocity v is the mechanical output variable:

$$\frac{v(s)}{F_{d1}(s)} = \frac{sX(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_o^2 s}{s^2 + (\omega_o/Q)s + \omega_o^2}$$

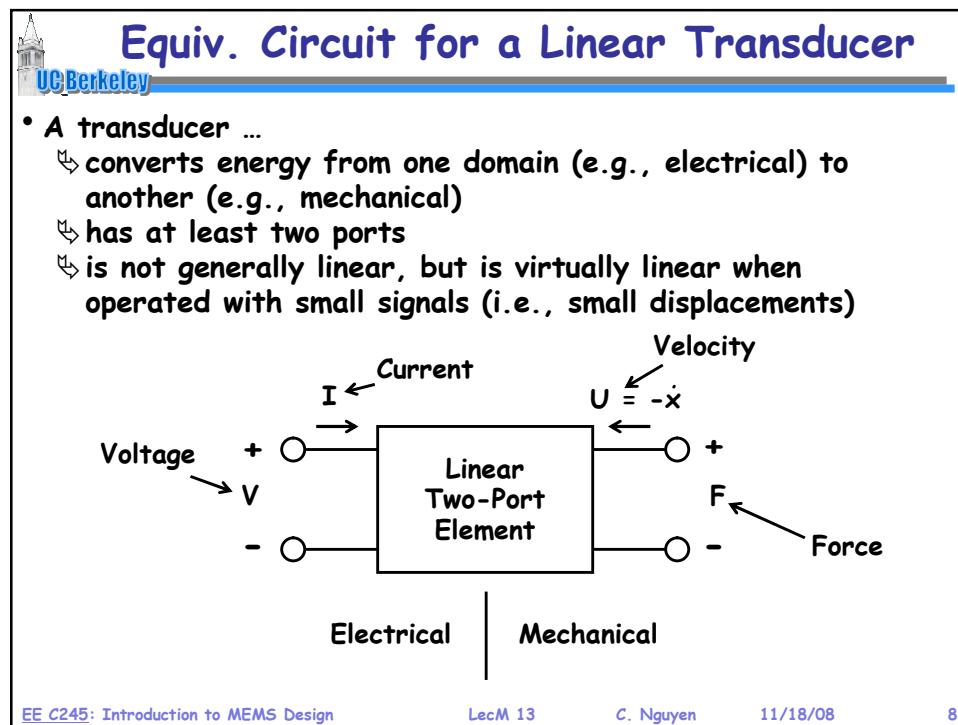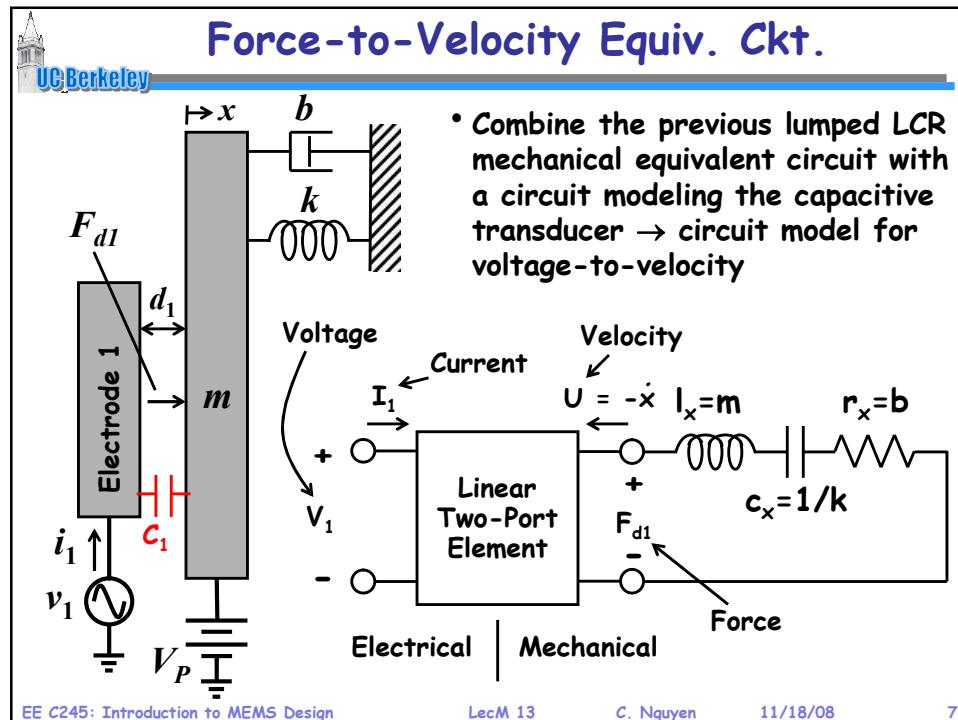EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 6



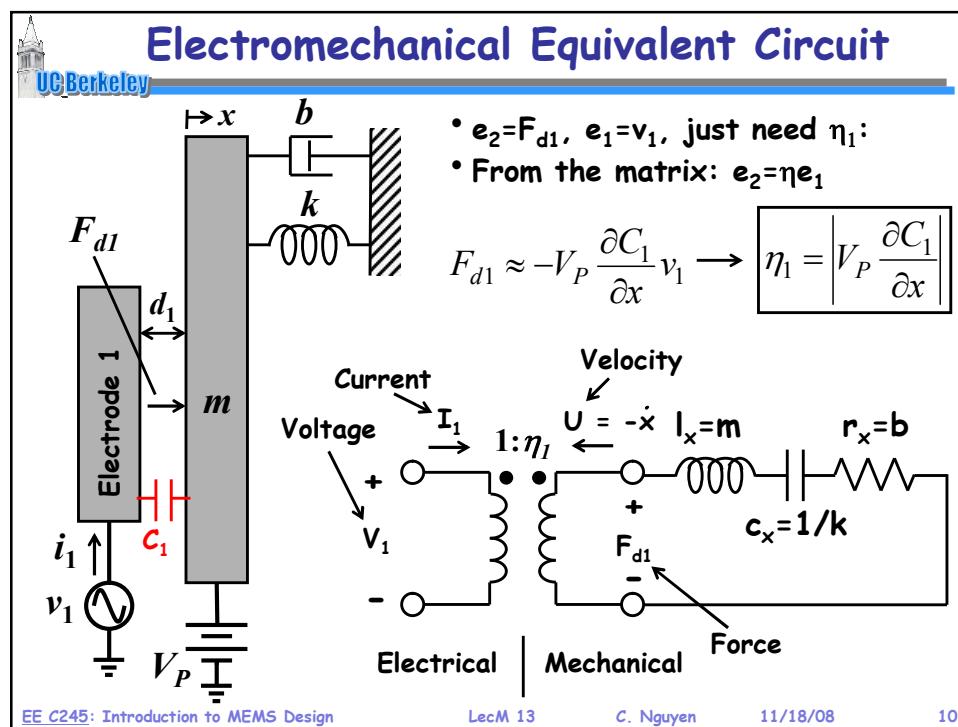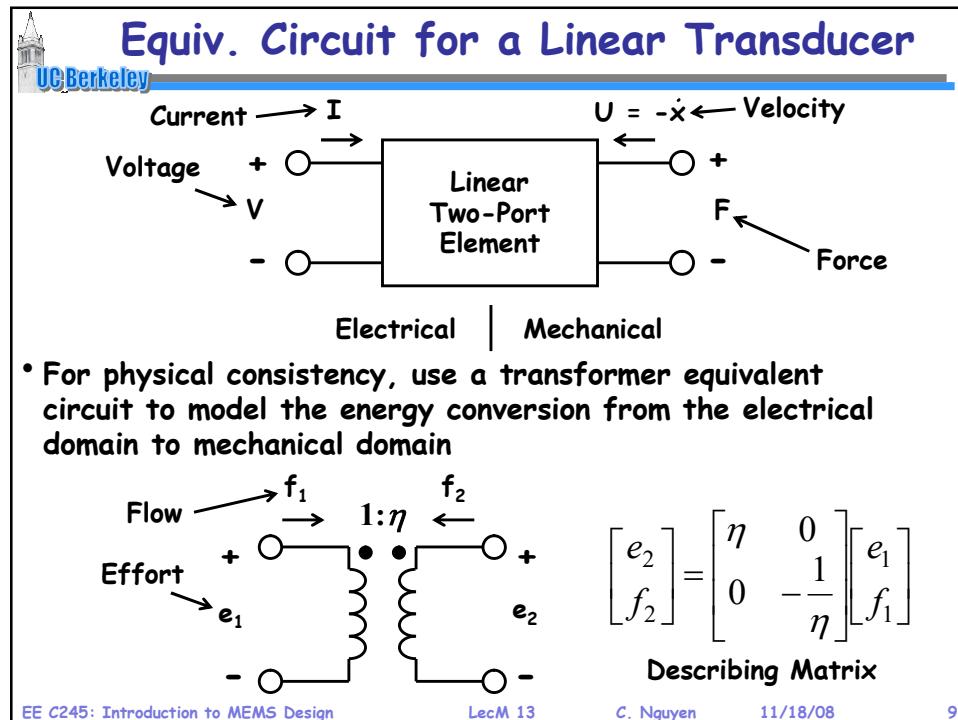


 UC Berkeley

Output Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 11

 UC Berkeley

Output Current Into Ground

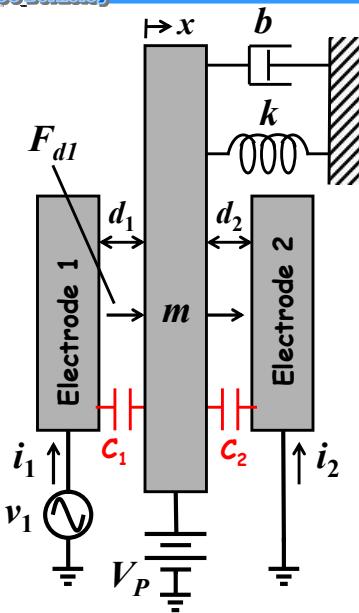

- When the mass moves with time-dependent displacement $x(t)$, the electrode-to-mass capacitors $C_1(x,t)$ and $C_2(x,t)$ vary with time
- This generates an output current:

$$[q = CV] \Rightarrow i = \frac{dq}{dt} = C \frac{\partial V}{\partial t} + V \frac{\partial C}{\partial t}$$

$$i_2(t) = C_2(x,t) \frac{\partial V_2(t)}{\partial t} + V_2(t) \frac{\partial C_2(x,t)}{\partial t}$$

$$[V_2(t) = -V_p] \Rightarrow i_2 = -V_p \frac{\partial C_2}{\partial t} = -V_p \frac{\partial C_2}{\partial x} \frac{\partial x}{\partial t}$$

In phasor form: $I_2(j\omega) = -V_p \frac{\partial C_2}{\partial x} (j\omega X)$

$$\boxed{I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 12

Output Current Into Ground

$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X = -V_p \frac{\partial C_2}{\partial x} U$

90° phase lag (+) $\rightarrow I_2 = (-)$ when $x = (0)$ ✓

- Again, model with a transformer:

Velocity $\rightarrow U = \dot{x}$

Current $\rightarrow I_2$

$f_2 = -\frac{1}{\eta_2} f_1 \rightarrow f_1 = -\eta_2 f_2$

$[f_1 = I_2, f_2: U] \Rightarrow I_2 = -\eta_2 U$

$\therefore \boxed{\eta_2 = |V_p \frac{\partial C_2}{\partial x}|}$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 13

Input Current Expression

Get $I_1(j\omega)$:

$$i_1(t) = C_1(x, t) \frac{dV_1(t)}{dt} + V_1(t) \frac{dC_1(x, t)}{dt}$$

$$[V_1(t) \cdot N_i - V_p] \Rightarrow i_1 = C_1 \frac{dV_1}{dt} + [N_i - V_p] \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$$\therefore I_1(j\omega) = C_1(j\omega V_1) + V_1 \frac{\partial C_1}{\partial x} (j\omega x) - V_p \frac{\partial C_1}{\partial x} (j\omega x)$$

$$= j\omega C_1 V_1 + j\omega V_1 \frac{\partial C_1}{\partial x} x - j\omega V_p \frac{\partial C_1}{\partial x} x$$

$$[V_1 \ll V_p] \Rightarrow I_1(j\omega) = j\omega C_1 V_1 - j\omega V_p \frac{\partial C_1}{\partial x} x$$



Feedthrough Current Motional Current (due to mass motion)

@DC: $x = \frac{F_{d1}}{k} = -\frac{1}{k} V_p \frac{\partial C_1}{\partial x} N_i$

@rerename: $x = \frac{Q F_{d1}}{jk} = -\frac{Q}{jk} V_p \frac{\partial C_1}{\partial x} N_i$

2 90° phase lag

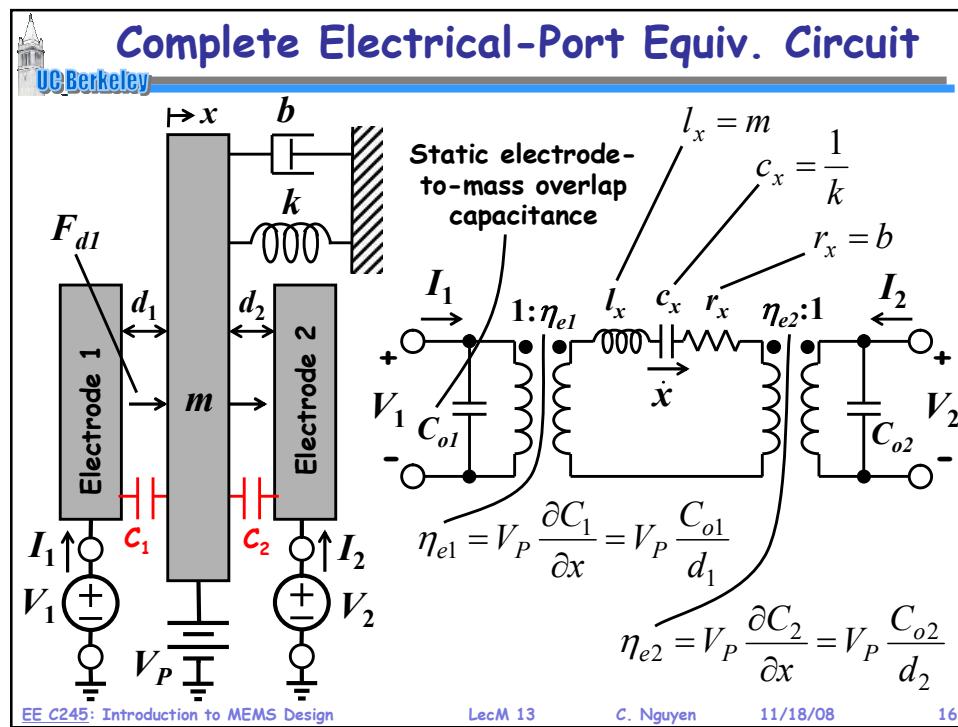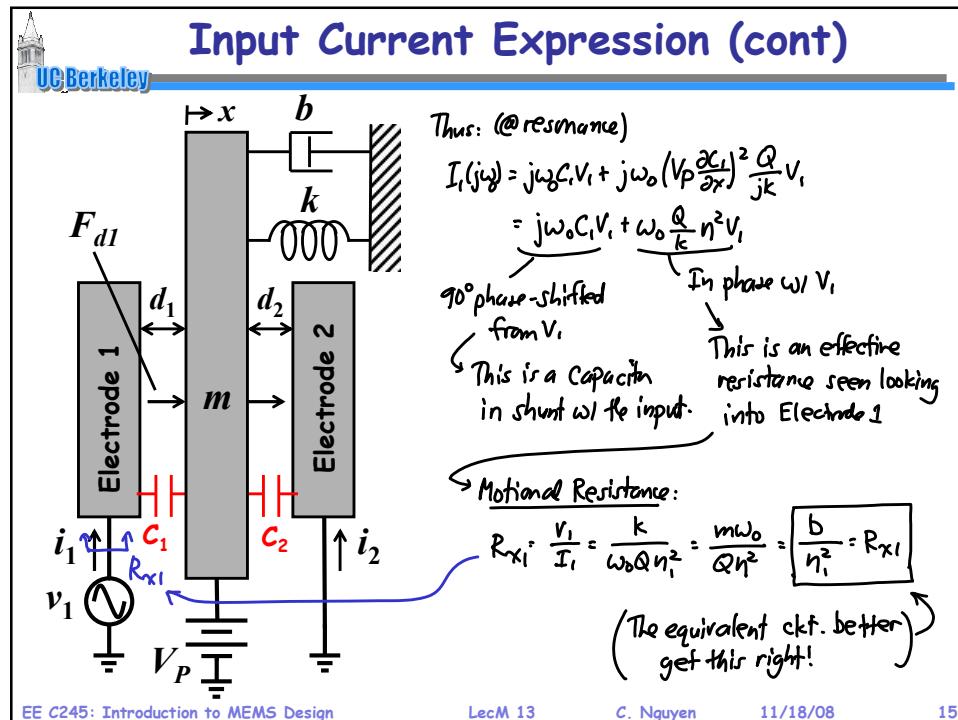EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 14



Input Impedance Into Port 1

• What is the impedance seen looking into port 1 with port 2 shorted to ground?

From our transformer model: $\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} n & 0 \\ 0 & -\frac{1}{n} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix} \Rightarrow e_2 = n e_1 \rightarrow e_1 = \frac{e_2}{n}$
 $f_2 = -\frac{1}{n} f_1 \rightarrow f_1 = -n f_2$

$$\frac{e_1}{f_1} = \frac{e_2}{n f_2} = -\frac{1}{n^2} \frac{e_2}{f_2} \rightarrow \frac{N_i}{i_x} = Z_i = -\frac{1}{n_{e1}^2} \frac{F_2}{f_2} = \frac{1}{n_{e1}^2} Z_x$$

$$Z_i = \frac{1}{n_{e1}^2} \left(j\omega l_x + \frac{1}{j\omega c_x} + r_x \right) = j\omega \underbrace{\left(\frac{l_x}{n_{e1}^2} \right)}_{L_{x1}} + \frac{1}{j\omega (n_{e1}^2 C_x)} + \frac{r_x}{n_{e1}^2} \underbrace{\frac{1}{R_{x1}}} \quad \text{Circuits shown: } \frac{i_x}{N_i} \rightarrow L_{x1}, R_{x1}, C_{x1}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 17

Input Impedance Into Port 2

• What is the impedance seen looking into port 2 with port 1 shorted to ground?

$$\frac{N_i}{i_x} = Z_i = \frac{1}{n_{e2}^2} \left(j\omega l_x + \frac{1}{j\omega c_x} + r_x \right) = j\omega \underbrace{\left(\frac{l_x}{n_{e2}^2} \right)}_{L_{x2}} + \frac{1}{j\omega (n_{e2}^2 C_x)} + \frac{r_x}{n_{e2}^2} \underbrace{\frac{1}{R_{x2}}} \quad \text{Circuits shown: } \frac{i_x}{N_i} \rightarrow L_{x2}, R_{x2}, C_{x2}$$

Note: These are not the same as L_{x1} , C_{x1} , & R_{x1} !

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 18

Port 1 to 2 TransG Across the Circuit

• What is the transconductance from port 1 to port 2 with port 2 shorted to ground?

$$\frac{i_0}{N_i}(j\omega)$$

$$i_0 = \frac{1}{\eta_{e1}} i_1 \rightarrow i_0 = \frac{\eta_{e2}}{\eta_{e1}} i_1 = \frac{\eta_{e2}}{\eta_{e1}} \left(\frac{N_i}{Z_i} \right) = \frac{\eta_{e2}}{\eta_{e1}} N_i \left[\eta_{e1}^2 \frac{1}{j\omega l_x + \frac{1}{j\omega C_{x1}} + r_x} \right]$$

$$\therefore \frac{i_0}{N_i}(j\omega) = \frac{\eta_{e1}\eta_{e2}}{j\omega l_x + \frac{1}{j\omega C_{x1}} + r_x} = \left[j\omega L_{X12} + \frac{1}{j\omega C_{X12}} + R_{X12} \right]^{-1} \begin{cases} L_{X12} = \frac{l_x}{\eta_{e1}\eta_{e2}} \\ C_{X12} = \eta_{e1}\eta_{e2}C_x \\ R_{X12} = \frac{r_x}{\eta_{e1}\eta_{e2}} \end{cases}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 19

Port 1 to 2 v_i -to- i_o Transfer Function

$$\frac{i_0}{N_i}(j\omega) = \frac{\eta_{e1}\eta_{e2}}{j\omega l_x + \frac{1}{j\omega C_x} + r_x} = \left[j\omega L_{X12} + \frac{1}{j\omega C_{X12}} + R_{X12} \right]^{-1} \begin{cases} L_{X12} = \frac{l_x}{\eta_{e1}\eta_{e2}} \\ C_{X12} = \eta_{e1}\eta_{e2}C_x \\ R_{X12} = \frac{r_x}{\eta_{e1}\eta_{e2}} \end{cases}$$

Separate freq. response & magnitude:

$$\frac{i_0}{N_i}(s) = \frac{1}{sL_x + \frac{1}{sC_x} + R_x} = \frac{sC_x}{s^2L_x + sC_x + R_x} = \frac{s(\frac{1}{L_x})}{s^2 + \frac{1}{LC_x} + s(\frac{R_x}{L_x})}$$

$$\left[\frac{1}{LC_x} = \omega_0^2, Q = \frac{\omega_0 L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0}{Q} \right] \Rightarrow \boxed{\frac{i_0}{N_i}(s) = \frac{1}{R_x} \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2} = \frac{1}{R_x} H(s)}$$

$$H(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$$\underline{s=0}: H(0)=0$$

$$\underline{s=j\omega_0}: H(j\omega_0)=1$$

$$\underline{s=\infty}: H(\infty)=0$$

$\left| \frac{i_0}{N_i}(s) \right|$

Gain Term Bandpass Biquad

This will always be the same. Thus, could just work @ resonance & just multiply by $H(s)$.

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 20

