

Lecture 1w: Admin & Overview


Lecture 1: Admin & Overview

- **Announcements:**
- **EE C247B/ME C218: Introduction to MEMS Design**
- **Instructor: Prof. Clark T.-C. Nguyen**
- -----
- **Lecture Topics:**
 - ↳ **Course Website**
 - ↳ **1st Day Handouts**
 - ↳ **Definitions for MEMS**
 - ↳ **MEMS roadmap**
 - ↳ **Benefits of Miniaturization**
- -----
- **Course Website:**
- **<https://inst.eecs.berkeley.edu/~ee247b/sp19/>**
- -----
- **I will record lectures on my computer and post them on the class website in the far right column of the Lecture table**
- **Not a good idea to rely on recorded lectures**
 - ↳ **Sometimes they don't record correctly**
 - ↳ **Most who say they will watch the video later won't due to other obligations**
 - ↳ **Thus, videos will post more than two days after the lecture**
- -----
- **Piazza is generally the best way to ask questions and communicate concerns**
- **You will be added to the Piazza course page**
 - ↳ **The access list will be updated weekly to account for newcomers and drops**

- **How many have taken EE 147/247A?**
- **How many have taken ME 119?**
- **How many know microfabrication basics, i.e., oxidation, diffusion, etc.?**
- **How many already know MEMS fabrication?**
- -----
- **Now, start going through Module 1: Admin & Overview**

What You Should Know

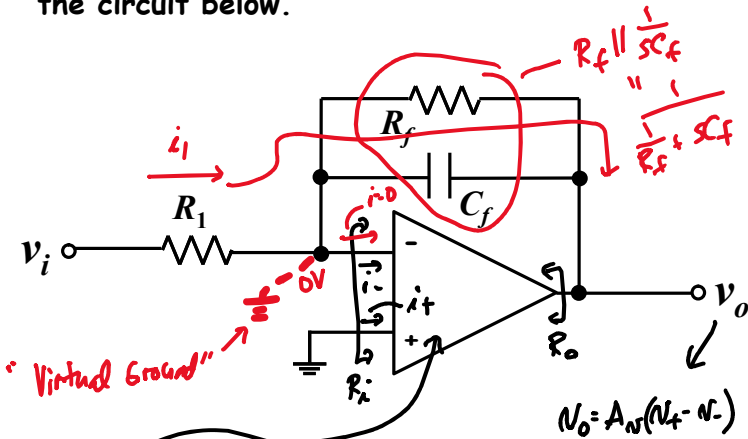- Basic circuit analysis & design using op amps
- Example: Find the transfer function $v_o(s)/v_i(s)$ of the circuit below.



Ideal Op Amp Rules:

- ① $R_i = \infty \rightarrow i_- = i_+ = 0$
 - ② $R_o = 0 \Omega$
 - ③ Gain, $A_v = \infty \rightarrow N_o = \infty (N_+ - N_-) = \text{finite}$
 - ④ $N_+ = N_-$
- Feedback
↓
 $N_+ \cdot N_- = 0 \rightarrow N_+ = N_-$

$$i_1 = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$$

$$N_o = -i_1 (R_f \parallel \frac{1}{sC_f}) = -\frac{v_i}{R_1} \left(\frac{R_f}{1 + sR_f C_f} \right) \rightarrow \omega_0 = \frac{1}{R_f C_f}$$

$$\frac{N_o}{v_i}(s) = -\frac{R_f}{R_1} \frac{1}{1 + sR_f C_f} = -\frac{R_f}{R_1} \frac{1}{1 + \frac{s}{\omega_0}}$$