

UC Berkeley

EE C247B - ME C218 Introduction to MEMS Design Spring 2019

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences
 University of California at Berkeley
 Berkeley, CA 94720

Lecture Module 13: Equivalent Circuits II

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 1

UC Berkeley

Lecture Outline

- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
 - ↳ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↳ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↳ Impedance & Transfer Functions

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 2

UC Berkeley

Input Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 3

UC Berkeley

Electromechanical Analogies

$F(t) = F \cos(\omega t) \rightarrow x(t) = X \cos \omega t$
 Equation of Motion:
 $m_{eq} \ddot{x} + c_{eq} \dot{x} + k_{eq} x = F(t)$
 \Rightarrow using phasor concepts:
 $F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + c_{eq} \dot{x}$
 \Rightarrow by analogy:

$F \rightarrow N$	$m_{eq} \rightarrow l_x$	$c_{eq} \rightarrow r_x$
$\dot{x} \rightarrow i$	$k_{eq} \rightarrow \frac{1}{c_x}$	

Impedance looking in:
 $\frac{N}{i} = j\omega l_x + \frac{1}{j\omega c_x} + r_x$
 $N = j\omega l_x i + \frac{(1/c_x)}{j\omega} i + r_x i$

Parameter Relationships in the Current Analogy

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 4

Bandpass Biquad Transfer Function

UC Berkeley

$$F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + C_{eq} \dot{x}$$

$$\Rightarrow \text{Converting to full phasor form:}$$

$$F = (j\omega)(j\omega x) m_{eq} + \frac{k_{eq}}{j\omega} (j\omega x) + C_{eq} (j\omega x)$$

$$\frac{X}{F}(j\omega) = \frac{1}{k_{eq}} \left[-\omega^2 \frac{m_{eq}}{k_{eq}} + 1 + j \frac{C_{eq}\omega}{k_{eq}} \right]^{-1} = \frac{1}{k_{eq}} \left[-\left(\frac{\omega}{\omega_0}\right)^2 + 1 + j \frac{\omega}{Q\omega_0} \right]^{-1}$$

$$\left[\frac{k_{eq}}{m_{eq}} = \omega_0^2, Q = \frac{m_{eq}\omega_0}{C_{eq}} = \frac{k_{eq}}{\omega_0 C_{eq}} \rightarrow \frac{k_{eq}}{C_{eq}} = Q\omega_0 \right]$$

$$\left| \frac{X}{F}(j\omega) \right|$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 5

Force-to-Velocity Relationship

UC Berkeley

• The relationship between input voltage v_1 and force F_{d1} :

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1$$

• When displacement x is the mechanical output variable:

$$\frac{X(s)}{F_{d1}(s)} = \frac{1}{k} \frac{s^2 \omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$
 (labeled as a 'lowpass biquad')

• When velocity v is the mechanical output variable:

$$\frac{v(s)}{F_{d1}(s)} = \frac{sX(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_0^2 s}{s^2 + (\omega_0/Q)s + \omega_0^2}$$
 (labeled as a 'bandpass biquad')

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 6

Force-to-Velocity Equiv. Ckt.

UC Berkeley

• Combine the previous lumped LCR mechanical equivalent circuit with a circuit modeling the capacitive transducer → circuit model for voltage-to-velocity

Linear Two-Port Element:

$$I_x = m \dot{U} = -\dot{x}$$

$$F_x = b U = -F$$

$$c_x = 1/k$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 7

Equiv. Circuit for a Linear Transducer

UC Berkeley

• A transducer ...

- converts energy from one domain (e.g., electrical) to another (e.g., mechanical)
- has at least two ports
- is not generally linear, but is virtually linear when operated with small signals (i.e., small displacements)

Electrical | Mechanical

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 8

Equiv. Circuit for a Linear Transducer

UC Berkeley

Current $\rightarrow I$

Voltage $+ \rightarrow V$

$-$

Linear Two-Port Element

$U = -\dot{x}$ \leftarrow Velocity

$+ \leftarrow F$ Force

$-$

Electrical | Mechanical

- For physical consistency, use a transformer equivalent circuit to model the energy conversion from the electrical domain to mechanical domain

Flow $\rightarrow f_1$

Effort $+ \rightarrow e_1$

$-$

$1:\eta$

f_2

$+ \leftarrow e_2$

$-$

$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix}$$

Describing Matrix

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 9