

Lecture 22: Equivalent Circuits II

- **Announcements:**
- Project Slide Set #2 due Friday, April 19
- HW#6 online and due Tuesday, 4/23, at 9 a.m.
- Module 13 on Equivalent Circuits II online
- I am traveling, so this is a video lecture
 - ↳ I should be back Thursday morning, 4/18 but we'll see if my plane lands in enough time for me to do the lecture
 - ↳ If not, the lecture will be via video

- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:

↳ **Input Modeling**

- Force-to-Velocity Equiv. Ckt.
- Input Equivalent Ckt.


↳ **Current Modeling**

- Output Current Into Ground
- Input Current
- Complete Electrical-Port Equiv. Ckt.

↳ **Impedance & Transfer Functions**

• **Last Time:**

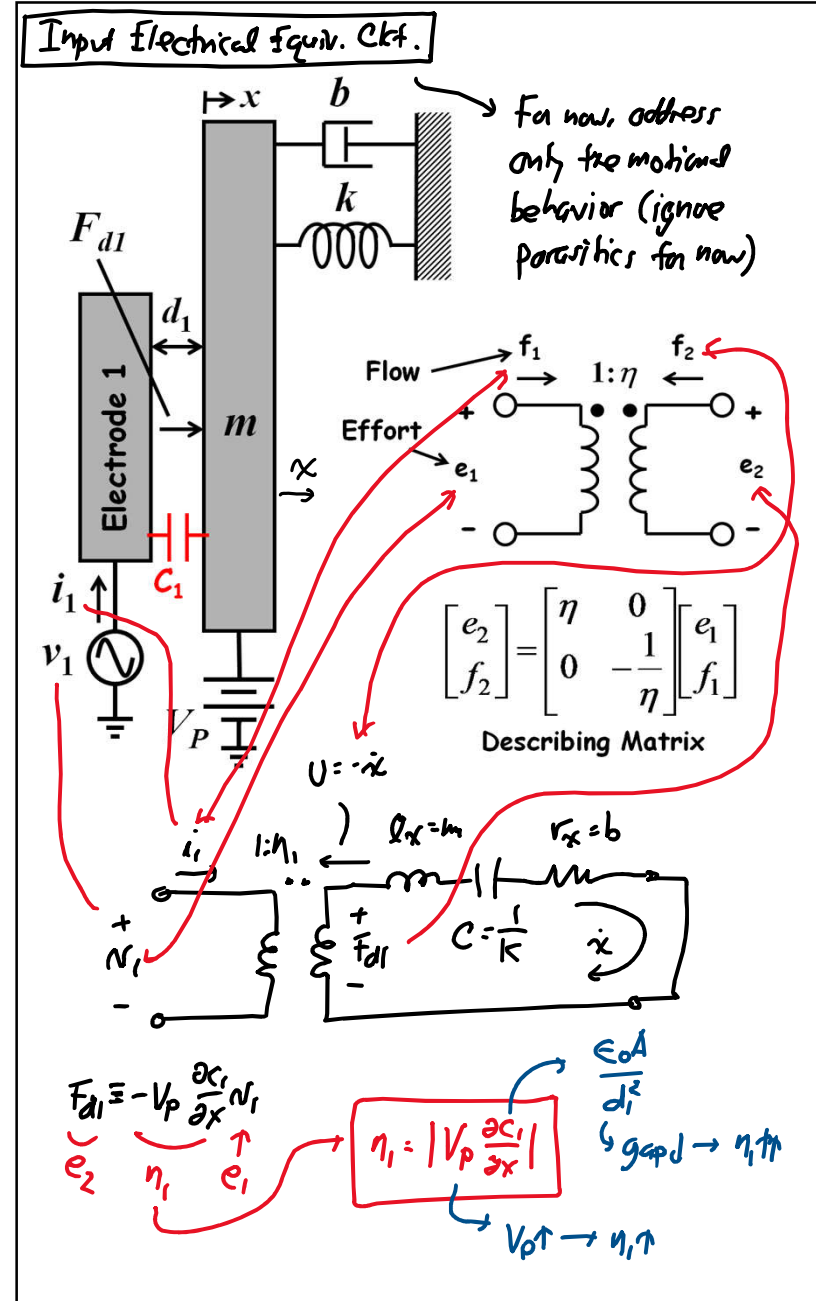- In the process of developing an equivalent circuit for a capacitive-gap transduced mechanical structure
- Now, continue with this ...



Output Current Into Ground

What's this model?

$q = CV$

$i = \frac{dq}{dt} = C \frac{dv}{dt} + V \frac{dC}{dt}$

output current $C_2 = f(t) + \text{time}$

$i_2 = C_2(x,t) \frac{dV_2(t)}{dt} + V_2(t) \frac{dC_2(x,t)}{dt}$

$[V_2(t) = -V_p \neq f(t)] \Rightarrow i_2 = -V_p \frac{dC_2}{dt} = -V_p \frac{\partial C_2}{\partial x} \frac{\partial x}{\partial t}$

In phasor form: $I_2(j\omega) = -V_p \frac{\partial C_2}{\partial x} (j\omega X)$

$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X$
output motional current

$I_2(j\omega) = -j\omega V_p \frac{\partial C_2}{\partial x} X = -V_p \frac{\partial C_2}{\partial x} \dot{x}$
velocity

90° phase lag $\left. \begin{matrix} \uparrow \\ \uparrow \\ \uparrow \end{matrix} \right\} I_2 = (-) \text{ when } X = (+)$

Velocity \dot{x} f_2 $\eta_2:1$ f_1 I_2

$f_2 = -\frac{1}{\eta_2} f_1 \rightarrow f_1 = -\eta_2 f_2$

$[f_1 = I_2, f_2 = \dot{x}] \Rightarrow I_2 = -\eta_2 \dot{x}$

$\therefore \eta_2 = \left| V_p \frac{\partial C_2}{\partial x} \right|$

Flow f_1 f_2 $1:\eta$

Effort e_1 e_2

Describing Matrix $\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix}$

Input Current Expression \Rightarrow then yields complete equivalent input ckt

Get $I_1(j\omega)$:

$$i_1(t) = C_1(x,t) \frac{dv_1(t)}{dt} + v_1(t) \frac{dC_1(x,t)}{dt}$$

$$(v_1(t) = v_1 - v_p) \Rightarrow i_1 = C_1 \frac{dv_1}{dt} + (v_1 - v_p) \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

\uparrow $f(t)$ \leftarrow magnitude of $v_1 = v_1 \cos \omega t$

$$\therefore I_1(j\omega) = \underbrace{j\omega C_1 v_1}_{\text{Feedthrough Current}} + \underbrace{j\omega v_1 \frac{\partial C_1}{\partial x} X}_{\text{Motional Current due to mass motion}} - j\omega v_p \frac{\partial C_1}{\partial x} X \quad *$$

@DC: $x = \frac{F_d1}{k} = -\frac{1}{k} v_p \frac{\partial C_1}{\partial x} n_1$

@ resonance: $x = \frac{Q F_d1}{k} = -\frac{Q}{jk} v_p \frac{\partial C_1}{\partial x} n_1 = X$

ω_0 \uparrow 90° phase lag \leftarrow plug in to *

Thus: (@ resonance)

$$I_1(j\omega) = j\omega_0 C_1 |v_1| + j\omega_0 \left(v_p \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{jk} |v_1|$$



$$= \underbrace{j\omega_0 C_1 |v_1|}_{90^\circ \text{ phase-shifted from } v_1} + \underbrace{\omega_0 \frac{Q^2}{k} n_1^2 |v_1|}_{\text{In phase w/ } v_1!}$$



\downarrow This is a capacitor in shunt w/ input! \uparrow This is an effective resistance @ ω_0 seen looking into the electrode!

Motional Resistance:

$$R_{x1} = \frac{V_1}{I_1} = \frac{k}{\omega_0 Q n_1^2} = \frac{m \omega_0}{Q n_1^2} = \frac{b}{n_1^2} = R_{x1}$$

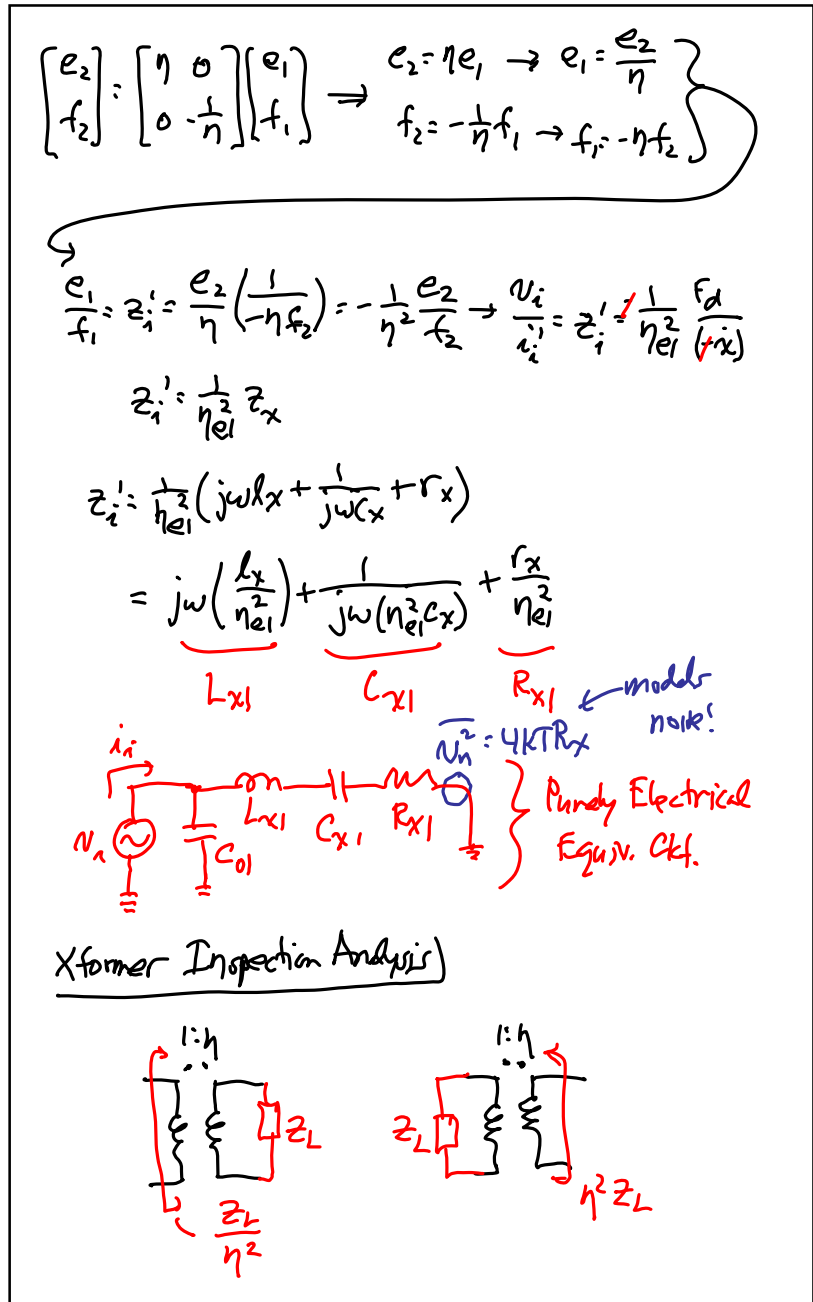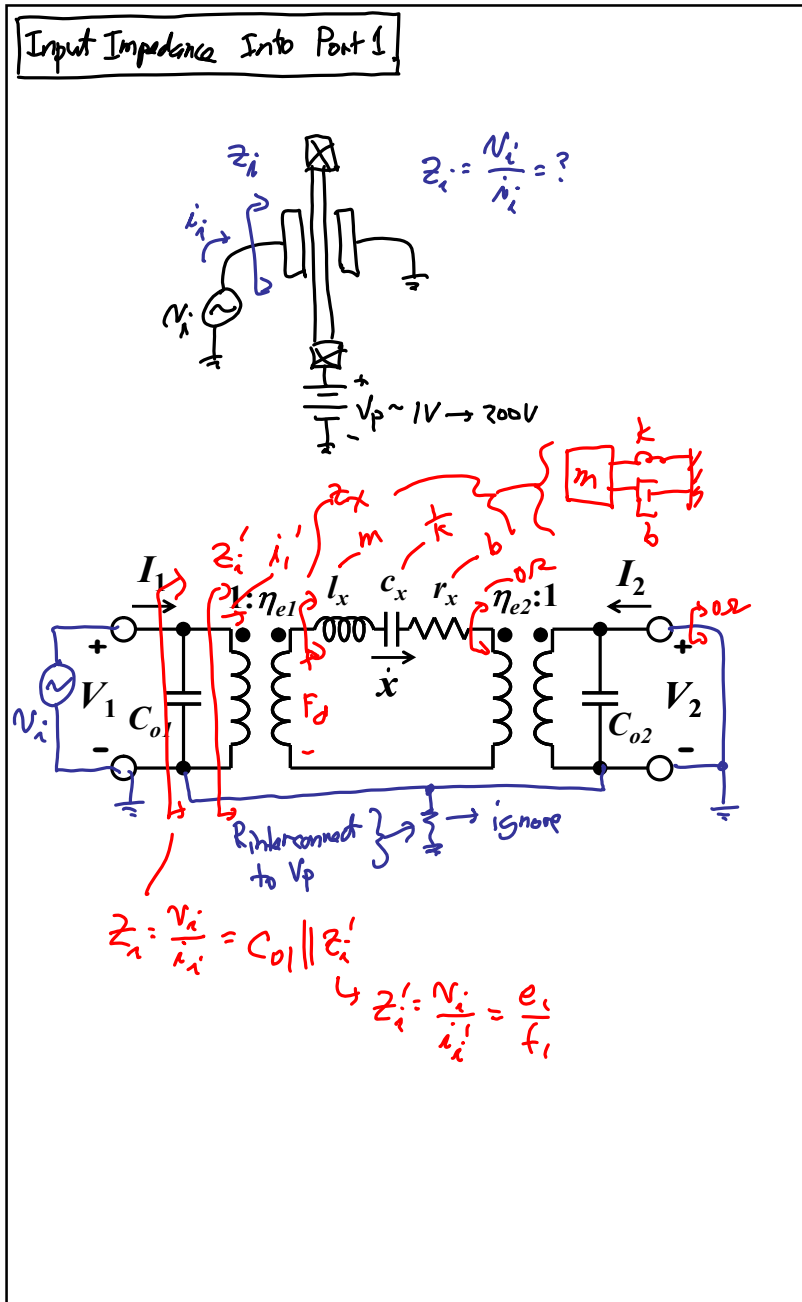The equivalent ckt. better get this right!



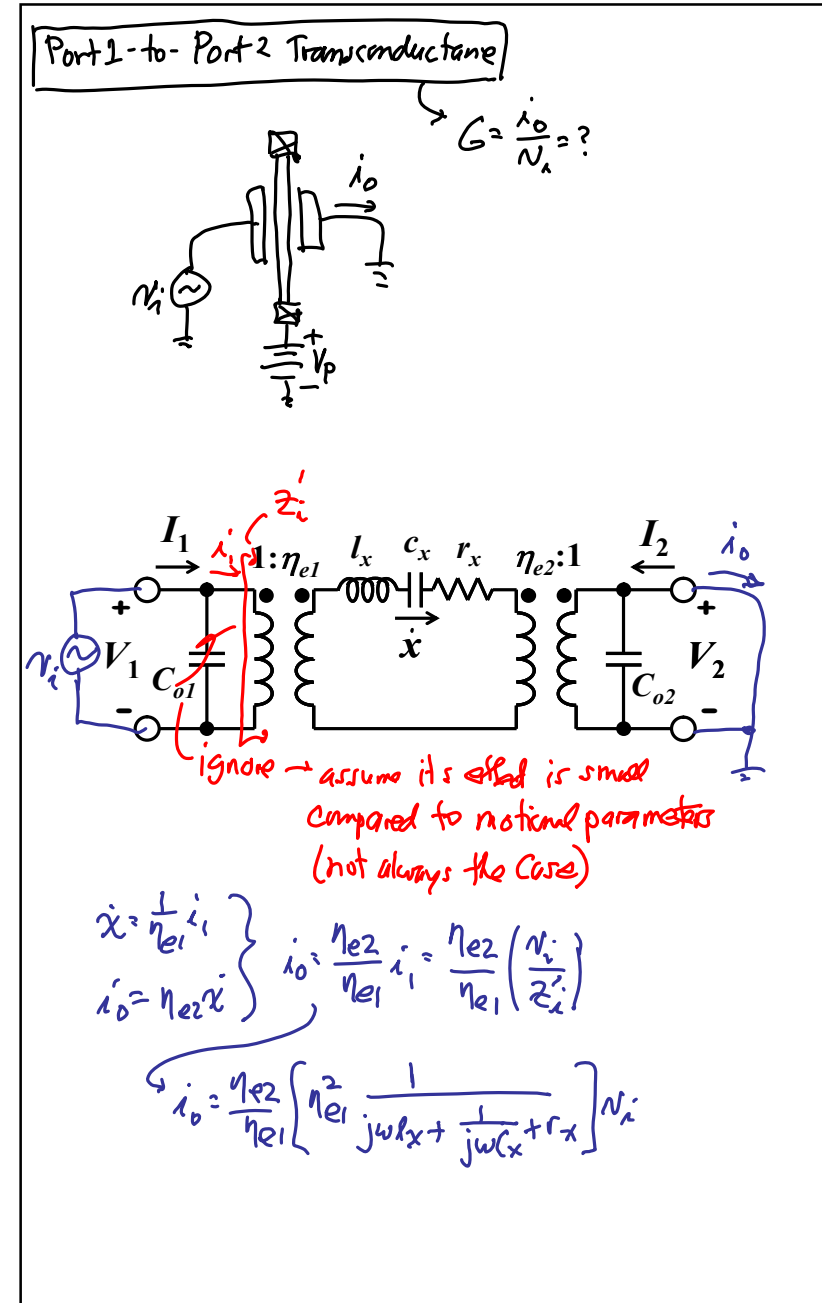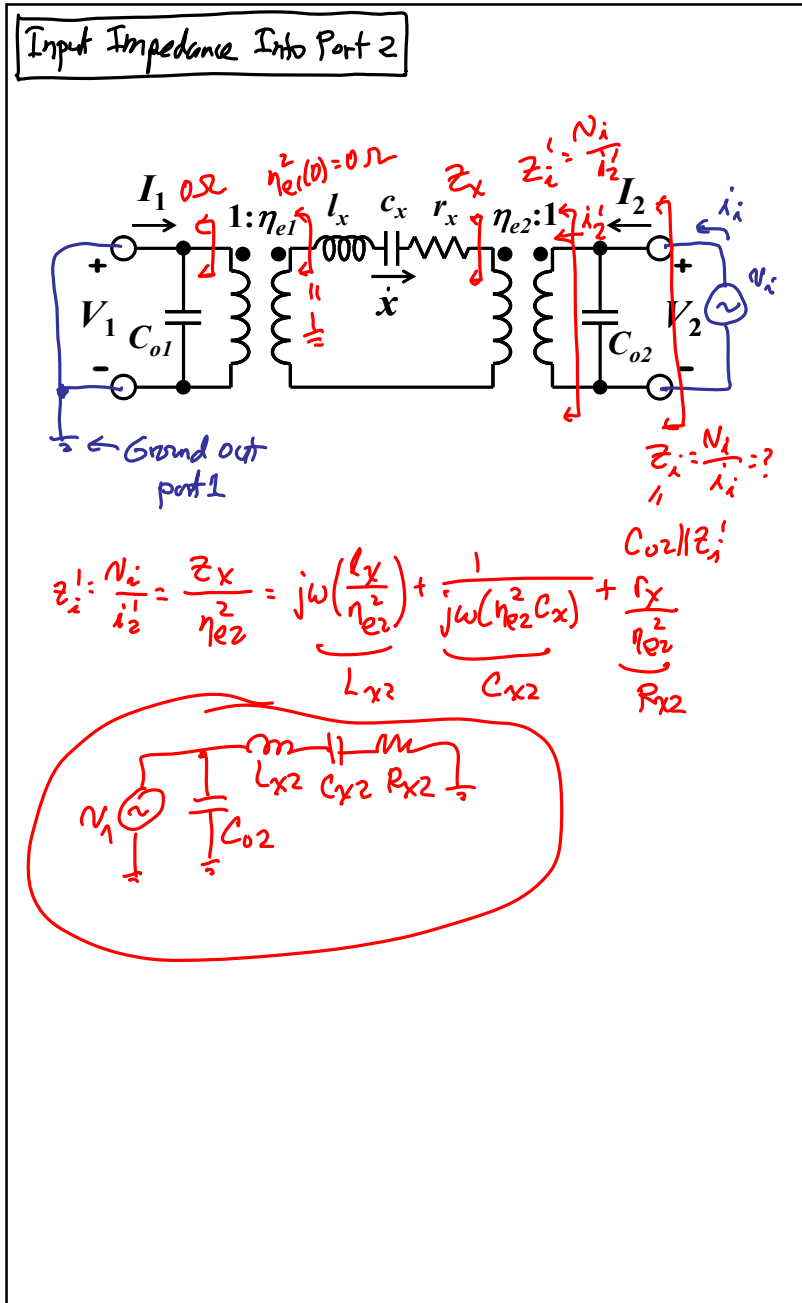

$$\therefore \frac{i_o}{N_i}(j\omega) = \frac{N_e N_{e2}}{j\omega L_x + \frac{1}{j\omega C_x} + R_x}$$

$$\frac{i_o}{N_i}(j\omega) = \left[j\omega L_{x12} + \frac{1}{j\omega C_{x12}} + R_{x12} \right]^{-1}$$

where $L_{x12} = \frac{R_x}{N_e N_{e2}}$, $C_{x12} = N_e N_{e2} C_x$

$$R_{x12} = \frac{R_x}{N_e N_{e2}}$$

\Rightarrow separate into magnitude & freq. response components

$$\frac{i_o}{N_i}(s) = \frac{1}{sL_x + \frac{1}{sC_x} + R_x} = \frac{s(\frac{1}{L_x})}{s^2 + \frac{1}{L_x C_x} + s(\frac{R_x}{L_x})}$$

$\left(\frac{1}{L_x C_x} = \omega_0^2, Q = \frac{\omega_0 L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0}{Q} \right)$

$$\frac{i_o}{N_i}(s) = \frac{1}{R_x} \frac{s(\frac{\omega_0}{Q})}{s^2 + s(\frac{\omega_0}{Q}) + \omega_0^2} = \frac{1}{R_x} \textcircled{H}(s)$$

\uparrow Gain Term \uparrow Frequency Shaping Term \uparrow resonance magnitude

*

$\frac{i_o}{N_i}(s)$ vs ω

$\frac{1}{R_x}$

ω_0

* Bandpass Signal

To analyze mechanical ckt. problems:

- ① Just solve the ckt. @ resonance \rightarrow easy, since L & C cancel
- ② Then multiply the result by $\textcircled{H}(s)$!

- Now, go through slide 21 in Module 13
- Then, start gyroscopes in Module 15