
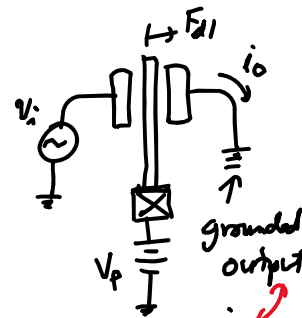
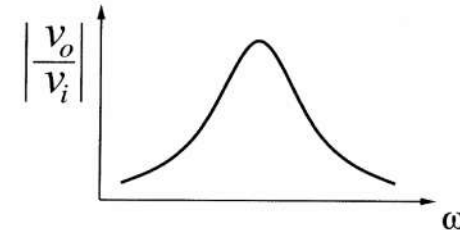


Lecture 23: Gyroscopes & Sensing Circuits I

- Announcements:
- Project Slide Set #2 due Friday, April 19
- HW#6 due Tuesday, 4/23, at 9 a.m.
- Module 14 on Sensing Circuits online
- Module 15 on Gyros, Noise, & MDS online (actually with last lecture)
- -----
- Reading: Senturia, Chpt. 14, Chpt. 16, Chpt. 21
- Lecture Topics:
 - ↳ Gyroscopes
- Reading: Senturia, Chpt. 14
- Lecture Topics:
 - ↳ Detection Circuits
 - Velocity Sensing
 - Position Sensing
- -----
- Last Time:
- Started gyroscopes by going through slides 1-6 in Module 15
- Now, continue with this ...

Velocity-to-Voltage Conversion

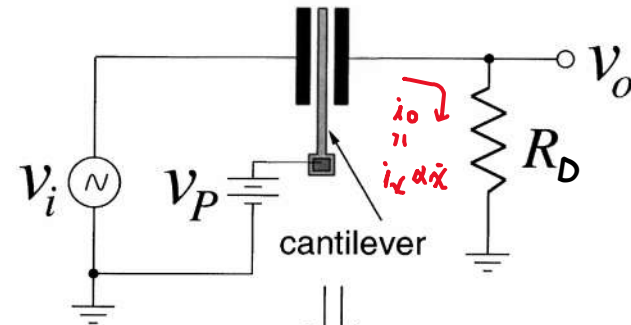


$$\frac{x}{F_{dl}}(s) = \frac{\omega_0 Q}{k} \mathcal{H}(s)$$

$$\left\{ F_{dl} = \eta_{e1} N_i \right\} \quad \frac{1}{R_{x12}}$$

$$\frac{x}{N_i}(s) = \eta_{e1} \frac{C_b Q}{k} \mathcal{H}(s)$$

$$\left[i_0 = \eta_{e2} \dot{x} \right] \Rightarrow \frac{i_0}{N_i}(s) = \eta_{e1} \eta_{e2} \frac{\omega_0 Q}{k} \mathcal{H}(s) \cdot \frac{\eta_{e1} \eta_{e2} Q}{m \omega_0} \mathcal{H}(s)$$

Now, include R_D : (detection resistor)

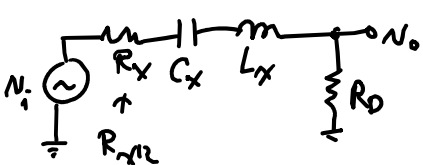

$$\frac{N_o}{N_i}(s) = \frac{R_D}{R_x + \frac{1}{sC_x} + sL_x + R_D} = \dots \text{make} \dots$$

$$= \frac{R_D}{R_x + R_D} \frac{s \left(\frac{R_x + R_D}{L_x} \right)}{s^2 + s \left(\frac{R_x + R_D}{L_x} \right) + \frac{1}{L_x C_x}}$$


Gain Term Freq. Shaping Term

$$\left[Q = \frac{\omega_0 L_x}{R_x} \rightarrow Q' = \frac{\omega_0 L_x}{R_x + R_D} \rightarrow \frac{R_x + R_D}{L_x} = \frac{\omega_0}{Q'} \right]$$

$$\frac{N_o}{N_i}(s) = \frac{R_D}{R_x + R_D} \frac{s(\omega_0/Q')}{s^2 + s(\omega_0/Q') + \omega_0^2}$$

$$\frac{N_o}{N_i}(s) = \frac{R_D}{R_x + R_D} \mathcal{H}(s, Q')$$

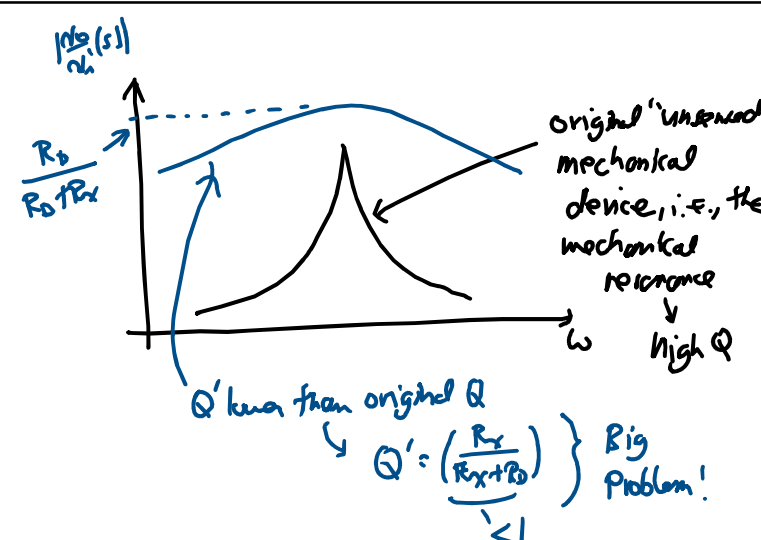
$\hookrightarrow Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$



original "unloaded" mechanical device, i.e., the mechanical resonance
high Q

Q' lower than original Q
 $Q' = \left(\frac{R_x}{R_x + R_D} \right) < 1$ } Big Problem!

Analysis @ Resonance:


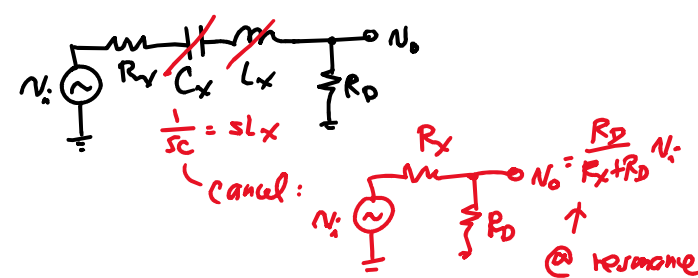


cancel: @ resonance

convert to general freq. by $\times \mathcal{H}(s, Q')$

$$\frac{N_o}{N_i}(s) = \frac{R_D}{R_x + R_D} \mathcal{H}(s, Q'), \text{ where } Q' = Q \left(\frac{R_x}{R_x + R_D} \right)$$

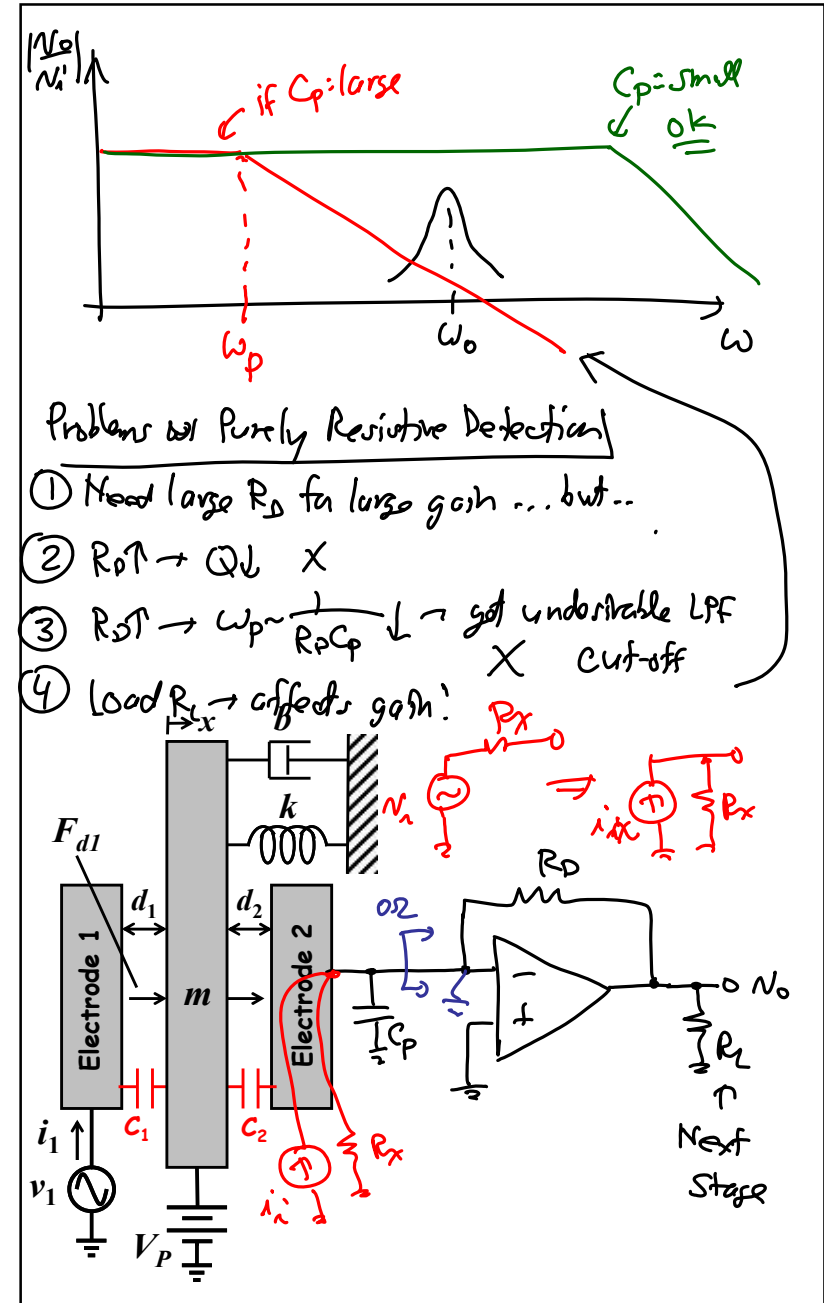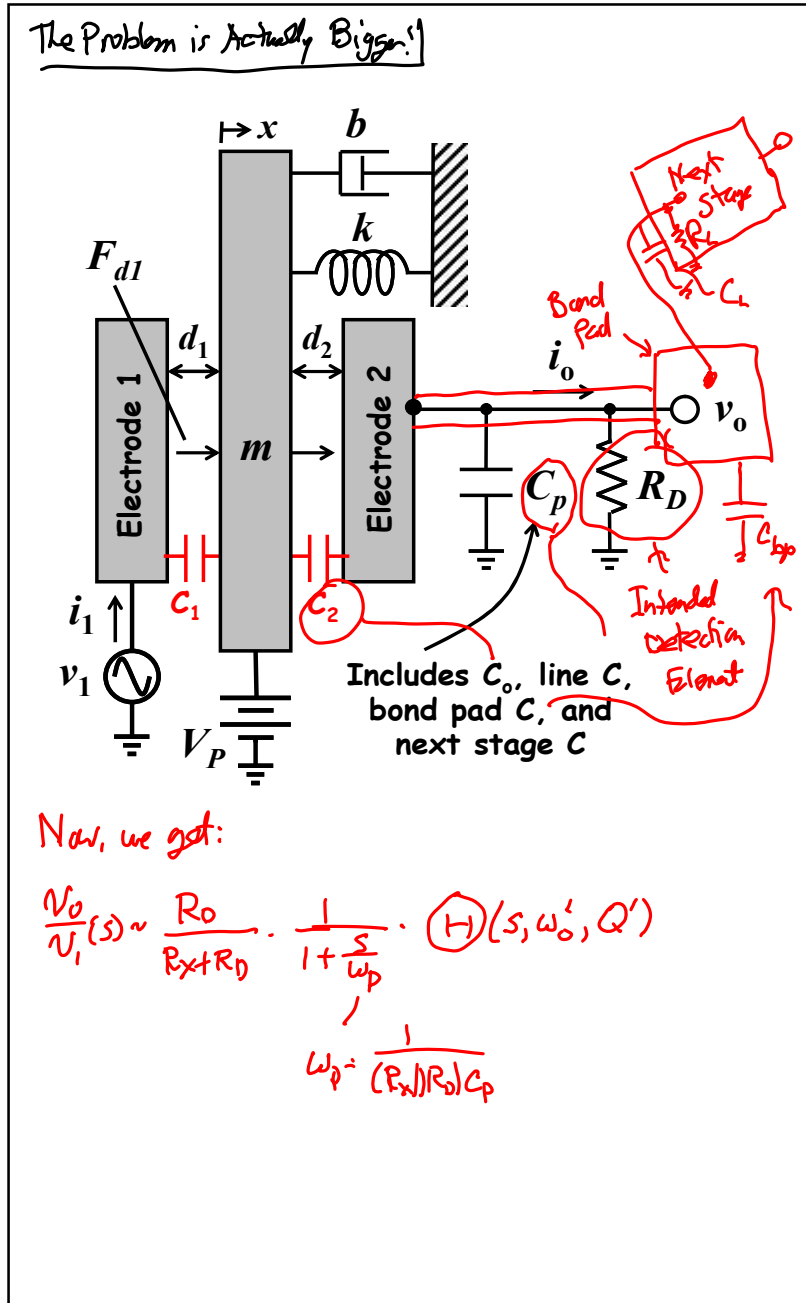(a fast way to solve R_D -loaded LCR problems)



Ideal Op Amp Laws:

- ① $R_i \rightarrow \infty \rightarrow i = 0, i_f = 0$
- ② $R_o = 0$
- ③ Gain $A_o = \infty$

neg. FB $\rightarrow v_o = \infty(v_+ - v_-) = \text{finite}$
 $0 \rightarrow v_+ = v_-$

can't say "mir!"

~~Blows Up! (+) FB~~

neg. FB ✓ that's good

"virtual ground"
 since there are no voltage variations across C_p !

no Q degradation

$v_o = -i_i R_D$

$\frac{v_o}{i_i} = -R_D$ @ resonance

$\frac{v_o(s)}{i_i(s)} = -\frac{R_D}{R_x} (1) (s)$

$(v_+ = i_i R_x)$