

UC Berkeley

Noise Sources

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 12

UC Berkeley

Thermal Noise

- **Thermal Noise in Electronics:** (Johnson noise, Nyquist noise)
 - ↳ Produced as a result of the thermally excited random motion of free e-'s in a conducting medium
 - ↳ Path of e-'s randomly oriented due to collisions
- **Thermal Noise in Mechanics:** (Brownian motion noise)
 - ↳ Thermal noise is associated with all dissipative processes that couple to the thermal domain
 - ↳ Any damping generates thermal noise, including gas damping, internal losses, etc.
- **Properties:**
 - ↳ Thermal noise is white (i.e., constant w/ frequency)
 - ↳ Proportional to temperature
 - ↳ Not associated with current
 - ↳ Present in any real physical resistor

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 13

UC Berkeley

Circuit Representation of Thermal Noise

- Thermal Noise can be shown to be represented by a series voltage generator $\overline{v_R^2}$ or a shunt current generator $\overline{i_R^2}$

actual

noiseless

noiseless

Note: These are one-sided mean-square spectral densities! To make them 2-sided, must divide by 2.

$$\frac{\overline{i_R^2}}{\Delta f} = \frac{4kT}{R}$$

$$\frac{\overline{v_R^2}}{\Delta f} = 4kTR$$

where $4kT = 1.66 \times 10^{-20} V \cdot C$ and where these are spectral densities.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 14

UC Berkeley

Noise in Capacitors and Inductors?

- Resistors generate thermal noise
- Capacitors and inductors are noiseless → why?

Can oscillate forever

- Now, add a resistor:

Decays to zero

But this violates the laws of thermodynamics, which require that things be in constant motion at finite temperature

Need to add a forcing function, like a noise voltage $\overline{v_R^2}$ to keep the motion going → and this noise source is associated with R

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 15

Why 4kTR?

UC Berkeley

- Why is $\overline{v_r^2} = 4kTR\Delta f$ (a heuristic argument)
- The Equipartition Theorem of Statistical Thermodynamics says that there is a mean energy $(1/2)kT$ associated w/ each degree of freedom in a given system
- An electronic circuit possesses two degrees of freedom:
 - Current, i , and voltage, v
 - Thus, we can write:

$$\frac{1}{2}Li^2 = \frac{1}{2}k_B T, \quad \frac{1}{2}Cv^2 = \frac{1}{2}k_B T$$
- Similar expressions can be written for mechanical systems
 - For example: for displacement, x

$$\frac{1}{2}kx^2 = \frac{1}{2}k_B T$$

Spring constant $\frac{1}{2}kx^2 = \frac{1}{2}k_B T$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 16

Shot Noise

UC Berkeley

- Associated with direct current flow in diodes and bipolar junction transistors
- Arises from the random nature by which e^- 's and h^+ 's surmount the potential barrier at a pn junction
- The DC current in a forward-biased diode is composed of h^+ 's from the p-region and e^- 's from the n-region that have sufficient energy to overcome the potential barrier at the junction
 - noise process should be proportional to DC current
- Attributes:
 - Related to DC current over a barrier
 - Independent of temperature
 - White (i.e., const. w/ frequency)
 - Noise power $\sim I_D$ & bandwidth

$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D$$

Charge on an e^- ($=1.6 \times 10^{-19}C$)
 DC Current

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 19

Flicker (1/f) Noise

UC Berkeley

- In general, associated w/ random trapping & release of carriers from "slow" states
- Time constant associated with this process gives rise to a noise signal w/ energy concentrated at low frequencies
- Often, get a mean-square noise spectral density that looks like this:

$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D + K \left(\frac{I_D^a}{f^b} \right)$$





I_D = DC current
 K = const. for a particular device
 $a = 0.5 \rightarrow 2$
 $b \sim 1$

1/f Noise Corner Frequency

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 20

Back to Determining Sensor Resolution

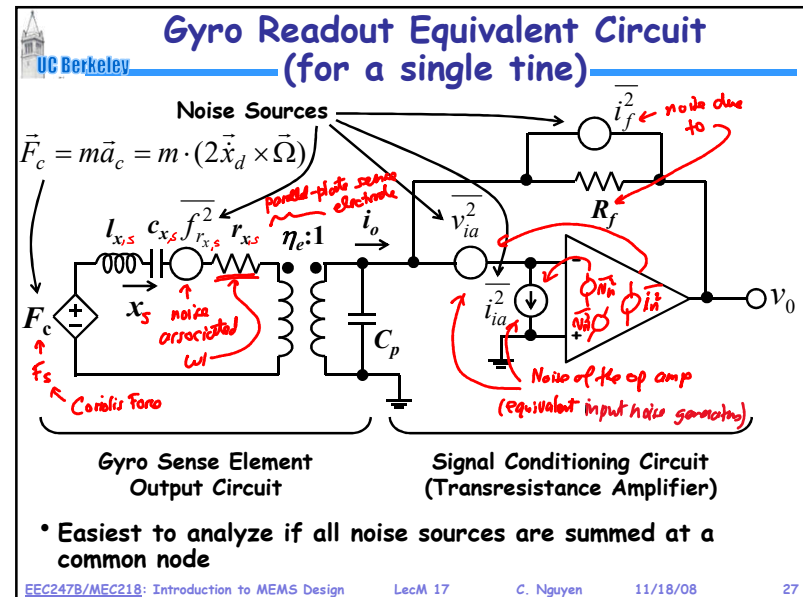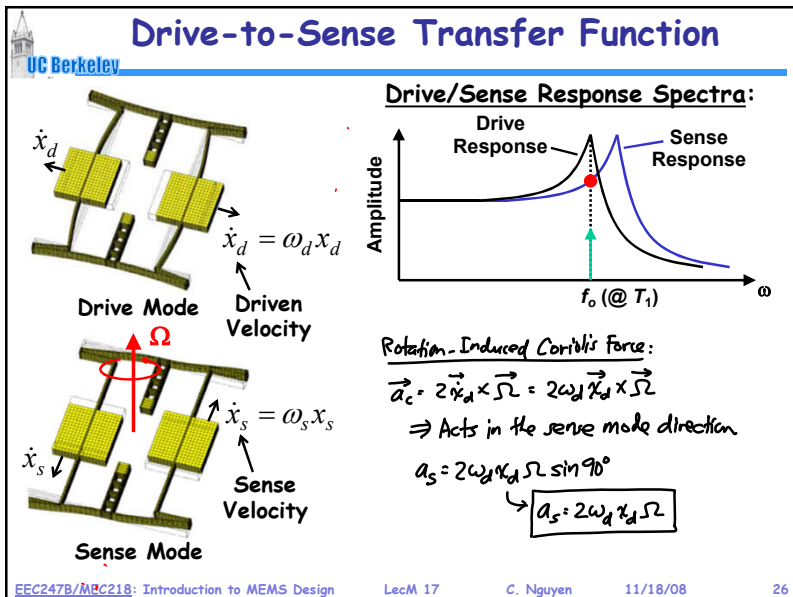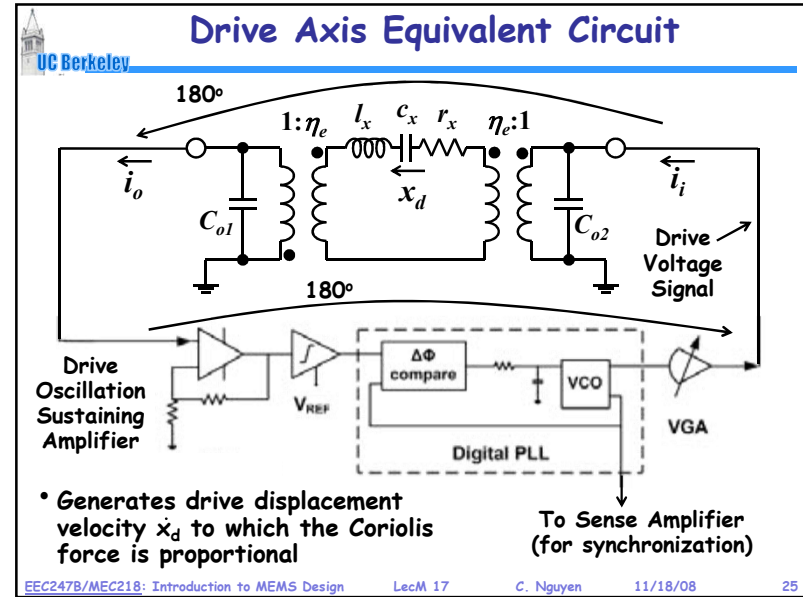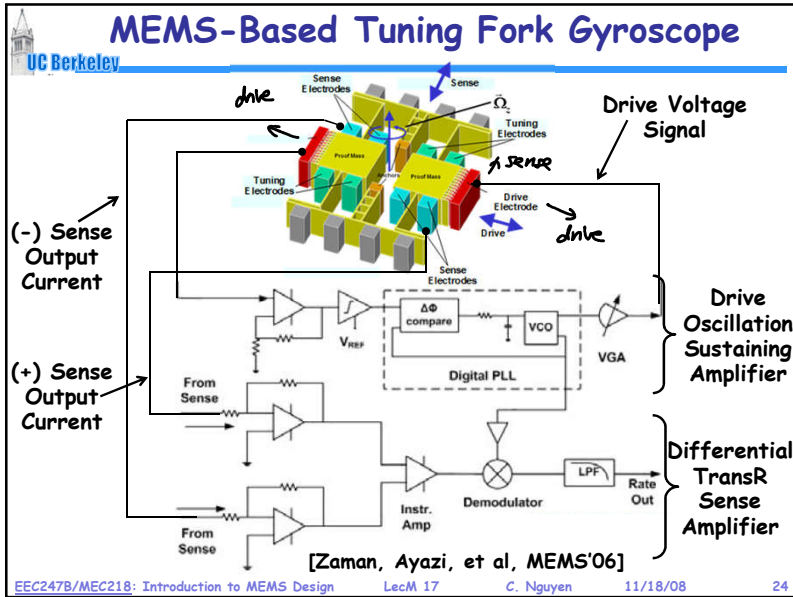EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 23



Minimum Detectable Signal (MDS)

UC Berkeley

- Minimum Detectable Signal (MDS): Input signal level when the signal-to-noise ratio (SNR) is equal to unity

- The sensor scale factor is governed by the sensor type
- The effect of noise is best determined via analysis of the equivalent circuit for the system

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 28

Move Noise Sources to a Common Point

UC Berkeley

- Move noise sources so that all sum at the input to the amplifier circuit (i.e., at the output of the sense element)
- Then, can compare the output of the sensed signal directly to the noise at this node to get the MDS

EE247B/ME218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 29