


EE C247B - ME C218
Introduction to MEMS Design
Spring 2019

Prof. Clark T.-C. Nguyen

Dept. of Electrical Engineering & Computer Sciences
University of California at Berkeley
Berkeley, CA 94720

Lecture Module 13: Equivalent Circuits II

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 1



Lecture Outline

- Reading: Senturia, Chpt. 6, Chpt. 14
- Lecture Topics:
 - ↗ Input Modeling
 - Force-to-Velocity Equiv. Ckt.
 - Input Equivalent Ckt.
 - ↗ Current Modeling
 - Output Current Into Ground
 - Input Current
 - Complete Electrical-Port Equiv. Ckt.
 - ↗ Impedance & Transfer Functions

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 2

UC Berkeley

Input Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 3

UC Berkeley

Electromechanical Analogies

$F(t) = F \cos(\omega t) \rightarrow x(t) = X \cos \omega t$
Equation of Motion:
 $m_{eq} \ddot{x} + c_{eq} \dot{x} + k_{eq} x = F(t)$
 \Rightarrow using phasor concepts:
 $F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + c_{eq} \dot{x}$
 \Rightarrow by analogy:

$F \rightarrow N$	$m_{eq} \rightarrow l_x$	$c_{eq} \rightarrow r_x$
$\dot{x} \rightarrow i$	$k_{eq} \rightarrow \frac{1}{c_x}$	

 [Parameter Relationships in the Current Analogy]

$N(t) = V \cos \omega t \rightarrow i(t) = I \cos \omega t$
Impedance looking in:
 $\frac{N}{i} = j\omega l_x + \frac{1}{j\omega c_x} + r_x$
 $N = j\omega l_x i + \frac{(1/c_x)}{j\omega} i + r_x i$

current i charge q
 $i = \dot{q}$

$N \leftarrow$ voltage

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 4

Bandpass Biquad Transfer Function

UC Berkeley

$F = j\omega m_{eq} \dot{x} + \frac{k_{eq}}{j\omega} x + c_{eq} \dot{x}$
 \Rightarrow Converting to full phasor form:
 $F = (j\omega)(j\omega x) m_{eq} + \frac{k_{eq}}{j\omega} (j\omega x) + c_{eq} (j\omega x)$

$$\frac{X}{F}(j\omega) = \frac{1}{k_{eq}} \left[-\omega^2 \frac{m_{eq}}{k_{eq}} + 1 + j \frac{c_{eq}\omega}{k_{eq}} \right]^{-1} = \frac{1}{k_{eq}} \left[-\left(\frac{\omega}{\omega_0}\right)^2 + 1 + j \frac{\omega}{Q\omega_0} \right]^{-1}$$

$$\left[\frac{k_{eq}}{m_{eq}} = \omega_0^2, Q = \frac{m_{eq}\omega_0}{c_{eq}} = \frac{k_{eq}}{\omega_0 c_{eq}} \rightarrow \frac{k_{eq}}{c_{eq}} = Q\omega_0 \right]$$

$$\frac{X}{F}(j\omega) = \frac{k_{eq}^{-1}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j \frac{\omega}{Q\omega_0}}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 5

Force-to-Velocity Relationship

UC Berkeley

- The relationship between input voltage v_1 and force F_{d1} :

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1$$
- When displacement x is the mechanical output variable:

$$\frac{X(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$
- When velocity v is the mechanical output variable:

$$\frac{v(s)}{F_{d1}(s)} = \frac{sX(s)}{F_{d1}(s)} = \frac{1}{k} \frac{\omega_0^2 s}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 6

Force-to-Velocity Equiv. Ckt.

UC Berkeley

• Combine the previous lumped LCR mechanical equivalent circuit with a circuit modeling the capacitive transducer → circuit model for voltage-to-velocity

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 7

Equiv. Circuit for a Linear Transducer

UC Berkeley

- A transducer ...
 - ↔ converts energy from one domain (e.g., electrical) to another (e.g., mechanical)
 - ↔ has at least two ports
 - ↔ is not generally linear, but is virtually linear when operated with small signals (i.e., small displacements)

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 8

Equiv. Circuit for a Linear Transducer

UC Berkeley

Current $\rightarrow I$ Velocity $U = -\dot{x} \leftarrow$

Voltage $\rightarrow V$ Force $\leftarrow F$

Linear Two-Port Element

Electrical | Mechanical

- For physical consistency, use a transformer equivalent circuit to model the energy conversion from the electrical domain to mechanical domain

Flow $\rightarrow f_1$ Effort $\rightarrow e_1$

Flow $\leftarrow f_2$ Effort $\rightarrow e_2$

1: η

$$\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix}$$

Describing Matrix

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 9

Electromechanical Equivalent Circuit

UC Berkeley

F_{d1} x b k

Electrode 1 d_1 m V_P C_1

i_1 v_1

Current $\rightarrow I_1$ Velocity $U = -\dot{x} \quad I_x = m$

Voltage $\rightarrow V_1$ Force $\leftarrow F_{d1}$

1: η_1 $r_x = b$ $c_x = 1/k$

Electrical | Mechanical

- $e_2 = F_{d1}$, $e_1 = v_1$, just need η_1 :
- From the matrix: $e_2 = \eta_1 e_1$

$$F_{d1} \approx -V_P \frac{\partial C_1}{\partial x} v_1 \rightarrow \eta_1 = \left| V_P \frac{\partial C_1}{\partial x} \right|$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 10

UC Berkeley

Output Modeling

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 11

UC Berkeley

Output Current Into Ground

- When the mass moves with time-dependent displacement $x(t)$, the electrode-to-mass capacitors $C_1(x,t)$ and $C_2(x,t)$ vary with time
- This generates an output current:

$$[q = CV] \Rightarrow i = \frac{dq}{dt} = C \frac{\partial V}{\partial t} + V \frac{\partial C}{\partial t}$$

$$i_2(t) = C_2(x,t) \frac{dV_2(t)}{dt} + V_2(t) \frac{dC_2(x,t)}{dt}$$

$$[V_2(t) = -V_P] \Rightarrow i_2 = -V_P \frac{dC_2}{dt} = -V_P \frac{\partial C_2}{\partial x} \frac{\partial x}{\partial t}$$

In phasor form: $I_2(j\omega) = -V_P \frac{\partial C_2}{\partial x} (j\omega X)$

$$I_2(j\omega) = -j\omega V_P \frac{\partial C_2}{\partial x} X$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 12

Output Current Into Ground

$I_2(j\omega) = -j\omega V_P \frac{\partial C_2}{\partial x} X = -V_P \frac{\partial C}{\partial x} U$
 90° phase lag $\begin{matrix} \uparrow \\ (+) \end{matrix} \begin{matrix} \uparrow \\ (+) \end{matrix} \rightarrow I_2 = (-) \text{ when } x = (+)$ ✓

- Again, model with a transformer:

Velocity $\rightarrow U = \dot{x}$ Current I_2

$f_2 = -\frac{1}{\eta_2} f_1 \rightarrow f_1 = -\eta_2 f_2$
 $[f_1 = I_2, f_2 = U] \Rightarrow I_2 = -\eta_2 U$
 $\therefore \eta_2 = \left| V_P \frac{\partial C}{\partial x} \right|$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 13

Input Current Expression

Get $I_1(j\omega)$:

$$i_1(t) = C_1(x,t) \frac{dv_1(t)}{dt} + v_1(t) \frac{dC_1(x,t)}{dt}$$

$$[v_1(t) \cdot N_1 - V_P] \Rightarrow i_1 = C_1 \frac{dv_1}{dt} + [N_1 - V_P] \frac{\partial C_1}{\partial x} \frac{\partial x}{\partial t}$$

$$\therefore I_1(j\omega) = C_1(j\omega v_1) + v_1 \frac{\partial C_1}{\partial x} (j\omega x) - V_P \frac{\partial C_1}{\partial x} (j\omega x)$$

$$= j\omega C_1 v_1 + j\omega v_1 \frac{\partial C_1}{\partial x} X - j\omega V_P \frac{\partial C_1}{\partial x} X$$

$[v_1 \ll V_P] \Rightarrow I_1(j\omega) = \underbrace{j\omega C_1 v_1}_{\text{Feed-through Current}} - \underbrace{j\omega V_P \frac{\partial C_1}{\partial x} X}_{\text{Motional Current (due to mass motion)}}$

@ DC: $x = \frac{F_{dl}}{k} = -\frac{1}{k} V_P \left(\frac{\partial C_1}{\partial x} \right) v_1$
 @ resonance: $x = \frac{Q F_{dl}}{jk} = -\frac{Q}{jk} V_P \frac{\partial C_1}{\partial x} v_1$
 $\hookrightarrow 90^\circ$ phase lag

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 14

Input Current Expression (cont)

UC Berkeley

Thus: (@resname)

$$I_1(j\omega) = j\omega C_1 V_1 + j\omega_0 \left(V_P \frac{\partial C_1}{\partial x} \right)^2 \frac{Q}{jk} V_1$$

$$= j\omega_0 C_1 V_1 + \omega_0 \frac{Q}{k} \eta^2 V_1$$

90° phase-shifted from V_1 → This is a Capacitor in shunt w/ the input.
 In phase w/ V_1 → This is an effective resistance seen looking into Electrode 1

Motional Resistance:

$$R_{xi} \frac{V_1}{I_1} = \frac{k}{\omega_0 Q \eta^2} = \frac{m \omega_0}{Q \eta^2} = \frac{b}{\eta^2} = R_{xi}$$

(The equivalent ckt. better get this right!)

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 15

Complete Electrical-Port Equiv. Circuit

UC Berkeley

Static electrode-to-mass overlap capacitance

$l_x = m$
 $c_x = \frac{1}{k}$
 $r_x = b$

$\eta_{e1} = V_P \frac{\partial C_1}{\partial x} = V_P \frac{C_{o1}}{d_1}$
 $\eta_{e2} = V_P \frac{\partial C_2}{\partial x} = V_P \frac{C_{o2}}{d_2}$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 16

Input Impedance Into Port 1

• What is the impedance seen looking into port 1 with port 2 shorted to ground?

From our transformer model: $\begin{bmatrix} e_2 \\ f_2 \end{bmatrix} = \begin{bmatrix} \eta & 0 \\ 0 & -\frac{1}{\eta} \end{bmatrix} \begin{bmatrix} e_1 \\ f_1 \end{bmatrix} \Rightarrow e_2 = \eta e_1 \rightarrow e_1 = \frac{e_2}{\eta}$
 $f_2 = -\frac{1}{\eta} f_1 \rightarrow f_1 = -\eta f_2$

$\frac{e_1}{f_1} = \frac{e_2}{\eta} \left(\frac{1}{-\eta f_2} \right) = -\frac{1}{\eta^2} \frac{e_2}{f_2} \rightarrow \frac{V_1}{i_1} = z_i = -\frac{1}{\eta_{e1}^2} \frac{F_2}{F_2} = \frac{1}{\eta_{e1}^2} z_x$

$z_i = \frac{1}{\eta_{e1}^2} \left(j\omega L_x + \frac{1}{j\omega C_x} + r_x \right) = j\omega \left(\frac{L_x}{\eta_{e1}^2} \right) + \frac{1}{j\omega \left(\eta_{e1}^2 C_x \right)} + \frac{r_x}{\eta_{e1}^2}$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 17

Input Impedance Into Port 2

• What is the impedance seen looking into port 2 with port 1 shorted to ground?

$\frac{V_2}{i_2} = z_i = \frac{1}{\eta_{e2}^2} \left(j\omega L_x + \frac{1}{j\omega C_x} + r_x \right) = j\omega \left(\frac{L_x}{\eta_{e2}^2} \right) + \frac{1}{j\omega \left(\eta_{e2}^2 C_x \right)} + \frac{r_x}{\eta_{e2}^2}$

Note: These are not the same as L_{x1} , C_{x1} , & R_{x1} !

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 18

Port 1 to 2 TransG Across the Circuit

• What is the transconductance from port 1 to port 2 with port 2 shorted to ground? $\frac{i_o}{N_i}(j\omega)$

$$\dot{x} = \frac{1}{\eta_{e1}} i_i$$

$$i_o = \eta_{e2} \dot{x} \rightarrow i_o = \frac{\eta_{e2}}{\eta_{e1}} i_i = \frac{\eta_{e2}}{\eta_{e1}} \left(\frac{N_i}{Z_i} \right) = \frac{\eta_{e2}}{\eta_{e1}} N_i \left[\eta_{e1}^2 \frac{1}{j\omega L_x + \frac{1}{j\omega C_x} + r_x} \right]$$

$$\therefore \frac{i_o}{N_i}(j\omega) = \frac{\eta_{e1}\eta_{e2}}{j\omega L_x + \frac{1}{j\omega C_x} + r_x} = \left[j\omega L_{x12} + \frac{1}{j\omega C_{x12}} + R_{x12} \right]^{-1} \begin{cases} L_{x12} = \frac{L_x}{\eta_{e1}\eta_{e2}} \\ C_{x12} = \eta_{e1}\eta_{e2}C_x \\ R_{x12} = \frac{r_x}{\eta_{e1}\eta_{e2}} \end{cases}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 19

Port 1 to 2 v_i -to- i_o Transfer Function

$$\frac{i_o}{N_i}(j\omega) = \frac{\eta_{e1}\eta_{e2}}{j\omega L_x + \frac{1}{j\omega C_x} + r_x} = \left[j\omega L_{x12} + \frac{1}{j\omega C_{x12}} + R_{x12} \right]^{-1} \begin{cases} L_{x12} = \frac{L_x}{\eta_{e1}\eta_{e2}} \\ C_{x12} = \eta_{e1}\eta_{e2}C_x \\ R_{x12} = \frac{r_x}{\eta_{e1}\eta_{e2}} \end{cases}$$


Separate freq. response & magnitude:

$$\frac{i_o}{N_i}(s) = \frac{1}{sL_x + \frac{1}{sC_x} + R_x} = \frac{sC_x}{s^2L_xC_x + 1 + sC_xR_x} = \frac{s(\frac{1}{L_x})}{s^2 + \frac{1}{L_xC_x} + s(\frac{R_x}{L_x})}$$

$$\left[\frac{1}{L_xC_x} = \omega_0^2, Q = \frac{\omega_0 L_x}{R_x} \rightarrow \frac{R_x}{L_x} = \frac{\omega_0}{Q} \right] \Rightarrow \frac{i_o}{N_i}(s) = \frac{1}{R_x} \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2} = \frac{1}{R_x} \mathcal{H}(s)$$

$$\mathcal{H}(s) = \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

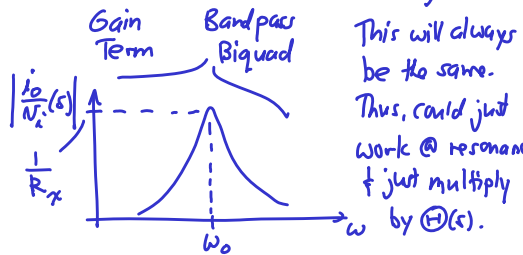$s=0: \mathcal{H}(0) = 0$
 $s=j\omega_0: \mathcal{H}(j\omega_0) = 1$
 $s=\infty: \mathcal{H}(\infty) = 0$



EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 20

Condensed Equiv. Circuit (Symmetrical)

UC Berkeley

If $\eta_{e1} = \eta_{e2}$, then ...

where

$$L_x = \frac{m}{\eta_e^2}$$

$$C_x = \frac{\eta_e^2}{k}$$

$$R_x = \frac{b}{\eta_e^2}$$

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 21

Phasings of Signals

UC Berkeley

• Below: plots of resonance electrical and mechanical signals vs. time, showing the phasings between them

EE C245: Introduction to MEMS Design LecM 13 C. Nguyen 11/18/08 22