



EE C247B - ME C218 Introduction to MEMS Design Fall 2019

Prof. Clark T.-C. Nguyen



Dept. of Electrical Engineering & Computer Sciences
University of California at Berkeley
Berkeley, CA 94720

Module 17: Noise & MDS



Lecture Outline

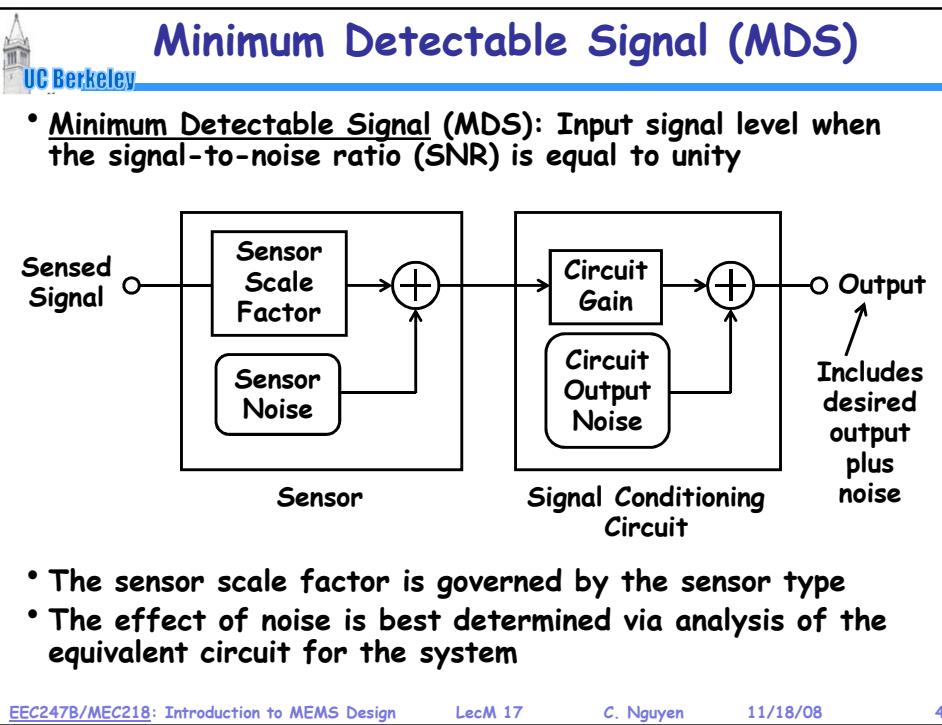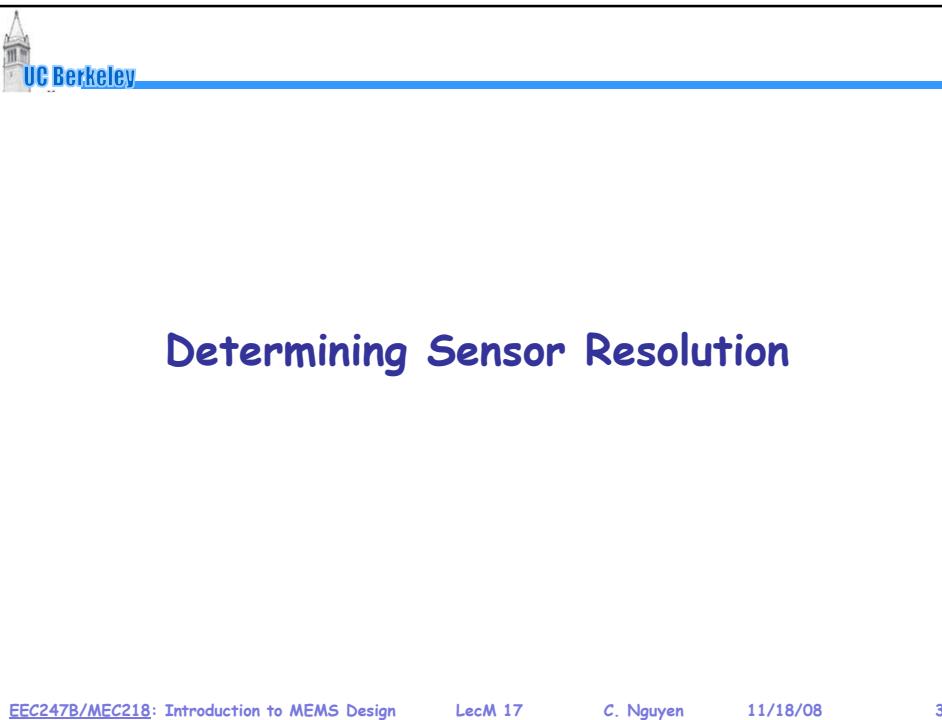- Reading: Senturia Chpt. 16
- Lecture Topics:
 - ↳ Minimum Detectable Signal
 - ↳ Noise
 - Circuit Noise Calculations
 - Noise Sources
 - Equivalent Input-Referred Noise
 - ↳ Gyro MDS
 - Equivalent Noise Circuit
 - Example ARW Determination



 UC Berkeley

Noise


EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 5

 UC Berkeley

Noise

- **Noise:** Random fluctuation of a given parameter $I(t)$
- In addition, a noise waveform has a zero average value


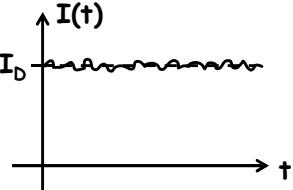
Avg. value (e.g. could be DC current) → I_D



- We can't handle noise at instantaneous times
- But we can handle some of the averaged effects of random fluctuations by giving noise a power spectral density representation
- Thus, represent noise by its mean-square value:
Let $i(t) = I(t) - I_D$

Then $\overline{i^2} = \overline{(I - I_D)^2} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T |I - I_D|^2 dt$

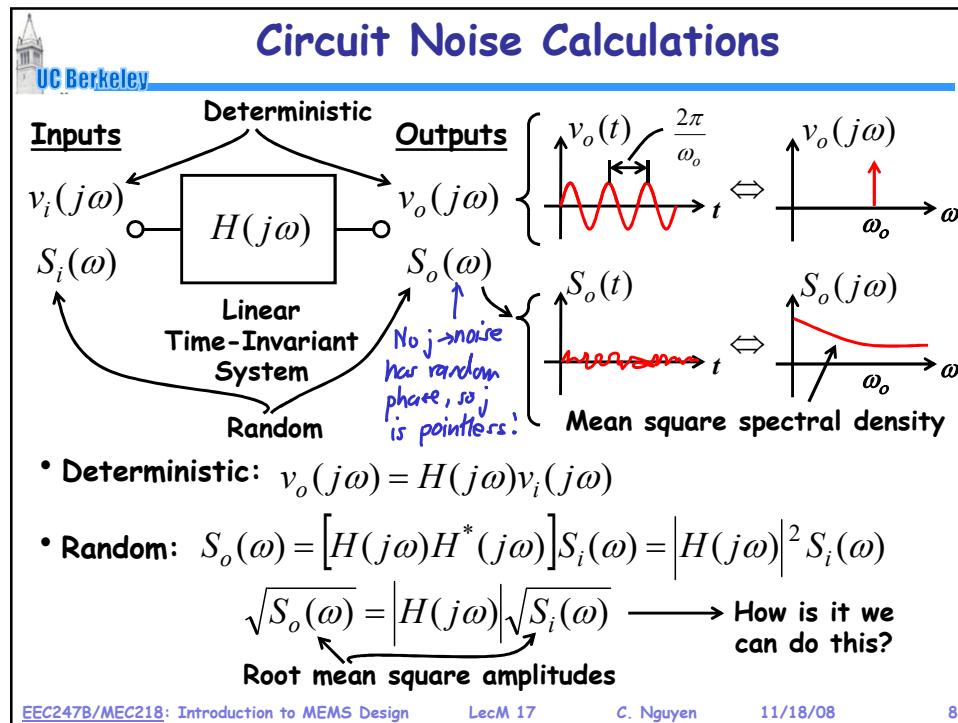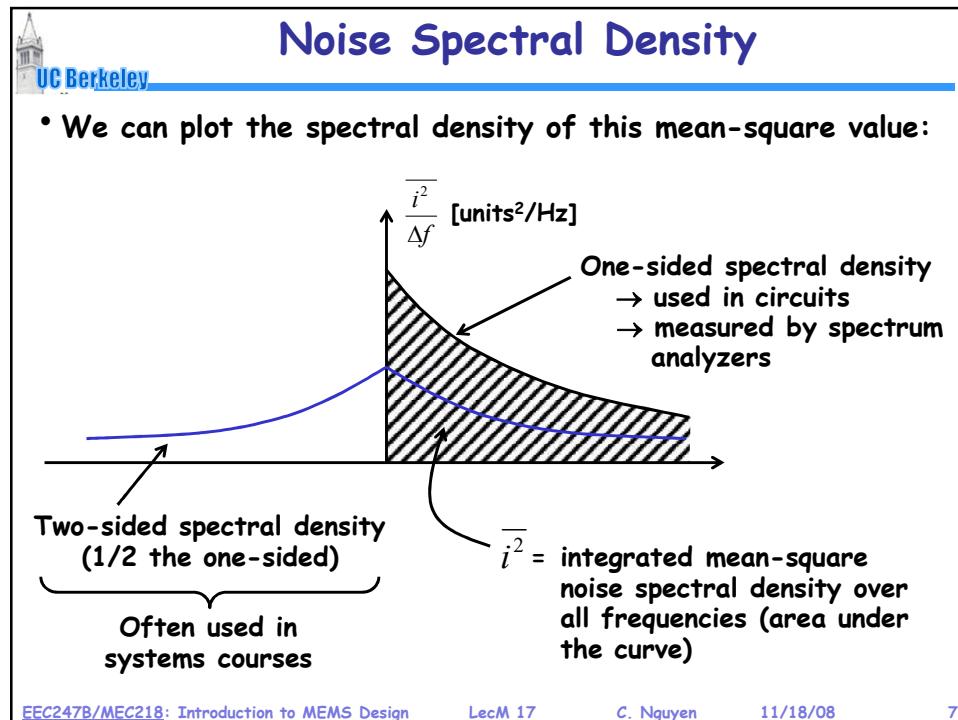EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 6



Handling Noise Deterministically

UC Berkeley

- Can do this for noise in a tiny bandwidth (e.g., 1 Hz)

$\frac{v_{n1}^2}{\Delta f} = S_1(f) \rightarrow v_{n1} = \sqrt{S_1(f) \cdot B}$ → Can approximate this by a sinusoidal voltage generator (especially for small B, say 1 Hz)

$S_n(j\omega)$

$v_o(t) \sim |A| \cos \omega_o t$

$\tau \sim \frac{1}{B}$

[This is actually the principle by which oscillators work → oscillators are just noise going through a tiny bandwidth filter]

Why? Neither the amplitude nor the phase of a signal can change appreciably within a time period $1/B$.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 9

Systematic Noise Calculation Procedure

UC Berkeley

General Circuit With Several Noise Sources

$H_2(j\omega)$

$H_5(j\omega)$

$H_1(j\omega)$

v_{n2}^2

v_{n3}^2

i_{n5}^2

i_{n1}^2

i_{n4}^2

v_{n6}^2

v_{on}^2

- Assume noise sources are uncorrelated
- 1. For i_{n1}^2 , replace w/ a deterministic source of value

$$i_{n1} = \sqrt{\frac{i_{n1}^2}{\Delta f}} \cdot (1 \text{ Hz})$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 10

Systematic Noise Calculation Procedure



2. Calculate $v_{on1}(\omega) = i_{n1}(\omega)H(j\omega)$ (treating it like a deterministic signal)
3. Determine $v_{on1}^2 = i_{n1}^2 \cdot |H(j\omega)|^2$
4. Repeat for each noise source: $i_{n1}^2, v_{n2}^2, v_{n3}^2$
5. Add noise power (mean square values)

$$\overline{v_{onTOT}^2} = \overline{v_{on1}^2} + \overline{v_{on2}^2} + \overline{v_{on3}^2} + \overline{v_{on4}^2} + \dots$$

$$v_{onTOT} = \sqrt{\overline{v_{on1}^2} + \overline{v_{on2}^2} + \overline{v_{on3}^2} + \overline{v_{on4}^2} + \dots}$$

Total rms value



Noise Sources

Thermal Noise

UC Berkeley

- **Thermal Noise in Electronics:** (Johnson noise, Nyquist noise)
 - ↳ Produced as a result of the thermally excited random motion of free e's in a conducting medium
 - ↳ Path of e's randomly oriented due to collisions
- **Thermal Noise in Mechanics:** (Brownian motion noise)
 - ↳ Thermal noise is associated with all dissipative processes that couple to the thermal domain
 - ↳ Any damping generates thermal noise, including gas damping, internal losses, etc.
- **Properties:**
 - ↳ Thermal noise is white (i.e., constant w/ frequency)
 - ↳ Proportional to temperature
 - ↳ Not associated with current
 - ↳ Present in any real physical resistor

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 13

Circuit Representation of Thermal Noise

UC Berkeley

- Thermal Noise can be shown to be represented by a series voltage generator $\overline{v_R^2}$ or a shunt current generator $\overline{i_R^2}$

Note: These are one-sided mean-square spectral densities! To make them 2-sided, must divide by 2.

$$\left\{ \begin{array}{l} \overline{i_R^2} = \frac{4kT}{R} \\ \overline{v_R^2} = 4kTR \end{array} \right.$$

where $4kT = 1.66 \times 10^{-20} V \cdot C$
 and where these are spectral densities.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 14

Noise in Capacitors and Inductors?

UC Berkeley

- Resistors generate thermal noise
- Capacitors and inductors are noiseless → why?

Now, add a resistor:

Need to add a forcing function, like a noise voltage v_R^2 to keep the motion going → and this noise source is associated with R

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 15

Why $4kT\Delta f$?

UC Berkeley

- Why is $\overline{v_R^2} = 4kT\Delta f$ (a heuristic argument)
- The Equipartition Theorem of Statistical Thermodynamics says that there is a mean energy $(1/2)kT$ associated w/ each degree of freedom in a given system
- An electronic circuit possesses two degrees of freedom:
 - ↳ Current, i , and voltage, v
 - ↳ Thus, we can write:
$$\frac{1}{2}Li^2 = \frac{1}{2}k_B T \quad , \quad \underbrace{\frac{1}{2}Cv^2}_{\text{Energy}} = \frac{1}{2}k_B T$$
- Similar expressions can be written for mechanical systems
 - ↳ For example: for displacement, x
$$\text{Spring constant } \frac{1}{2}kx^2 = \frac{1}{2}k_B T$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 16

Why $4kT\Delta f$? (cont)

UC Berkeley

- Why is $\overline{v_R^2} = 4kT\Delta f$? (a heuristic argument)
- Consider an RC circuit:

$$E = \frac{1}{2} kT = \frac{1}{2} C \overline{v_c^2}$$

$$\therefore \overline{v_c^2} = \frac{kT}{C}$$

\leftarrow integrated noise over all freqs.
 (total mean square voltage integrated over all freqs.)

Question: What value of $\frac{\overline{v_R^2}}{\Delta f}$ (assuming white noise) gives us this?

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 17

Why $4kT\Delta f$? (cont)

UC Berkeley

Question: What value of $\frac{\overline{v_R^2}}{\Delta f}$ (assuming white noise) gives us $\overline{v_c^2} = \frac{kT}{C}$?

$$\overline{v_c^2} = \int_0^\infty \left| \frac{1}{1+j\omega RC} \right|^2 \frac{\overline{v_R^2}}{\Delta f} d\omega$$

[noise is white] $\rightarrow = \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \int_0^\infty \frac{\omega_b^2}{\omega_b^2 + \omega^2} d\omega$

$\left[\int \frac{dx}{x^2 + a^2} = \frac{1}{a} \tan^{-1}\left(\frac{x}{a}\right) \right]$

$$= \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \frac{\omega_b^2}{\omega_b} \tan^{-1}\left(\frac{\omega}{\omega_b}\right) \Big|_0^\infty = \frac{1}{2\pi} \frac{\overline{v_R^2}}{\Delta f} \left(\frac{\pi}{2} - 0 \right)$$


$$= \frac{1}{4} \omega_b \frac{\overline{v_R^2}}{\Delta f} = \frac{kT}{C} \rightarrow \frac{\overline{v_R^2}}{\Delta f} = 4kT \left(\frac{C}{\omega_b} \right) \Rightarrow \boxed{\frac{\overline{v_R^2}}{\Delta f} = 4kT\Delta f}$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 18

Shot Noise

 UC Berkeley

- Associated with direct current flow in diodes and bipolar junction transistors
- Arises from the random nature by which e⁻'s and h⁺'s surmount the potential barrier at a pn junction
- The DC current in a forward-biased diode is composed of h⁺'s from the p-region and e⁻'s from the n-region that have sufficient energy to overcome the potential barrier at the junction
 → noise process should be proportional to DC current
- Attributes:**
 - Related to DC current over a barrier
 - Independent of temperature
 - White (i.e., const. w/ frequency)
 - Noise power $\sim I_D$ & bandwidth

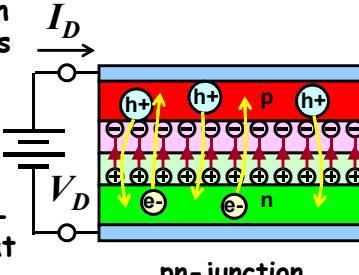

$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D$$

Charge on an e⁻
 $(=1.6 \times 10^{-19} C)$


DC Current

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 19

Flicker (1/f) Noise

 UC Berkeley

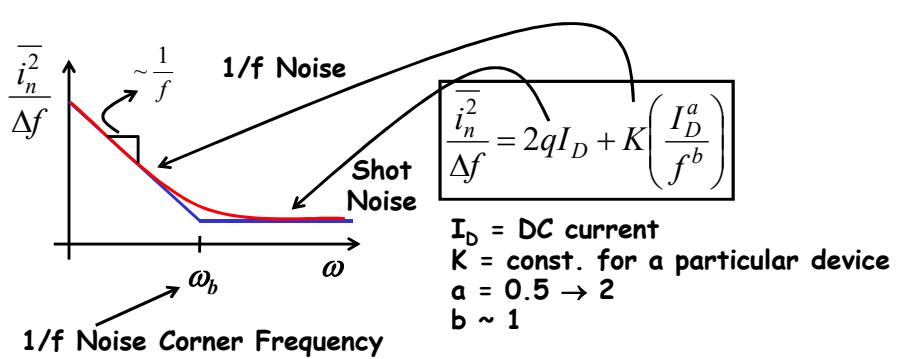- In general, associated w/ random trapping & release of carriers from "slow" states
- Time constant associated with this process gives rise to a noise signal w/ energy concentrated at low frequencies
- Often, get a mean-square noise spectral density that looks like this:



$$\frac{\overline{i_n^2}}{\Delta f} = 2qI_D + K\left(\frac{I_D^a}{f^b}\right)$$

I_D = DC current
 K = const. for a particular device
 $a = 0.5 \rightarrow 2$
 $b \sim 1$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 20

Example: Typical Noise Numbers

UC Berkeley

- Hookup the circuit below and make some measurements

Measure w/ AC voltmeter
 Measure w/ spectrum analyzer
 Get Gaussian amplitude distribution

Probability

Amplitude

68% within $\pm \sigma$
 99.7% within $\pm 3\sigma$

$\frac{N_R^2}{\delta f} = \frac{4kT}{2\pi RC}$

$\frac{1}{2\pi RC} = 4nV/\sqrt{Hz}$ (for every 1K of R)

$\frac{1}{1pF} \cdot \sqrt{\frac{kT}{C}} = 64\mu V \text{ rms}$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 21

Example: Typical Noise Numbers

UC Berkeley

- Hookup the circuit below and make some measurements

Measure w/ AC voltmeter
 Measure w/ spectrum analyzer

AC Voltmeter

$$\sqrt{N_o^2} = (100)(64\mu V \text{ rms}) = 6.4mV \text{ rms}$$

Spectrum Analyzer



$$\frac{1}{(2\pi)(1k)(1p)} = 60MHz$$



400 nV/V \sqrt{Hz}



20 dB/dec

one-sided spectral density

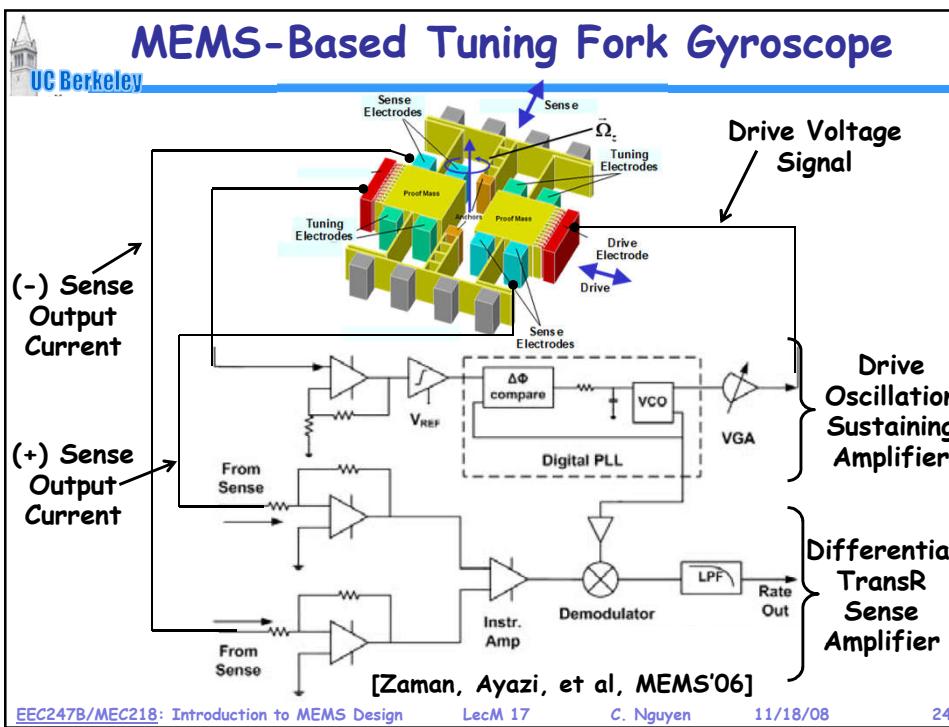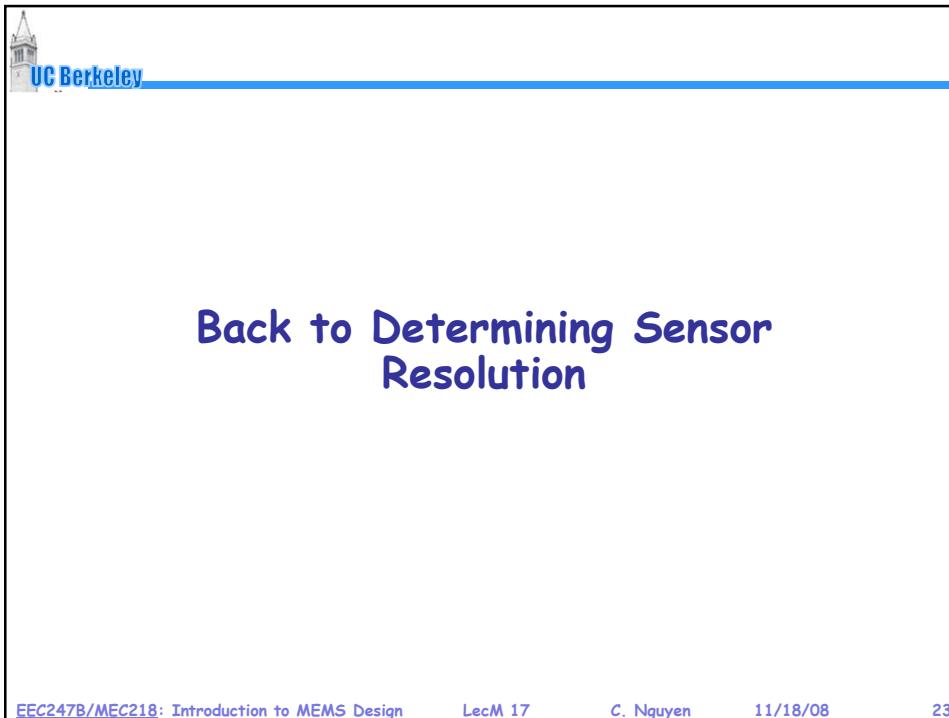EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 22



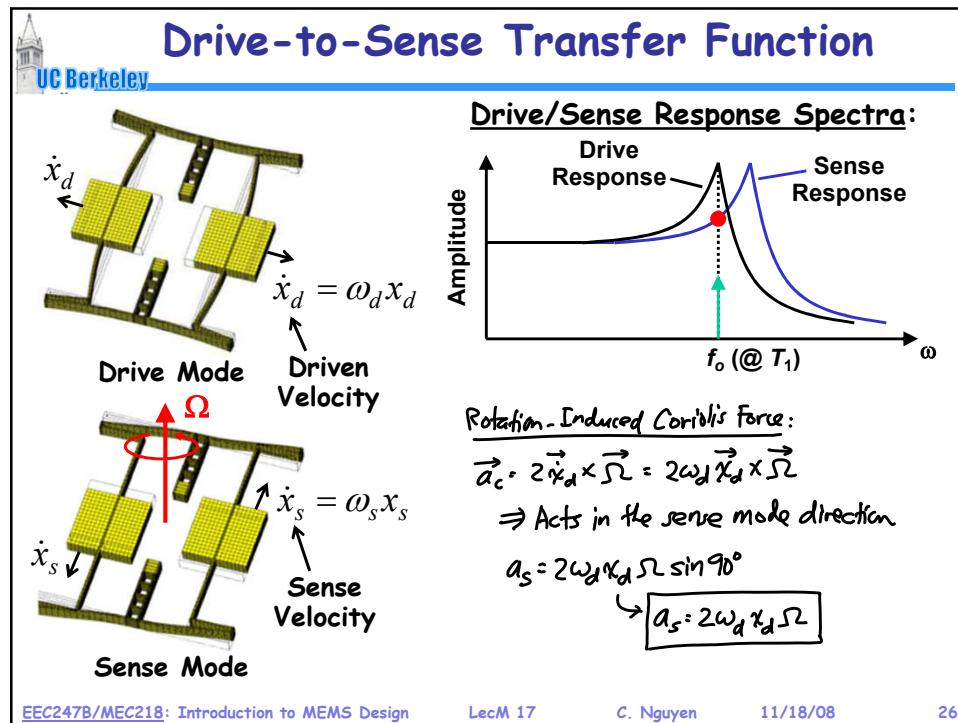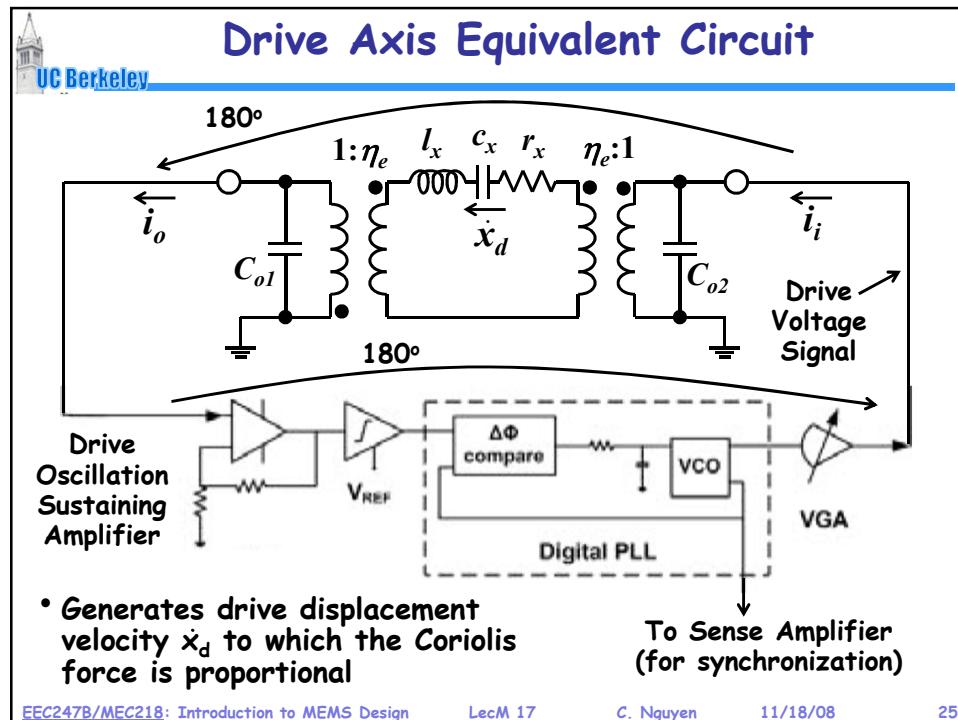

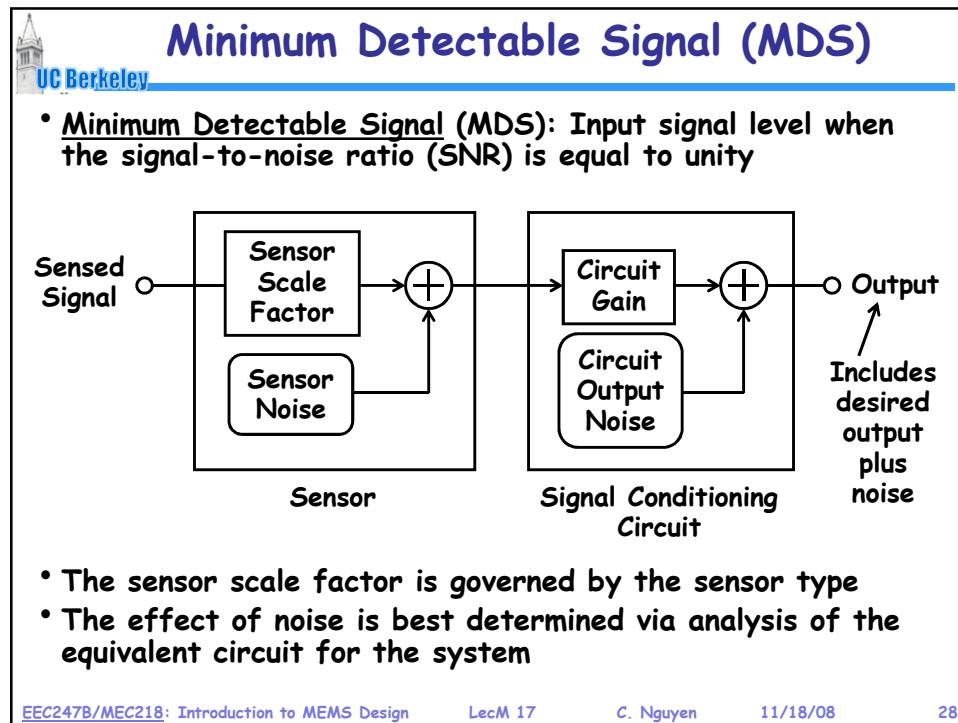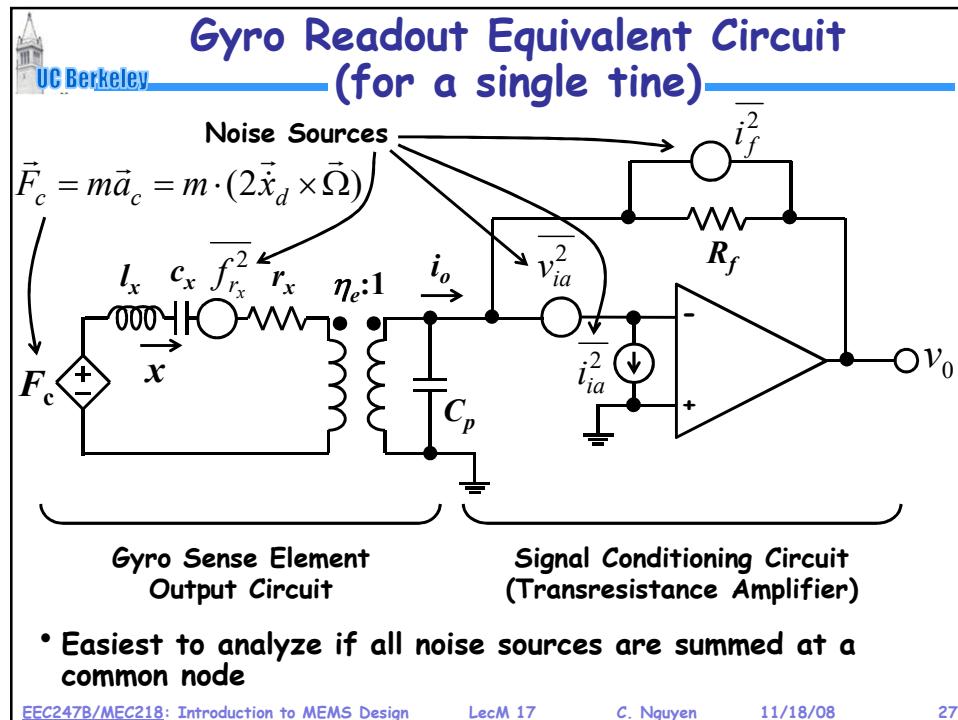

Move Noise Sources to a Common Point

UC Berkeley

- Move noise sources so that all sum at the input to the amplifier circuit (i.e., at the output of the sense element)
- Then, can compare the output of the sensed signal directly to the noise at this node to get the MDS

The diagram illustrates a signal processing chain. It starts with a 'Sensed Signal' entering a 'Sensor' block. Inside the Sensor block, there are two parallel paths: one for the 'Sensor Scale Factor' and another for 'Sensor Noise'. These paths converge at a summing junction (indicated by a circle with a plus sign). The output of this junction then enters a second summing junction. This second junction also receives input from a 'Circuit Input-Referred Noise' block. The output of this junction is multiplied by 'Circuit Gain' (represented by a rectangle) to produce the final 'Output'. An annotation points to the output, stating 'Includes desired output plus noise'.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 29

Equivalent Input-Referred Voltage and Current Noise Sources


UC Berkeley

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 30

Equivalent Input v , i Noise Generators



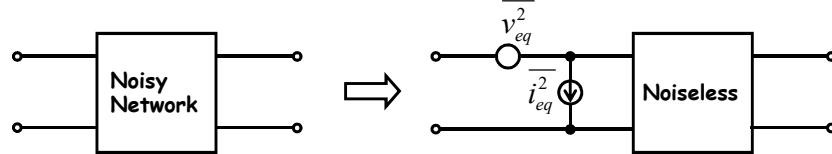- Take a noisy 2-port network and represent it by a noiseless network with input v and i noise generators that generate the same total output noise



- Remarks:


- Works for linear time-invariant networks
- v_{eq} and i_{eq} are generally correlated (since they are derived from the same sources)
- In many practical circuits, one of v_{eq} and i_{eq} dominates, which removes the need to address correlation
- If correlation is important → easier to return to original network with internal noise sources

Calculation of $\overline{v_{eq}^2}$ and $\overline{i_{eq}^2}$




a) To get $\overline{v_{eq}^2}$ for a two-port:

Case I

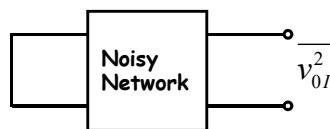

Case II

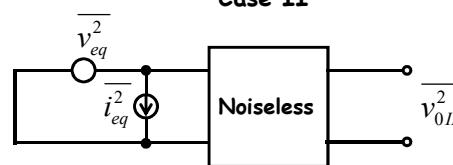

1) Short input, find $\overline{v_{0I}^2}$ (or $\overline{i_{0I}^2}$)

2) For eq. network, short input, find $\overline{v_{eq}^2}$ (or $\overline{i_{eq}^2}$)

$$f\left(\overline{v_{eq}^2}\right) \quad f\left(\overline{v_{eq}^2}\right)$$

3) Set $\overline{v_{0I}^2} = \overline{v_{0II}^2} \rightarrow$ solve for $\overline{v_{eq}^2}$ (or $\overline{i_{0I}^2} = \overline{i_{0II}^2}$)

Calculation of $\overline{v_{eq}^2}$ and $\overline{i_{eq}^2}$ (cont)

b) To get $\overline{i_{eq}^2}$ for a 2-port:

1) Open input, find $\overline{v_{0I}^2}$ (or $\overline{i_{0I}^2}$)
 2) Open input for eq. circuit, find $\overline{v_{0II}^2}$ (or $\overline{i_{0II}^2}$)
 3) Set $\overline{v_{0I}^2} = \overline{v_{0II}^2}(\overline{i_{eq}^2}) \rightarrow$ solve for $\overline{i_{eq}^2}$ (or $\overline{i_{0I}^2} = \overline{i_{0II}^2}(\overline{i_{eq}^2})$)

- Once the equivalent input-referred noise generators are found, noise calculations become straightforward as long as the noise generators can be treated as uncorrelated

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 33

Cases Where Correlation Is Not Important

There are two common cases where correlation can be ignored:

- Source resistance R_s is **small** compared to input resistance $R_i \rightarrow$ i.e., voltage source input
- Source resistance R_s is **large** compared to input resistance $R_i \rightarrow$ i.e., current source input

1) R_s = small (ideally = 0 for an ideal voltage source):

$\overline{i_{eq}^2}$ Current shorted out!

.. For R_s small, $\overline{i_{eq}^2}$ can be neglected \rightarrow only $\overline{v_{eq}^2}$ is important!
 (Thus, we need not deal with correlation)

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 34

Cases Where Correlation Is Not Important

UC Berkeley

2) $R_s = \text{large}$ (Ideally = ∞ for an ideal current source)

$$v_i = \frac{R_{in}}{\infty + R_{in}} v_{eq}^2 = 0!$$

\therefore For $R_s = \text{large}$, v_{eq}^2 can be neglected!
 → only i_{eq}^2 is important!

(... and again, we need not deal with correlation)

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 35

Example: TransR Amplifier Noise

UC Berkeley

Input-referred current noise:
 Open inputs; equate output voltage noise.

Case I:

$$N_{OI} = i_{ia} R_f$$

$$N_{OII} = i_f R_f$$

$$N_{OI3} = N_{ia} \xrightarrow{R_i} N_{ia}$$

Case II:



$$N_{OI} = i_{eq} R_f^2 + i_f^2 R_f^2 + N_{ia}^2$$



$$N_{OII} = i_{eq} R_f^2$$

$$i_{eq}^2 = i_{ia}^2 + i_f^2 + \frac{N_{ia}^2}{R_f^2}$$

This is unity gain!

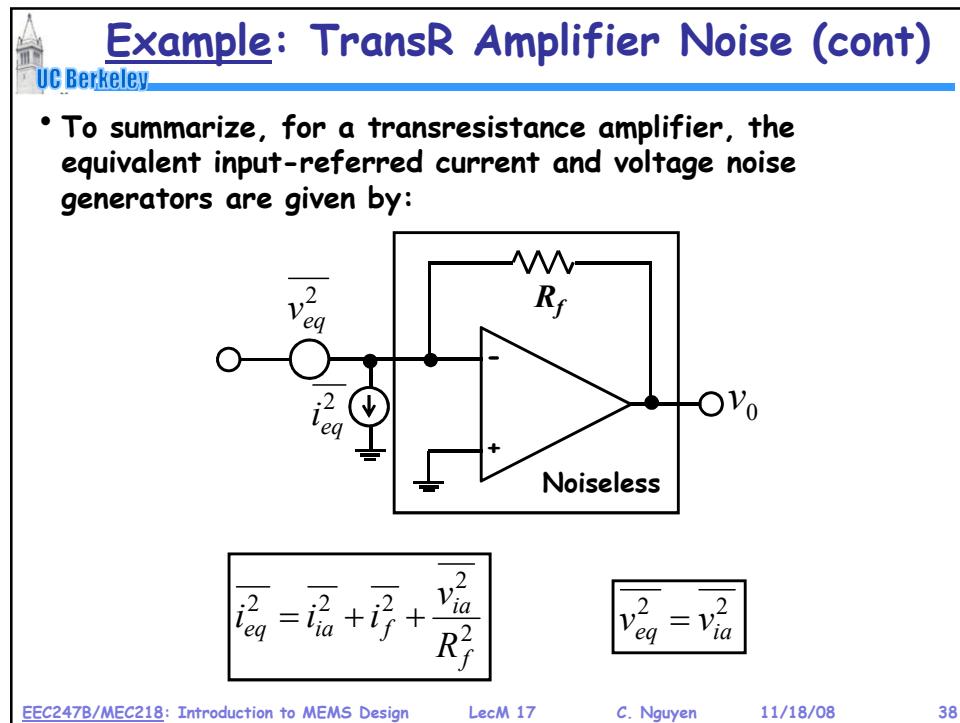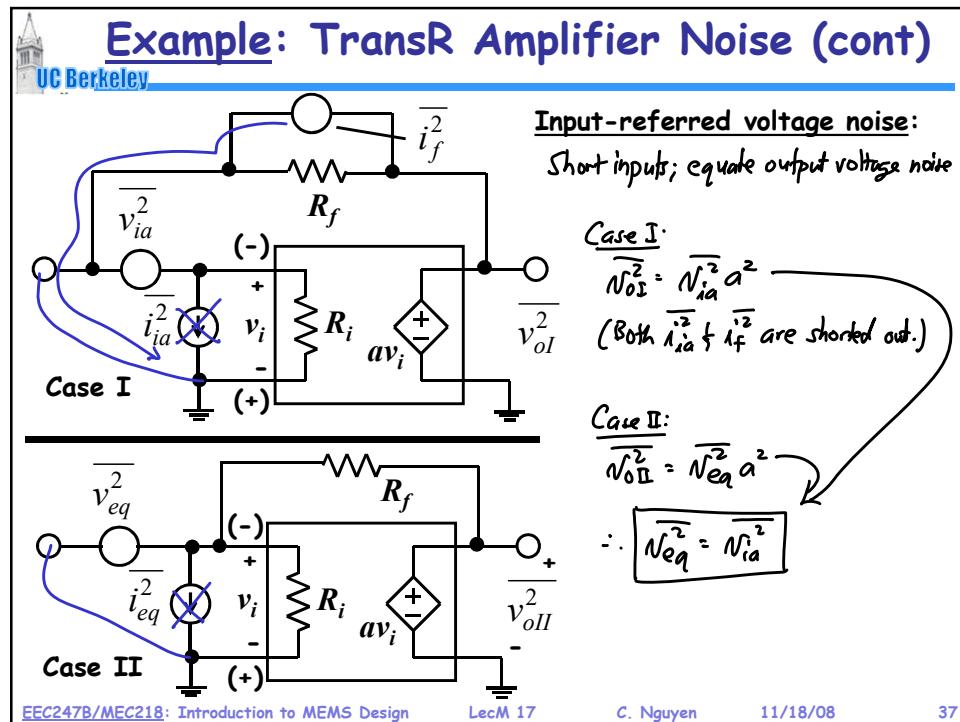EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 36



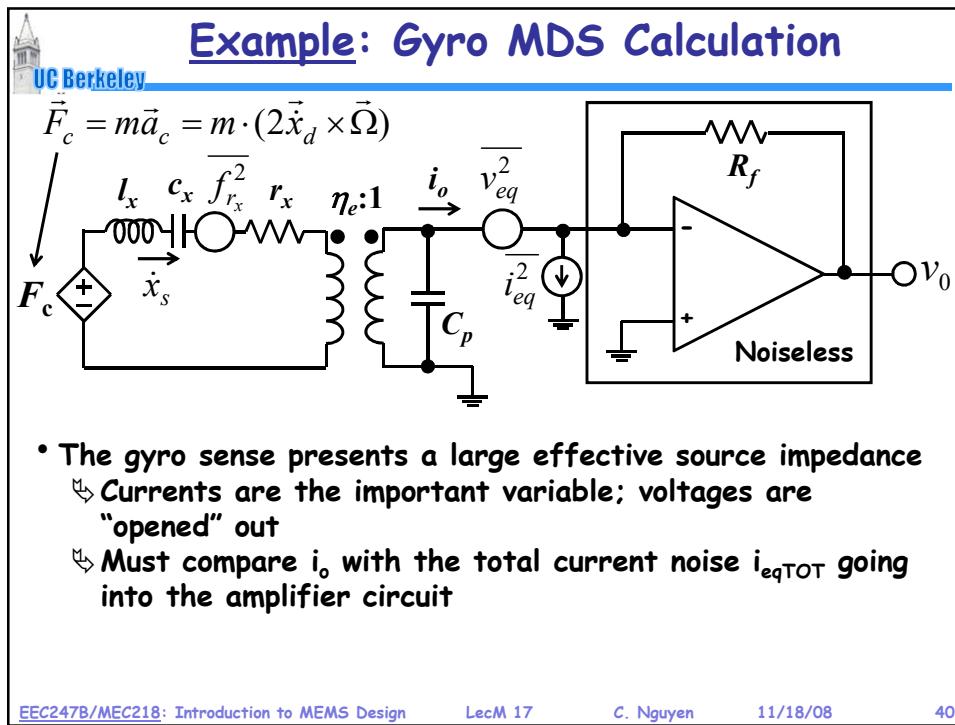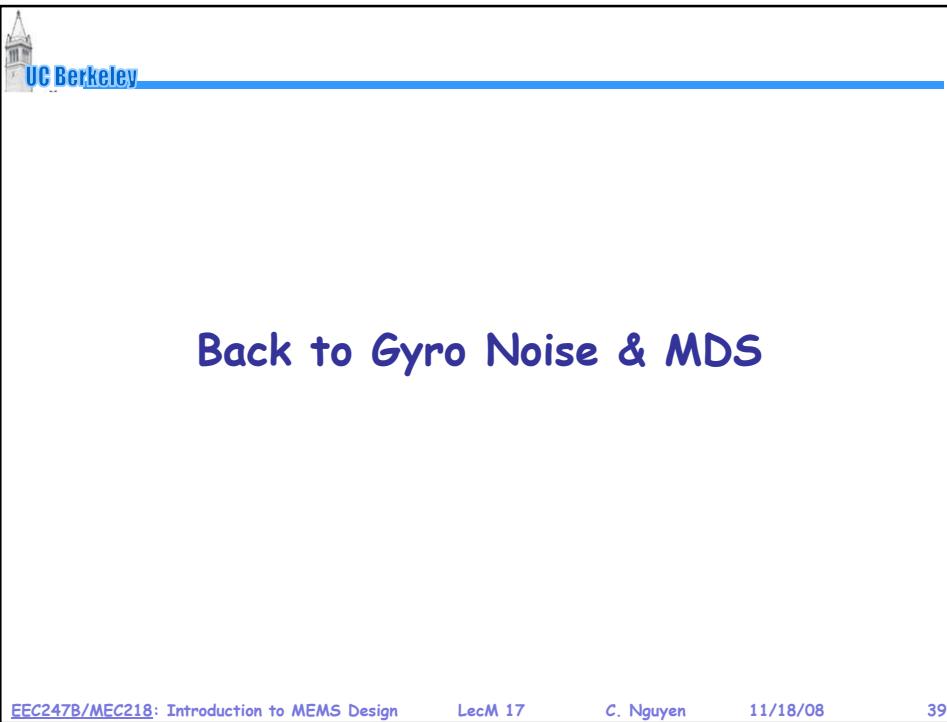

Example: Gyro MDS Calculation (cont)

$$\vec{F}_c = m\vec{a}_c = m \cdot (2\vec{x}_d \times \vec{\Omega})$$

$$F_c = \eta_e i_o$$

$$i_o = \frac{v_{eq}^2}{R_f}$$

$$v_0 = -v_{eq}^2$$

• First, find the rotation to i_o transfer function:

$$i_s = \frac{\omega_s Q_s H_s(j\omega_d)}{k_s} F_s = \frac{\omega_s Q_s \cdot 2\omega_d \chi_d \zeta_m}{k_s} H_s(j\omega_d)$$

$$[F_s = F_c = 2\omega_d \chi_d \zeta_m]$$

$$i_s = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d H_s(j\omega_d) \cdot \zeta_m$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 41

Example: Gyro MDS Calculation (cont)

$$i_o = \eta_e i_s = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d \eta_e H_s(j\omega_d) \cdot \zeta_m \quad \rightarrow \quad i_o = A \zeta_m$$

where $A = 2 \frac{\omega_d}{\omega_s} Q_s \chi_d \eta_e H_s(j\omega_d)$

When $\zeta_m = \zeta_{min} \triangleq MDS$, $i_o = i_{eqTOT}$ \leftarrow input-referred noise current entering the sense amplifier \rightarrow in pA/\sqrt{Hz}

$$\therefore i_{eqTOT} = A \zeta_{min} \rightarrow \zeta_{min} = \frac{i_{eqTOT}}{A} \left(\frac{3600s}{hr} \right) \left(\frac{180^\circ}{\pi} \right) \left[(\%) / \sqrt{Hz} \right]$$

$$\text{Angle Random Walk} = ARW = \frac{1}{60} \zeta_{min} [\% / hr]$$

Easier to determine directional error as a function of elapsed time.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 42

Example: Gyro MDS Calculation (cont)

The diagram illustrates the calculation of Gyro MDS. On the left, a mechanical system is shown with a force $F_c = m\vec{a}_c = m \cdot (2\vec{x}_d \times \vec{\Omega})$ and a displacement \dot{x}_s . This is connected to a sense element with parameters L_x , C_x , f_{rx}^2 , and r_x . A transformer couples this to an electronic circuit. The electronic circuit includes a noise source i_{eq} with noise power $\frac{i_{eq}^2}{R_s}$, a resistor R_f , and an operational amplifier. The output voltage is V_0 . A note indicates that R_s is large, so i_{eq} is "opened" out.

Now, find the $i_{eq,TOT}$ entering the amplifier input:

$$i_{eq,TOT} = i_s + i_{eq} \rightarrow i_{eq,TOT} = \frac{i_s^2}{R_s} + \frac{i_f^2}{R_f} + \frac{i_{ia}^2}{R_f} + \frac{i_{eq}^2}{R_s}$$

Annotations explain:

- Brownian motion noise of the sense element → determined entirely by the noise in $r_x \rightarrow f_{rx}^2$
- easiest to convert to an all electrical equiv. ckt.

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 43

Example: Gyro MDS Calculation (cont)

The diagram shows a detailed circuit for Gyro MDS calculation. It includes a sense element with parameters L_x , C_x , and R_x , and a noise source $N_{R_x}^2 = 4kT R_x$. The circuit branches into two paths. One path goes through a resistor R_f to an amplifier input, contributing noise $\frac{i_{eq,TOT}^2}{R_f}$. The other path goes through resistors R_s and R_f to ground, contributing noise $\frac{i_s^2}{R_s} + \frac{i_{eq}^2}{R_s}$. The total noise is $i_{eq,TOT}^2 = \frac{i_s^2}{R_s} + \frac{i_{eq}^2}{R_s} + \frac{i_{ia}^2}{R_f} + \frac{i_f^2}{R_f}$.

Where $L_{rx} = \frac{R_x}{N_{R_x}^2}$, $C_{rx} = \eta_e^2 C_x$, $R_{rx} = \frac{r_x}{\eta_e}$.

$\therefore i_s = N_{R_x} \left(\frac{1}{R_x} \right) \Theta_s(j\omega_d) \rightarrow \frac{i_s^2}{\Delta f} = 4kT R_x \left(\frac{1}{R_x^2} \right) |\Theta_s(j\omega_d)|^2$

Thus:

$$\frac{i_{eq,TOT}^2}{\Delta f} = \frac{4kT}{R_x} |\Theta_s(j\omega_d)|^2 + \frac{4kT}{R_f} + \frac{i_{ia}^2}{\Delta f} + \frac{N_{eq}^2}{\Delta f} \left(\frac{1}{R_f^2} \right)$$

Learn to get these from EE240.
or just get them from a data sheet ...

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 44

LF356 Op Amp Data Sheet

UC Berkeley

LF155/LF156/LF256/LF257/LF355/LF356/LF357 JFET Input Operational Amplifiers

General Description

These are the first monolithic JFET input operational amplifiers to incorporate well matched, high voltage JFETs on the same chip with standard bipolar transistors (Bi-FET™ Technology). These amplifiers feature low input bias and offset currents/low offset voltage and offset voltage drift, coupled with offset adjust which does not degrade drift or common-mode rejection. The devices are also designed for high slew rate, wide bandwidth, extremely fast settling time, low voltage and current noise and a low $1/f$ noise corner.

Features

- Replace expensive hybrid and module FET op amps
- Rugged JFETs allow blow-out free handling compared with MOSFET input devices
- Excellent for low noise applications using either high or low source impedance — very low $1/f$ corner
- Offset adjust does not degrade drift or common-mode rejection as in most monolithic amplifiers
- New output stage allows use of large capacitive loads (5,000 pF) without stability problems
- Internal compensation and large differential input voltage capability

Applications

- Precision high speed integrators
- Fast D/A and A/D converters
- High impedance buffers
- Wideband, low noise, low drift amplifiers

Common Features

- Low input bias current: 30 pA
- Low Input Offset Current: 3 pA
- High input impedance: $10^{12} \Omega$
- Low input noise current: $0.01 \text{ pA}/\sqrt{\text{Hz}}$
- High common-mode rejection ratio: 100 dB
- Large dc voltage gain: 106 dB

Uncommon Features

	LF155/ LF355	LF156/ LF256	LF257/ LF357	Units
Extremely fast settling time to 0.01%	4	1.5	1.5	μs
Fast slew rate	5	12	50	V/μs
Wide gain bandwidth	2.5	5	20	MHz
Low input noise voltage	20	12	12	nV/ $\sqrt{\text{Hz}}$


(Handwritten notes: $i_{ia} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$ and $v_{ia} = 12 \text{ nV}/\sqrt{\text{Hz}}$)

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 45

Example ARW Calculation

UC Berkeley

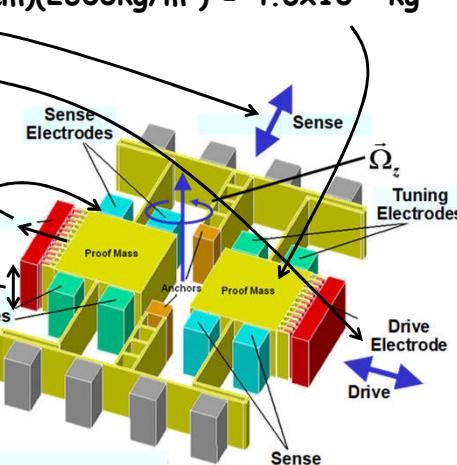- Example Design:**
 - Sensor Element:**
 $m = (100\mu\text{m})(100\mu\text{m})(20\mu\text{m})(2300\text{kg/m}^3) = 4.6 \times 10^{-10}\text{kg}$
 $\omega_s = 2\pi(15\text{kHz})$
 $\omega_d = 2\pi(10\text{kHz})$
 $k_s = \omega_s^2 m = 4.09 \text{ N/m}$
 $x_d = 20 \mu\text{m}$
 $Q_s = 50,000$
 $V_p = 5\text{V}$
 $h = 20 \mu\text{m}$
 $d = 1 \mu\text{m}$
 - Sensing Circuitry:**
 $R_f = 100\text{k}\Omega$
 $i_{ia} = 0.01 \text{ pA}/\sqrt{\text{Hz}}$
 $v_{ia} = 12 \text{ nV}/\sqrt{\text{Hz}}$



EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 46

Example ARW Calculation (cont)

Get rotation rate to output current scale factor:

$$A = 2 \frac{w_d}{w_s} Q_s \eta_e |\Theta(j\omega_d)| = 2 \left(\frac{10k}{15k} \right) (50k) (20\mu) (5) (2000\epsilon_0) (0.000024) = \underline{2.83 \times 10^{-12} C}$$

$$\left[\Theta_s(j\omega_d) = \frac{(j\omega_d)(w_s/Q_s)}{-\omega_d^2 + j\omega_d w_s + \omega_s^2} = \frac{j(10k)(15k)/(50k)}{(15k)^2 - (10k)^2 + j(10k)(15k)/50k} = \frac{j(3k)}{1.25 \times 10^8 + j(3k)} \right]$$

$$\rightarrow |\Theta_s(j\omega_d)| = \frac{3k}{\sqrt{(1.25 \times 10^8)^2 + (3k)^2}} = \frac{0.000024}{8.854 \times 10^{-8} F/m}$$

$$\left[\frac{\partial C}{\partial x} = \frac{C_0}{d} = \frac{\epsilon_0 h w_p}{d} = \frac{\epsilon_0 (20\mu)(100\mu)}{(1\mu)^2} = 2000\epsilon_0 \rightarrow \eta_e = V_p \frac{\partial C}{\partial x} = \frac{5(2000\epsilon_0)}{8.854 \times 10^{-12} F/m} \right]$$

Assume electrode covers the whole sidewall.

Then, get noise:

$$\frac{i_{eq,TOT}^2}{\Delta f} = \frac{4kT}{R_X} |\Theta_s(j\omega_d)|^2 + \frac{4kT}{R_f} + \frac{i_{ia}^2}{\Delta f} + \frac{N_{ia}^2}{\Delta f} \left(\frac{1}{R_f^2} \right)$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 47

Example ARW Calculation (cont)

$R_X = \frac{w_s m}{Q_s \eta_e} = \frac{2\pi(15k)(4.6 \times 10^{-10})}{(50k)(8.854 \times 10^{-8})^2} = 110.6 k\Omega$

$$\frac{i_{eq,TOT}^2}{\Delta f} = \underbrace{\frac{(1.66 \times 10^{-29})}{(110.6k)} (0.000024)^2}_{8.64 \times 10^{-75} A^2/Hz} + \underbrace{\frac{(1.66 \times 10^{-29})}{1M}}_{1.66 \times 10^{-26} A^2/Hz} + \underbrace{(0.01\rho)^2}_{1 \times 10^{-28} A^2/Hz} + \underbrace{\frac{(12\mu)^2}{(1M)^2}}_{1.44 \times 10^{-28} A^2/Hz}$$

sensor element noise noise from R_f dominates!

$$\therefore \frac{i_{eq,TOT}^2}{\Delta f} = 1.68 \times 10^{-26} A^2/Hz \rightarrow i_{eq,TOT} = \sqrt{\frac{i_{eq,TOT}^2}{\Delta f}} = 1.30 \times 10^{-13} A/\sqrt{Hz}$$

$$\therefore S2_{min} = \frac{i_{eq,TOT}}{A} \left(\frac{3600\pi}{hr} \right) \left(\frac{180}{\pi} \right) = \frac{1.30 \times 10^{-13}}{2.83 \times 10^{-12}} (3600) \left(\frac{180}{\pi} \right) = \underline{9448 (\%/hr)/\sqrt{Hz}}$$

And finally:

$$ARW = \frac{1}{60} S2_{min} = \frac{1}{60} (9448) = \boxed{157 \%/\sqrt{hr} = ARW} \Rightarrow \text{Almost turned around in 1 hour!}$$

EEC247B/MEC218: Introduction to MEMS Design LecM 17 C. Nguyen 11/18/08 48



What if $\omega_d = \omega_s$?

If $\omega_d = \omega_s = 15\text{kHz}$, then $|H_s(j\omega_d)| = 1$ and

$$A = 2 \frac{\omega_d}{\omega_s} Q_s X_d \eta_e |H_s(j\omega_d)| = 2 Q_s X_d \eta_e = 2(50k)(20\mu)(5)(2000\epsilon_0) = 1.77 \times 10^{-7} \text{C}$$

$$\frac{i_{eq,TOT}^2}{\Delta f} = \underbrace{\frac{(1.66 \times 10^{-29})}{(110.6k)} (1)^2}_{1.51 \times 10^{-25} \text{A}^2/\text{Hz}} + \underbrace{\frac{(1.66 \times 10^{-29})}{1M}}_{1.66 \times 10^{-26} \text{A}^2/\text{Hz}} + \underbrace{(0.01\rho)^2}_{1 \times 10^{-28} \text{A}^2/\text{Hz}} + \underbrace{\frac{(12n)^2}{(1M)^2}}_{1.44 \times 10^{-28} \text{A}^2/\text{Hz}}$$

Now, the sensor element dominates!

$$\therefore \frac{i_{eq,TOT}^2}{\Delta f} = 1.67 \times 10^{-25} \text{A}^2/\text{Hz} \rightarrow i_{eq,TOT} = \sqrt{\frac{i_{eq,TOT}^2}{\Delta f}} = 4.08 \times 10^{-13} \text{A}/\sqrt{\text{Hz}}$$

$$\therefore S2_{min} = \frac{i_{eq,TOT}}{A} \left(\frac{3600\pi}{hr} \right) \left(\frac{180^\circ}{\pi} \right) = \frac{4.08 \times 10^{-13}}{1.77 \times 10^{-7}} (3600) \left(\frac{180}{\pi} \right) = 0.476 (\%/\text{hr})/\sqrt{\text{Hz}}$$

And finally:

$$ARW = \frac{1}{60} S2_{min} = \frac{1}{60} (0.476) = 0.0079 \%/\sqrt{\text{hr}} = ARW \Rightarrow \text{Navigation grade!}$$