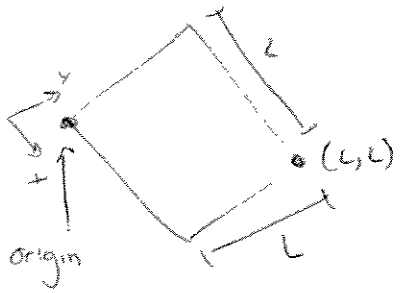


① Problem 2. (Senturia 9.7)



Fixed boundary conditions: $z(0,0) = z(0,L) = z(L,0) = z(L,L) = 0$

Removal of infinite series: Hint. $\int_0^\pi \sin ax \cdot \sin bx dx = 0 \forall a \neq b$


$$\iint_0^L \sum_{x,y} z_{x,y} \sin A_x x \sin B_y y = ? \text{ hard to solve}$$

$$\begin{aligned} & (\sin A_x x \sin B_y y) \iint_0^L \sum z_{x,y} \sin A_x x \sin B_y y \\ & = (\quad) \iint (\sin A_1 x + \dots + \sin A_n x) (\sin B_1 y + \dots + \sin B_n y) \\ & = \iint \sin^2 A_x x \sin^2 B_y y \cdot z_{x,y} \end{aligned}$$

② Domain Analogues (Senturia 5)

	Relation	Relation	Quantities		
Electrical:	$V = IR$	$Q = CV$	$(V, F, \Delta T)$	(I, \dot{x}, P)	(Q, x, Q)
Mechanical:	$F = \dot{x} b$	$x = \frac{1}{k} F$	represent effort variables	represent flow variables	is the accumulation (integral) of flow
Thermal:	$\Delta T = P \cdot R_{th}$	$Q = m c_p \Delta T$	(R, b, R_{th})	$(C, \frac{1}{k}, m c_p)$	
	resistive relation	capacitive relation	represent resistance to flow	represent capacity to store effort	

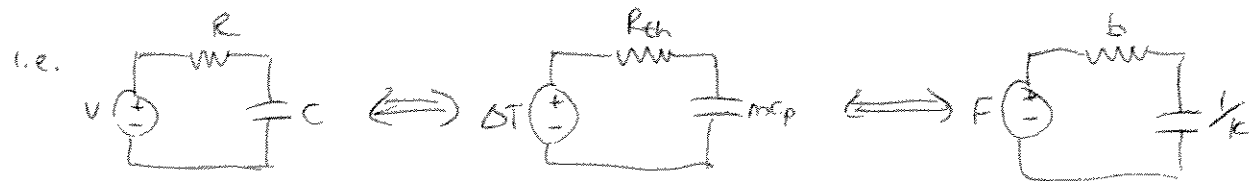So an electrical RC circuit behaves the same in response to voltage/current as a thermal circuit does to temperature/heat flow (power).



all circuits have the same time constant $\tau = RC$!


they also have the same steady state response in terms of their respective domains

For thermal circuits remember:



can use exact same circuit techniques to solve

③ Thermal circuit example

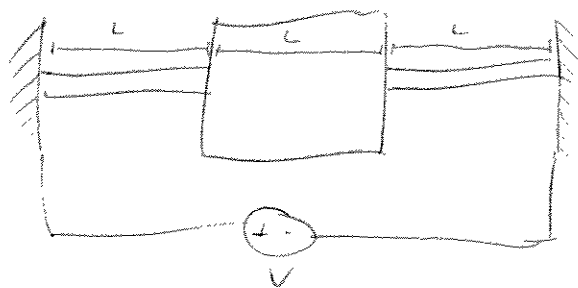


This is a multiphysical problem - need to solve in 2 domains

Important to understand.


- * This is first an electrical circuit! Directly apply V
- * Joule heating phenomenon brings into thermal domain
- * assume thermal domain does not affect electrical properties

Electrical ckt:

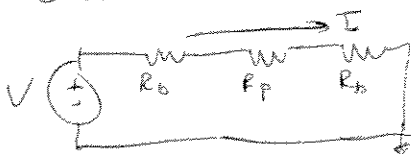


Simple enough. Given dimensions we can solve for each resistance using $R = \frac{\rho L}{A}$. Remember A is cross-sectional area NORMAL to direction of current flow. Then solve for I.

Thermal ckt:

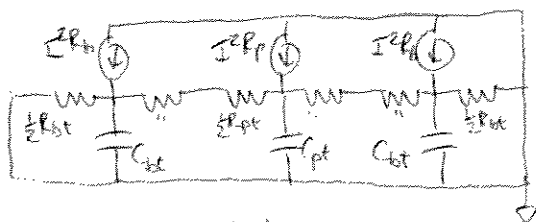

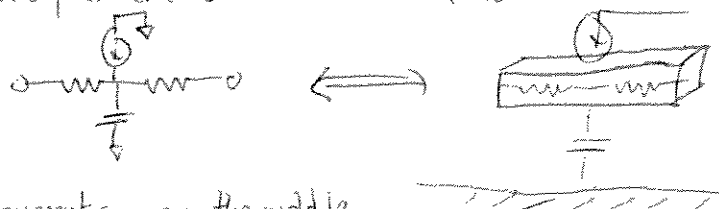Basics: Every element is modeled in thermal domain as




We place current source in the middle otherwise results look nonsensical.

(assume heating occurs throughout beam)

Simplify!


can remove \rightarrow & \leftarrow of items with large area

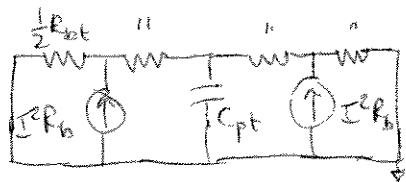can remove \parallel of items with small area



Note power sources are based on electrical resistance!

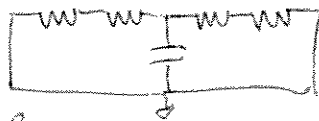Time constant: * remove current/power sources, replace with open;




* look at node (only one here) and determine R_{eq} & C_{eq}


here $R_{eq} = (\frac{1}{2}R_{bc} + \frac{1}{2}R_{bc}) \parallel (\frac{1}{2}R_{bc} + \frac{1}{2}R_{bc}) = \frac{1}{2}R_{bc}$ & $C_{eq} = C_{pt}$

$\Rightarrow \tau = \frac{1}{2}R_{bc} C_{pt}$ (check units - this should be in seconds!)

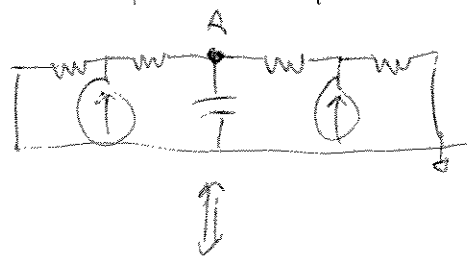(1) Steady state analysis. Proceed with Kirchoff Laws and superposition.




Want to find T_A .

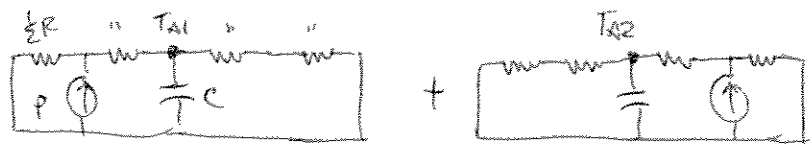

Superposition allows us to deal with one source at a time.

Can easily solve with conventional techniques.

Source 1:

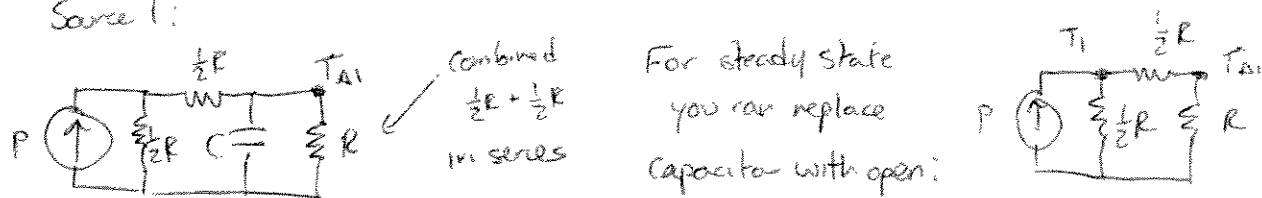

For steady state you can replace capacitor with open:

Now use voltage division to get $\frac{T_{A1}}{T_1}$, and ohm's law to get $\frac{T_1}{P}$, to get transfer function between T_{A1} & P . (Do same for P & T_{A2} , then add $T_{A1} + T_{A2} = T_A$)

$$\frac{T_{A1}}{T_1} = \frac{R}{R + \frac{1}{2}R}, \quad \frac{T_1}{P} = \frac{1}{2}R \parallel (\frac{1}{2}R + R) = \frac{3}{8}R \Rightarrow \frac{T_{A1}}{P} = \frac{1}{4}R \quad (T_{A1} = \frac{1}{4}PR)$$

So $T_A = \frac{1}{2}PR$. Does this make sense?

To first order yes - roughly half the input power will heat the plate, the other half shunts through the beams to ground.

The way we have modeled the circuit places the beams/plate at same temp!

Can fix this by DISTRIBUTING the model:

