

The following information is designed to help you get a feel for some of the sensors and electronics available for improving your tutebot.

All of the material came from Radio Shack's series of pamphlets called Engineer's Mini Notebook,

all written by Forrest M. Mims III.

The following titles were used here:


- Basic Semiconductor Circuits
- Op Amp IC Circuits
- Optoelectronics Circuits
- Sensor Projects

For more information and ideas, refer to the books themselves, as well as other books in the series.


153

LIGHT-EMITTING DIODES

THE LIGHT-EMITTING DIODE (LED) IS A SEMICONDUCTOR PN JUNCTION DIODE THAT EMITS VISIBLE LIGHT OR NEAR-INFRARED RADIATION, WHEN FORWARD BIASED. VISIBLE LEDs EMIT RELATIVELY NARROW BANDS OF GREEN, YELLOW, ORANGE, OR RED LIGHT. INFRARED DIODES EMIT IN ONE OF SEVERAL BANDS JUST BEYOND RED LIGHT. LEDs SWITCH OFF AND ON RAPIDLY, ARE VERY EFFICIENT, HAVE A VERY LONG LIFETIME, AND ARE EASY TO USE. LEDs ARE CURRENT DEPENDENT SOURCES, AND THEIR LIGHT OUTPUT IS DIRECTLY PROPORTIONAL TO THE FORWARD CURRENT.

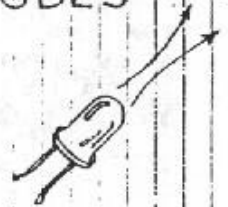


LIGHT SOURCE SPECTRA

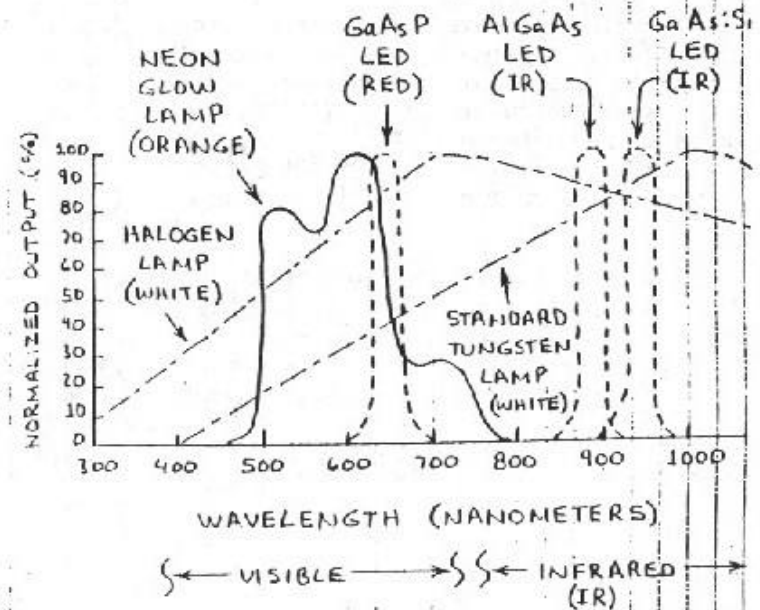

HOW TO USE LEDs

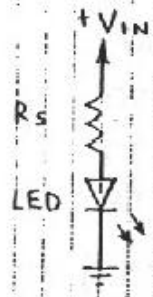USE A SERIES RESISTOR (R_s) TO LIMIT THE CURRENT THROUGH AN LED TO A SAFE VALUE.



USE THIS FORMULA TO DETERMINE THE RESISTANCE OF R_s :


$$R_s = \frac{V_{IN} + V_{LED}}{I_{LED}}$$

I_{LED} IS THE SPECIFIED FORWARD CURRENT.


V_{LED} IS THE LED VOLTAGE DROP. IT RANGES FROM ABOUT 1.3 VOLTS (940NM INFRARED EMITTERS) TO ABOUT 2.5 VOLTS (GREEN EMITTERS).

154

SAMPLE LED CIRCUIT

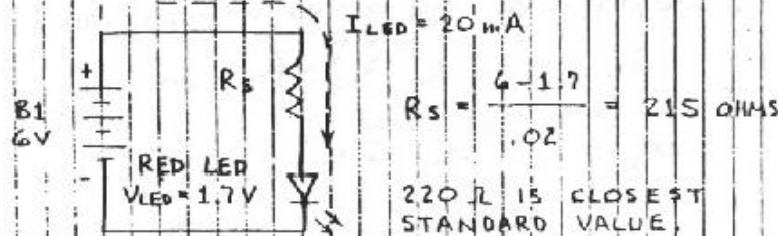


LIGHT-ACTIVATED FLASHER

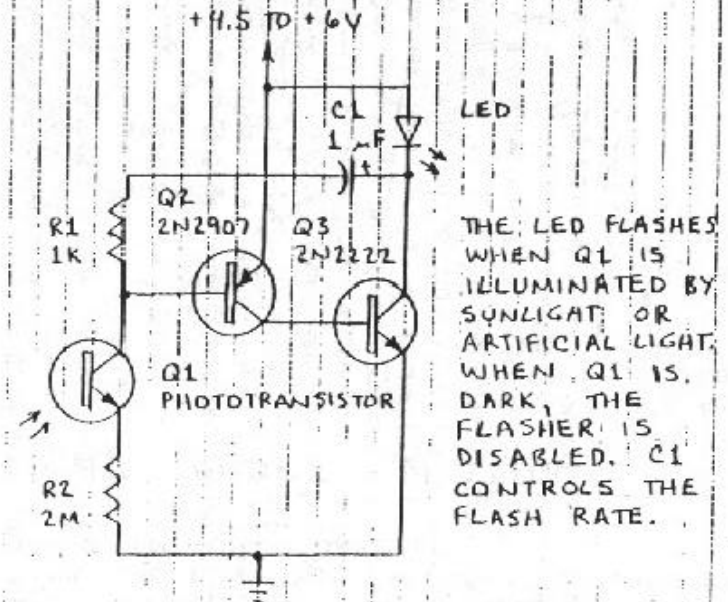

THE LED FLASHES WHEN $Q1$ IS ILLUMINATED BY SUNLIGHT OR ARTIFICIAL LIGHT. WHEN $Q1$ IS DARK, THE FLASHER IS DISABLED. $C1$ CONTROLS THE FLASH RATE.

DARK-ACTIVATED FLASHER

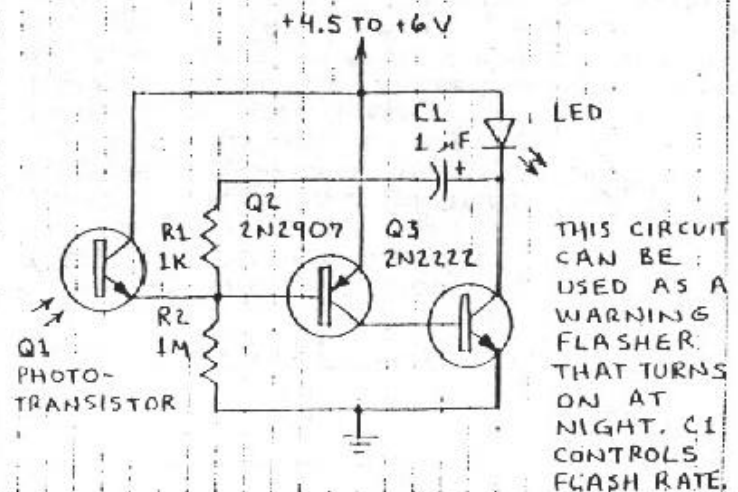

THIS CIRCUIT CAN BE USED AS A WARNING FLASHER THAT TURNS ON AT NIGHT. $C1$ CONTROLS FLASH RATE.

54

ANALOG SENSORS

MANY KINDS OF ANALOG SENSORS ARE READILY AVAILABLE. SOME OF THE MOST COMMON ARE DESCRIBED HERE.

PHOTORESISTOR

LIGHT-SENSITIVE RESISTOR WHOSE RESISTANCE CHANGES WITH LIGHT.




PHOTODIODE

LIGHT-SENSITIVE DIODE WHICH PRODUCES A CURRENT IN RESPONSE TO LIGHT.




THERMISTOR

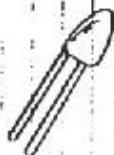TEMPERATURE-SENSITIVE RESISTOR WHOSE RESISTANCE CHANGES WITH TEMPERATURE.



MICROPHONE

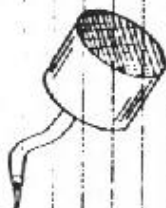SOUND-SENSITIVE SENSOR WHICH PRODUCES A VOLTAGE OR CHANGES A CAPACITANCE AS THE SOUND LEVEL CHANGES.




PIEZOELECTRIC

VARIOUS CRYSTALS OR CERAMICS WHICH PRODUCE A VOLTAGE WHEN BENT, VIBRATED OR SUBJECTED TO MECHANICAL SHOCK.




BASIC SENSOR CIRCUITS

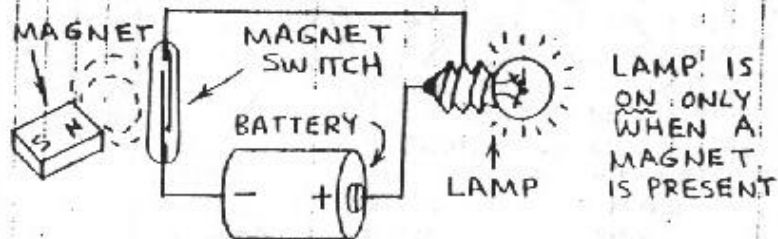
ELECTRONIC SENSORS REQUIRE A DEVICE THAT INDICATES WHEN SOMETHING HAS BEEN SENSED. THE INDICATOR FOR A SIMPLE GO-NO-GO SENSOR SUCH AS A MAGNET SWITCH CAN BE A LAMP, LED OR BUZZER.



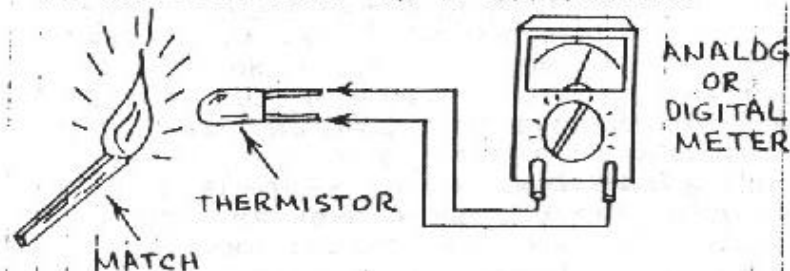THE OUTPUT DEVICE FOR AN ANALOG SENSOR CAN BE AN ANALOG OR DIGITAL METER, AN OSCILLOSCOPE OR A COMPUTER.



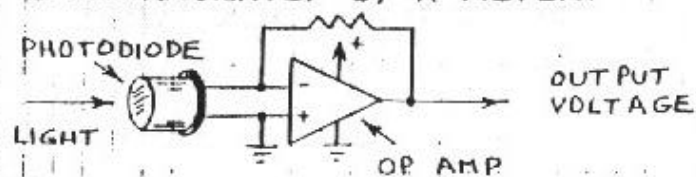MANY ANALOG SENSORS REQUIRE A CIRCUIT TO PREPARE THE SIGNAL FOR AN OUTPUT INDICATOR. AN ESPECIALLY USEFUL CIRCUIT IS THE OPERATIONAL AMPLIFIER (OP AMP). THE OP AMP CAN TRANSFORM THE TINY CURRENT FROM A PHOTODIODE INTO A VOLTAGE THAT IS EASILY INDICATED BY A METER.



LIGHT SENSORS

MANY LIGHT SENSORS ARE AVAILABLE FOR OPTOELECTRONIC PROJECTS. THE MOST COMMONLY USED SENSORS INCLUDE:

PHOTORESISTORS




THE ELECTRICAL RESISTANCE OF A DARK PHOTORESISTOR IS ORDINARILY VERY HIGH, UP TO 1,000,000 OHMS OR MORE. THE RESISTANCE MAY FALL TO AS LITTLE AS A FEW HUNDRED OHMS WHEN THE PHOTORESISTOR IS ILLUMINATED. THE MOST COMMON SEMICONDUCTOR USED TO MAKE PHOTORESISTORS IS CADMIUM SULFIDE (CdS). IT IS PRIMARILY SENSITIVE TO GREEN LIGHT. PHOTORESISTORS EXHIBIT A "MEMORY EFFECT" IN THAT THEY MAY REQUIRE A SECOND OR MORE TO RETURN TO THEIR HIGH-RESISTANCE STATE AFTER A LIGHT SOURCE IS REMOVED. THOUGH THIS SLOWS THEIR RESPONSE TIME, THEY ARE VERY

PHOTOTRANSISTORS

ALL TRANSISTORS ARE LIGHT SENSITIVE. PHOTOTRANSISTORS ARE DESIGNED TO EXPLOIT THIS PHENOMENON. THOUGH A BIPOLAR TRANSISTOR HAS THREE LEADS, A PHOTOTRANSISTOR MAY NOT HAVE A BASE LEAD. MOST PHOTOTRANSISTORS ARE NPN DEVICES WITH A BASE REGION MUCH LARGER THAN THAT OF A STANDARD NPN TRANSISTOR. THEY HAVE A RESPONSE TIME OF 1 MICROSECOND IN SOME CIRCUITS. THE DARLINGTON PHOTO TRANSISTOR INCLUDES A SECOND ON-CHIP TRANSISTOR TO AMPLIFY THE SIGNAL GENERATED BY THE PHOTO TRANSISTOR. IT GIVES MORE SENSITIVITY BUT IS SLOWER.




SENSOR SPECTRAL RESPONSE

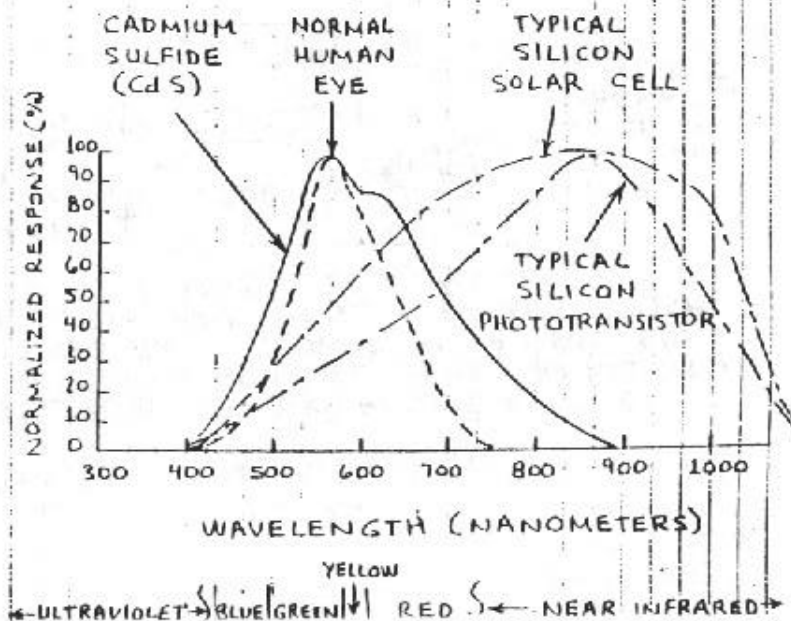


LIGHT-ACTIVATED RELAYS

PHOTORESISTOR

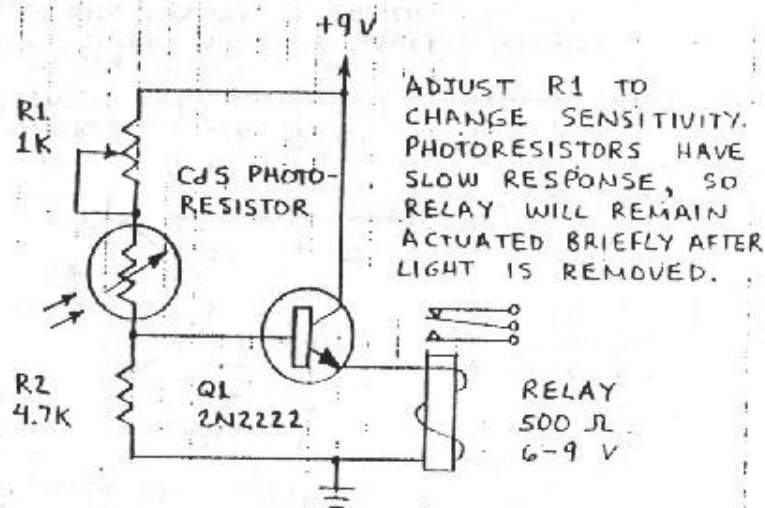


PHOTOTRANSISTOR

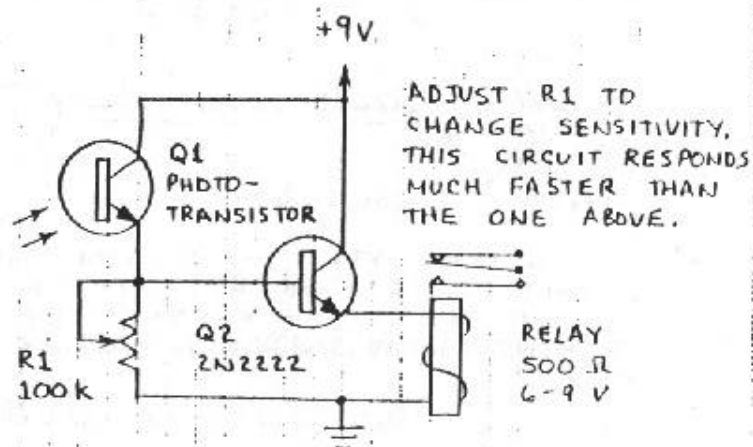


NOTE: USE LIGHT SHIELD AT DETECTOR OF BOTH CIRCUITS TO PREVENT FALSE TRIGGERING.

DARK-ACTIVATED RELAYS

PHOTORESISTOR

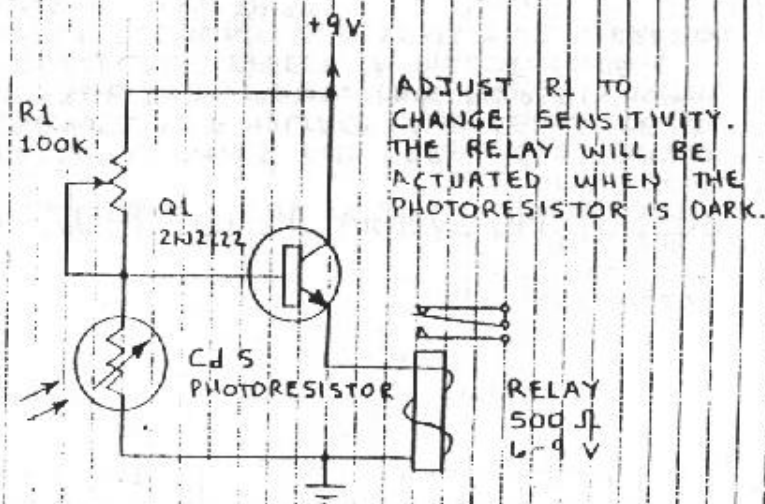


PHOTOTRANSISTOR

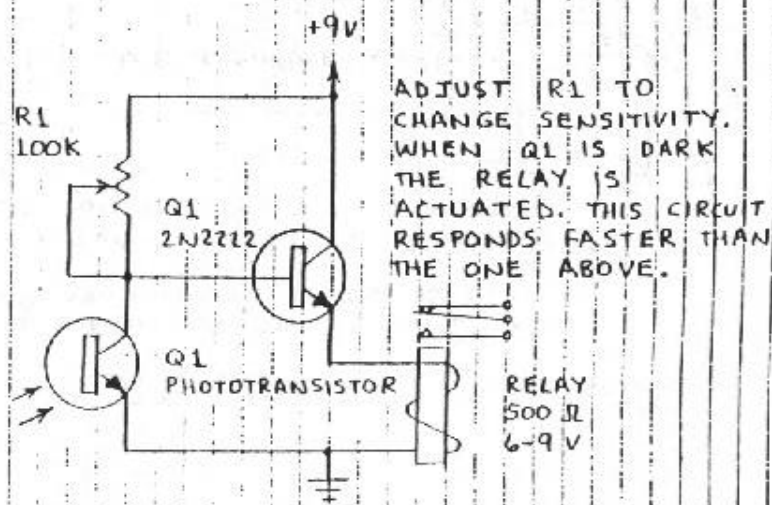


INFRARED SENSOR

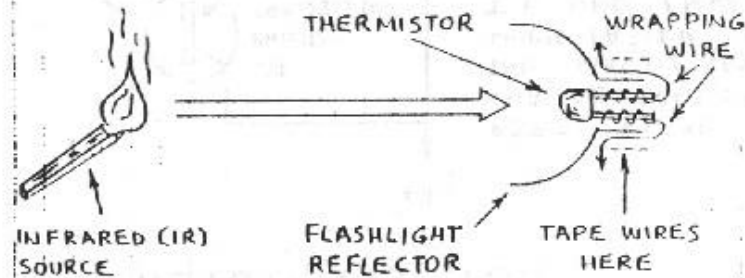A THERMISTOR IS A TEMPERATURE-SENSITIVE RESISTOR. INSTALL A THERMISTOR AT THE FOCAL POINT OF A FLASHLIGHT REFLECTOR TO DETECT INFRARED RADIATION FROM HEAT SOURCES.



INFRARED SWITCH

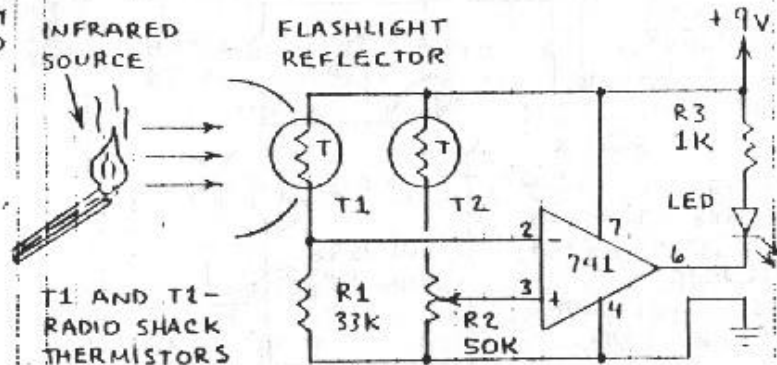


T1 AND T2 - RADIO SHACK THERMISTORS

CONNECT BATTERY AND WAIT SEVERAL SECONDS TO ALLOW THERMISTORS TO STABILIZE. ADJUST R2 UNTIL LED JUST SWITCHES OFF. PLACE YOUR HAND NEAR REFLECTOR AND LED SHOULD TURN ON. A MATCH WILL TRIGGER THE CIRCUIT FROM UP TO 1 METER (ABOUT 3 FEET) OR MORE. NOTE THAT CHANGES IN AIR TEMPERATURE CAUSE EQUAL CHANGES IN T1 AND T2. BUT AN INFRARED SOURCE AFFECTS ONLY T1. TO ADD RELAY SEE SIMILAR CIRCUITS IN THIS BOOK.


IR REMOTE CONTROL SENSOR

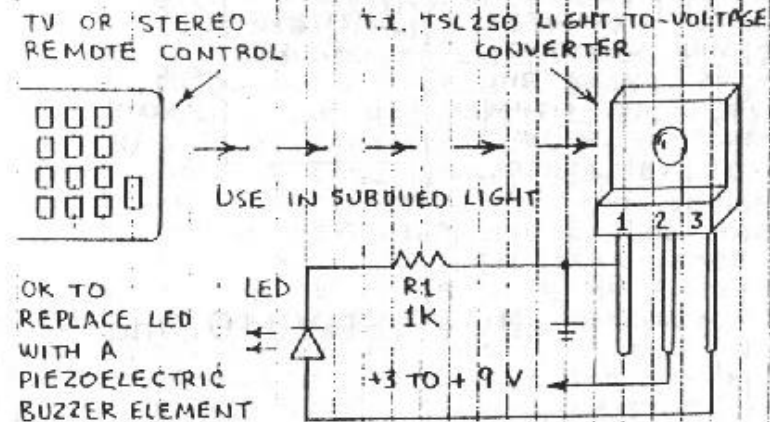LED WILL GLOW OR PULSATE IF IR REMOTE CONTROL TRANSMITTER IS TRANSMITTING.



PIEZOELECTRIC VIBRATION SENSOR

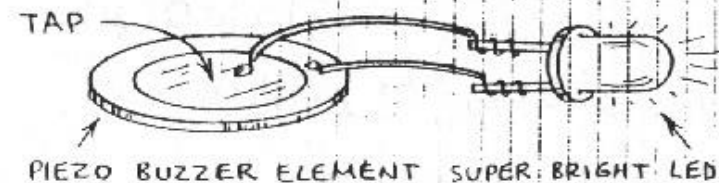CERTAIN CRYSTALS AND CERAMICS BEND IN RESPONSE TO A VOLTAGE AND GENERATE A VOLTAGE WHEN BENT. THIS PROPERTY IS THE PIEZOELECTRIC EFFECT. A PIEZOELECTRIC BUZZER ELEMENT IS A SENSITIVE VIBRATION SENSOR. TRY THIS:




TAP THE PIEZO ELEMENT WITH A PENCIL WHILE LOOKING INTO THE END OF THE LED. EACH TAP

PIEZOELECTRIC BUZZERS

PIEZO BUZZERS DELIVER EAR-PIERCING TONE AT LOW DRIVE CURRENT AND VOLTAGE.


CAUTION: USE EAR PROTECTORS WHEN EXPERIMENTING WITH PIEZO BUZZERS AT CLOSE RANGE FOR MORE THAN BRIEF INTERVALS.

BELL


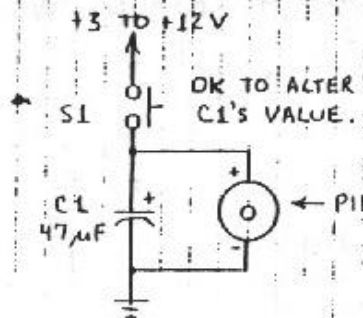


PRESS AND RELEASE S1 TO SIMULATE BELL.

VOLUME CONTROL

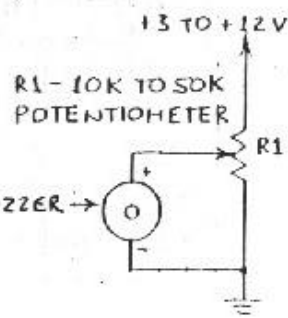


LOGIC INTERFACES

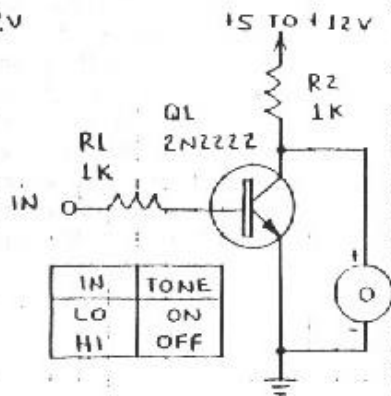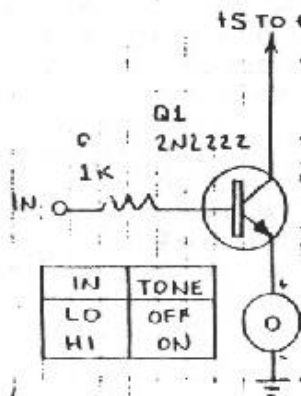


PIEZO-ELEMENT DRIVERS


FIXED TONE

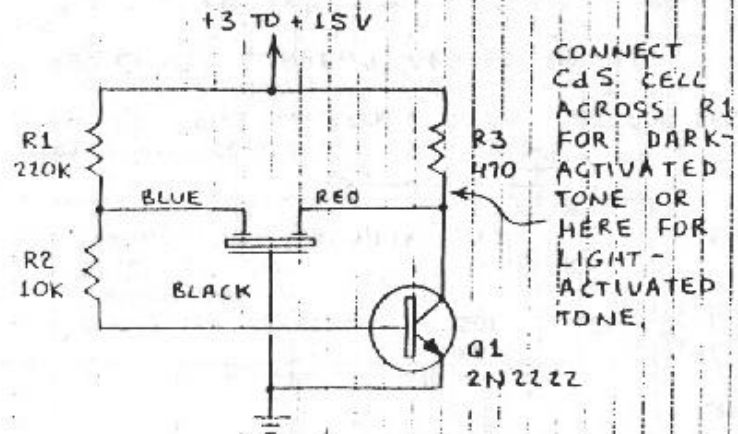

ADJUSTABLE FREQUENCY

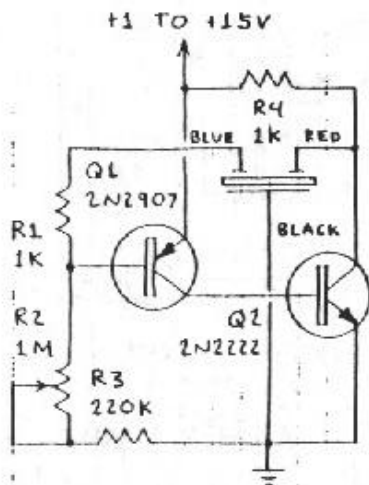

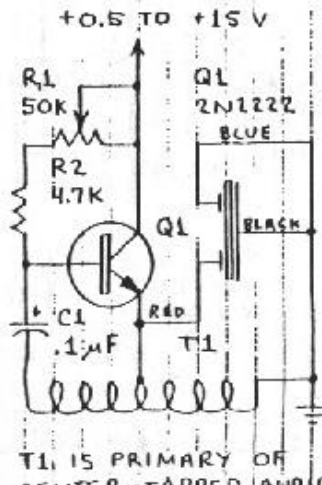
THIS CIRCUIT CAN BE EASILY MINIATURIZED. R2 CONTROLS FREQUENCY.



T1 IS PRIMARY OF CENTER-TAPPED AUDIO TRANSFORMER (RADIO SHACK 273-1380). R1 CONTROLS FREQUENCY.

HI-Z MICROPHONE PREAMPLIFIER

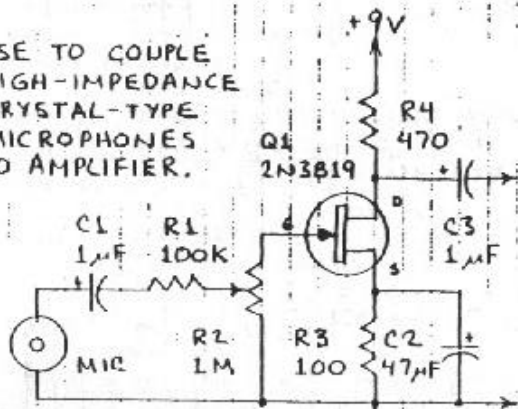USE TO COUPLE
HIGH-IMPEDANCE
CRYSTAL-TYPE
MICROPHONES
TO AMPLIFIER.




R2 IS GAIN
CONTROL.

TO
AMPLIFIER

KEEP LEADS TO MICROPHONE

AM LIGHTWAVE TRANSMITTER

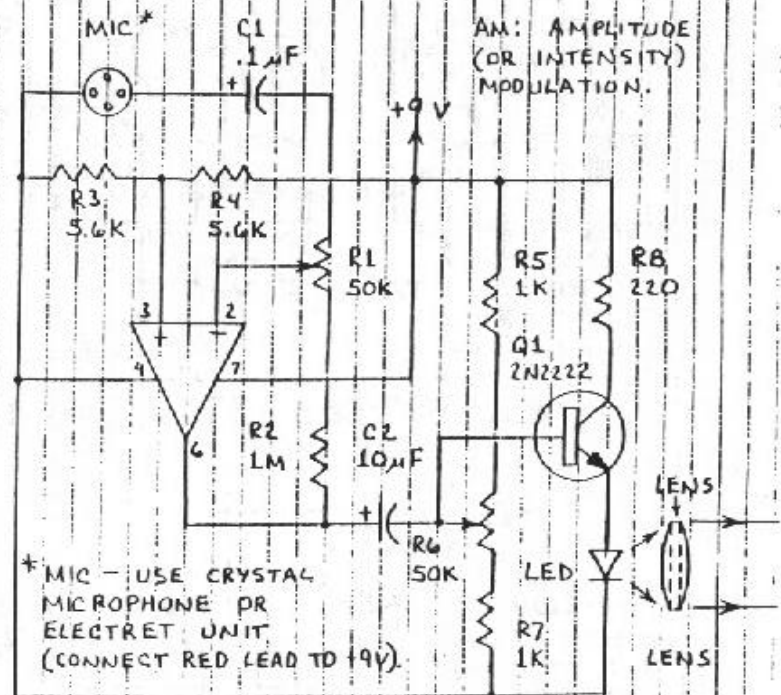

AM: AMPLITUDE
(OR INTENSITY)
MODULATION.

* MIC - USE CRYSTAL
MICROPHONE OR
ELECTRET UNIT
(CONNECT RED LEAD TO +9V).


R1 - GAIN CONTROL

R6 - LED BIAS CONTROL. ADJUST R6 FOR BEST
SOUND QUALITY.

R8 - LIMITS CURRENT APPLIED TO LED.

THE 741 AMPLIFIES VOICE SIGNALS FROM THE
MICROPHONE AND COUPLES THEM THROUGH C2
TO MODULATOR TRANSISTOR Q1. USE A HIGH-
BRIGHTNESS RED OR HIGH-POWER INFRARED
LED FOR BEST RESULTS. FOR A FREE-SPACE
RANGE OF UP TO 1,000 FEET (AT NIGHT),
USE A LENS TO COLLIMATE THE LED
BEAM. OR USE THIS CIRCUIT AS AN
OPTICAL FIBER TRANSMITTER.


SOUND-LEVEL METER

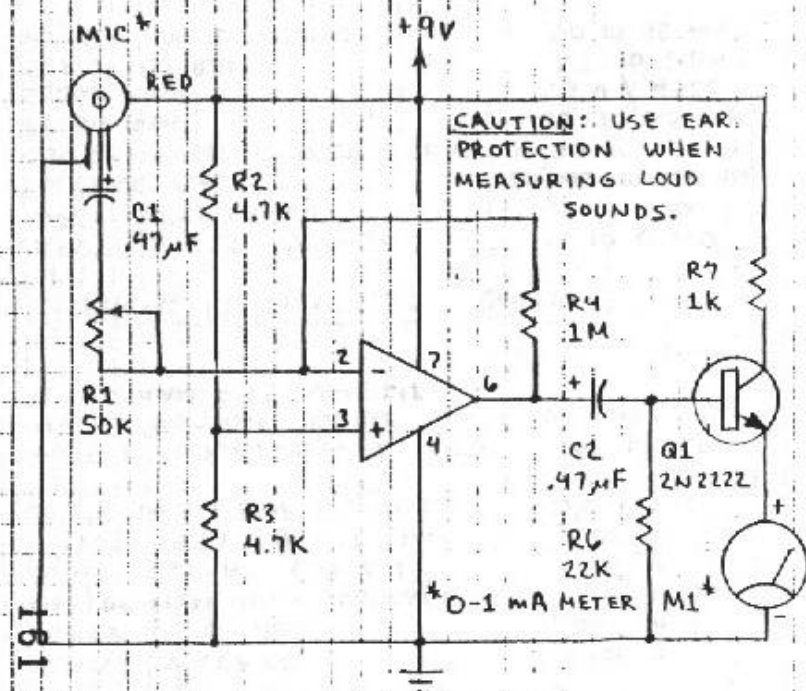

* MICROPHONE (RADIO SHACK 270-092 OR SIMILAR).

THIS SIMPLE CIRCUIT IS AN EFFECTIVE SOUND-LEVEL METER. R1 CONTROLS THE GAIN OF THE 741 OP-AMP, HENCE THE SENSITIVITY OF THE CIRCUIT. THE METER CAN BE A PANEL METER OR A MULTIMETER SET TO READ CURRENT. THE CIRCUIT WAS TESTED WITH A PIEZO "R" THAT EMITTED A 6.5 KHz TONE AT A PRESSURE OF 90dB. WHEN THE BUZZ WAS 2" FROM THE MICROPHONE AND IT WAS SET FOR MAXIMUM GAIN, THE METER INDICATED 1 mA. AT 12" THE OUTPUT FELL TO 0.4 mA. NORMAL SPEECH AT 12" GAVE FLUCTUATING SIGNAL UP TO 10 µA.

SOUND-ACTIVATED RELAY

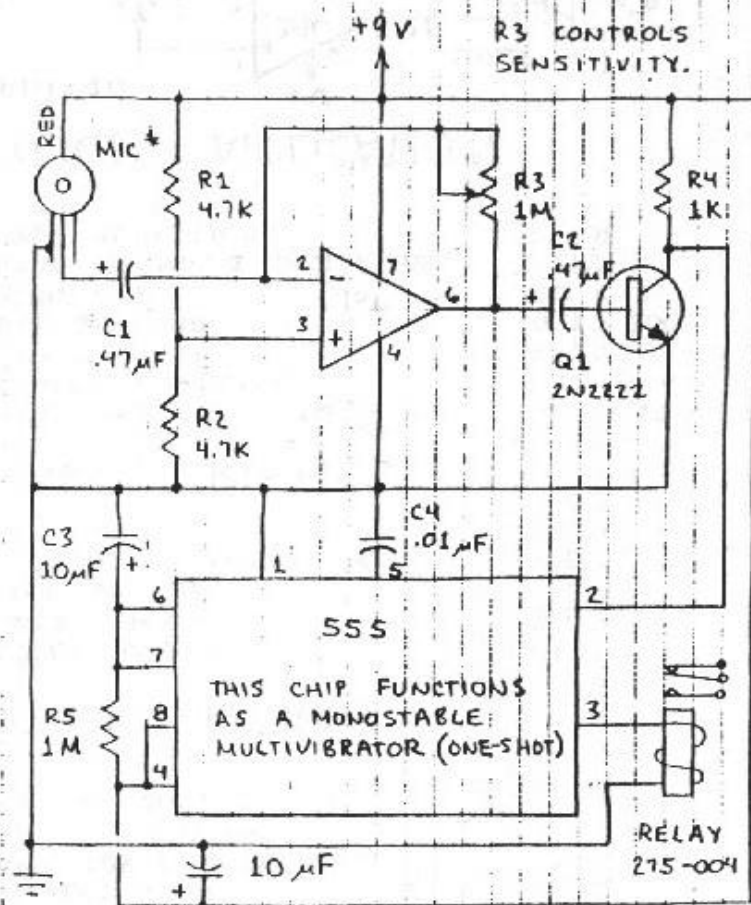

* MICROPHONE (RADIO SHACK 270-092 OR SIMILAR).

THIS CIRCUIT TRIPS RELAY IN RESPONSE TO LOUD SOUND (VOICE, CLAP, ETC.). R5 AND C3 CONTROL TIME RELAY STAYS PULLED IN (VALUES SHOWN GIVE ~12 SECONDS). IMPORTANT: USE 0.1µF CAPACITOR ACROSS POWER SUPPLY PINS OF BOTH THE 741 AND 555. REDUCE RESISTANCE OF R3 TO REDUCE SENSITIVITY.