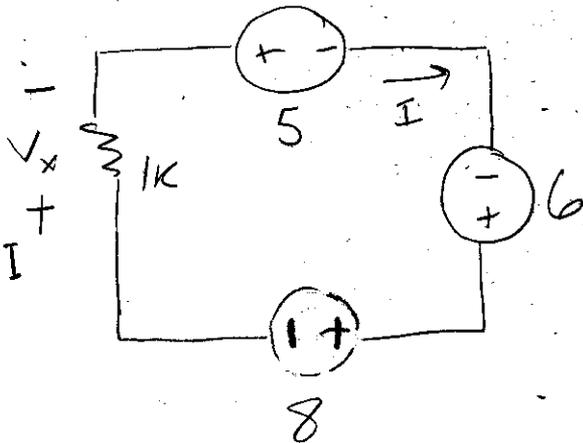


# Pradice Exam Solutions

## Problem 1:

Assign a voltage to the resistor & do KVL:

assigned in this direction so I can find I



KVL: (clockwise, starting at top)

$$5 - 6 + 8 + x = 0$$

$$x = 6 - 8 - 5 = -7 \text{ V}$$

So 
$$I = \frac{-7 \text{ V}}{1 \text{ k}} = -7 \text{ mA}$$

So positive current flows clockwise thru the circuit.


Positive current flows + to - thru 6V battery:

6V battery is charging (absorbing power)

Positive current flows - to + thru 5 + 8 V batteries:

5 + 8 V batteries are discharging (releasing)

## Problem 2:

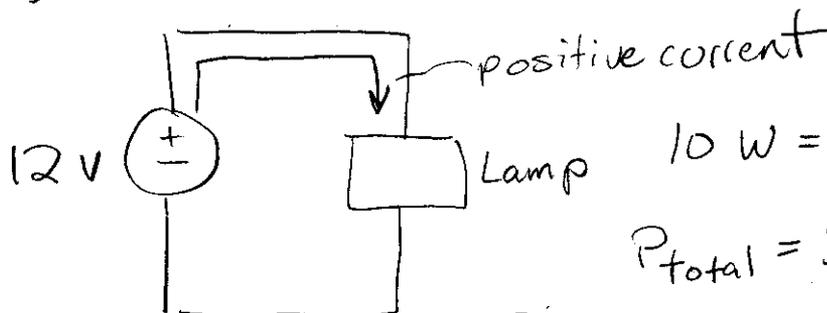


$10 \text{ W} = 0.28 P_{\text{total}}$  (total power absorbed by lamp)

$$P_{\text{total}} = 35.7 \text{ W}$$


$$P_{\text{total}} = VI \quad I = \frac{P_{\text{total}}}{V} = \frac{35.7}{12}$$

$I = 2.975 \text{ A}$

Problem 3:

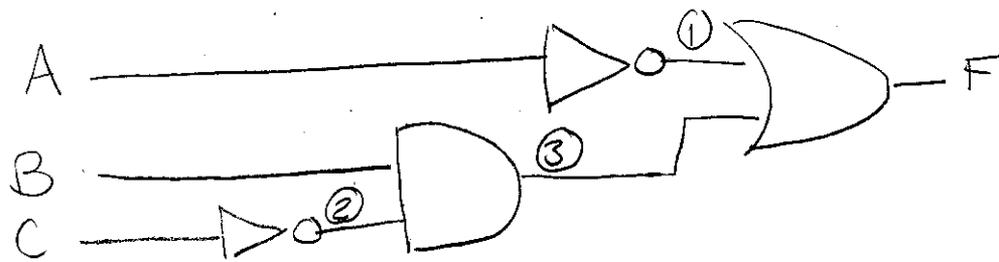


A, B, C

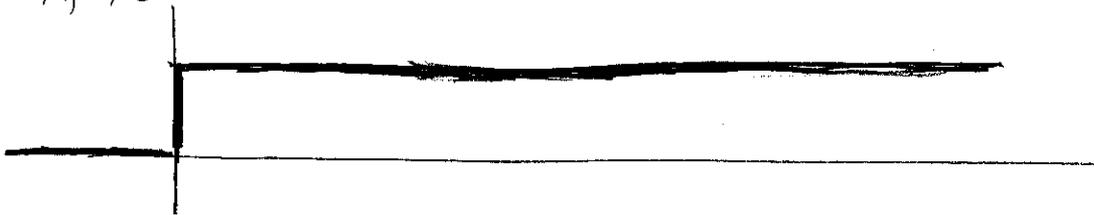


① and ② ( $\bar{A}$  and  $\bar{C}$ ) have the same graph:





③ ( $B\bar{C}$ )

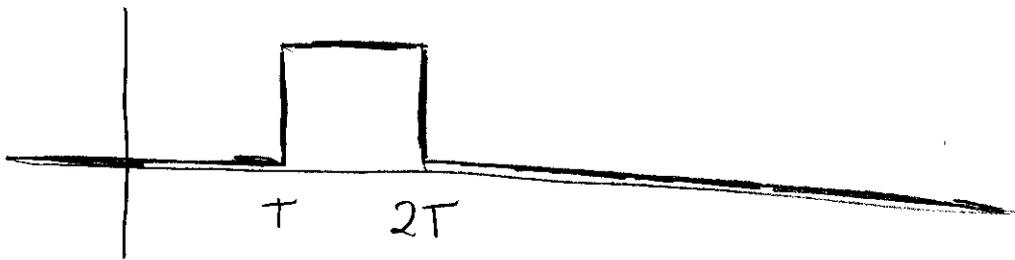


F ( $\bar{A} + B\bar{C}$ )

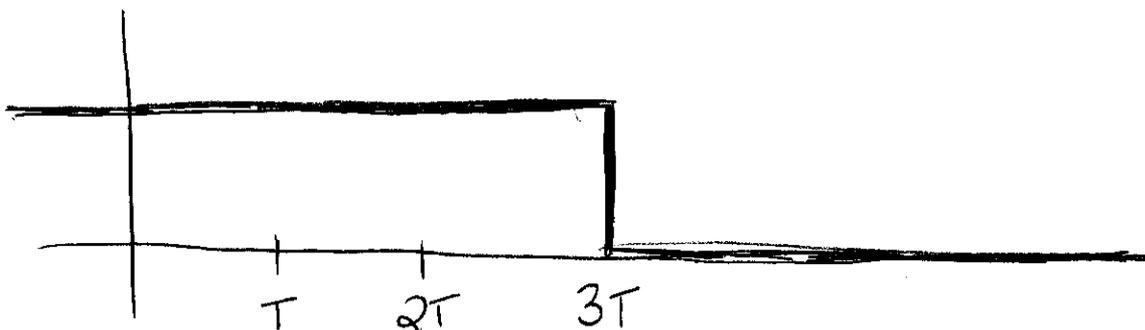


### Problem 4:

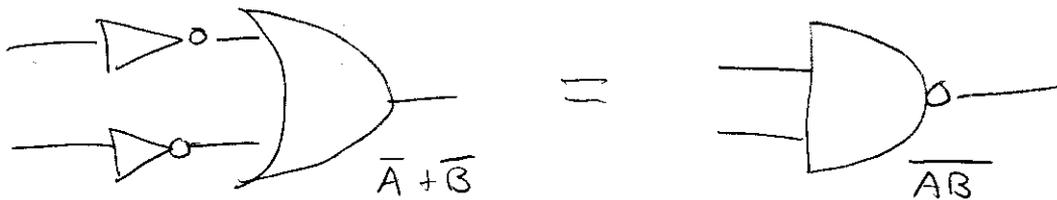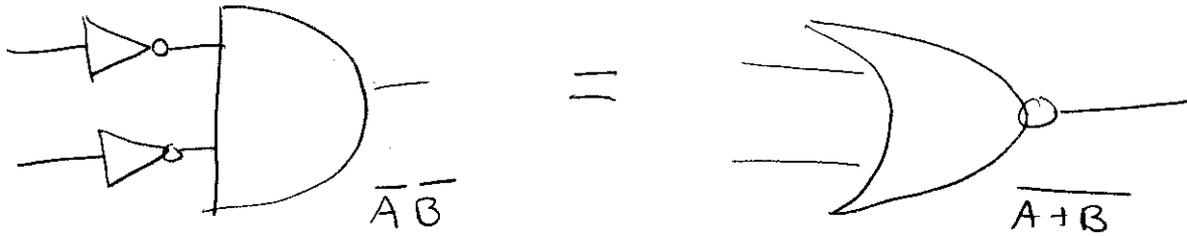

Both are consequences of DeMorgan's Law.

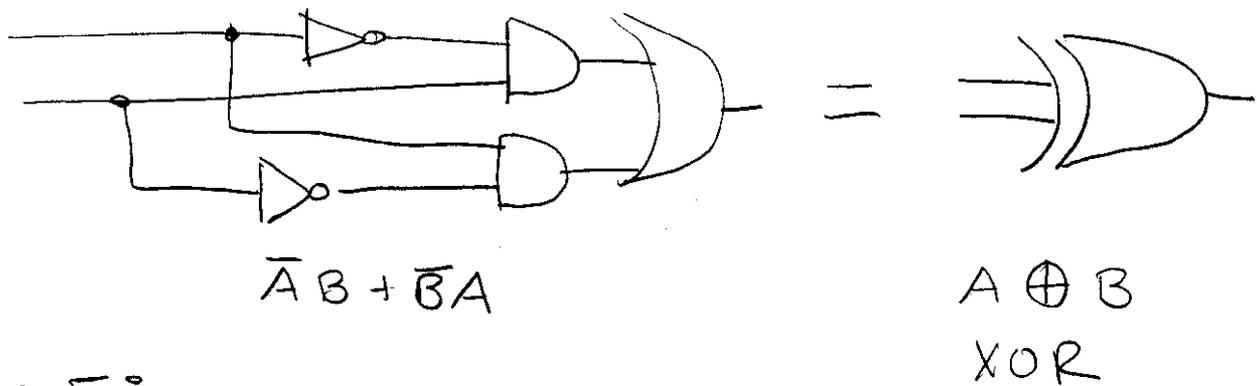

### Problem 5:

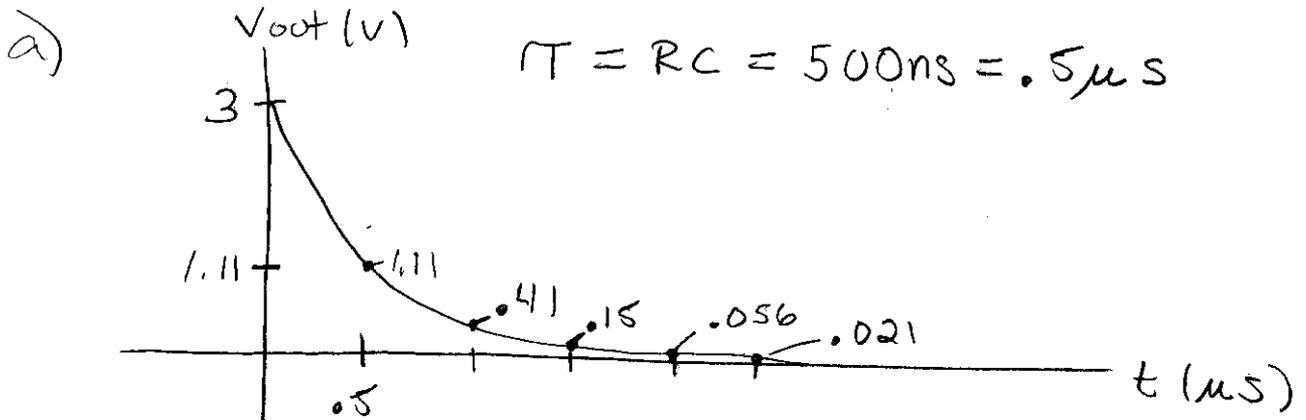

b)

$$V_{out}(t) = V_{in} + (V_{out}(t=0) - V_{in}) e^{-t/\tau}$$

$$= 3 e^{-t/500 \text{ ns}} \text{ V}$$

c) 2 ways:  $i(t) = C \frac{dV_{out}}{dt}$  or

$$i(t) = \frac{V_R(t)}{R} = \frac{V_{in} - V_{out}(t)}{R}$$

resistor voltage

$$i(t) = \frac{-3 e^{-t/500ns}}{10k\Omega} = -0.3 e^{-t/500ns} \text{ mA}$$

d)  $E = \int_0^\infty \underbrace{R(i(t))^2}_{P_R(t)} dt = \int_0^\infty 10 \times 10^3 (-3 \times 10^{-3} e^{-t/500ns})^2 dt$

nope I did my math right...

$$= \int_0^\infty 0.9 \times 10^{-3} e^{-t/250ns} dt$$

$$= (250 \times 10^{-9}) (0.9 \times 10^{-3}) e^{-t/250ns} \Big|_0^\infty$$

$$= (250 \times 10^{-9}) (0.9 \times 10^{-3}) = 225 \times 10^{-12} = 225 \text{ pJ}$$

e) The resistor dissipated the energy that was stored in the capacitor.

f) energy produced by capacitor =  $\frac{1}{2} C V_{out}(0)^2$   
energy at start of dissipation  
 $= \frac{1}{2} \cdot 50 \times 10^{-12} \cdot 3^2 = 225 \times 10^{-12} = 225 \text{ pJ}$   
 Same as resistor dissipated!