


EECS 40 Midterm II Review Problems

Bharathwaj Muthuswamy

1 Circuit Analysis

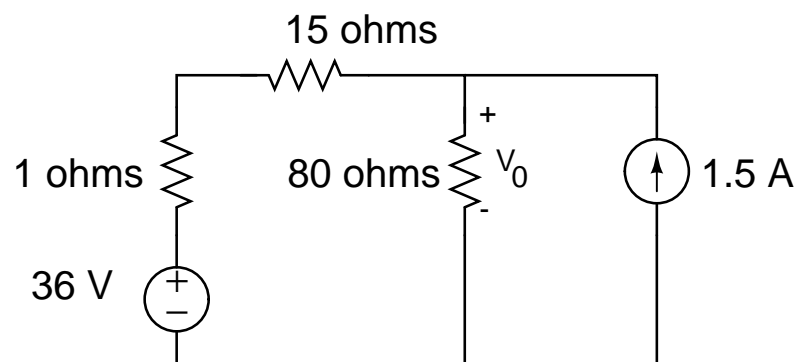
1. Warmup Problem I

Find v_0 in the circuit below using NODAL analysis.




2. Warmup Problem II

Using NODAL analysis, find v .

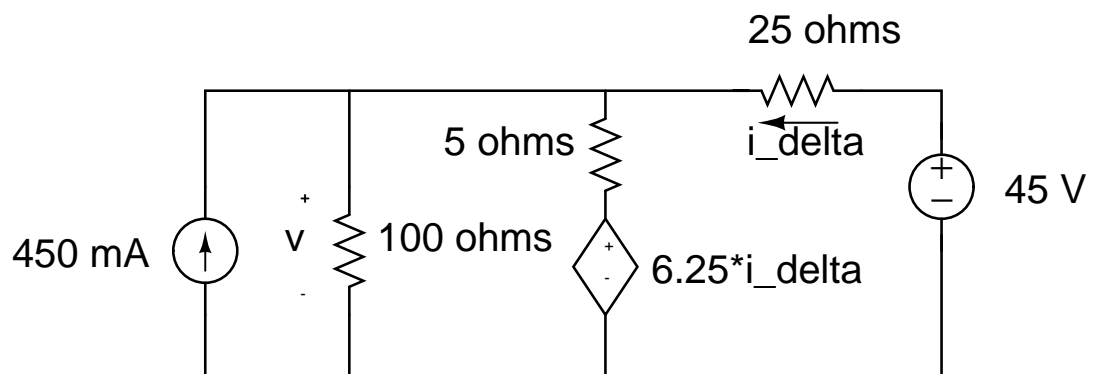

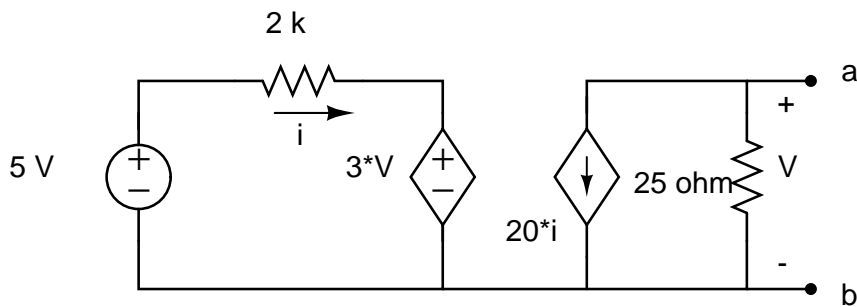3. Thevenin equivalent with dependent and independent sources


Find the thevenin equivalent of the following circuit with respect to terminals ab .



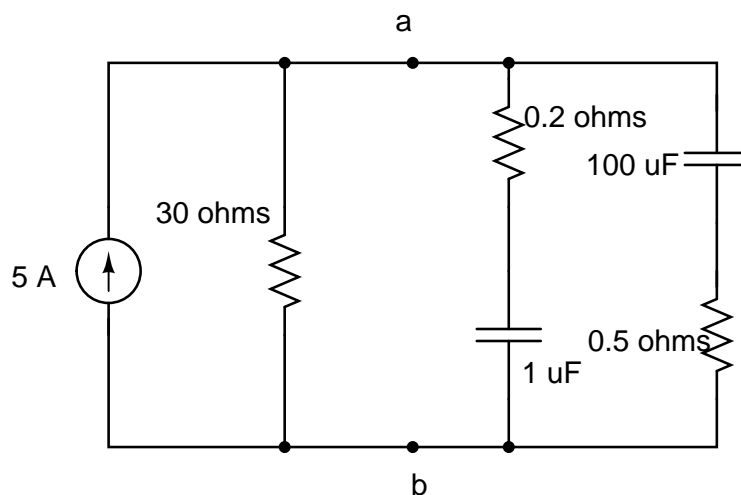4. Short circuits

After the circuit below has been in operation for a long time, good ol' Bart comes along and by "abusing his power", connects a screwdriver between terminals a and b. Assume the resistance of the screwdriver is negligible.


- Find the current in the screwdriver at $t = 0^+$ and $t \rightarrow \infty$.
- Derive the expression for the current in the screwdriver for $t \geq 0^+$.



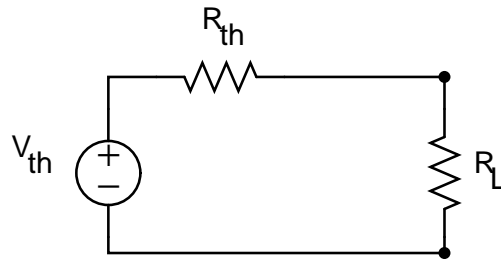5. Maximum Power Transfer Theorem

In the circuit below, find the value of R_L that maximizes the power delivered to R_L ¹.


¹Hint: Express the power delivered to R_L as a function of V_{th} , R_{th} and R_L . Then use calculus.



2 Operational Amplifiers

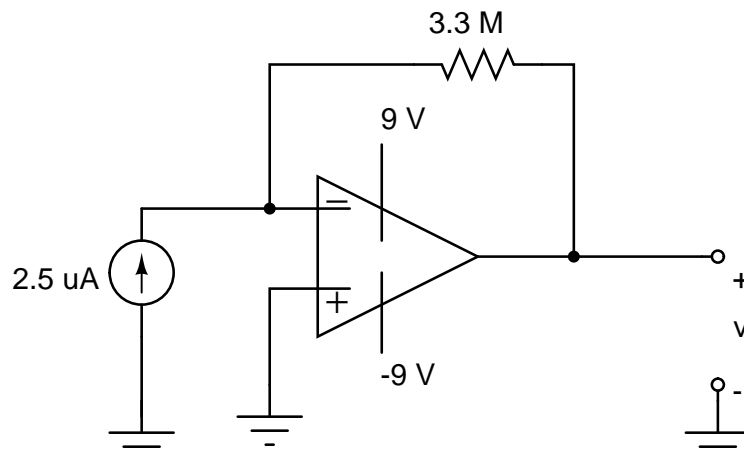
6. Warmup Problem I

In the op-amp circuit below, find v . Assume the op-amp output WILL rail, if $v \geq 9\text{ V}$ or $v \leq -9\text{ V}$.



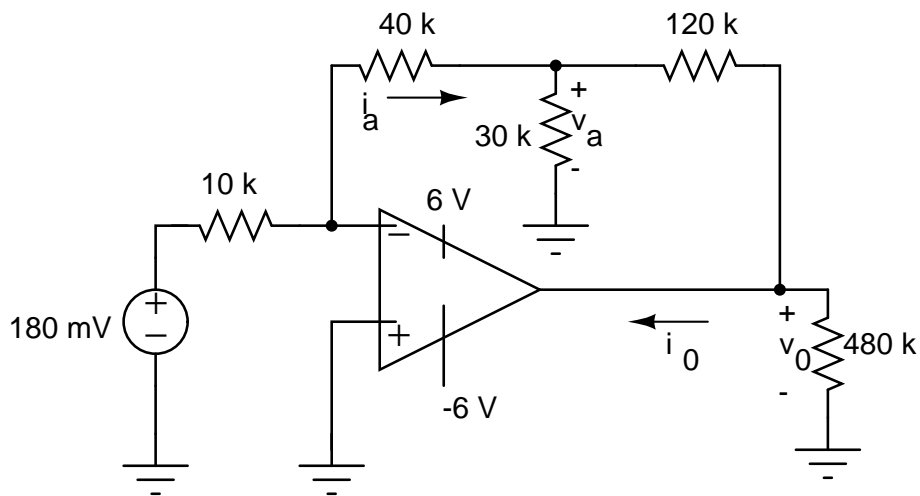
7. Warmup Problem II

In the op-amp circuit below, find v_a , v_o , i_a and i_o . Assume the op-amp output WILL rail, if $v_o \geq 6\text{ V}$ or $v_o \leq -6\text{ V}$.



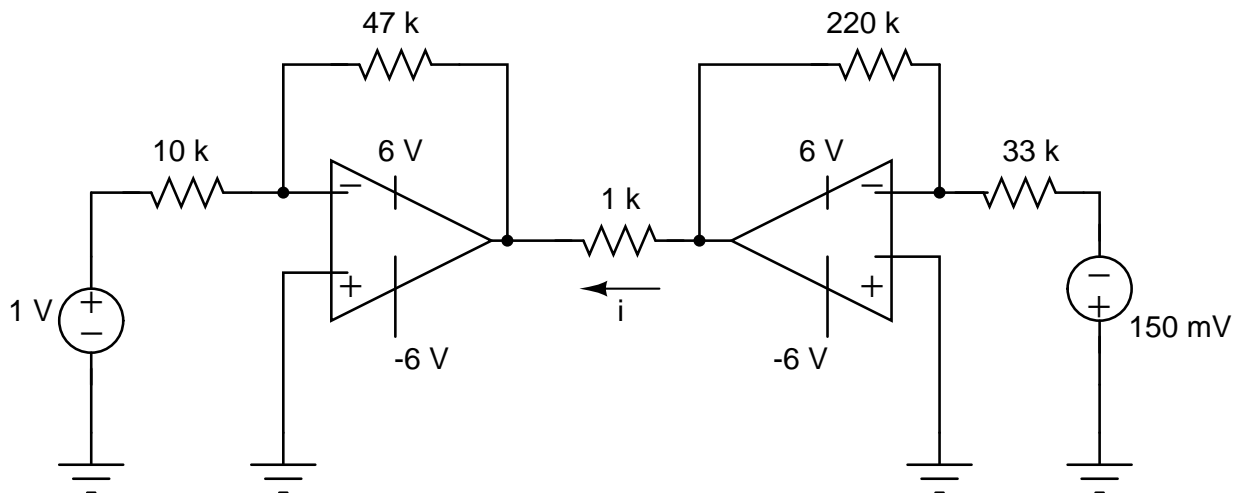8. Ohm's law


In the op-amp circuit below, find i . Assume the op-amp outputs WILL rail, if the output voltages of the two op-amps become greater than 6 V or less than -6 V.



9. Help the Batman²

The Riddler claims the circuit below will produce an output voltage that will vary between ± 9 V as V_g varies between 0 and 6 V. Assume the op-amp outputs WILL rail, if V_0 goes above 10 V or below -10 V.

²Bart's favourite superhero!

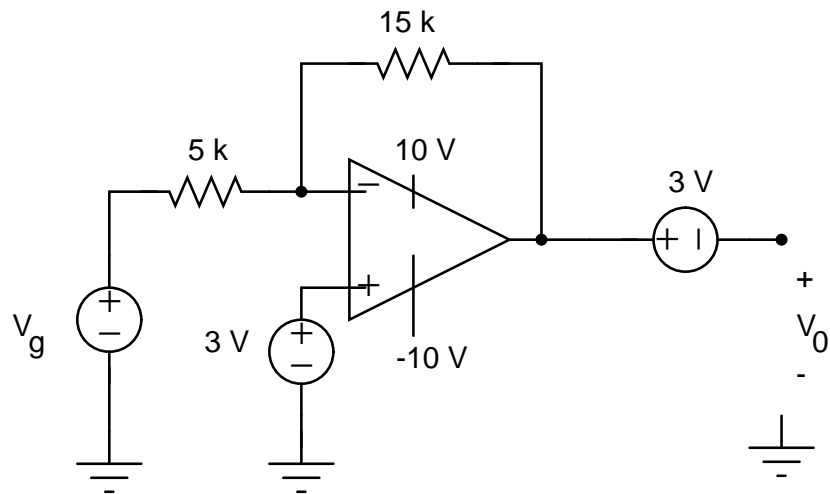

Obviously, the Dark Knight detective is called into action. Unfortunately, the Batman took EECS 40 a long time ago and his circuits knowledge is a little rusty. He doesn't have enough time to review his skills, so you get to help the Batman!

- Draw a graph of the output voltage V_0 as a function of the input voltage V_g for $0 \leq V_g \leq 6$ V.
- Should the Batman agree with the Riddler's claim? (the fate of Gotham city rests in your hands!)