

# EE 40

## Homework #5


Due October 18, 2002

Nearly all problems taken from *Electric Circuits* by Nilsson and Riedel


Notation: The extra connections coming out of the amplifier indicate the “rails”.
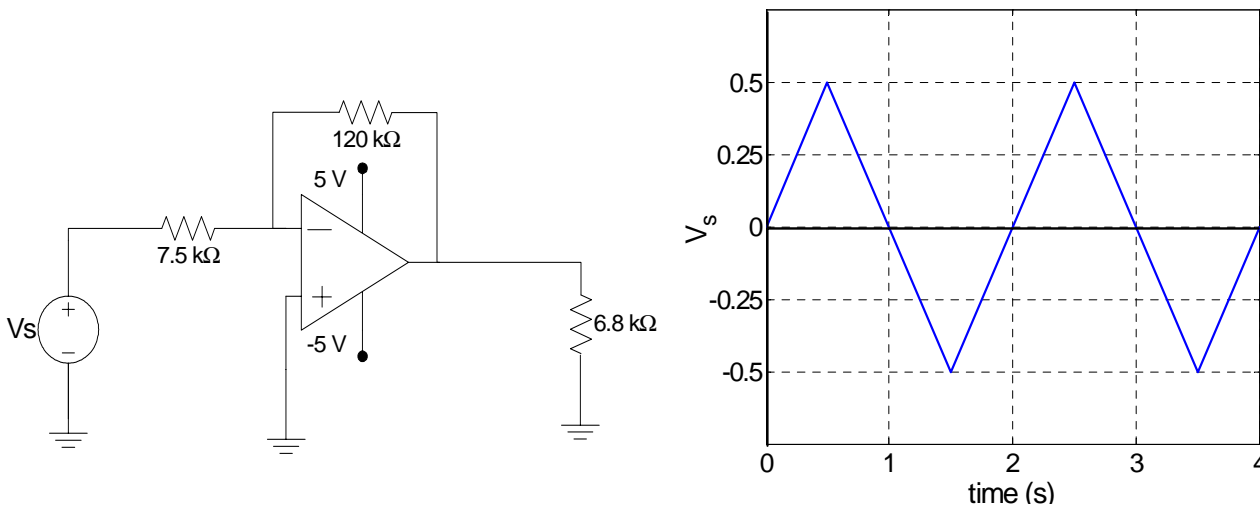
### Problem 1:

For the time-varying input voltage  $V_s$  and ideal operational amplifier circuit below, sketch  $V_O$  as a function of time.



### Problem 2:

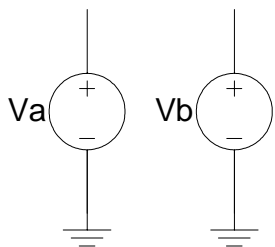


Given two input voltages  $V_a$  and  $V_b$ , which cannot be detached from ground, design an ideal operational amplifier circuit which has the average of  $V_a$  and  $V_b$  as its output voltage. Assume that the amplifier will always be operating in its linear region (i.e., ignore the rail voltages).

### Problem 3:

Assume that the ideal operational amplifier on the next page is operating in its linear region (i.e., ignore the rail voltages).


- Calculate the power delivered to the  $16\text{ k}\Omega$  resistor.
- Repeat part a) with the amplifier removed from the circuit; that is, with the  $16\text{ k}\Omega$  resistor connected in series with the voltage source and the  $64\text{ k}\Omega$  resistor.
- Find the ratio of the power found in part (a) to that found in part (b).

**Problem 3 continued:**

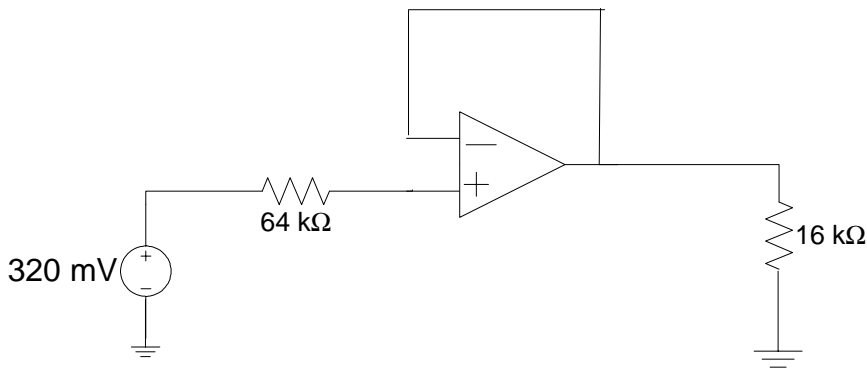


**Problem 4:**

Consider the operational amplifier circuit below, with the variable (max 50 kΩ) resistor in the feedback path. Will the amplifier operate in its linear region for all  $\alpha$  between 0 and 1? If not, for what range of  $\alpha$  does the amplifier operate linearly (i.e., not hit the rails)?

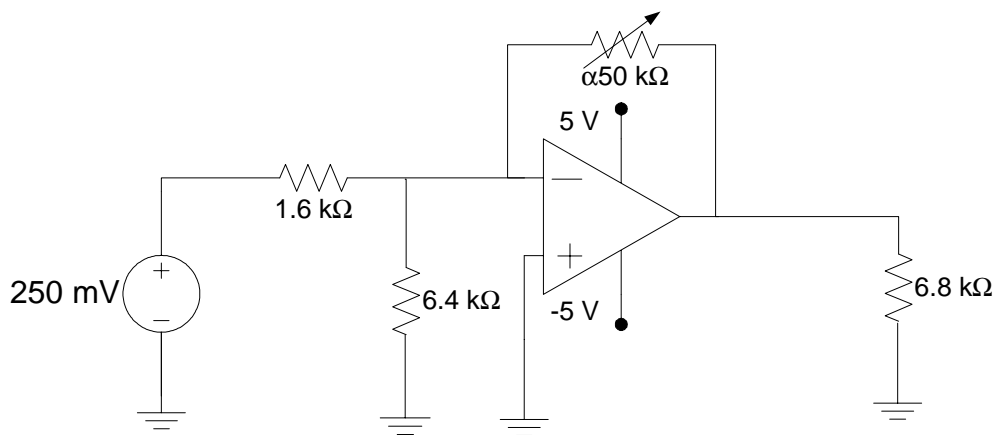

**Problem 5:**

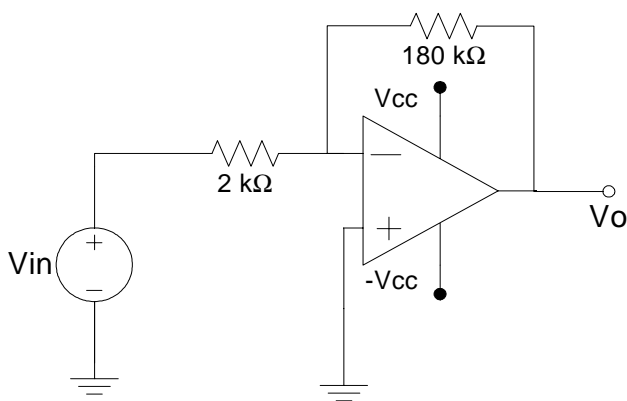

The inverting amplifier in the circuit at left has an input resistance  $R_i$  of 500 kΩ, an output resistance  $R_o$  of 5 kΩ, and an open loop gain  $A$  of 250,000. Assume that the amplifier is operating in its linear region (i.e., ignore the rails).

- a) Calculate the voltage gain  $V_o/V_{in}$ .
- b) Repeat part a) using the ideal op-amp model.