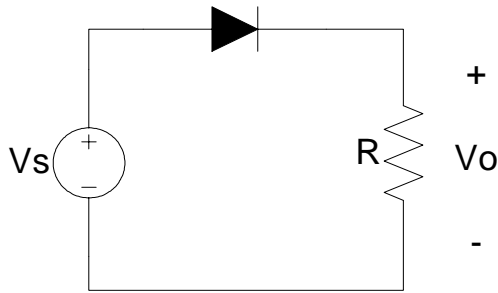


EE 40

Homework #6

Due Tuesday, November 5

Problem 1: 20 Points Possible



Let $V_s = 1\text{ V}$, $R = 1\text{ k}\Omega$.


Use the load-line method to find V_o at left.

For the nonlinear element (the diode), use the most realistic I-V relationship

$$I_D = I_0 \left(e^{\frac{qV}{kT}} - 1 \right)$$

with $I_0 = 10^{-15}$ and $kT/q = 0.026\text{ V}$.


Problem 2: 20 Points Possible

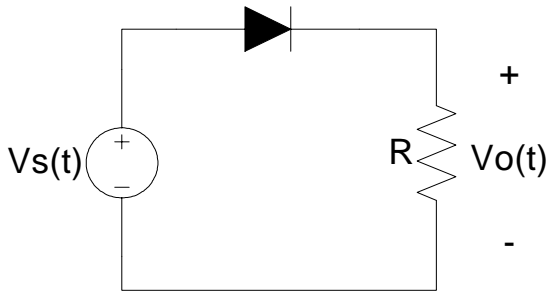

Let $V_s(t) = \sin(t)$.

- a) Sketch the output $V_o(t)$ assuming the ideal diode model.
- b) Sketch the output $V_o(t)$ assuming the large signal diode model.


Problem 3: 20 Points Possible

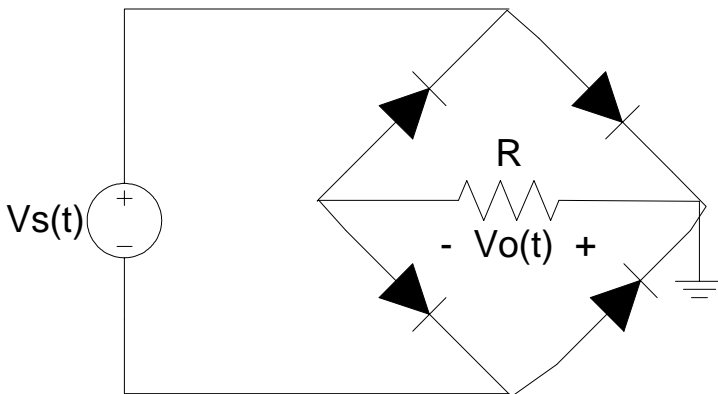

Let $V_s(t) = \sin(t)$.

- c) Sketch the output $V_o(t)$ assuming the ideal diode model.
- d) Sketch the output $V_o(t)$ assuming the large signal diode model.

Problem 4: 20 Points Possible

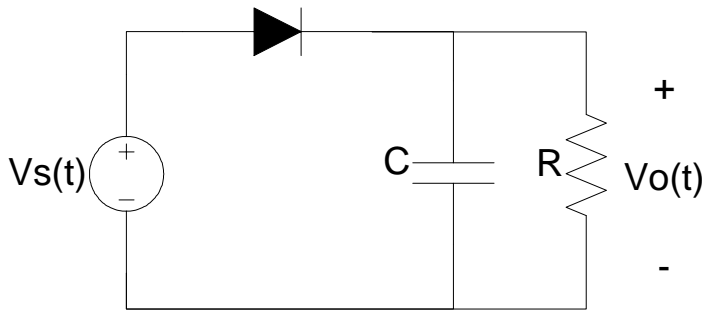


Let $V_s(t)$ be a square wave of amplitude 1, frequency 1 Hz and duty cycle 50%. This means

$$V_s(t) = \begin{cases} 1 & \text{if } \sin(2\pi t) > 0 \\ 0 & \text{if } \sin(2\pi t) = 0 \\ -1 & \text{if } \sin(2\pi t) < 0 \end{cases}$$

With $V_o(t=0)=0$, $R = 10 \text{ k}\Omega$ and $C = 50 \text{ }\mu\text{F}$, sketch $V_o(t)$ for $t = 0$ to $t = 3$ seconds.

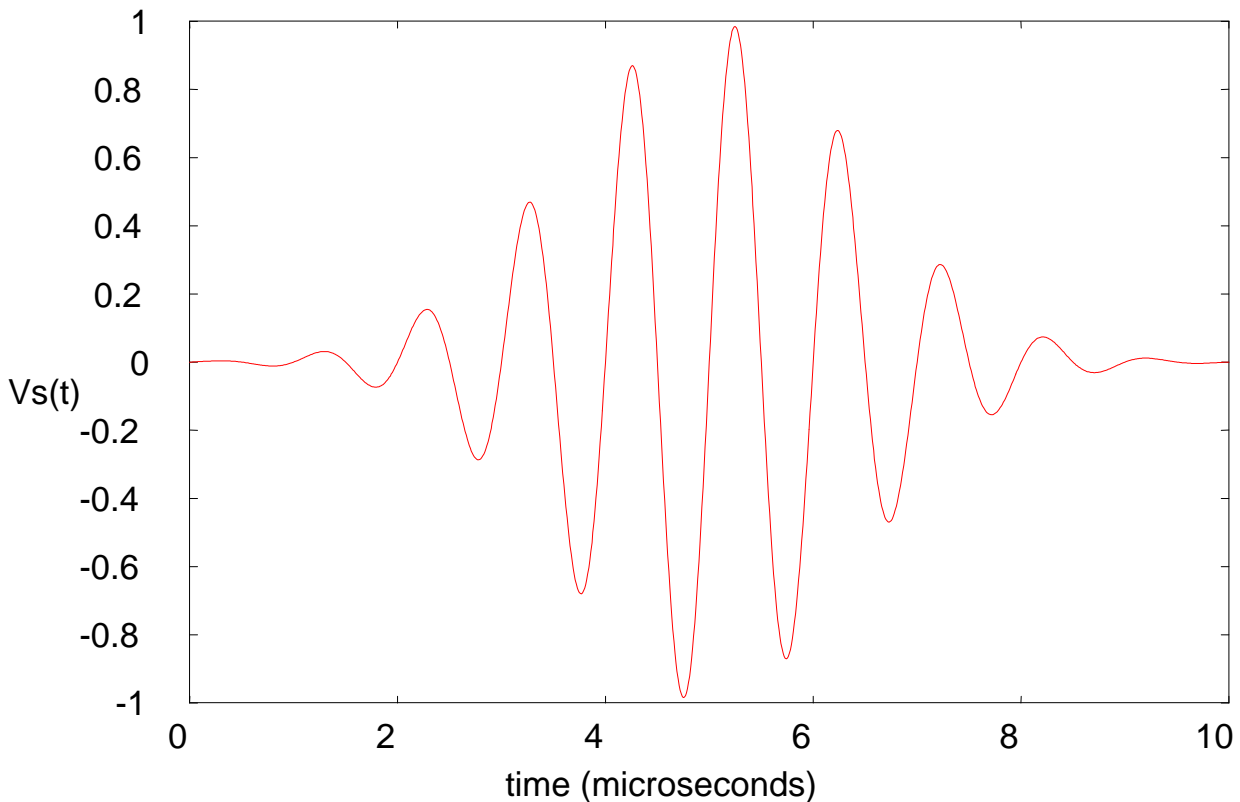Problem 5: 20 Points Possible

Suppose I want to use the circuit from Problem 4 as a **peak detector** or **envelope detector**. I want the output to trace the envelope (i. e., connect the peaks) of a typical AM signal:



- Make a **rough** sketch of the output $V_o(t)$ for the Problem 4 circuit with the above input signal when the time constant is approximately the period of the carrier signal ($1 \mu\text{s}$).
- What factors should be considered when designing the time constant of the circuit to perform this envelope detection task? What are the benefits and drawbacks of a small time constant? What are the benefits and drawbacks of a large time constant?