

EE 40

Homework #8

Due Friday, December 6, 2002 at 2 PM

Problem 1:

Consider the CMOS inverter circuit. Let V_M be the input voltage which makes V_{OUT} equal to V_{IN} . For this input voltage, both the PMOS and NMOS transistors will be in saturation mode.

Let λ equal zero for both transistors, so $I_D = I_{DSAT}$ for each transistor. With

$$I_{DSAT(N)} = \frac{W_N}{2L_N} \mu_N C_{OX} (V_{GS(N)} - V_{T(N)})^2 \quad I_{DSAT(P)} = -\frac{W_P}{2L_P} \mu_P C_{OX} (V_{GS(P)} - V_{T(P)})^2$$

$$V_{T(N)} = -V_{T(P)} = 1 \text{ V}$$

$$C_{OX} = 5 \text{ fF}/\mu\text{m}^2$$

$$L_N = L_P = 1.5 \mu\text{m}$$

$$\mu_N = 500 \text{ cm}^2/(\text{Vs})$$

$$\mu_P = 250 \text{ cm}^2/(\text{Vs})$$

$$W_P = 10 \mu\text{m}$$

find the value of W_N that will lead to $V_M = 1.5 \text{ V}$.

Problem 2:

Suppose we have connected the output of CMOS inverter 1 to the input of CMOS inverter 2, where both of the inverters have the following characteristics:

$$V_{T(N)} = -V_{T(P)} = 1 \text{ V}$$

$$L_N = L_P = 2 \mu\text{m}$$

$$W_N = 6 \mu\text{m}$$

$$\mu_N = 500 \text{ cm}^2/(\text{Vs})$$

$$\mu_P = 250 \text{ cm}^2/(\text{Vs})$$

$$W_P = 12 \mu\text{m}$$

$$t_{OX} = 10 \text{ nm (oxide thickness)}$$

$$k_{OX} = 4 \text{ (oxide dielectric constant)}$$

$$V_{DD} = 5 \text{ V}$$

$$L_I = 30 \mu\text{m (interconnect length)}$$

$$W_I = 1 \mu\text{m (interconnect width)}$$

$$C_{DB(P)} = C_{DB(N)} = 50 \text{ fF}$$

Find the propagation delay from the input of inverter 1 to the output of inverter 1 for a perfect high to low input transition.

Use W_N , L_N , W_P , L_P as the channel dimensions (for calculating I_{DSAT}) as well as the gate dimensions (for calculating C_{GB}). Let λ equal zero for all transistors.

Problem 3:

Consider a CMOS inverter with


$$R_N = 3 \text{ k}\Omega \quad C_{DB(P)} = C_{DB(N)} = C_{GB(P)} = 50 \text{ fF}$$

$$R_P = 2 \text{ k}\Omega \quad C_{GB(N)} = 75 \text{ fF}$$

The output of this inverter is connected to the input of several other identical inverters, as shown at right.

Each inverter connected at the output adds an interconnect capacitance C_i of 100 fF.

Determine the number of inverters that can be connected (the “fan-out”) if the propagation delay from the input to output of the first inverter may not exceed 20 ns.

 

Problem 4:

Consider a CMOS inverter with output connected to both inputs of a NAND gate and both inputs of a NOR gate as shown.

Using the resistance and capacitance values given in Problem 3 for the transistors, determine the propagation delay from the inverter input to inverter output for both low to high and high to low (perfect) input transitions.

