

EE 40




Homework #5

Solutions and grading

Nearly all problems taken from *Electric Circuits* by Nilsson and Riedel

Notation: The extra connections coming out of the amplifier indicate the “rails”.

Problem 1: 20 Points

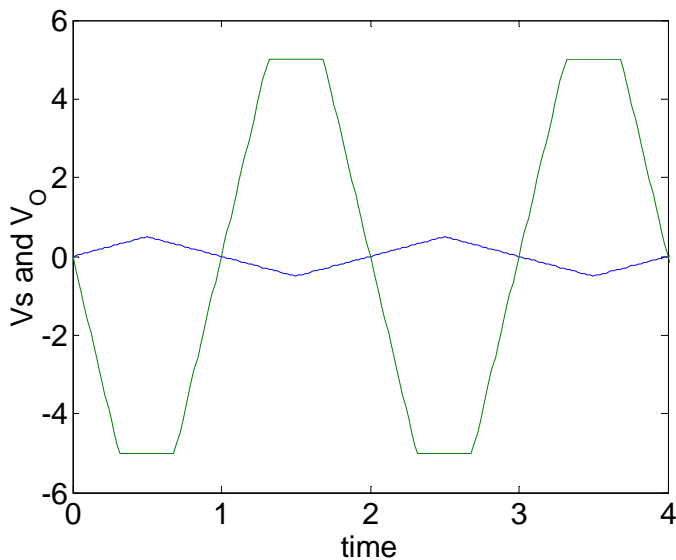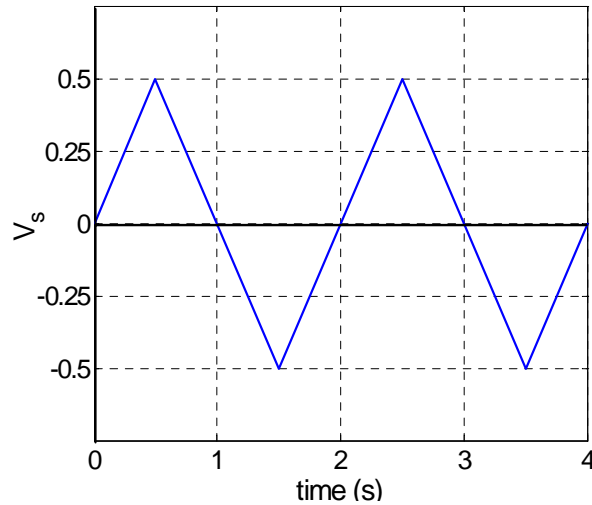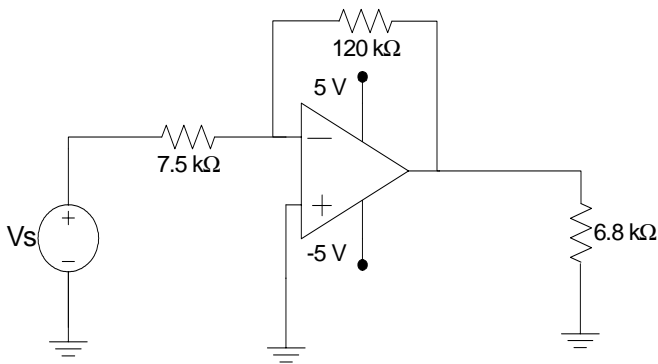

The amplifier above is an inverting amplifier.

We showed in class that the output

$V_O = -R_F/R_1 V_i$, so in this case

$V_O = -120\text{k}/7.5\text{k} V_s = -16 V_s$.

We also know that V_O cannot exceed the rail voltages. So V_O is limited to -5 to 5 V.

The amplifier will hit the rails when

$5 \text{ V} = V_O = -16 V_s$, or

$V_s = -5/16 = -0.3125 \text{ V}$. Similarly, we hit the bottom rail when $V_s = 0.3125 \text{ V}$.

From this, we can draw the graph: the input is inverted, with slope 16 in the linear regions, and we have just defined where the rails occur.


20 points for a correct graph

Subtract 5 points for wrong gain or not inverting

Subtract 10 points for ignoring rails

Minimum credit is 0 points

Problem 2: 20 Points

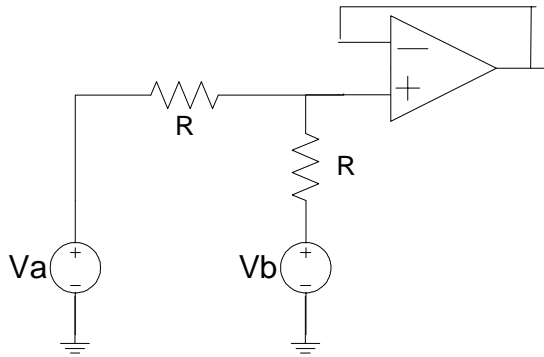

This is one of many possible answers for Problem 2.


Notice that the resistor in series with V_b carries a voltage of $(V_a - V_b)/2$.

(Why? Since there is no current going into the op-amp, the resistors are effectively in series and we perform voltage division).

The node voltage at the noninverting terminal, also known as V_p , is thus $V_p = (V_a - V_b)/2 + V_b$. Since the amplifier here is a “voltage-follower”, the output voltage is the same as V_p . Thus, $V_o = (V_a - V_b)/2$.

20 Points for ANY circuit that works (even if it does not have an op-amp, although contrary to specs!)
 10 Points for “best effort” circuit; one that may not be the right form but most analysis is correct
 Subtract 2 points for each math error
 Use judgement for other partial credit; minimum score 0 points

Problem 3: 20 Points

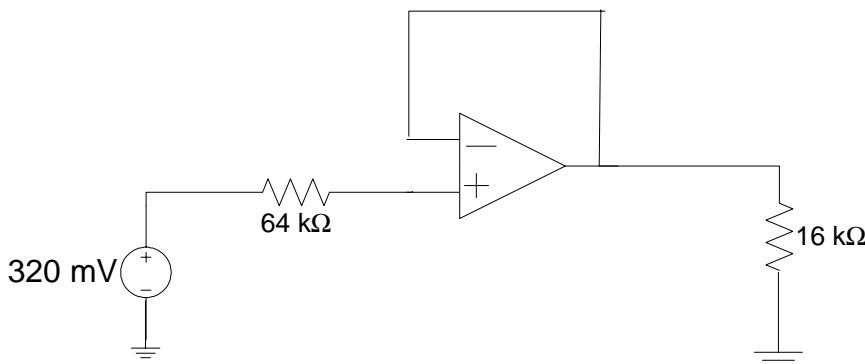

a) Since this is again a voltage-follower amplifier, the output voltage is the same as V_p . Since no current can flow into the amplifier input, the $64\text{ k}\Omega$ resistor carries no current and therefore no voltage. V_p , and thus V_o , are 320 mV .

$$P = I^2 R = V^2 / R$$

$$= (320 \times 10^{-3})^2 / (16 \times 10^3) = 6.4 \mu\text{W}$$


b) Here, by voltage division, the $16\text{ k}\Omega$ resistor will take $320\text{ mV} \frac{16\text{ k}\Omega}{16\text{ k}\Omega + 64\text{ k}\Omega} = 64\text{ mV}$.

$$P = I^2 R = V^2 / R = (64 \times 10^{-3})^2 / (16 \times 10^3) = 256\text{ nW}$$

c) $6.4 \times 10^{-6} / 256 \times 10^{-9} = 25$

10 points for part a, 5 points for part b, 5 points for part c
 Subtract 2 points for each math error
 No other partial credit

Problem 4: 20 Points

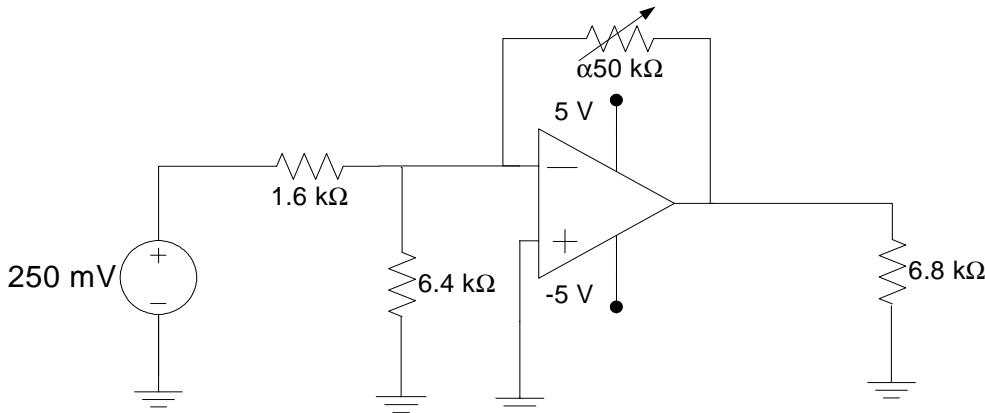

Notice that the 6.4 kW resistor carries a voltage of $V_n - V_p$, which we assume is zero. Thus, no current flows through this resistor, and the resistor has no effect on the rest of the circuit.

This leaves us with a basic inverting amplifier.

$$V_o = -R_f/R_i V_i = -(\alpha 50 \text{ k}\Omega / 1.6 \text{ k}\Omega)(250 \text{ mV}) = -\alpha 7.8125 \text{ V}$$

The bottom rail, -5 V, will be hit when $\alpha = -5 / -7.8125 = 0.64$; α can be between 0 and 0.64 .


Since this is an inverting amplifier with positive input voltage, and α must be positive (otherwise the feedback resistance will be negative), the output must always be negative. Therefore, we cannot hit the top rail of 5 V.

20 Points for correct range for α

Subtract 5 points for each significant error in analysis

Subtract 2 points for each math error, or for saying α can be negative (no negative resistance)

Problem 5: 20 Points

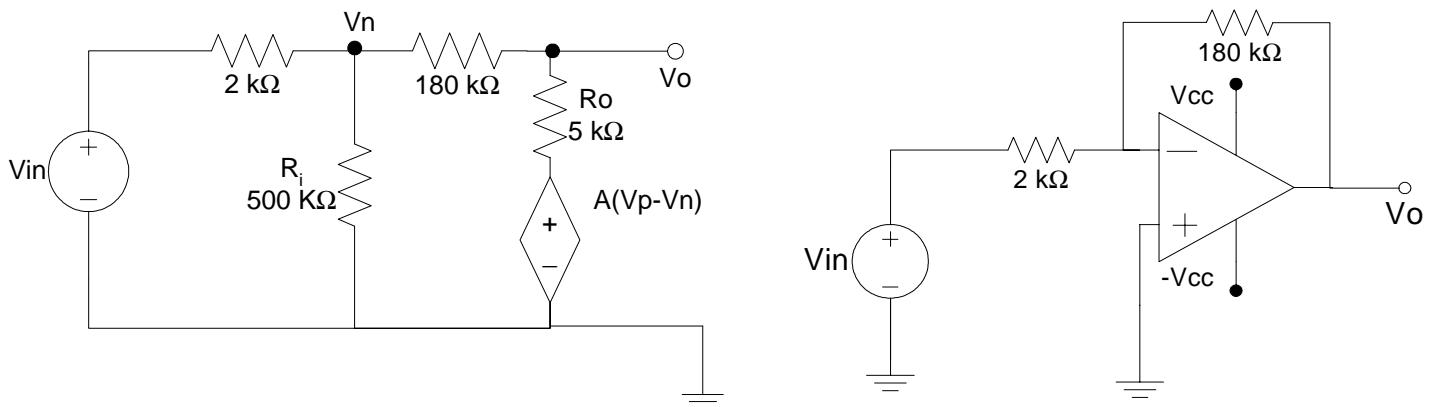

a) On the left, we see the non-ideal op-amp circuit, with the op-amp replaced by its circuit equivalent. We analyze it using nodal analysis to find V_o in terms of V_{in} . Writing equations at V_n and V_o ,

$$\frac{V_n - V_{in}}{2 \text{ k}\Omega} + \frac{V_n}{500 \text{ k}\Omega} + \frac{V_n - V_o}{180 \text{ k}\Omega} = 0 \quad \frac{V_o - V_n}{180 \text{ k}\Omega} + \frac{V_o - A(V_p - V_n)}{5 \text{ k}\Omega} = 0 \Rightarrow \frac{V_o - V_n}{180 \text{ k}\Omega} + \frac{V_o + 250,000 V_n}{5 \text{ k}\Omega} = 0$$

Manipulating the second equation, we find

$$V_n = \frac{37}{[1 - (36)(250,000)]} V_o$$

Manipulating the first equation, we find

$$V_{in} = \left(\frac{1}{250} + \frac{1}{90} + 1 \right) V_n - \frac{1}{90} V_o = \left[\left(\frac{1}{250} + \frac{1}{90} + 1 \right) \left(\frac{37}{[1 - (36)(250,000)]} \right) - \frac{1}{90} \right] V_o$$

Therefore the gain

$$\frac{V_o}{V_{in}} = \left[\left(\frac{1}{250} + \frac{1}{90} + 1 \right) \left(\frac{37}{[1 - (36)(250,000)]} \right) - \frac{1}{90} \right]^{-1} = -89.966$$

b) Using the ideal op-amp model at right, we are dealing with the usual inverting amplifier.

$$V_o = -R_f/R_1 V_{in} = -(180 \text{ k}\Omega / 2 \text{ k}\Omega) V_{in} = -90 V_{in}$$

Thus, $V_o/V_{in} = 90$ for the ideal op-amp circuit.

20 Points for correct gains (something close to -89 in part a is ok)

Subtract 5 points for each significant error (putting resistors in the wrong place, V_p-V_n upside down...)

Subtract 2 points for each math error