

Lecture #3

OUTLINE

- Power calculations
- Circuit elements
 - Voltage and current sources
 - Electrical resistance (Ohm's law)
- Kirchhoff's laws


Reading

Chapter 2

Review: Power

If an element is absorbing power (*i.e.* if $p > 0$), positive charge is flowing from higher potential to lower potential.

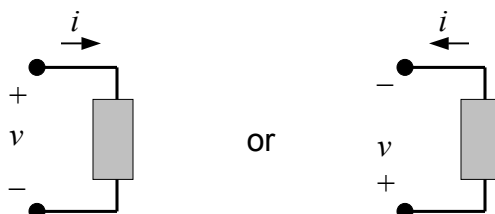$p = vi$ if the “passive sign convention” is used:




How can a circuit element absorb power?

By converting electrical energy into heat (resistors in toasters), light (light bulbs), or acoustic energy (speakers); by storing energy (charging a battery).

Power Calculation Example

Find the power absorbed by each element:

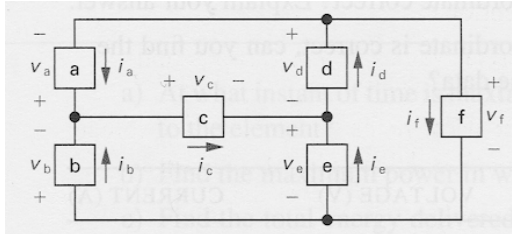

Conservation of energy
 → total power delivered
 equals
 total power absorbed

ELEMENT	VOLTAGE (V)	CURRENT (A)	v_i (W)	p (W)
a	-18	-51	918	
b	-18	45	- 810	
c	2	-6	- 12	
d	20	-20	- 400	
e	16	-14	- 224	
f	36	31	1116	

Circuit Elements

- There are 5 ideal basic circuit elements:
 - voltage source
 - current source
 - resistor
 - inductor
 - capacitor
- } **active elements**, capable of generating electric energy
 } **passive elements**, incapable of generating electric energy
- Many practical systems can be modeled with just sources and resistors
 - The basic analytical techniques for solving circuits with inductors and capacitors are the same as those for resistive circuits

Electrical Sources

- An **electrical source** is a device that is capable of converting non-electric energy to electric energy and *vice versa*.

Examples:


- battery: chemical \longleftrightarrow electric
- dynamo (generator/motor): mechanical \longleftrightarrow electric

→ Electrical sources can either deliver or absorb power


Ideal Voltage Source

- Circuit element that maintains a prescribed voltage across its terminals, **regardless of the current flowing in those terminals**.
 - Voltage is known, but current is determined by the circuit to which the source is connected.
- The voltage can be either **independent** or **dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.


Circuit symbols:

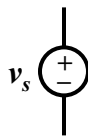

independent

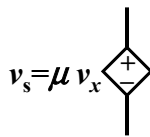

voltage-controlled

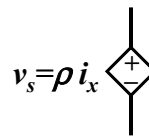


current-controlled


Ideal Current Source

- Circuit element that maintains a prescribed current through its terminals, **regardless of the voltage across those terminals**.
 - Current is known, but voltage is determined by the circuit to which the source is connected.
- The current can be either **independent or dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.


Circuit symbols:

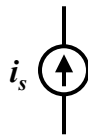

independent

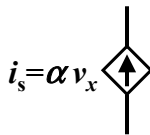

voltage-controlled

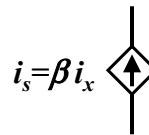

current-controlled

Electrical Resistance

- **Resistance** is the capacity of a material to impede the flow of electric charge. The circuit element used to model this behavior is the **resistor**.

Circuit symbol:



Units: Volts per Ampere \equiv ohms (Ω)

- The current flowing in the resistor is proportional to the voltage across the resistor:

$$v = i R \quad (\text{Ohm's Law})$$

where v = voltage (V), i = current (A), and R = resistance (Ω)

Electrical Conductance

- **Conductance** is the reciprocal of resistance.

Symbol: G

Units: siemens (S) or mhos (Ω)

Example:

Consider an $8\ \Omega$ resistor. *What is its conductance?*

Short Circuit and Open Circuit

Wire (“short circuit”):

- $R = 0 \rightarrow$ **no voltage difference exists**
(all points on the wire are at the same potential)
- Current can flow, as determined by the circuit

Air (“open circuit”):

- $R = \infty \rightarrow$ **no current flows**
- Voltage difference can exist,
as determined by the circuit

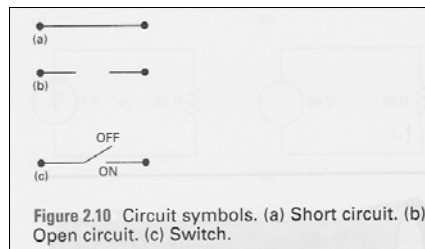


Figure 2.10 Circuit symbols. (a) Short circuit. (b) Open circuit. (c) Switch.

Circuit Nodes and Loops

- A **node** is a point where two or more circuit elements are connected.
- A **loop** is formed by tracing a closed path in a circuit through selected basic circuit elements without passing through any intermediate node more than once

Example:

Kirchhoff's Laws

- **Kirchhoff's Current Law (KCL):**
 - The algebraic sum of all the currents at any node in a circuit equals zero.
- **Kirchhoff's Voltage Law (KVL):**
 - The algebraic sum of all the voltages around any loop in a circuit equals zero.

Example: Power Absorbed by a Resistor


$$p = vi = (iR)i = i^2R$$

$$p = vi = v(v/R) = v^2/R$$

Note that $p > 0$ always, for a resistor.

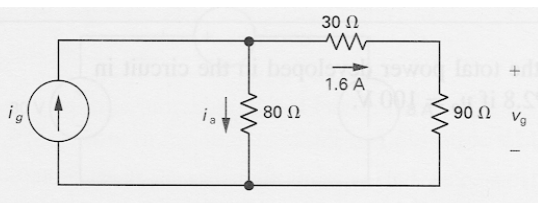Example:

- Calculate the voltage v_g and current i_a .
- Determine the power dissipated in the 80Ω resistor.



More Examples

- Are these interconnections permissible?

