

## Lecture #5

### OUTLINE


- Resistors in series
  - equivalent resistance
  - voltage-divider circuit
  - measuring current
- Resistors in parallel
  - equivalent resistance
  - current-divider circuit
  - measuring voltage
- Circuit w/ dependent source example

### Reading

Chapter 3.1-3.5

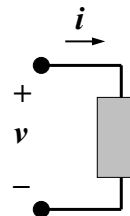
## Clarification of Terms

- If  $p > 0$ , then the circuit element is **absorbing electric power** from the rest of the circuit.  
(Power is delivered to the element.)
  - For a resistor, energy is **dissipated** in the form of heat
  - For a source, energy is stored
- If  $p < 0$ , then the circuit element is **supplying electric power** to the rest of the circuit.  
(The element is said to be **developing power** or **generating power**; this power is delivered to the rest of the circuit.)


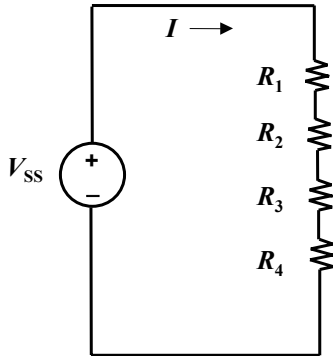
## Resistors in Series


Consider a circuit with multiple resistors connected in series. Find their “equivalent resistance”.



- KCL tells us that the same current ( $I$ ) flows through every resistor
- KVL tells us


**Equivalent resistance of resistors in series is the sum**

## Voltage Divider

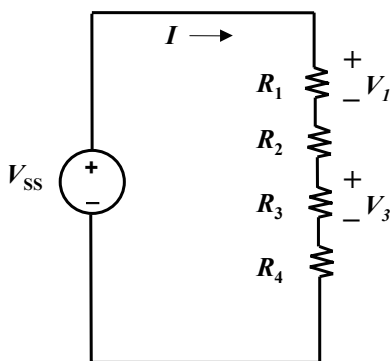


$$I = V_{SS} / (R_1 + R_2 + R_3 + R_4)$$
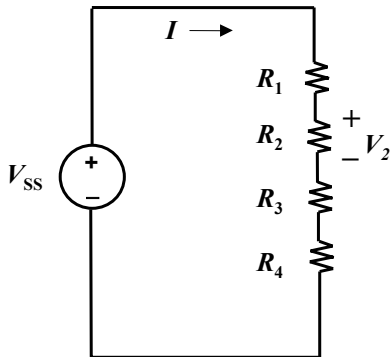
## When can the Voltage Divider Formula be Used?



$$V_2 = \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

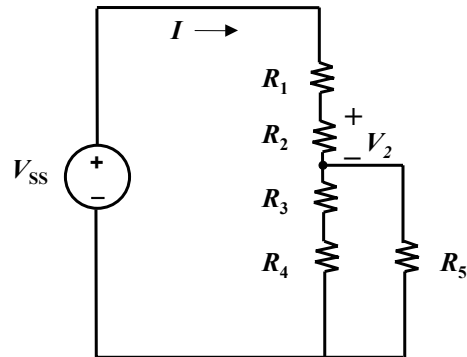Correct, if nothing else  
is connected to nodes




$$V_2 \neq \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

because  $R_5$  removes condition  
of resistors in series
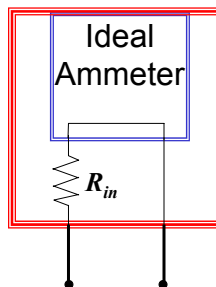
## Measuring Current

To measure the current flowing through an element in a real circuit, insert an ammeter (digital multimeter in current mode) **in series** with the element.


Ammeters are characterized by their “ammeter input resistance” ( $R_{in}$ ). Ideally, this should be very low (typical value  $1\Omega$ ).



## Effect of Ammeter


Measurement error due to non-zero input resistance:

undisturbed circuit

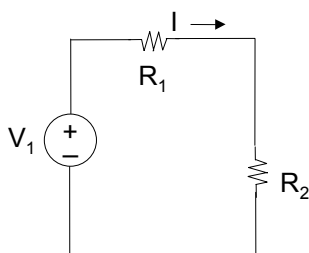

$$I = \frac{V_1}{R_1 + R_2}$$

circuit with ammeter inserted

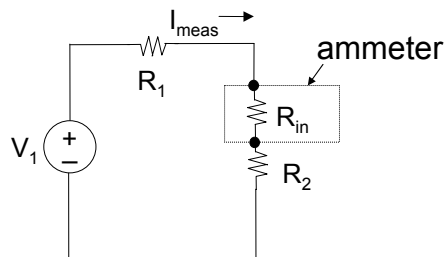


$$I_{\text{meas}} = \frac{V_1}{R_1 + R_2 + R_{\text{in}}}$$

Example:  $V_1 = 1 \text{ V}$ ,  $R_1 = R_2 = 500 \Omega$ ,  $R_{\text{in}} = 1 \Omega$

$$I = \frac{1\text{V}}{500\Omega + 500\Omega} = 1\text{mA}, \quad I_{\text{meas}} = \frac{1\text{V}}{500\Omega + 500\Omega + 1\Omega} \cong 0.999 \text{ mA}$$
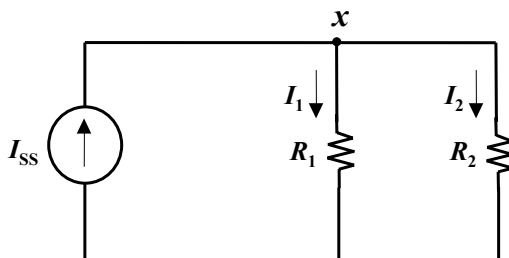
## Resistors in Parallel

Consider a circuit with two resistors connected in parallel. Find their “equivalent resistance”.




- KVL tells us that the same voltage is dropped across each resistor

$$V_x = I_1 R_1 = I_2 R_2$$

- KCL tells us

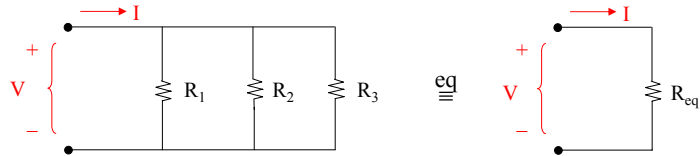
## General Formula for Parallel Resistors

What single resistance  $R_{eq}$  is equivalent to three resistors in parallel?




**Equivalent conductance of resistors in parallel is the sum**

## Current Divider

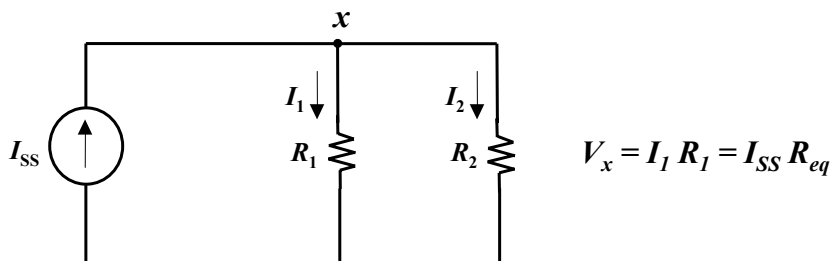
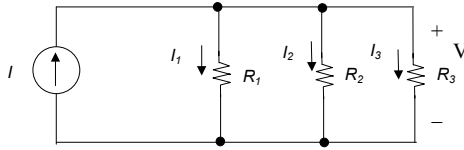
## Generalized Current Divider Formula

Consider a current divider circuit with >2 resistors in parallel:




$$V = \frac{I}{\left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2}\right) + \left(\frac{1}{R_3}\right)}$$

$$I_3 = \frac{V}{R_3} = I \left[ \frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3} \right]$$
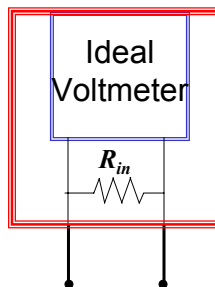
## Measuring Voltage


To measure the voltage drop across an element in a real circuit, insert a voltmeter (digital multimeter in voltage mode) **in parallel** with the element.

Voltmeters are characterized by their “voltmeter input resistance” ( $R_{in}$ ). Ideally, this should be very high (typical value 10 M $\Omega$ )




## Effect of Voltmeter

undisturbed circuit

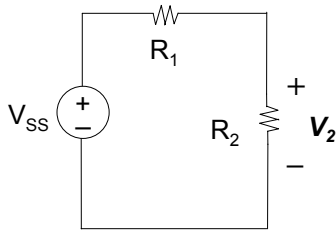

$$V_2 = V_{SS} \left[ \frac{R_2}{R_1 + R_2} \right]$$

circuit with voltmeter inserted

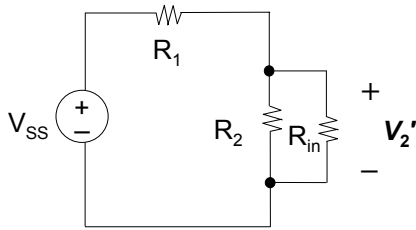


$$V'_2 = V_{SS} \left[ \frac{R_2 \parallel R_{in}}{R_2 \parallel R_{in} + R_1} \right]$$

Example:  $V_{SS} = 10\text{V}$ ,  $R_2 = 100\text{K}$ ,  $R_1 = 900\text{K} \Rightarrow V_2 = 1\text{V}$

If  $R_{in} = 10\text{M}$ ,  $V'_2 = 0.991\text{V}$ ,

## Circuit w/ Dependent Source Example


Find  $i_2$ ,  $i_1$  and  $i_o$

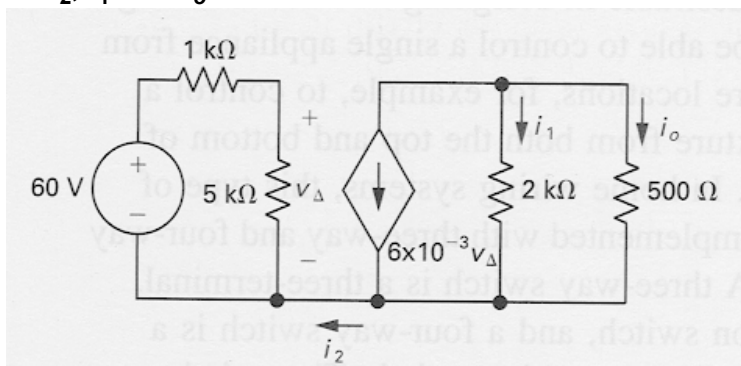

## Using Equivalent Resistances


Simplify a circuit before applying KCL and/or KVL:

Example: Find  $I$

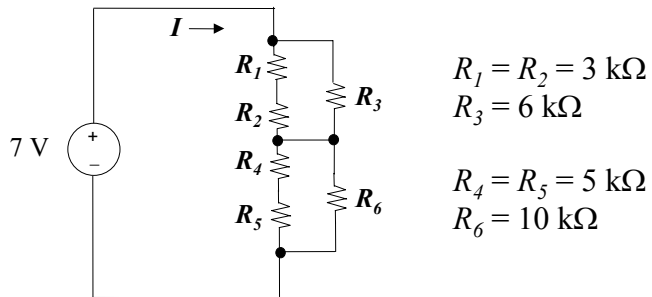
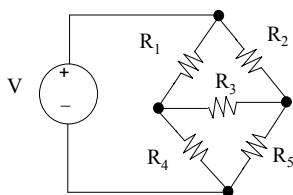
## Identifying Series and Parallel Combinations

Some circuits *must* be analyzed (not amenable to simple inspection)



Special cases:  
 $R_3 = 0$  OR  $R_3 = \infty$

