

Lecture #10 (with Prof. Neureuther)

OUTLINE

- Inverting-amplifier circuit
- Summing-amplifier circuit
- Noninverting-amplifier circuit
- Difference-amplifier circuit



Reading

Chapter 5.3-5.7



Review: Negative Feedback

- Negative feedback is used to “linearize” a high-gain differential amplifier.


Without feedback

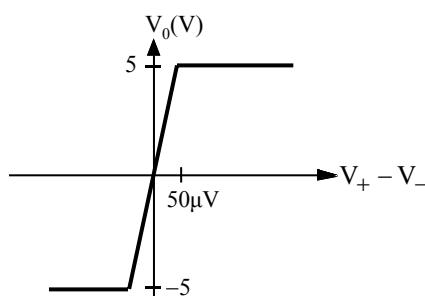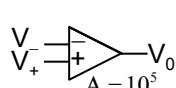

With feedback

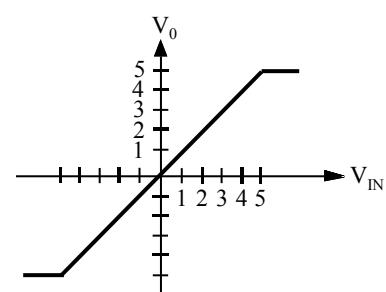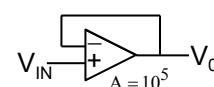

Inverting Amplifier Circuit

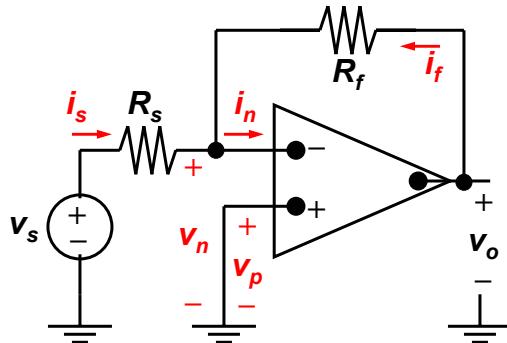

$$v_o = -\frac{R_f}{R_s} v_s$$

$$i_n = 0 \rightarrow i_s = -i_f$$

$$v_p = 0 \rightarrow v_n = 0$$

Analysis using Realistic Op Amp Model


- In the analysis on the previous slide, the op amp was assumed to be ideal, i.e.

$$R_i = \infty; A = \infty; R_o = 0$$

- In reality, an op amp has finite R_i , finite A , non-zero R_o , and usually is loaded at its output terminals with a load resistance R_L . It can be shown that

$$v_o = \frac{-A + (R_o / R_f)}{\frac{R_s}{R_f} \left(1 + A + \frac{R_o}{R_i} + \frac{R_o}{R_L} \right) + \left(1 + \frac{R_o}{R_L} \right) \left(1 + \frac{R_s}{R_i} \right) + \frac{R_o}{R_f}} v_s$$

Summing Amplifier Circuit

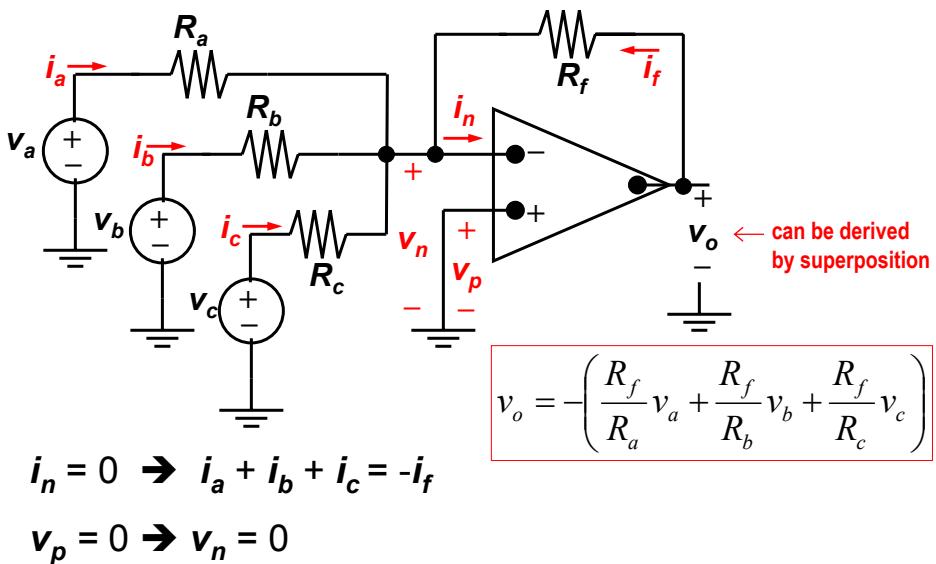

EECS40, Fall 2003


Lecture 10, Slide 5

Prof. King

Application: Digital-to-Analog Conversion

A DAC can be used to convert the digital representation of an audio signal into an analog voltage that is then used to drive speakers -- so that you can hear it!

“Weighted-adder D/A converter”

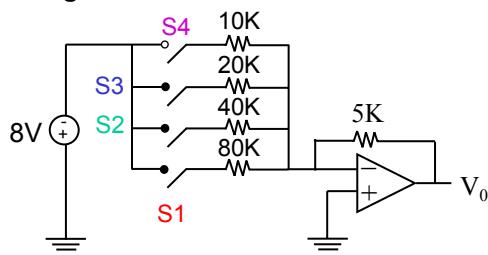

(Transistors are used
as electronic switches)


Binary number	Analog output (volts)
0 0 0 0	0
0 0 0 1	.5
0 0 1 0	1
0 0 1 1	1.5
0 1 0 0	2
0 1 0 1	2.5
0 1 1 0	3
0 1 1 1	3.5
1 0 0 0	4
1 0 0 1	4.5
1 0 1 0	5
1 0 1 1	5.5
1 1 0 0	6
S1 closed if LSB = 1	6.5
S2 " if next bit = 1	7
S3 " " " = 1	7.5
S4 " if MSB = 1	
MSB	↑
LSB	↑

EECS40, Fall 2003

Lecture 10, Slide 6

Prof. King

Characteristic of 4-Bit DAC

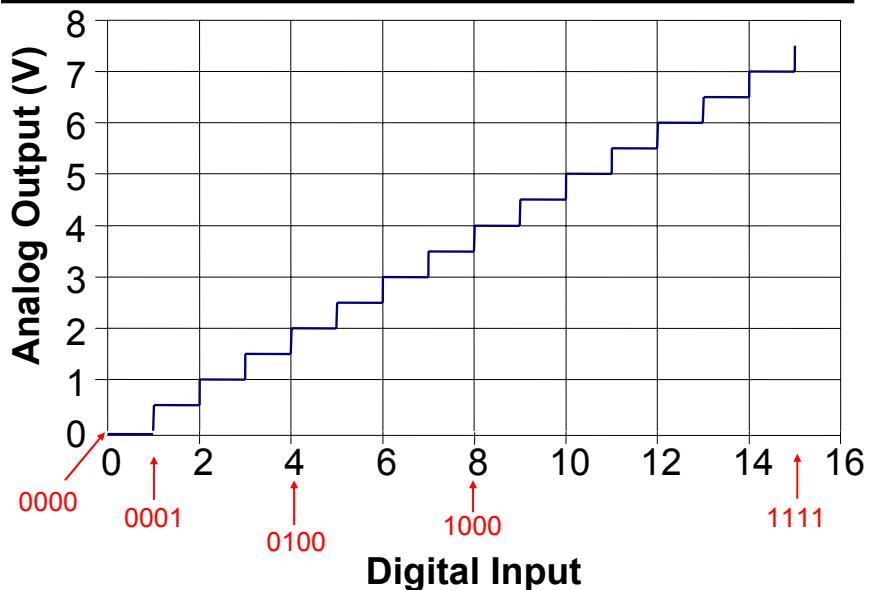


EECS40, Fall 2003

Lecture 10, Slide 7

Prof. King

Noninverting Amplifier Circuit

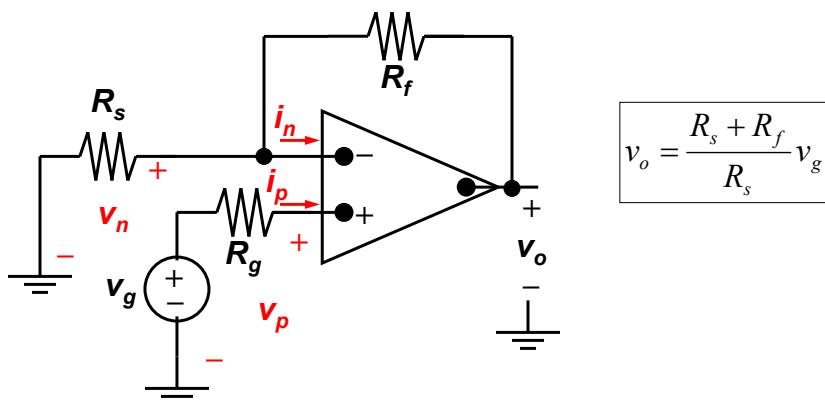

$$i_p = 0 \rightarrow v_p = v_g \rightarrow v_n = v_g$$


$i_n = 0 \rightarrow R_s \& R_f$ form a voltage divider

EECS40, Fall 2003

Lecture 10, Slide 8

Prof. King

Difference Amplifier Circuit

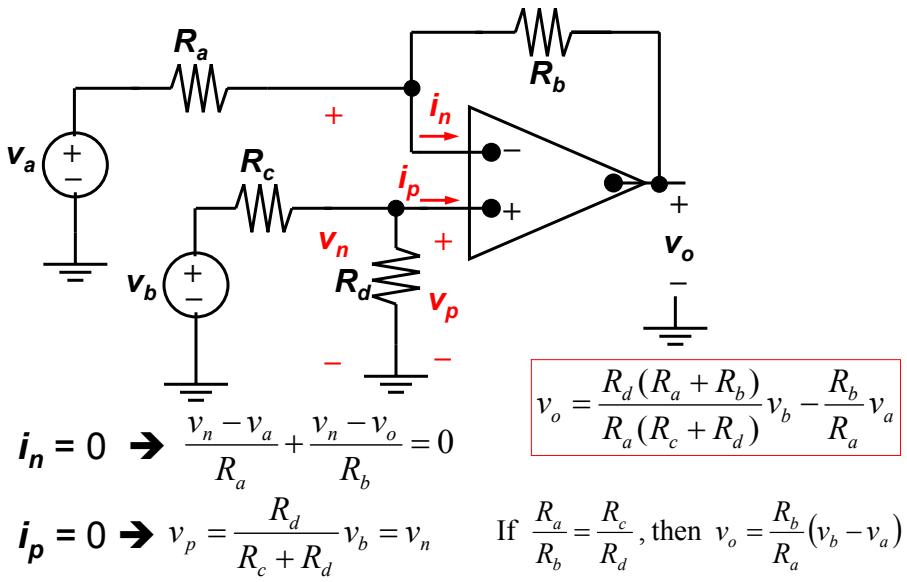

EECS40, Fall 2003

Lecture 10, Slide 9

Prof. King

Difference Amplifier – Another Perspective

Redefine the inputs in terms of two other voltages:

1. **differential mode input** $v_{dm} \equiv v_b - v_a$
2. **common mode input** $v_{cm} \equiv (v_a + v_b)/2$

so that

$$v_a = v_{cm} - (v_{dm}/2) \quad \text{and} \quad v_b = v_{cm} + (v_{dm}/2)$$

Then it can be shown that

$$v_o = A_{cm} v_{cm} + A_{dm} v_{dm}$$

$$\text{where } A_{cm} = \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)} \text{ and } A_{dm} = \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2 R_a (R_c + R_d)}$$

“common mode gain” “differential mode gain”

EECS40, Fall 2003

Lecture 10, Slide 10

Prof. King

Difference Amplifier (cont'd)


If $\frac{R_a}{R_b} = \frac{R_c}{R_d}$, then $v_{cm} = 0$ and $v_{dm} = \frac{R_b}{R_a} v_{dm}$

- An ideal difference amplifier amplifies only the differential mode portion of the input voltage, and eliminates the common mode portion.
 - provides immunity to noise (common to both inputs)
- If the resistors are not perfectly matched, the **common mode rejection ratio** (CMRR) is finite:

$$CMRR \equiv \left| \frac{A_{dm}}{A_{cm}} \right| \approx \frac{1 + R_b / R_a}{\varepsilon} \text{ if } \frac{R_a}{R_b} = (1 - \varepsilon) \frac{R_c}{R_d}$$

Summary

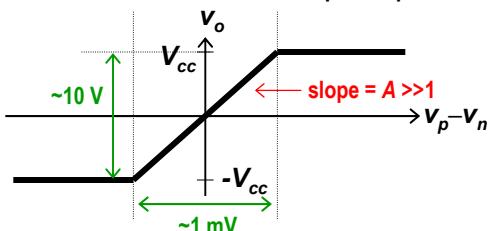- Voltage transfer characteristic of op amp:



- A feedback path between an op amp's output and its inverting input can force the op amp to operate in its linear region, where $v_o = A(v_p - v_n)$
- An **ideal op amp** has **infinite input resistance R_i** , **infinite open-loop gain A** , and **zero output resistance R_o** . As a result, the input voltages and currents are constrained:

$$v_p = v_n \text{ and } i_p = -i_n = 0$$