

Lecture #24

OUTLINE

- The common-source (CS) amplifier
 - load line analysis
 - DC bias circuit example
 - small-signal analysis of CS amplifier

Reference Reading


- **Howe & Sodini:** Chapter 8.1, 8.3
- **Hambley** (posted online): Chapter 12.2-12.5

Notation

- Subscript convention (Lecture 2, Slide 11):
 - $V_{DS} \equiv V_D - V_S$, $V_{GS} \equiv V_G - V_S$, *etc.*
- Double-subscripts denote DC sources (Lecture 23, Slide 7):
 - V_{DD} , V_{CC} , I_{SS} , *etc.*
- To distinguish between DC and AC components of an electrical quantity, the following convention is used:
 - DC quantity: upper-case letter with upper-case subscript
 - I_D , V_{DS} , *etc.*
 - AC quantity: lower-case letter with lower-case subscript
 - i_d , v_{ds} , *etc.*
 - Total (DC + AC) quantity:
lower-case letter with upper-case subscript
 - i_D , v_{DS} , *etc.*

P-Channel MOSFET Example

 - In a digital circuit, a p-channel MOSFET in the ON state is typically used to charge a capacitor connected to its drain terminal:
 - gate voltage $V_G = 0 \text{ V}$
 - source voltage $V_S = V_{DD}$ (power-supply voltage)
 - drain voltage V_D initially at 0 V , charging toward V_{DD}




$$R_{eq} \cong \frac{3}{4} \frac{V_{DD}}{|I_{DSATp}|} \left(1 - \frac{5}{6} \lambda_p V_{DD} \right)$$

$$I_{DSAT} = -\frac{k'_p}{2} \frac{W}{L} (V_{DD} - |V_{Tp}|)^2$$


Common-Source (CS) Amplifier

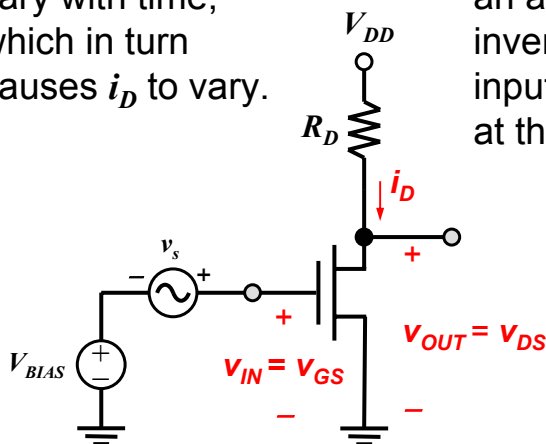- The input voltage v_s causes v_{GS} to vary with time, which in turn causes i_D to vary.
- The changing voltage drop across R_D causes an amplified (and inverted) version of the input signal to appear at the drain terminal.



Load-Line Analysis of CS Amplifier

 
- The operating point of the circuit can be determined by finding the intersection of the appropriate MOSFET i_D vs. v_{DS} characteristic and the load line:



load-line equation:

$$V_{DD} = R_D i_D + v_{DS}$$

Voltage Transfer Function

 

Goal:

Operate the amplifier in the high-gain region, so that small changes in v_{IN} result in large changes in v_{OUT}


- (1): transistor biased in cutoff region
- (2): $v_{IN} > V_T$; transistor biased in saturation region
- (3): transistor biased in saturation region
- (4): transistor biased in “resistive” or “triode” region

Quiescent Operating Point

- The operating point of the amplifier for zero input signal ($v_s = 0$) is often referred to as the **quiescent operating point** or **Q point**.
 - The Q point should be chosen so that the output voltage is approximately centered between V_{DD} and 0 V.
 - v_s varies the input voltage around the Q point.

Note: The relationship between v_{OUT} and v_{IN} is not linear; this results in a distorted output voltage signal. If the input signal amplitude is very small, however, we can have amplification with negligible distortion.


Bias Circuit Example

 

Rules for Small-Signal Analysis

- A DC supply voltage source acts as a short circuit
 - Even if AC current flows through the DC voltage source, the AC voltage across it is zero.
- A DC supply current source acts as an open circuit
 - Even if AC voltage is applied across the current source, the AC current through it is zero.

Small-Signal Equivalent Circuit

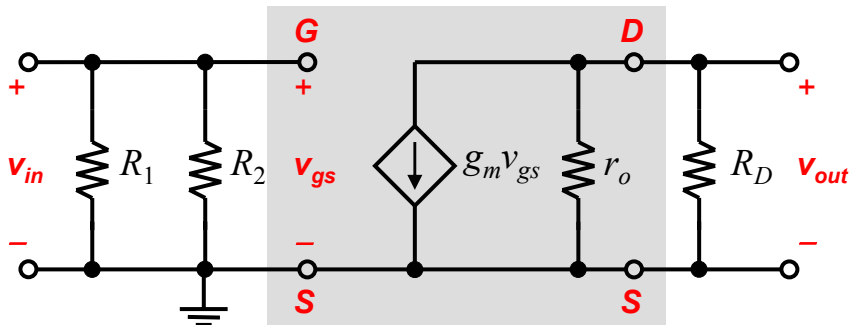

$$v_{out} = -g_m v_{gs} (r_o \parallel R_D)$$

voltage gain $A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R_D)$